



EAST WEST UNIVERSITY
Department of Computer Science and Engineering
B.Sc. in Computer Science and Engineering Program
Assignment, Fall 2024 Semester

Course: Electronic Circuits (CSE251/ICE213)
Full Marks: 15
Time: 1 Hour 10 Minutes

- From the circuit of **Figure 1** determine the currents and voltages of each branch. Considering R2 as load find the load line. Sketch the waveform for the voltage across R2 if the source voltage V1 is a 60Hz sinusoid of 10V peak amplitude. [CO2, C3, Mark: 5]

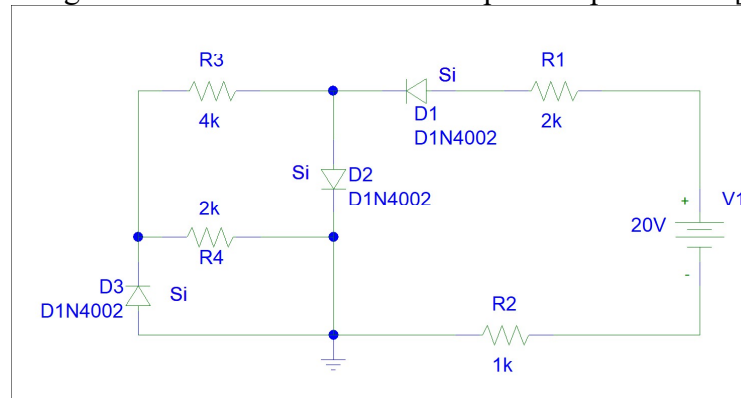


Figure 1

- Determine, I_B , I_C , V_C , and V_B for the circuit of **Figure 2**. Show the DC load line analysis and write what type of biasing the following circuit represents. [CO2, C3, Mark: 5]

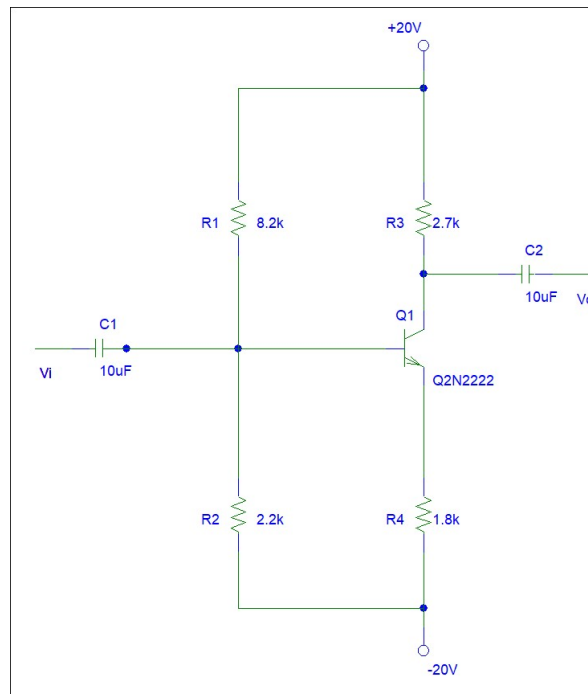


Figure. 2

3. Consider the ideal op-amp circuit in **Figure 3**. (a) Derive the expression for V_o as a function of V_{I1} and V_{I2} . (b) Find V_o for $V_{I1} = +0.25$ V and $V_{I2} = -0.40$ V. [CO2, C3, Mark: 5]

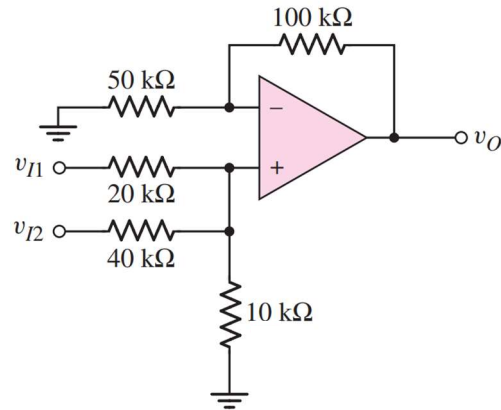


Figure. 3