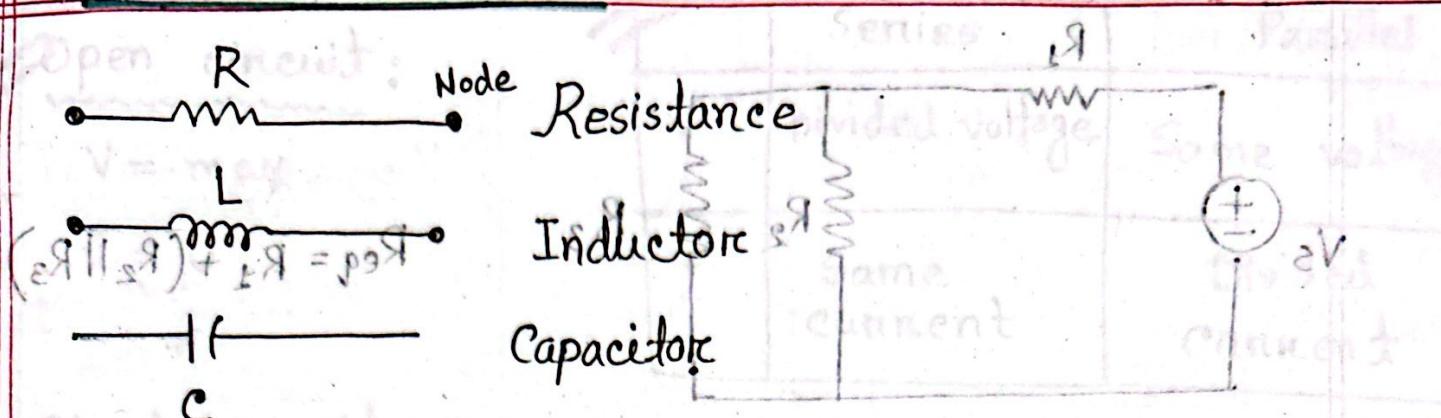


Passive elements:




Ohm's Law:

$$I = \frac{V}{R} ; R = \frac{V}{I} ; V = IR$$

Circuit:

① Series

② Parallel

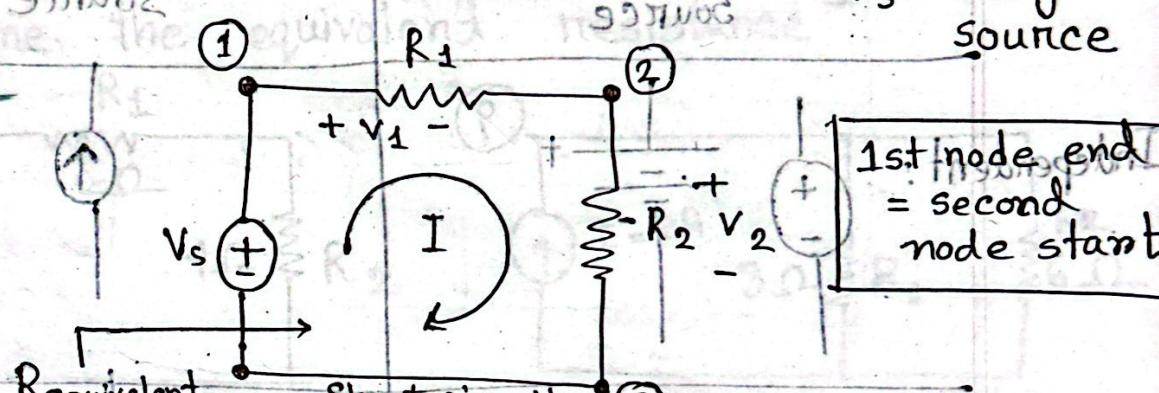

V_s = Voltage source

1st node end
= second
node start


Both are
close loop
circle

1st node end = 2nd end
2nd node start = 1st start

$$\text{Equivalent} = R_1 + R_2$$

Short circuit
(± wire between nodes)

③ Series circuit

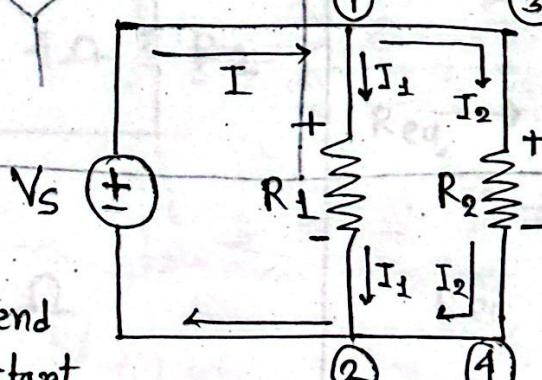


\therefore Equivalent Resistance

(Equivalent)


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 R_2}{R_1 + R_2}$$

④ Parallel circuit

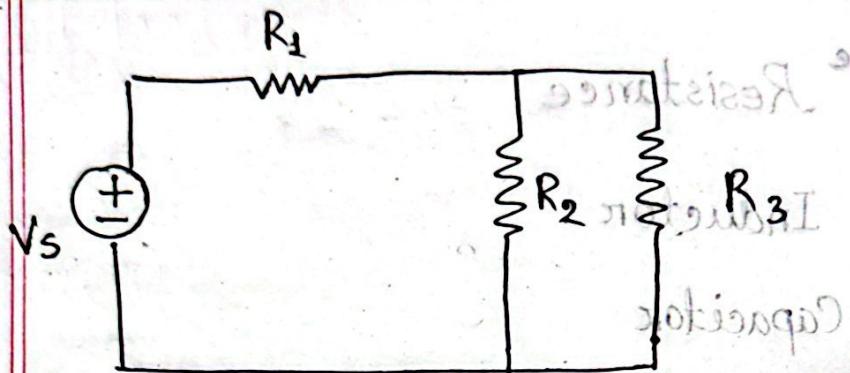

$$R_{eq} = R_1 + (R_2 || R_3)$$

S-P (Series- Parallel)

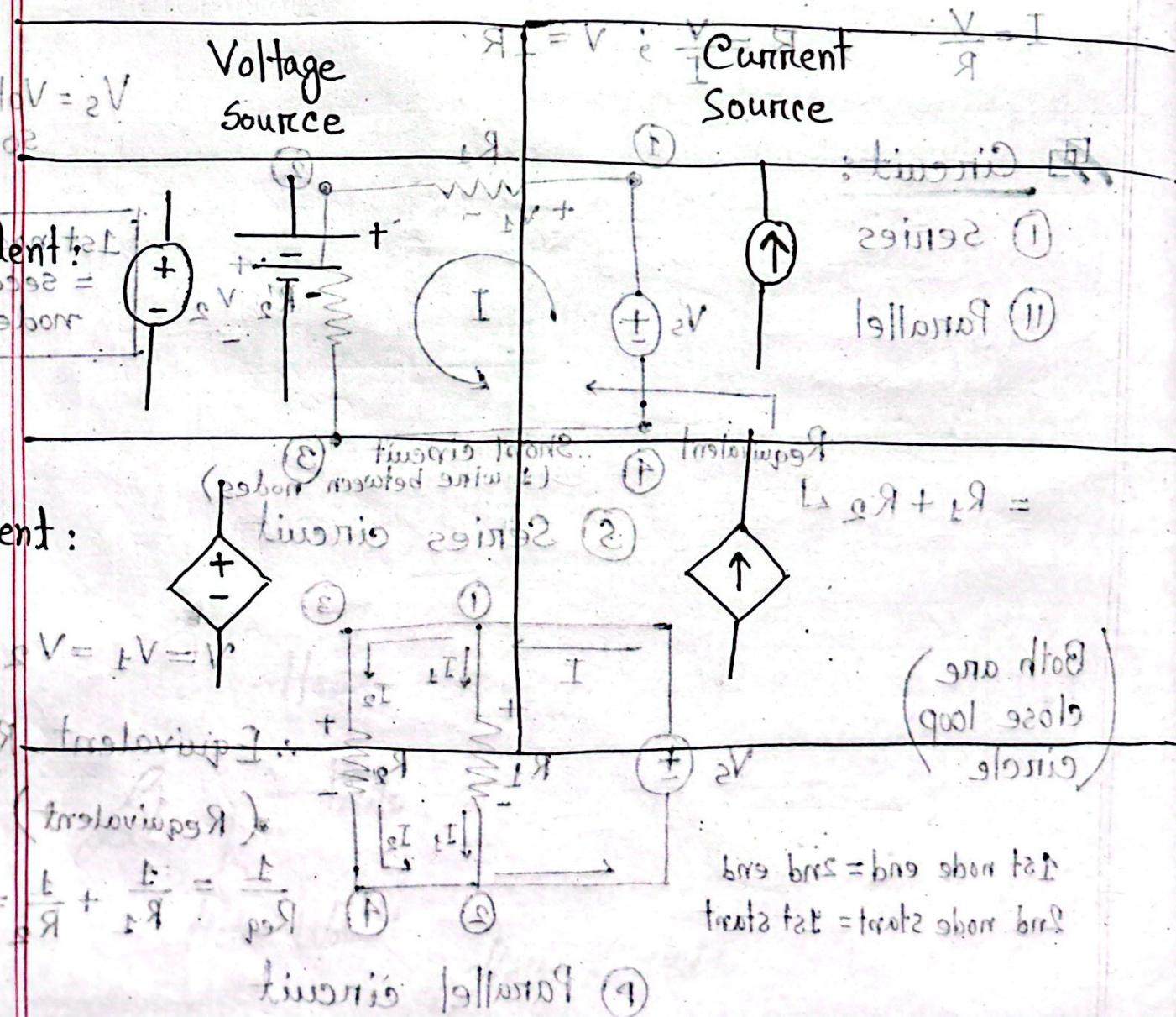

Open circuit:

$$V = \text{max} = 9V$$

$$I = 0$$



	Series	Parallel
V	Divided voltage	Same voltage
I	Same current	Divided current

Short circuit:

$$I = \text{max}$$


from $V = 0$. Determine the equivalent resistance.

Determine the equivalent resistance

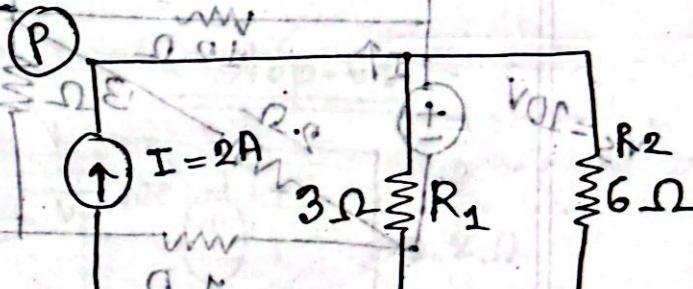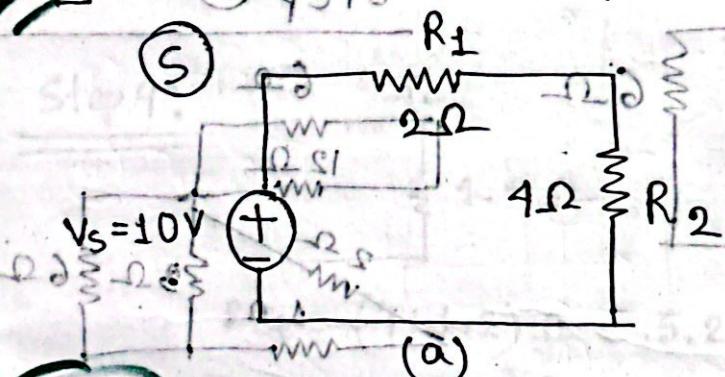

Soln:
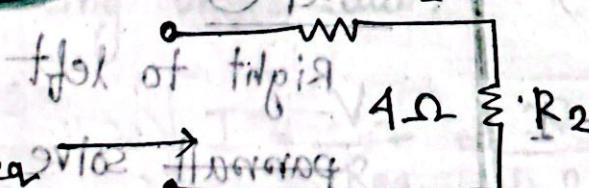
$$R_{eq} = 2\Omega + R_1 + (2 + \epsilon) + (3 + 6)$$



$$R_{eq} = \frac{2 \times 6}{2 + 6} + 3 + 6 = 6\Omega$$

$$R_{eq} = R_1 + R_2$$

$$= (2 + 4)\Omega$$


$$= 6\Omega$$

Prove

$$R_{eq} = \frac{3 \times 6}{3 + 6} \Omega$$

$$= 2\Omega$$

~~# Find Req:~~

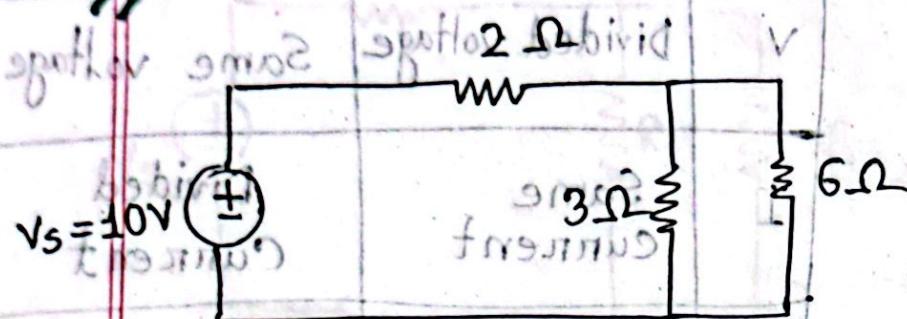


$$\begin{aligned} \text{Req} &= [2 + (3 \parallel 6)] \Omega \\ &= \left[2 + \frac{3 \times 6}{3+6} \right] \Omega \end{aligned}$$

$$= (2 + 2) \Omega$$


$$= 4 \Omega$$

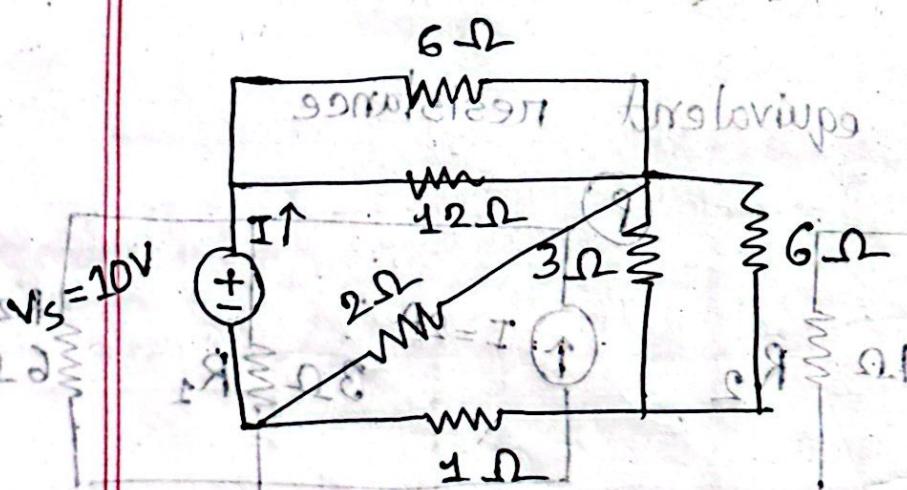~~# Determine the equivalent resistance and current~~



Step ①

6Ω

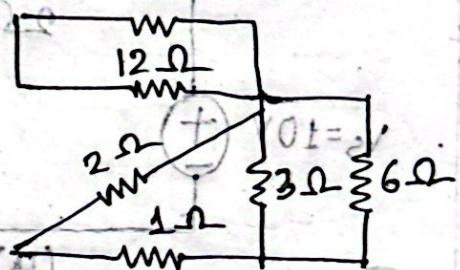

(a)

Step ②

Right to left

parallel solve parallel

$$2 + (6 \parallel 12) + (3 \parallel 6) + 1$$

$$\Rightarrow 2 + \frac{6 \times 12}{6+12} + \frac{3 \times 6}{3+6} + 1$$

$$\Rightarrow 2 + 4 + 2 + 1$$


$$\Rightarrow 9 \Omega$$

Step ③

Wrong Answer

$\Omega =$


Solution %

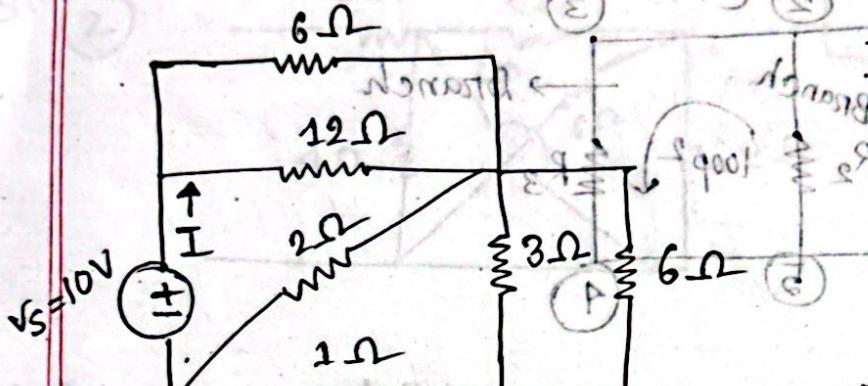


Step 1%

$$(6 \parallel 12) \Omega = 4 \Omega$$

$$(3 \parallel 6) = 2 \Omega$$

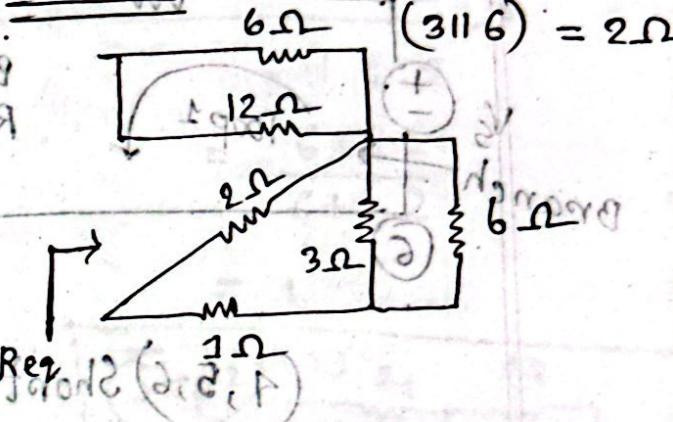


Step 2:

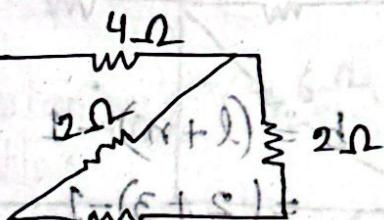


$$1 \Omega + (2+1) = 3 \Omega$$

Step 3:

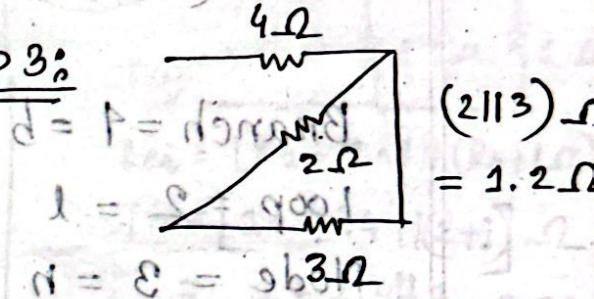


$$(2 \parallel 3) = 1.2 \Omega$$

Step 4:

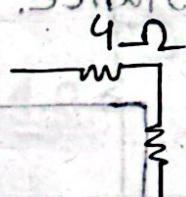

$$Req = (4+1.2) \Omega = 5.2 \Omega$$

Step-6:

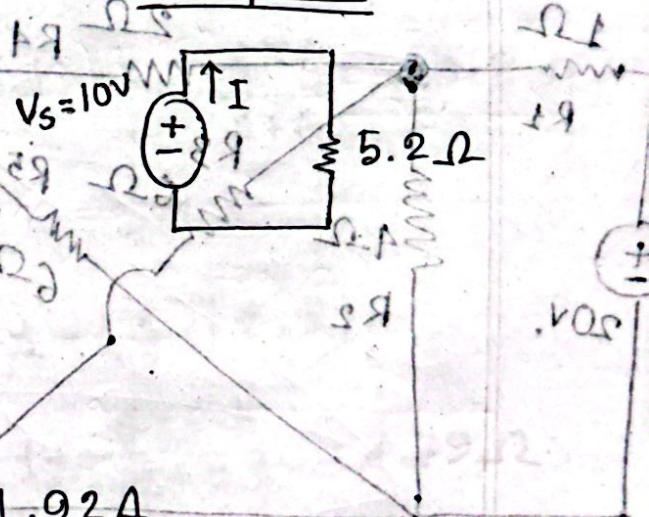

Using Ohm's law:


$$I = \frac{V_s}{Req} = \frac{10}{5.2} = 1.92A.$$


$$\Delta P.S = 211P.$$

$$\Delta S = 211S$$

$$S \parallel E :$$
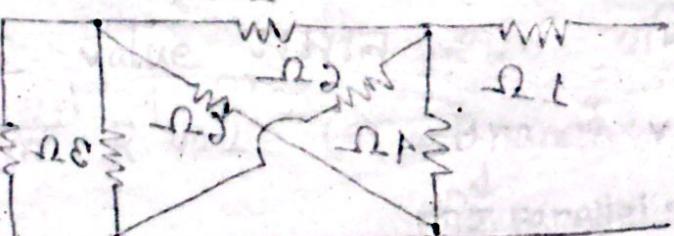
$$S \cdot I = \frac{S \times E}{S+E} = \frac{2 \times 1.92}{2+1.92} = 1.28A$$



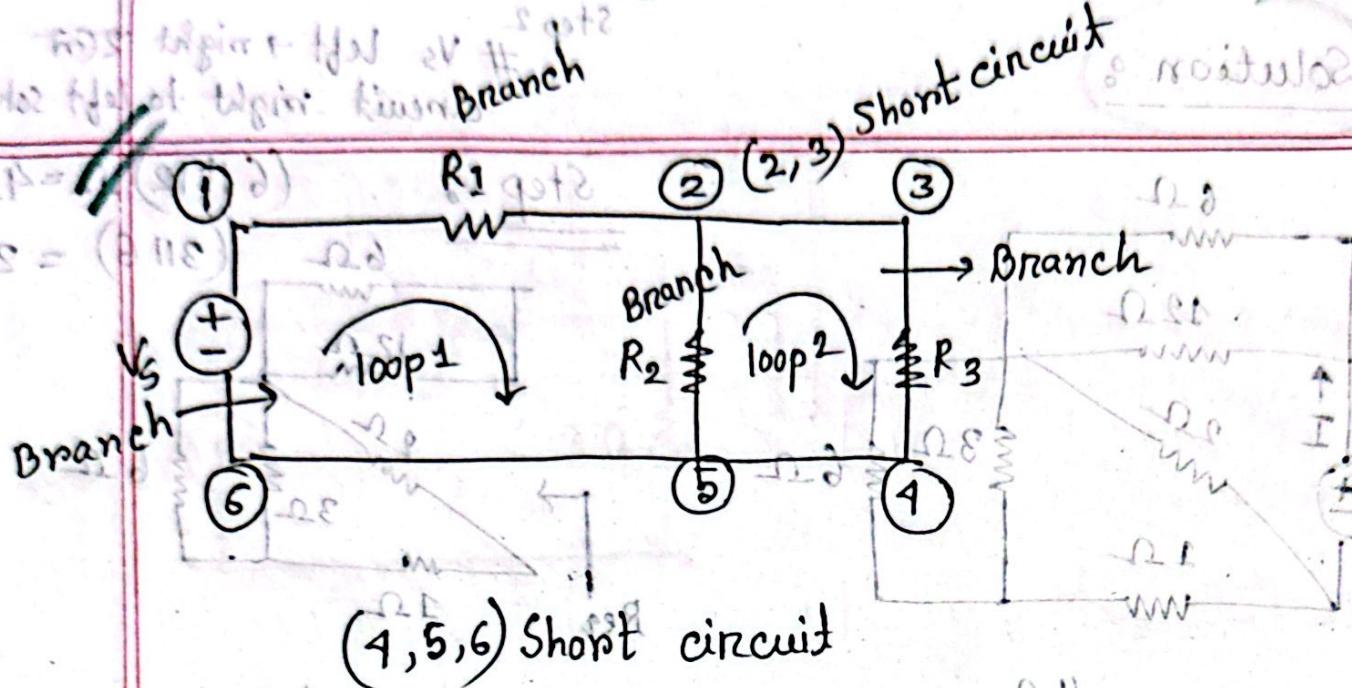


$$\text{Branch} = 4 = b$$

$$\text{Loop} = 2 = l$$



$$\text{Node} = 3 = n$$

$$b = (l+n)-1 \\ = (2+3)-1$$

Determine the equivalent resistance.

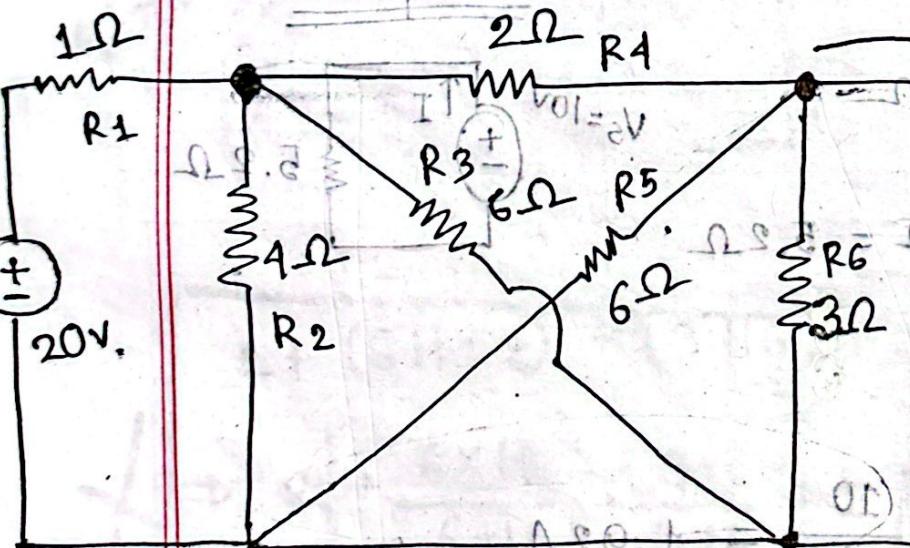






Step 1: Open Source

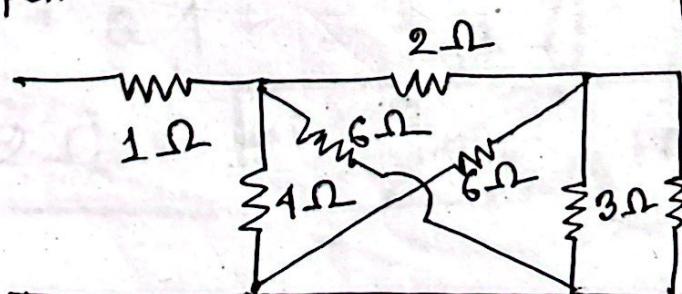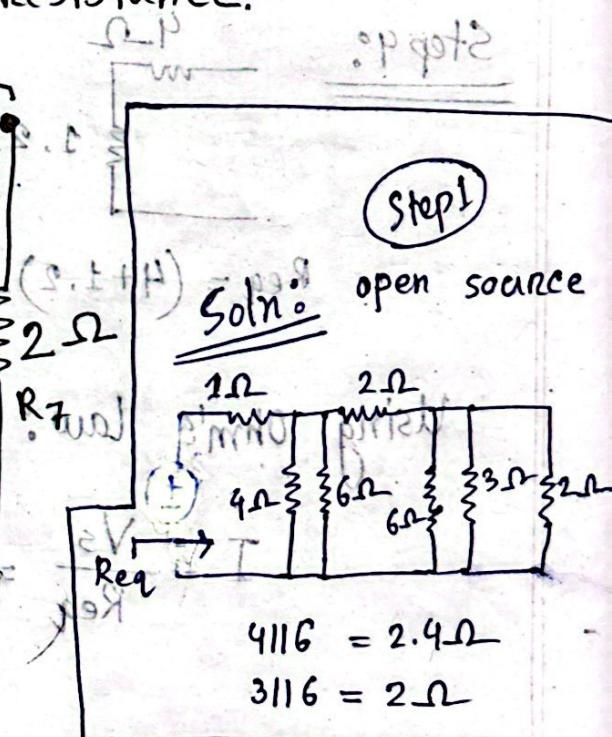

$$\therefore 3 \parallel 2$$

$$= \frac{3 \times 2}{3+2} = 1.2$$


(Step 2)

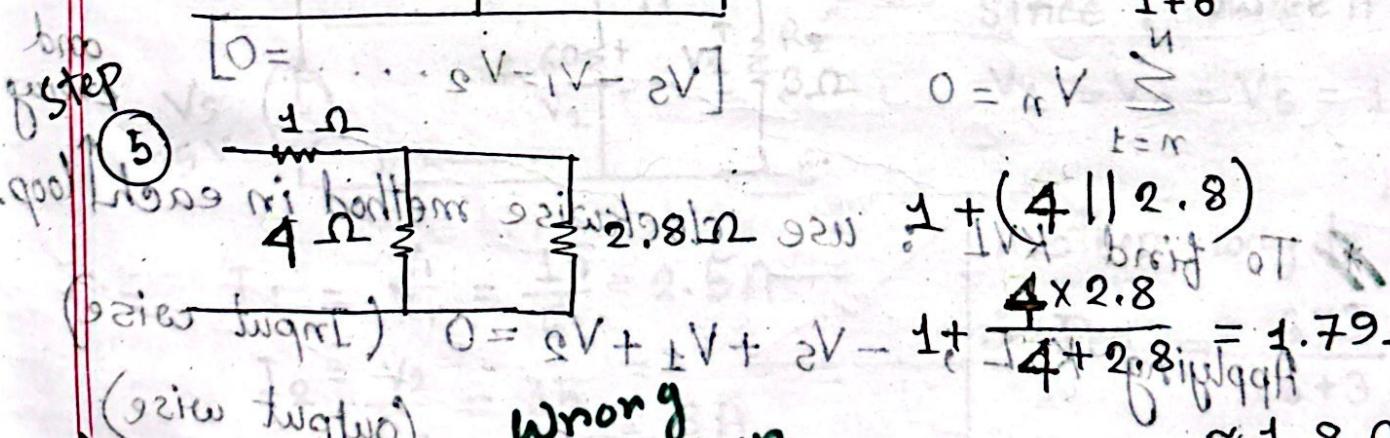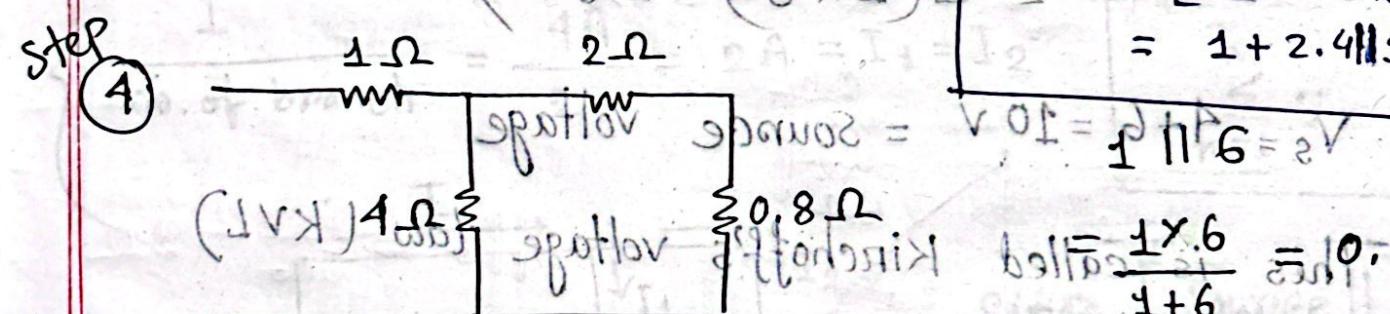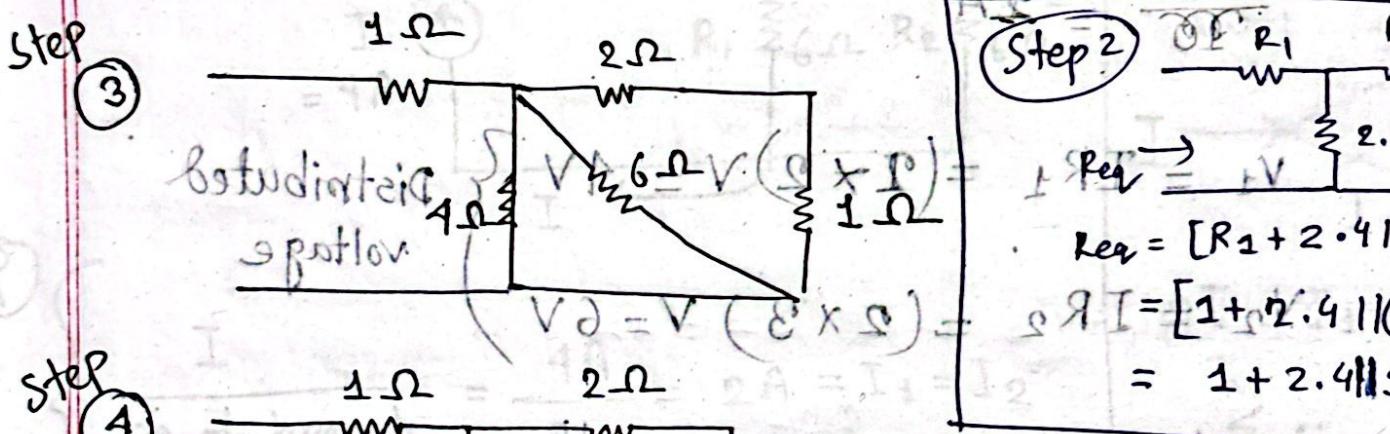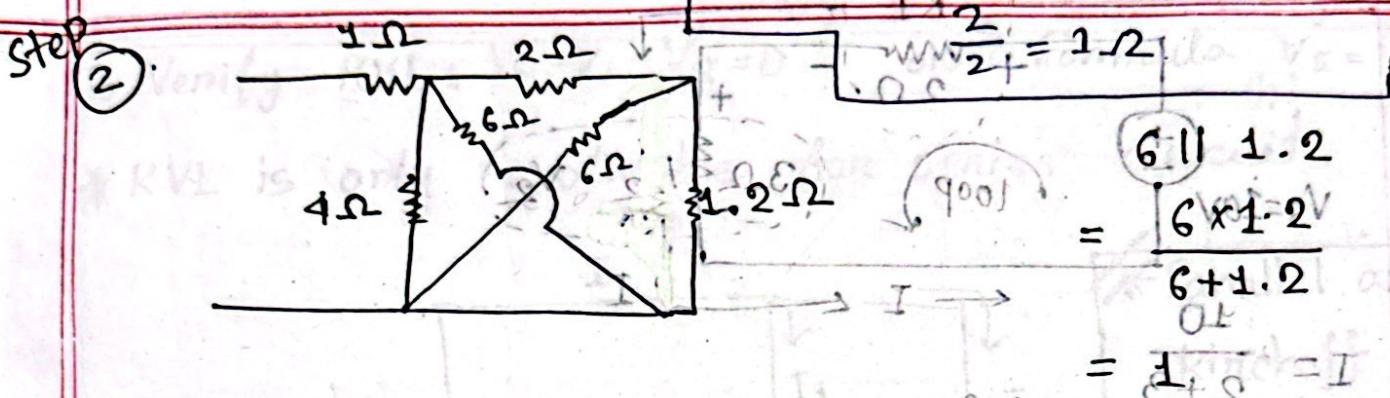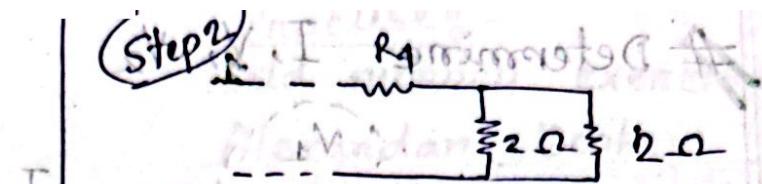

~~Parallel~~

* যদি Resistance value সমান হলে যদি series parallel হু গ্রহণ R value কে no. Branch value দিতে অস প্রযোগ যাব।

Determine I, V_1, V_2

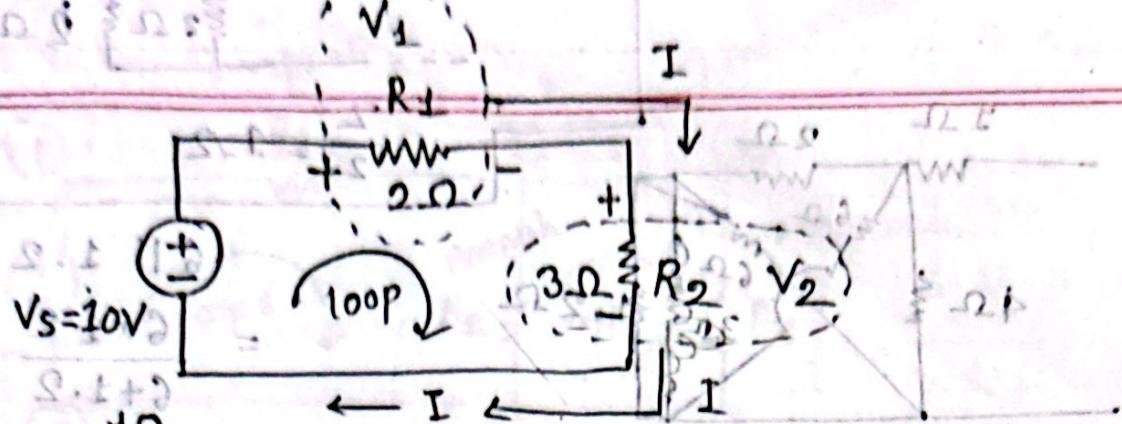

$$I = \frac{10}{2+3} = 2A$$

$$V_1 = IR_1 = (2 \times 2)V = 4V$$

} Distributed voltage

$$V_2 = IR_2 = (2 \times 3)V = 6V$$

$$V_s = 4 + 6 = 10V = \text{Source Voltage}$$

This is called Kirchoff's voltage law (KVL)

$$\sum_{n=1}^N V_n = 0 \quad [V_s - V_1 - V_2 \dots = 0] \quad \text{and every}$$

To find KVL : use clockwise method in each loop.

$$\text{Applying KVL ; } -V_s + V_1 + V_2 = 0 \quad (\text{Input wise})$$

$$V_s - V_1 - V_2 = 0 \quad (\text{Output wise})$$

$$10 - 4 - 6 = 0$$

$$\text{OR } -V_s + IR_1 + IR_2 = 0$$

$$10 - 4 - 6 = 0$$


Pracise-

odd number exercise

Alexandar Book

To Verify KVL: $V_s - V_1 - V_2 = 0$ or Formula $V_s = V_1 + V_2$

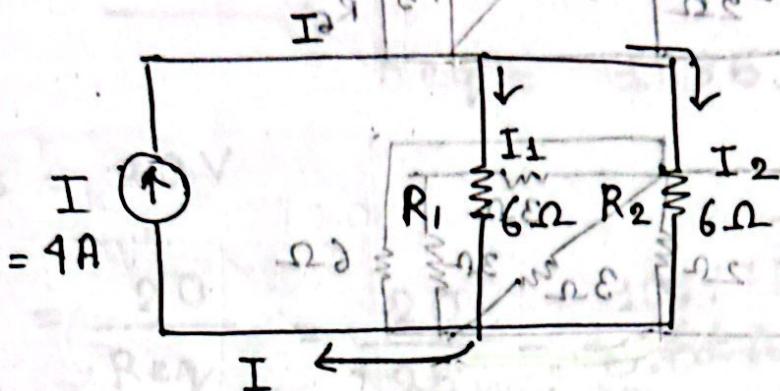* KVL is only applicable for series circuit.




* Parallel applicable
Kirchoff current law:
 $I = I_1 + I_2$

A diagram illustrating Kirchoff's Current Law (KCL). It shows a junction where a total current I enters from the left and splits into two branches, I_1 and I_2 , which then recombine at the junction.

$$\frac{I}{\text{no. of branch}} = \frac{4A}{2} = 2A = I_1 = I_2$$

$$\sum_{n=1}^m I_n = 0$$

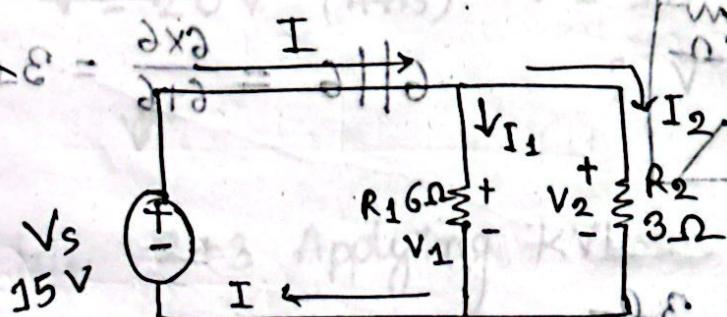

Since [Source || $R_1 \parallel R_2$]

$$V_1 = V_2 = V_s = 15V$$

Another way to find I

$$\therefore \text{Req} = \frac{6 \times 3}{6+3} = 2\Omega$$

Ohm's law,

$$I_s = \frac{V_s}{\text{Req}} = \frac{15V}{2\Omega}$$


$$I = 7.5A$$

Using KCL at node A


$$I = I_1 + I_2 = 2.5 + 5 = 7.5A$$

03/07/21

Determine the Req

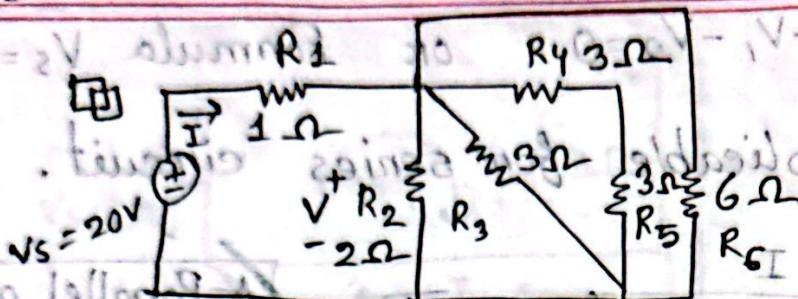


Step 1

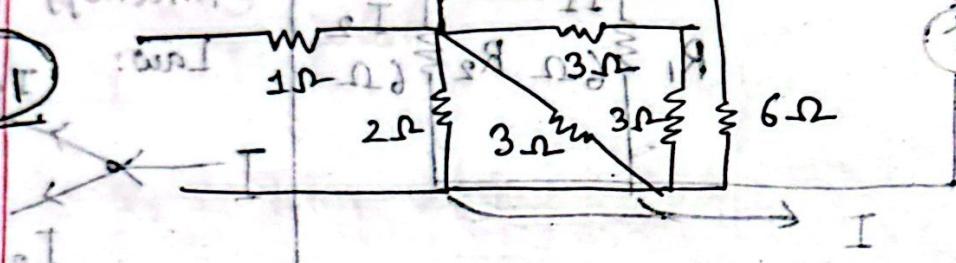

$$I + I \Rightarrow IR_4 + R_5 = 3 + 3 = 6 \Omega$$


$$0 = \alpha I \sum_{i=1}^n I = \frac{I}{A_f} = \frac{I}{\frac{6}{6+6}} = I$$

Step 2

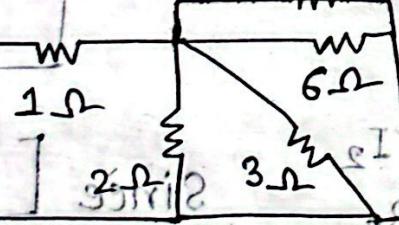

$$6 \parallel 6 = \frac{6 \times 6}{6+6} = 3 \Omega$$


Step 3

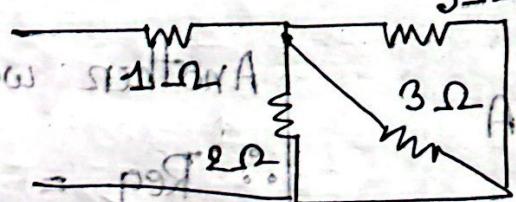

$$\alpha \cdot I = \frac{I}{A_f} = \frac{3 \times 3}{3+3} = 1.5$$

$$A_f = \frac{I}{I} = \frac{I}{1.5} = 1.5$$

Step 4

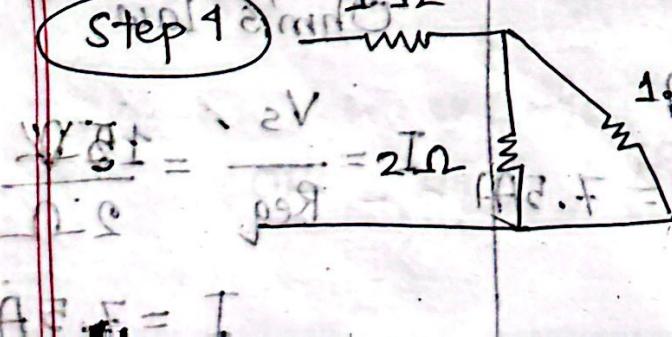


$$1.5 \parallel 1.5 = 0.85 \Omega$$

$$A_f = \frac{2 \times 1.5}{3.5} = \frac{1.5}{0.85} = 1.5$$

$$A_f \cdot I = I$$

Step 5

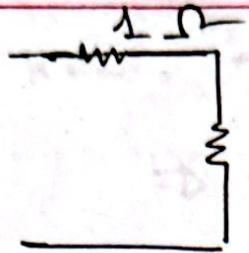

0.85

0.8Ω

Applying KVL in loop 1

~~Req = (R1 + R2) / 2~~

$$0 = 2 \times 8 + 0.8V \rightarrow V = -16V$$

$$Req = 4.86 \Omega \text{ Ans}$$

$V_s = 20V$

$$I = \frac{20}{Req}$$

$$\frac{20}{1.85}$$

$$10.77A$$

~~10.77A~~ (Ans)

V8-

$$0 = (10.77)(8) - 1.86I + 20 \rightarrow I = 10.77A$$

$V_s = V$

since, $(V_s || R_2)$

$$V = 20V \text{ (Ans)} \quad V = IR = 10.77 \times 0.86 \Omega$$


$$\therefore V = 9.25V$$

Q

2+3 Applying KVL

$$-V_s + I_2 + I_3 + I_5 = 0$$

$$\Rightarrow -20 + I(2+3+5) = 0$$

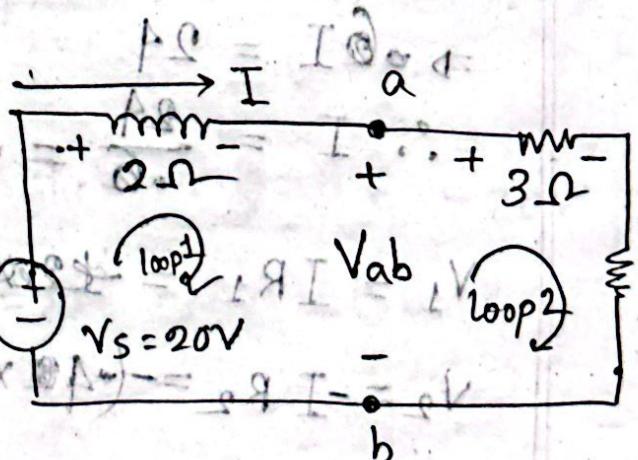

$$\Rightarrow I(10) = 20$$

$$\therefore I = \frac{20}{10} = 2A$$

Applying KVL in loop 1,

$$-20 + I_2 + V_{ab} = 0$$

$$\Rightarrow -20 + 2 \times 2 + V_{ab} = 0 \quad \therefore V_{ab} = 16V$$

Applying KVL in loop 2,

$$-V_{ab} + 3I + 5I = 0$$

$$\Rightarrow -V_{ab} + 8 \times 2 = 0$$

$$\therefore V_{ab} = 16V$$

Find V_1, V_2

Using KVL, $-V_2$

$$-32 + IR_1 - (-8)(-I) = 0$$

$$\Rightarrow -32 + 8 + I(4+2) = 0$$

$$\Rightarrow -24 + 6I = 0$$

$$\Rightarrow 6I = 24$$

$$\therefore I = \frac{24}{6} = 4A$$

$$V_1 = IR_1 = 4 \times 4 = 16V$$



$$V_2 = -I R_2 = -(4 \times 2) = -8V$$

find i and V_o

Using Ohm's law :

$$V_o = 12V + 6i + 0.2 - 4$$

$$i = 0.2$$

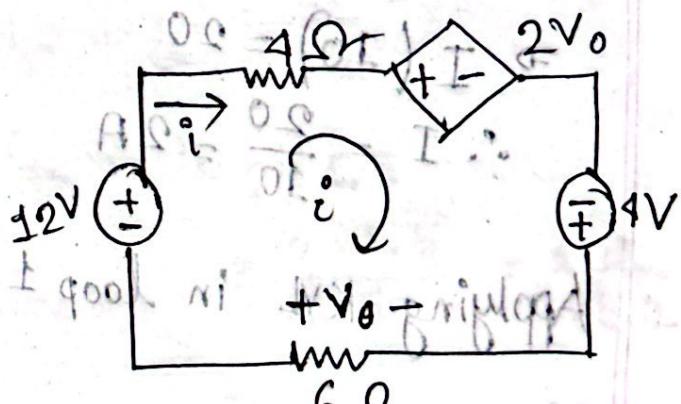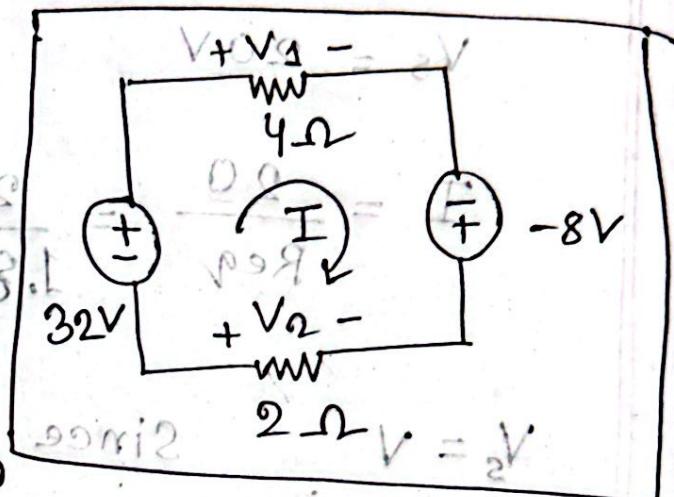

Applying KVL, $-12 + 4i + 2V_o - 4 + 6i = 0$

$$\Rightarrow -12 + 4i + 2 \times (-6i) - 4 + 6i = 0$$

$$\Rightarrow i = -8A$$

Q Find V_x and V_o .

Applying KVL,

$$+70 + 10I + 2 - V_o$$


$$\Rightarrow 70 + 10I + 2 - 5I = 0$$

$$\Rightarrow 72 + 5I = 70$$

$$\Rightarrow I = -2A$$

$$V_x = 10I = -2 \times 10 = -20V$$

$$V_o = 5I = -5 \times -2 = 10V$$

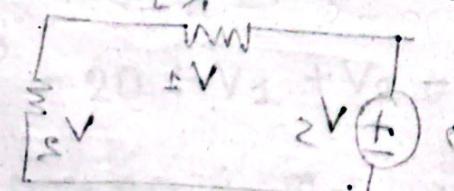

$$\frac{2V}{5\Omega + R_s} = V_o$$


$$\frac{2V}{R_s + 5\Omega} = V_o$$

$$V_o = \frac{2 \times 10}{15} = 2V$$

$$V_o = \frac{2 \times 10}{5} = 4V$$

I { + enter
- out

Find V_o and i_o

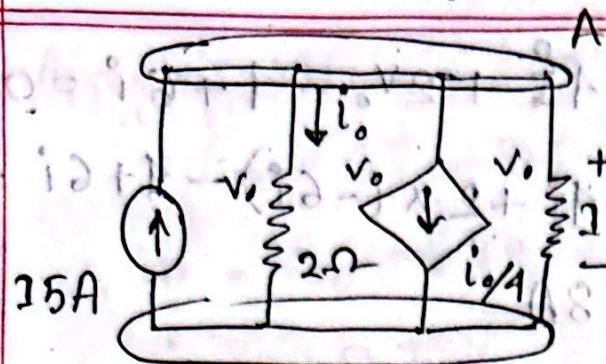

Applying KCL at node A

$$25 = i_o + \frac{i_o}{4} + i_1$$

$$\Rightarrow 25 = \frac{V_o}{2} + \frac{V_o}{4} + \frac{V_o}{12}$$


$$\Rightarrow 25 = \frac{V_o}{2} + \frac{V_o}{8} + \left(\frac{V_o}{12}\right)$$

$$\Rightarrow 25 = \frac{6V_o + 1.5V_o + V_o}{24} = \frac{8.5V_o}{24}$$

$$\therefore V = \frac{15 \times 12}{8.5} = \frac{15 \times 24}{17} = 21.176 V$$

$$\text{Ohm's law, } i_o = \frac{V_o}{2} = \frac{21.17}{2} = 10.58 A$$

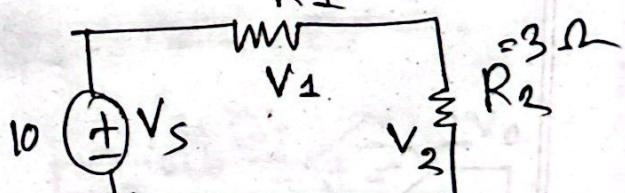■ Voltage divider Rule
Applicable for $\textcircled{5}$ circuit



$$V_1 = \frac{V_s R_1}{R_1 + R_2}$$

$$V_2 = \frac{V_s R_2}{R_1 + R_2}$$

$$V_1 = \frac{10 \times 2}{5} = 4 V$$

$$V_2 = \frac{10 \times 3}{5} = 6 V$$


यदि node A द्वारा 6A का Source Current

Current Divider Rule:

$$I_1 = \frac{I_s \times R_2}{R_1 + R_2} = \frac{6 \times 3}{5} = 3.6A$$

$$I_2 = \frac{I_s \times R_1}{R_1 + R_2} = \frac{6 \times 2}{5} = 2.4A$$

यदि यही थाएं $I_1 = I_s \times \frac{(R_2 || R_3)}{R_1 + R_2 + R_3}$

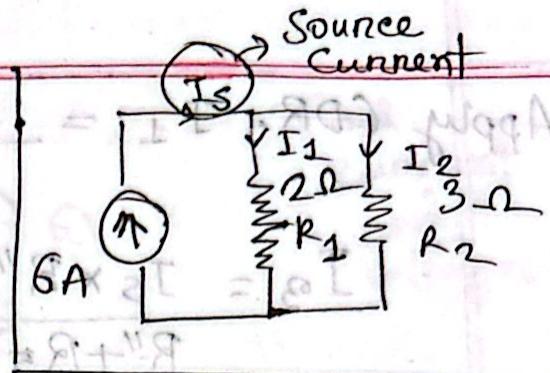

Find V_1, V_2, I, I_1, I_2 & I_3

$$R_3 || R_4 = 2\Omega$$

$$\begin{aligned} R_{eq} &= 2 + (2+2) || 4 \\ &= 2 + 4 || 4 \\ &= 2 + 2 = 4\Omega \end{aligned}$$

$$\therefore I_s = \frac{20}{4} = 5A \quad (\text{Ans})$$



another
way, KVL,

$$-20 + V_1 + V_2 = 0$$

$$\Rightarrow -20 + 2I_s + 2I_s = 0$$

$$\Rightarrow -20 + 4I_s = 0$$

$$\Rightarrow I_s = 5A$$

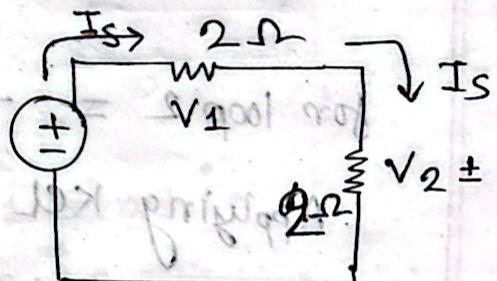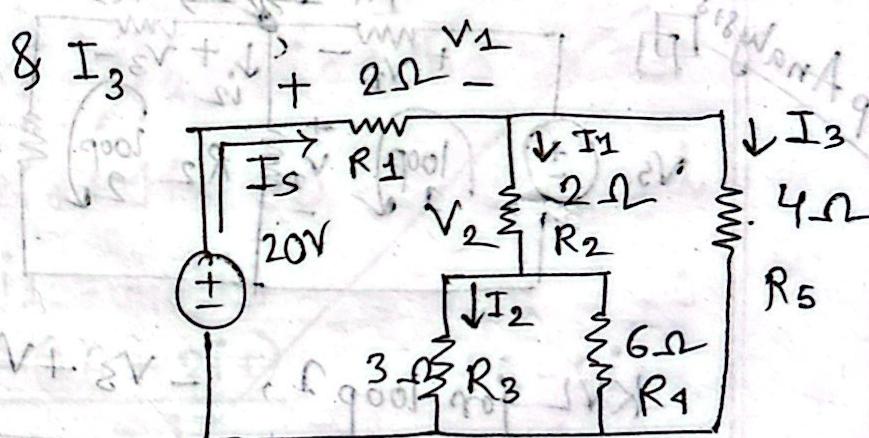

$$V_1 = 2I_s = 10V \quad (\text{Ans})$$

$$V_2 = 2I_s = 20V \quad (\text{Ans})$$


CDR,
 ~~$\therefore I_1 = I_2 = I_3 = \frac{I_s \times R_2}{2+2} = \frac{5 \times 2}{4} = 2.5A$~~

$$\text{Apply (DR, } I_1 = \frac{I_s \times R_5}{R'' + R_5} = \frac{5 \times 4}{4+4} = 2.5 \text{ A (Ans)}$$

$$I_2 = \frac{I_s \times R''}{R'' + R_5} = \frac{5 \times 4}{4+4} = 2.5 \text{ A (Ans)}$$

$$I_2 = \frac{I_1 \times R_4}{R_3 + R_4} = \frac{2.5 \times 6}{3+6} = 1.66 \text{ A (Ans)}$$

loop Analysis

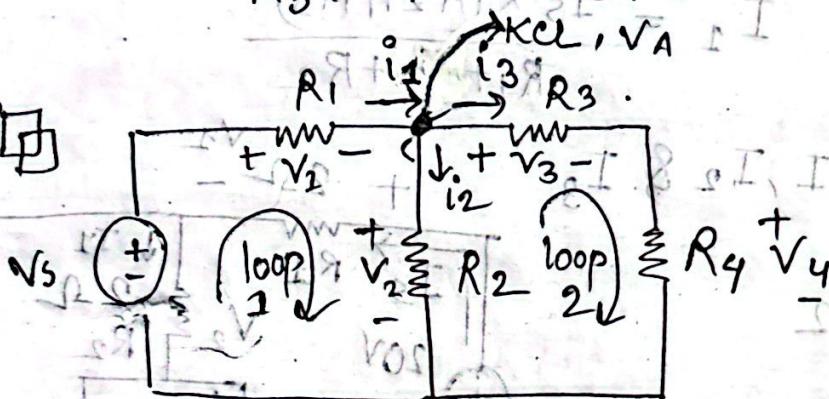

$$\text{KVL for loop 1, } -V_3 + V_1 + V_2 = 0$$

$$\text{for loop 2, } -V_2 + V_3 + V_4 = 0$$

Applying KCL in node A,


$$i_1 = i_2 + i_3$$

(wrt) Ohm's law ~~VIOL~~ \rightarrow Apply কানুন solve ব্যবস্থা

$$(wrt) V_{OP} = 2I_{in} = \frac{V_1}{R_1} : \quad i_2 = \frac{V_3}{R_3} \quad \boxed{V_1 = V_s - V_A}$$

$$\cancel{A.C.O.} \quad \cancel{I_2 = \frac{V_2}{R_2}} \quad \cancel{I_4 = \frac{V_4}{R_4}} \quad \boxed{A.D. = 2I_{in}}$$

C.W
08/07/2021

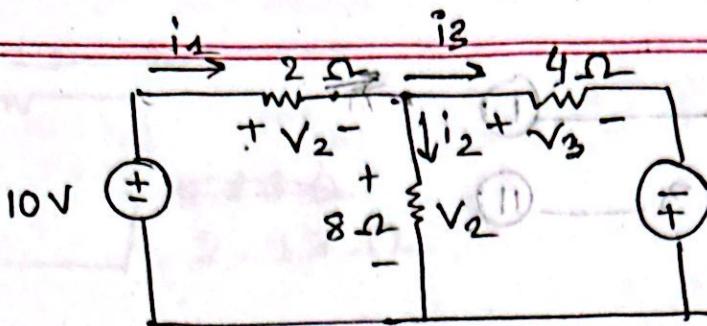

Find current and voltage

KVL,

~~$10 + 2i_1 + 8i_2 = 0 \quad \text{--- (I)}$~~

~~$-8i_2 + 4i_3 - 6 = 0 \quad \text{--- (II)}$~~

~~$(\text{I}) + (\text{II}) \Rightarrow -10 + 2i_1 + 8i_2 - 8i_2 + 4i_3 - 6 = 0$~~

~~$\Rightarrow -16 + 2i_1 + 4i_3 (0 \times 6) - 6 = 0$~~

~~$\Rightarrow -16 + 2i_1 - 4i_3 = 0 \quad \text{--- (III)}$~~

~~$i_3 = \frac{-(16 - 2i_1)}{4} = \frac{16 - 2i_1}{4}$~~

~~$-8i_2 - 16 + 2i_1 = -4i_2 - 2i_1$~~

Applying KCL at node A, $i_1 = i_3 + i_2$

~~$i_1 - i_2 - i_3 = 0 \quad \text{I b/w}$~~

Using ohms law,

~~$V_1 = 2i_1 = 2 \times 3 = 6V$~~

~~$V_2 = 8i_2 = 8 \times 2 = 16V$~~

~~$V_3 = 4i_3 = 4 \times 2.5 = 10V$~~

Qwiz - I

25/7/24

Monday

: 2/1A

{ 10.40am

$5i_2 + i_3 = 5 \quad \text{--- (I)}$
 $-4i_2 + 2i_3 = 3 \quad \text{--- (II)}$
 $i_3 = 5 - 5i_2$

(II) $-4i_2 + 2(5 - 5i_2) = 3$


$\Rightarrow -4i_2 + 10 - 10i_2 = 3 \quad 0 = 3 - 14i_2 \quad i_2 = \frac{3}{14} = 0.214$

$\Rightarrow -14i_2 = -7 \quad i_2 = \frac{-7}{-14} = \frac{1}{2} = 0.5$

$i_3 = 5 - (5 \times 0.5) = 2.5$


$i_1 = i_3 + i_2 = 2.5 + 0.5 = 3$

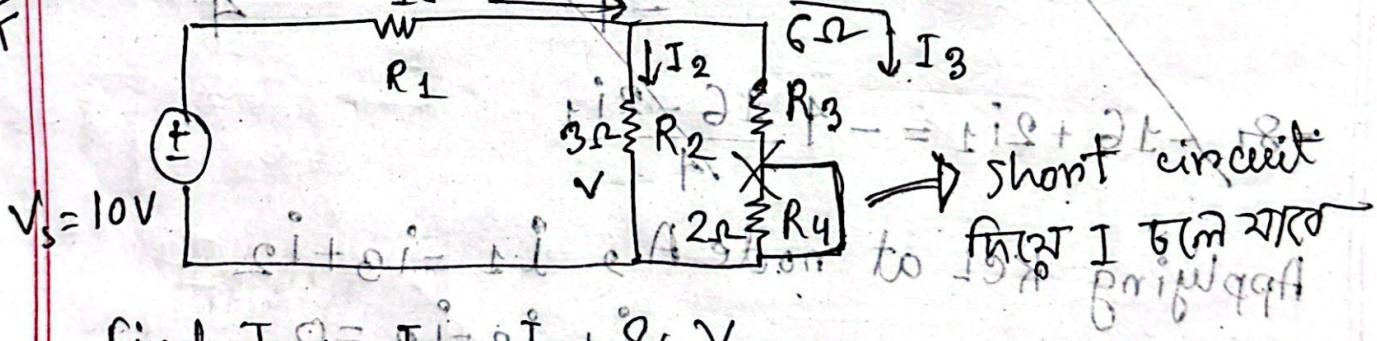$\frac{i_1}{1\Omega} = \frac{(i_2 - i_1)}{3\Omega}$




find I_1, I_2, I_3 & V .

Ans:

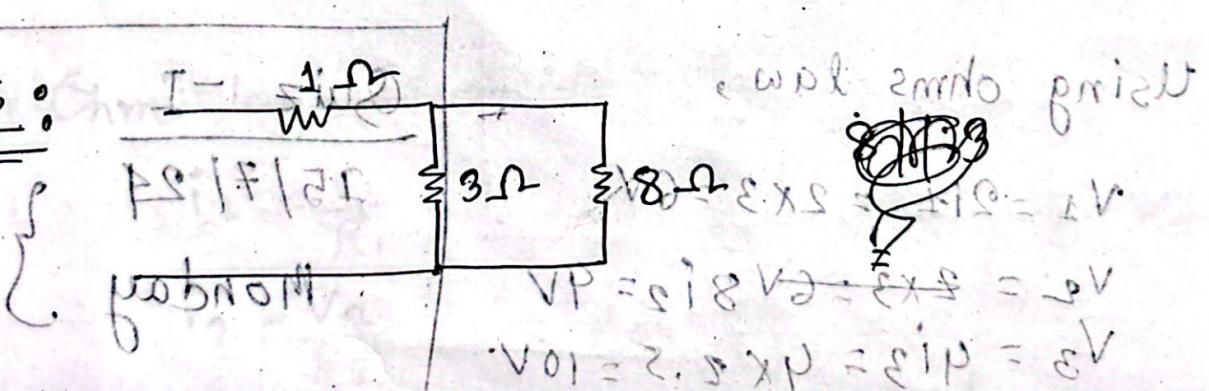

$V_{01} = 2.5 \times 1 = 2.5V$

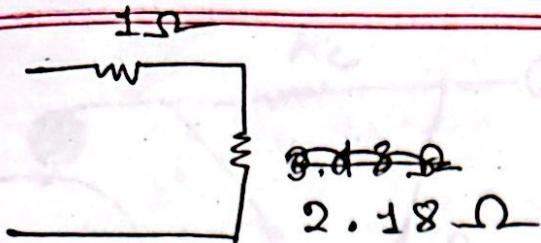

$$8 \parallel 3 = \cancel{2.18\Omega} \quad 2.18\Omega$$

$$\text{Req} = 1 + \cancel{2.18\Omega}$$

$$= \cancel{3.18\Omega}$$

$$V = I \times \text{Req}$$

$$= \cancel{3.18 \times 0.31\text{A}}$$

$$= \cancel{7.74} = 0.98\text{V}$$

$$I_1 = \frac{V_s}{\text{Req}}$$

$$= \frac{10}{3.18}$$

$$= 0.31\text{A}$$


$$3.14\text{A}$$

$$I_2 = \frac{I_1 \times (R_3 + R_4)}{3+2}$$

~~wrong~~

$$I_3 = \frac{I_s (R_2)}{3+2} = \cancel{0.186\text{A}} \quad 0.186\text{A}$$

~~Soln~~

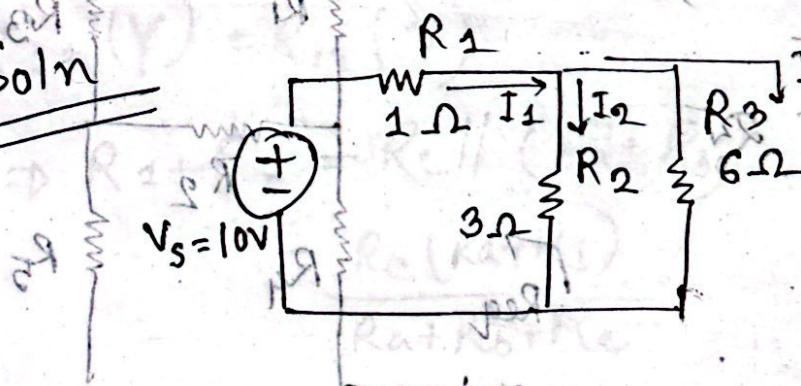

$$3 \parallel 6 = \frac{3 \times 6}{3+6} = 2\Omega$$

$$\text{Req} = 1+2 = 3\Omega$$

$$I_1 = \frac{10}{3} = 3.33\text{A}$$

$$I_2 = 0.22\text{A} \quad I_3 = 1.11\text{A}$$

~~We can also use~~

Applying KVL, loop 1

$$-V_s + I_1 1 + I_2 3 = 0$$


$$I_1 1 + I_2 3 = 10$$

Loop 2, $-3I_2 + 6I_3 = 0$

$$= -I_2 + 2I_3 = 0 \quad \text{--- (II)}$$

KCL,

$$\text{Node A} \quad I_1 = I_2 + I_3$$

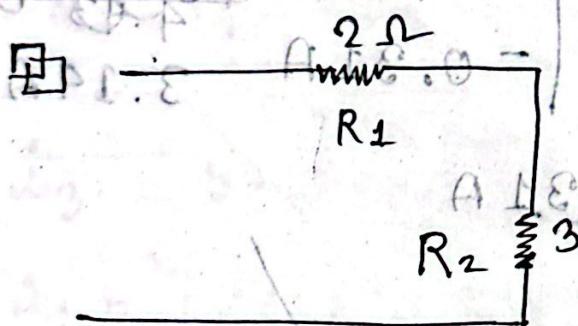


Conductance = $\frac{1}{R}$

$$G = \frac{1}{R} = \frac{1}{8\Omega} = 0.125 S$$

~~$$Req = 2 + 3 = 5 \Omega$$~~
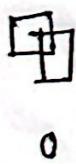
$$G_1 = \frac{1}{2}, \quad G_2 = \frac{1}{3}, \quad G_{eq} = \frac{2 \times 3}{3 + 2} = 1.2 S$$



WYE DELTA (Δ -Y)


Transformation


T-T \leftrightarrow Δ

$$2\Omega = 2 + 1 = 3\Omega$$

$$A_{EE} = \frac{01}{E} = \frac{1}{E}$$

$$A_{111} = E + A_{SS} = E$$

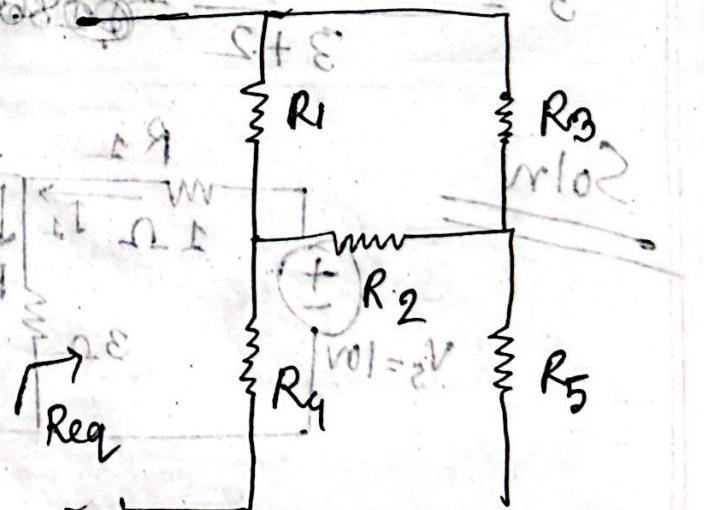

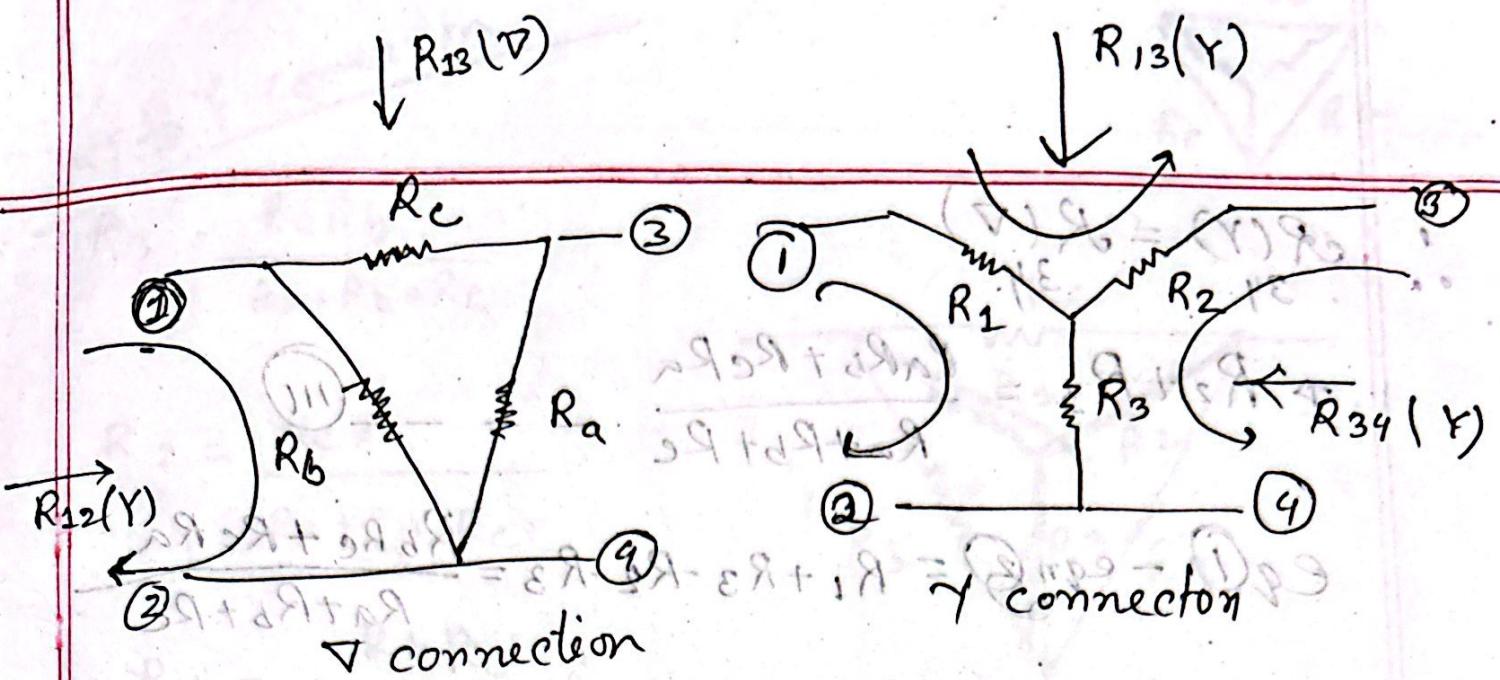

$$\textcircled{1} - R_{12}(\Delta) = R_{13} \cdot 1 / (R_c + R_a) \quad R_{12}(\Delta) = R_1 + R_3$$

$$R_{13}(\Delta) = R_c \parallel (R_a + R_b)$$

$$R_{13}(Y) = R_1 + R_2$$

$$R_{34}(\Delta) = R_a \parallel (R_b + R_c)$$

$$R_{34}(Y) = R_2 + R_3$$

$$R_{12}(Y) = R_{12}(\Delta)$$

$$\Rightarrow R_1 + R_3 = R_b \parallel (R_c + R_a)$$

$$= \frac{R_b(R_c + R_a)}{R_a + R_b + R_c}$$

$$= \frac{R_b R_c + R_b R_a}{R_a + R_b + R_c} \quad \text{--- } \textcircled{1}$$

$$\therefore R_{13}(Y) = R_{13}(\Delta)$$

$$\Rightarrow R_1 + R_2 = R_c \parallel (R_a + R_b)$$

$$= \frac{R_c(R_a + R_b)}{R_a + R_b + R_c}$$

for inititide

$$\therefore R_1 + R_2 = \frac{R_c R_a + R_c R_b}{R_a + R_b + R_c}$$

$$\therefore R(Y) = R(\Delta)$$

$$\Rightarrow R_2 + R_3 = \frac{R_a R_b + R_c R_a}{R_a + R_b + R_c}$$

$$eq \textcircled{1} - eq \textcircled{2} = R_1 + R_3 - R_2 - R_3 = \frac{R_b R_c + R_c R_a}{R_a + R_b + R_c}$$

$$R_1 - R_2 = \frac{R_b R_c + R_c R_a}{R_a + R_b + R_c} \quad \textcircled{v}$$

~~$$eq \textcircled{1} - eq \textcircled{4} = R_1 + R_3 - R_2 - R_3 = \frac{R_b R_c + R_c R_a}{R_a + R_b + R_c}$$~~

$$eq \textcircled{2} + eq \textcircled{4} = R_1 + R_2 + R_1 - R_2 = \frac{2 R_b R_c}{R_a + R_b + R_c}$$

$$= 2 R_1 = \frac{2 R_b R_c}{R_a + R_b + R_c}$$


$$= R_1 = \frac{R_b R_c}{R_a + R_b + R_c} \quad \textcircled{v}$$

~~$$eq \textcircled{v} \text{ in } \textcircled{ii}$$~~

$$R_2 = R_b + \frac{R_b R_c + R_c R_a}{R_a + R_b + R_c}$$

Substituting R_1 in eq \textcircled{ii}
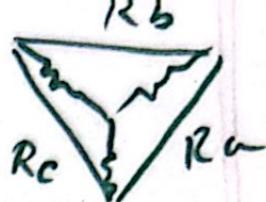
$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c} = \textcircled{vi}$$




$\Delta \rightarrow Y$ conversion

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$
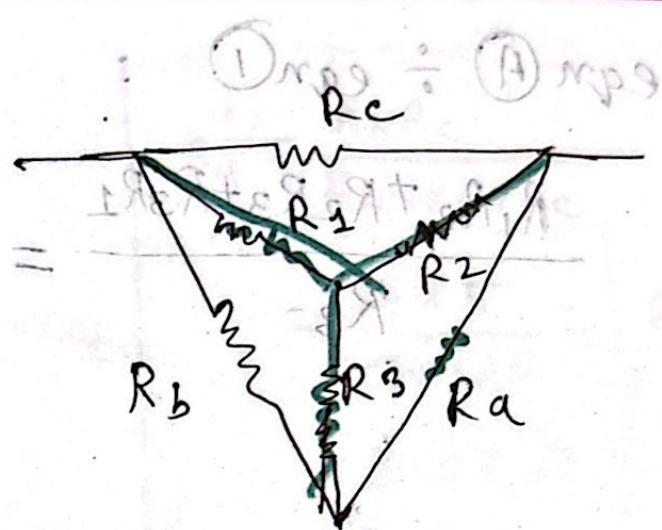
$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$



Δ conversion

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_b R_c (R_c R_a)}{(R_a + R_b + R_c)^2} + \frac{(R_c R_a)(R_a R_b)}{(R_a + R_b + R_c)^2}$$

$$= \frac{R_a R_b R_c^2 + R_a^2 R_b R_c + R_a R_b^2 R_c}{(R_a + R_b + R_c)^2}$$

$$= \frac{R_a R_b R_c (R_a + R_b + R_c)}{(R_a + R_b + R_c)^2}$$

$$= \frac{R_a R_b R_c}{R_a + R_b + R_c}$$

$$\therefore R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_a R_b R_c}{R_a + R_b + R_c}$$

eqn ① ÷ eqn ① :

$$\frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{\frac{R_a R_b R_c}{R_a + R_b + R_c}}{\frac{R_a + R_b}{R_a + R_b + R_c}} = R$$


$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{(R_1 + R_2)}$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1 + R_2 + R_3}$$


conversion of γ to V

由

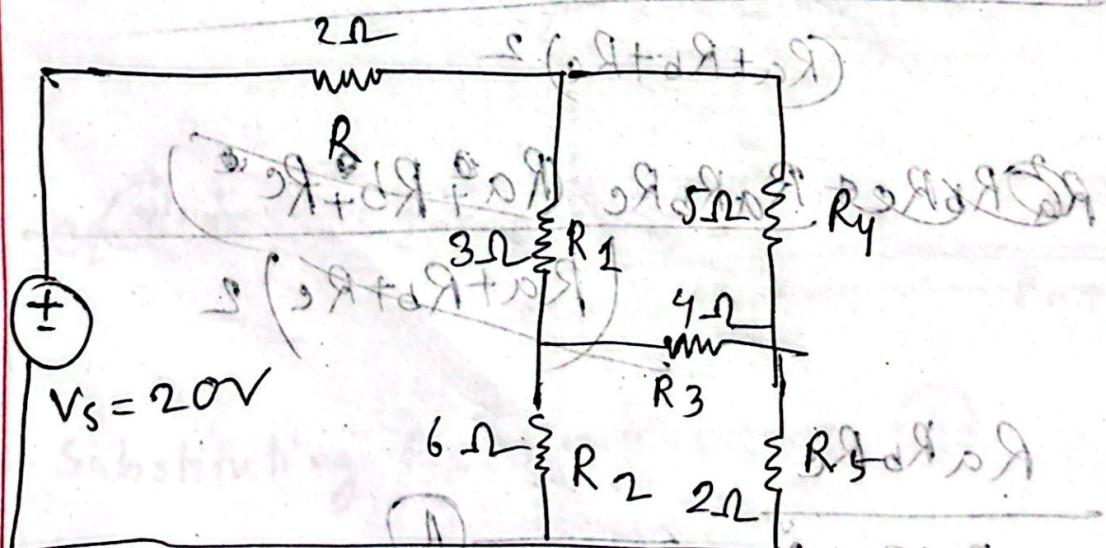

Find I

In V format,

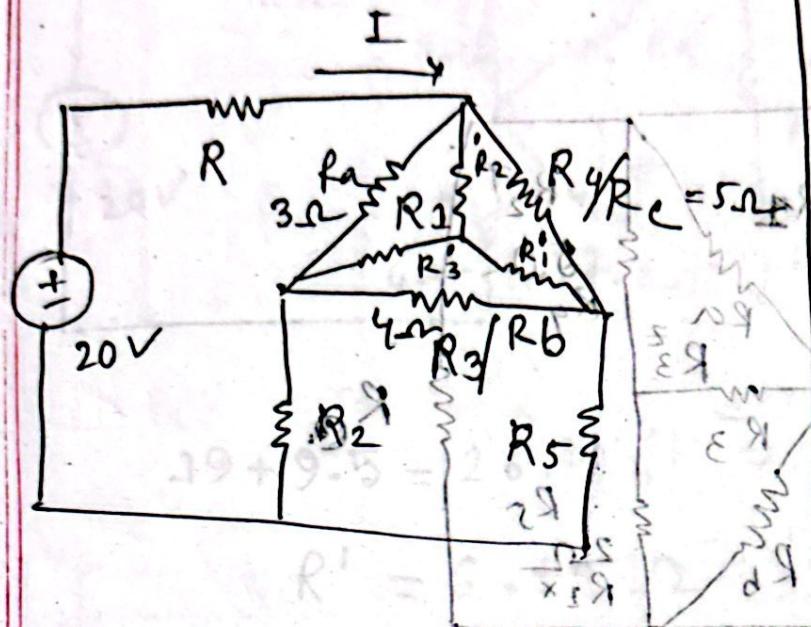

$$R'_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$


$$= \frac{4 \times 5}{3+4+5} = \frac{20}{12}$$

$$= 1.67 \Omega$$

$$R'_2 = \frac{R_a + R_c}{R_a + R_b + R_c} = \frac{15}{12} = 1.25 \Omega$$

$$R'_3 = \frac{12}{12} = 1 \Omega$$

Erase

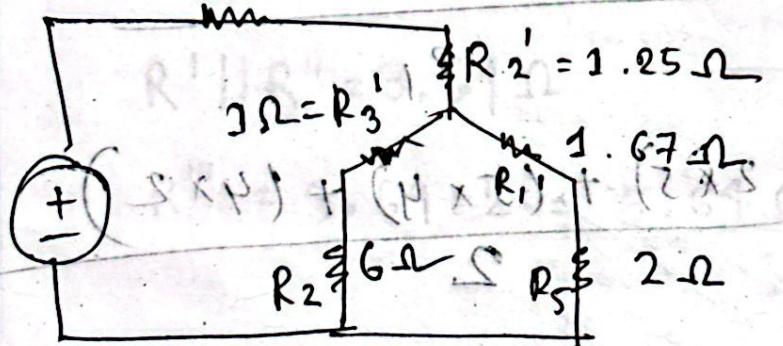

$$R'' = R_2 + R_3' = 6 + 1 = 7 \Omega$$

$$R''' = R_5 + R_1' = 2 + 1.67 = 3.67 \Omega$$

$$R^N = R_6 \cdot R'' \parallel R''' = \frac{7 \times 3.67}{7 + 3.67} = 2.407 \Omega$$

$$R^V = R^N + R'_2 = 3.65 \Omega$$

$$R^V = 2 + 3.65 = 5.65 \Omega$$

1 Ohm's law,

$$I = \frac{V_s}{R_{eq}} = \frac{20}{5.65} = 3.53 A$$

Form of $V \text{ nL}$

Y रूप संरचना,

$$I = \frac{V}{R} = \frac{V}{R_1 + R_2 + R_3}$$

$$\frac{V}{R_1} = \frac{2 \times 2}{2+3+4} = \frac{4}{9} V$$

$$\Delta F.d.c =$$

$$\frac{3R + R_1}{3R + R_1 + R_2} = \frac{3R + 2}{3R + 2 + 3} = \frac{3R}{5R} = \frac{3}{5}$$

$$S.E. = \frac{2R}{5R} = \frac{2}{5}$$

$$S.E. = \frac{2R}{5R} = \frac{2}{5}$$

$$S.E. = \frac{2R}{5R} = \frac{2}{5}$$

$$R_a = \frac{R_1^x + R_2^y + R_3^z + R_4^z + R_5^x}{5}$$

$$R_a = \frac{R_1^x + R_2^y + R_3^z + R_4^z + R_5^x}{5}$$

$$R_a = \frac{R_1^x + R_2^y + R_3^z + R_4^z + R_5^x}{5}$$

$$R_a = \frac{(2 \times 5) + (5 \times 4) + (4 \times 2)}{5} = 10 + 20 + 8 = 38$$

$$R_a = \frac{38}{5} = 7.6 \Omega$$

$$R_b = \frac{38}{R_2} = \frac{38}{5} = 7.6 \Omega$$

$$R_b = \frac{38}{R_2} = \frac{38}{5} = 7.6 \Omega$$

$$R_c = \frac{38}{4} = 9.5 \Omega$$

$$R_c = \frac{38}{4} = 9.5 \Omega$$

$$R_d = \frac{38}{2} = 19 \Omega$$

$$R_d = \frac{38}{2} = 19 \Omega$$

$$R_e = \frac{38}{1} = 38 \Omega$$


$$R_e = \frac{38}{1} = 38 \Omega$$

$$E = \frac{38}{38} = 1V$$

$$E = \frac{38}{38} = 1V$$

$$E = \frac{38}{38} = 1V$$

The Re Time

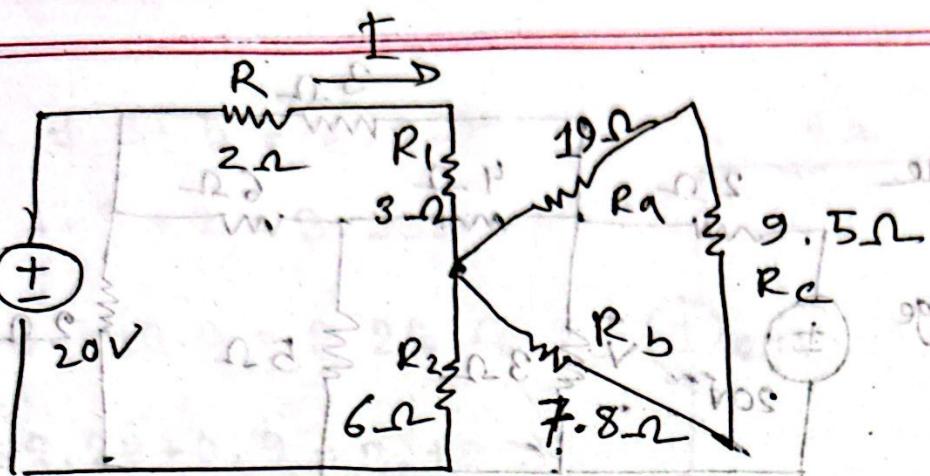


$$19 + 9.5 = 28.5$$

$$R' = 6 \parallel 12 \Omega$$


$$R'' = R_1 + R_2 = 9 \Omega$$

$$R' \parallel R'' = 3.61 \Omega$$

$$R''' = 3.61 + 2 = 5.61 \Omega$$

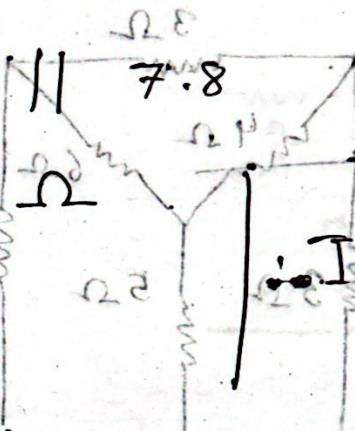
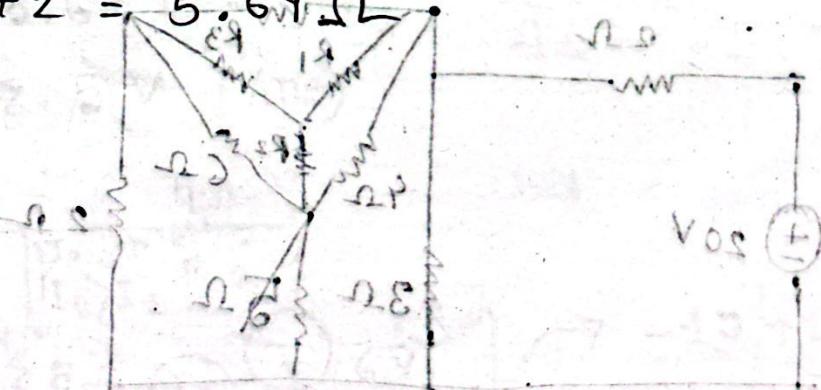
$$I = \frac{V_s}{R'''} = \frac{20}{5.61} = 3.54 \text{ A}$$



$$\Delta E.R = \frac{\delta \times \delta}{\delta + p + \epsilon} = 8.9$$


$$\Delta E.0 = \frac{\delta \times \delta}{\delta + p + \epsilon} = 19$$

$$\Delta E.1 = \frac{\delta \times p}{\delta + p + \epsilon} = 9$$



9/07/2024

Module III
Population and Environment

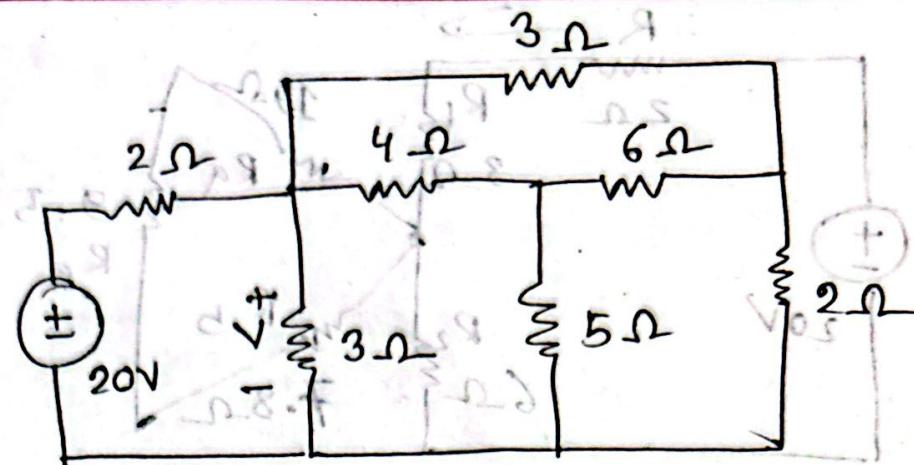Determine the current I and the voltage V.



Soln:

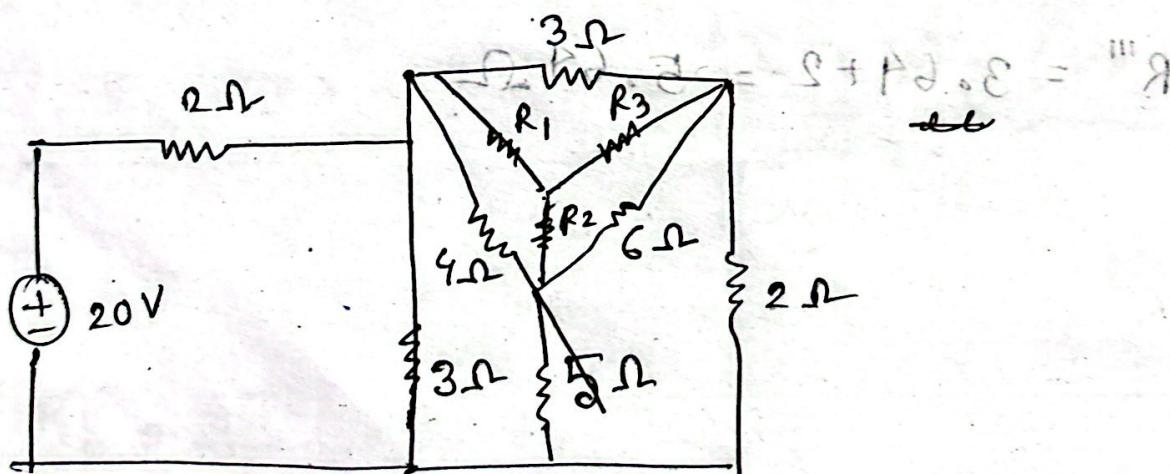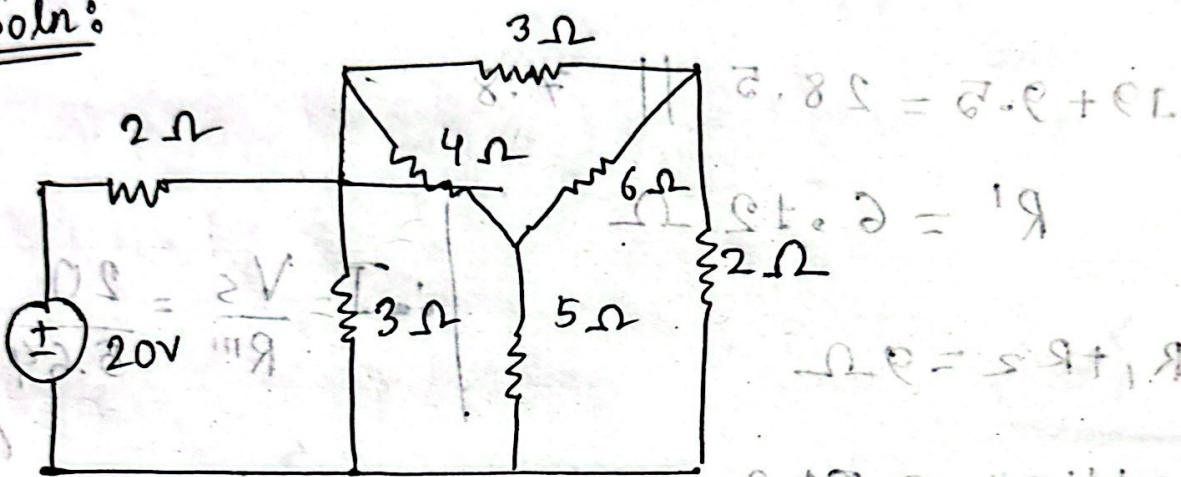

$$R_1 = \frac{3 \times 4}{3+4+6} = 0.9\Omega$$

$$R_2 = \frac{4 \times 6}{3+4+6} = 1.8\Omega$$

$$R_3 = \frac{3 \times 6}{3+4+6} = 1.3\Omega$$


$$1.8 + 5 = 6.8 \Omega$$

$$1.3 + 2 = 3.3 \Omega$$

$$6.8 \parallel 3.3 = 2.22 \Omega$$

$$2.22 + 0.9 = 3.12 \Omega$$

$$R' = 3.12 \parallel 3 = 1.53 \Omega$$

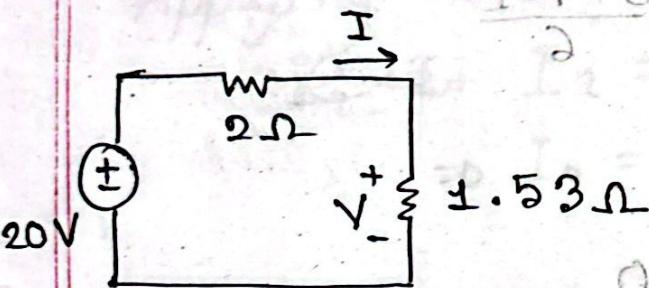


$$I = \frac{V_s}{R_{eq}} = \frac{20}{3.53} = 5.6 A \text{ (Ans)}$$

$$V = IR' = 5.6 \times 1.53$$

$$Ad \cdot S = 8.5 V \text{ (Ans)}$$

Mesh Analysis

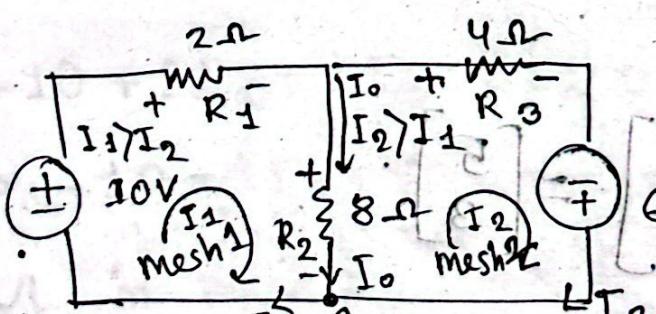

KVL in mesh 1,

$$-10 + 2I_1 + 8(I_1 - I_2) = 0$$

shared in both mesh

$$\begin{aligned} & -10 + 2I_1 + 8I_1 - 8I_2 = 0 \\ & \Rightarrow -10I_1 + 8I_2 = 10 \\ & \Rightarrow 5I_1 - 4I_2 = 5 \end{aligned}$$

(1)

For Mesh 2, KVL,

$$8(I_2 - I_1) + 4I_2 - 6 = 0$$

$$\Rightarrow 8I_2 - 8I_1 + 4I_2 = 6$$

$$\Rightarrow 12I_2 - 8I_1 = 6$$

$$28.2 = 6 + 8.1$$

$$28.8 = 0 + 8.1$$

$$25.2 = 6.8 || 8.2$$

$$\therefore 6I_2 - 4I_1 = 3 \quad \text{--- (ii)}$$

$$5I_1 - 4I_2 = 5 \quad \text{--- (i)}$$


$$6I_2 = 3 + 4I_1 \quad \therefore I_2 = \frac{3 + 4I_1}{6}$$

$$5I_1 - 4\left(\frac{3 + 4I_1}{6}\right) = 5$$

$$\Rightarrow 30I_1 - 12 - 16I_1 = 30$$

$$\Rightarrow 14I_1 = 42$$

$$\therefore I_1 = 3A$$

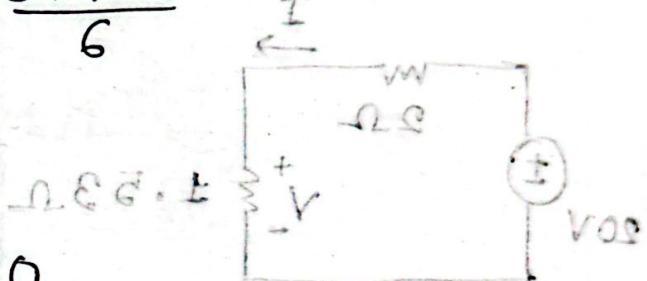

$$(emf) A 2.8 = \frac{0.2}{8 \times 8} = \frac{2V}{64\Omega} = I$$

$$(cd.) \therefore (5 \times 3) - 14I_1 = 5$$

$$(emf) V_{2.8} = 2.5A$$

Another way, Cramer's Rule,

$$0 = \begin{vmatrix} 5 & -4 \\ -4 & 6 \end{vmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 3 \end{bmatrix}$$

$$= \begin{vmatrix} 5 & -4 \\ -4 & 6 \end{vmatrix} \begin{bmatrix} 0 \\ 30 \end{bmatrix} = 140$$

$$\Delta = \begin{vmatrix} 5 & -4 \\ -4 & 6 \end{vmatrix}$$

$$= 30 - 16 = 140$$

$$\Delta_1 = \begin{bmatrix} 5 & -4 \\ 3 & 6 \end{bmatrix} = 42$$

$$\Delta_2 = \begin{bmatrix} 5 & 5 \\ -4 & 3 \end{bmatrix} = 35$$

$$I_1 = \frac{\Delta_1}{\Delta} = 3A \quad (\text{Ans})$$

$$I_2 = \frac{\Delta_2}{\Delta} = 2.5A \quad (\text{Ans})$$

Applying KCL in node A,

~~$I_1 = I_o + I_2$~~

~~$\Rightarrow I_o = I_1 - I_2 = 3 - 2.5 = 0.5A$~~

Find the mesh current

KVL in Mesh 1,

$$-10 + 2I_1 + 2(I_1 - I_2) = 0$$

$$\Rightarrow -10 + 2I_1 + 2I_1 - 2I_2 = 0$$


$$\Rightarrow -10 + 4I_1 - 2I_2 = 0 \quad ; \quad 4I_1 - 2I_2 = 10$$

KVL in mesh 2,

$$-5 + 2(I_2 - I_1) + 3I_2 + 4I_2 = 0$$

$$\Rightarrow -5 + 2I_2 - 2I_1 + 3I_2 + 4I_2 = 0$$
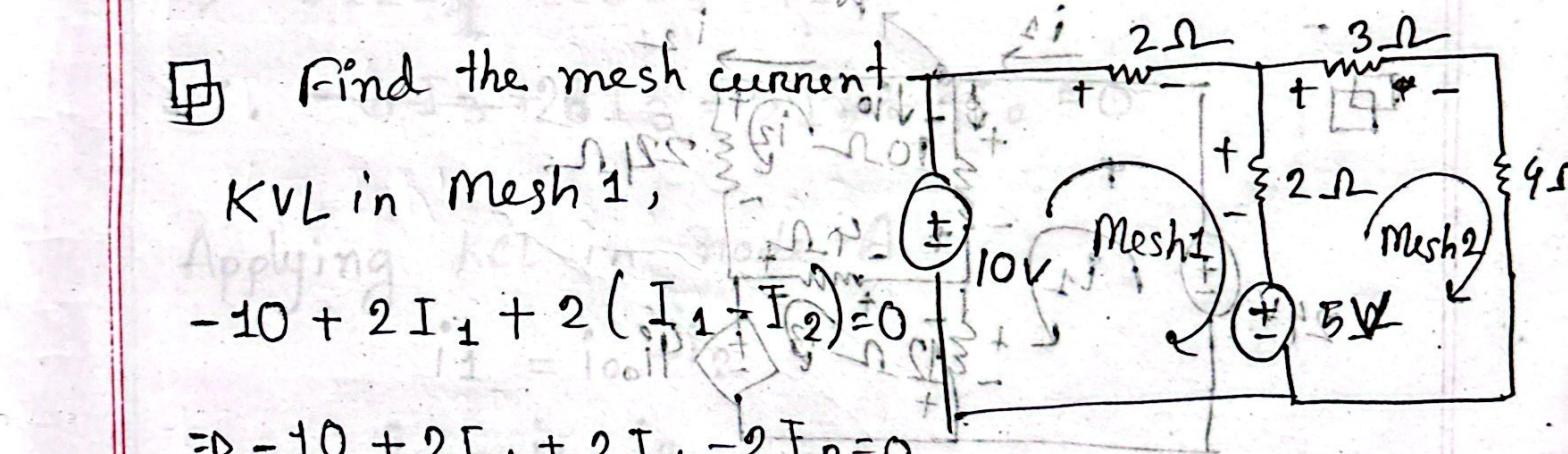
$$\therefore 5I_2 - 2I_1 + 9I_2 = 5 \quad ; \quad 9I_2 - 2I_1 = 5$$



$$5 \\ 9I_1 = 10 + 2I_2$$


$$\therefore I_1 = \frac{50 + 2I_2}{9}$$

$$9I_2 - 2\left(\frac{50 + 2I_2}{9}\right) = 5$$

$$\Rightarrow 30I_2 - 10 - 2I_2 = 20$$

$$\Rightarrow 28I_2 = 30 \quad \frac{30}{28} = 2.25A$$
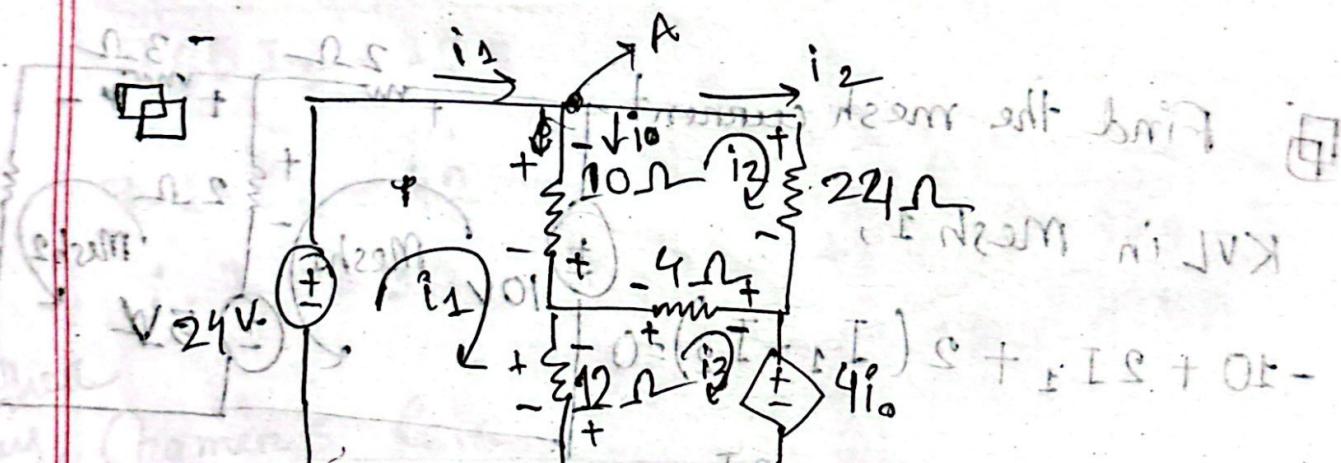
$$\therefore I_2 = \frac{2.25}{2} = 1.125A \quad I_1 = \frac{3.75}{2} = 1.875A$$



KVL in Mesh 1,

$$-24 + 10(I_1 - I_2) + 12(I_1 - I_3) = 0$$

$$\Rightarrow -24 + 10I_1 - 10I_2 + 12I_1 - 12I_3 = 0$$

$$\Rightarrow 22I_1 - 10I_2 - 12I_3 = 24$$

$$11I_1 - 5I_2 - 6I_3 = 12$$

KVL in Mesh 2,

$$(I_2 - I_3)$$

$$+10(I_2 - I_3) + 29I_2 + 4I_0 = 0$$

$$\Rightarrow +10I_2 + 10I_1 + 29I_2 + 4I_2 - 4I_3 = 0$$

$$\Rightarrow -10I_1 + 38I_2 - 4I_3 = 0$$

KVL in Mesh 3,

$$12(I_3 - I_1) + 4(I_3 - I_2) + 4I_0 = 0$$

$$\Rightarrow 12I_3 - 12I_1 + 4I_3 - 4I_2 + 4I_0 = 0$$

$$\Rightarrow -12I_1 + 16I_3 - 4I_2 + 4I_0 = 0$$

$$\therefore -6I_3 + 20I_3 - 2I_2 + 4I_0 = 0$$

Applying KCL in node A

$$i_1 = i_0 + i_2$$

$$i_0 = i_1 - i_2$$

Putting i_0 ,

$$2I_3 - 2I_2 + 4(I_1 - I_2) = 0$$

$$\Rightarrow 2I_3 - 2I_2 + 4I_1 - 4I_2 = 0$$

$$\therefore 4I_1 - 6I_2 + 2I_3 = 0$$

$$2I_1 - 8I_2 + I_3 = 0$$

$$-i_1 - i_2 + 2i_3 =$$

$$\Delta =$$

$$\begin{bmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & 1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta_1 = \begin{bmatrix} 12 & -5 & -6 \\ 0 & 19 & -2 \\ 0 & -1 & 2 \end{bmatrix} = 12(38 - 2)$$

$$\Delta_2 = \begin{bmatrix} 10 & 11 & 12 & -6 \\ -5 & 0 & 0 & 2 \\ 0 & -1 & 0 & 2 \end{bmatrix}$$

$$\Delta_3 = \begin{bmatrix} 11 & -5 & 12 \\ -5 & 19 & 0 \\ -1 & 1 & 0 \end{bmatrix} =$$

$$\Delta = I_1 = \frac{\Delta_1}{\Delta} = 1 = 1$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{12(38 - 2)}{12} = 36$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{12}{12} = 1$$

$$0 = \epsilon I + \epsilon I - \epsilon I$$

Find mesh currents

$$\text{mesh } 1, -15 + 3I_1 + 2I_2 = 0$$


$$\Rightarrow 5I_1 = 15 \therefore I_1 = 3A$$

KVL in mesh 2,

$$4I_2 + 3I_1 = 0$$

$$\Rightarrow 7I_2 = 0$$

\Rightarrow

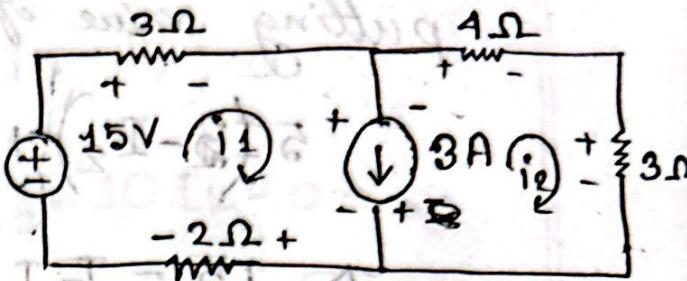

যদি mesh এর


অবস্থান current

source মধ্যে

গোড়াল supermesh

(পুরো circuit) mesh
এর ক্ষেত্রফল solve

বৃত্তবে

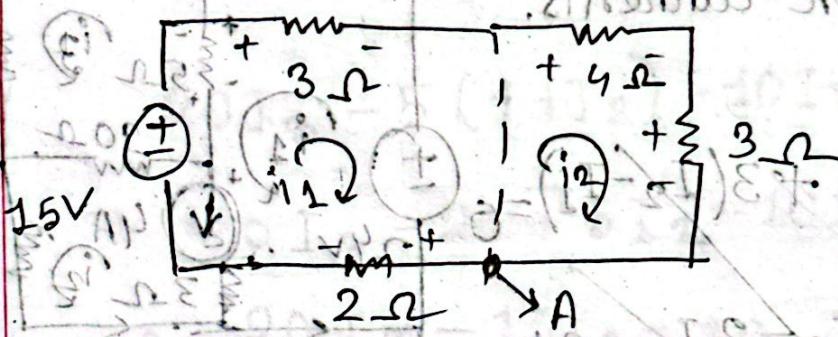

$$\begin{aligned} \text{KVL in Supermesh} & \left\{ -15 + 3I_1 + 4I_2 + 3I_2 + 2I_1 = 0 \right. \\ & \Rightarrow 5I_1 + 7I_2 = 15 \end{aligned} \quad \textcircled{1}$$

Applying KCL in node A,

$$I_s = I_1 + I_2$$

$$\Rightarrow I_1 + I_2 = 3A$$

$$\Rightarrow I_1 = 3 - I_2$$

AK

①

②

$$I_s = 12A - 3A + 3A \therefore$$

putting value of eq ⑪ in eq ②.

$$5(3 - I_2) + 7I_2 = 15$$

$$\Rightarrow 15 - 5I_2 + 7I_2 = 15$$

$$2I_2 = 0$$

$$\therefore I_2 = 0 \text{ A}$$

$$\therefore I_1 = 3 - 0 = 3 \text{ A}$$

Find mesh currents.

Supermesh 1

$$-24 + 5(I_3 - I_1) + 3(I_2 - I_1) = 6$$

$$\Rightarrow 5I_3 - 5I_1 + 3I_2 - 3I_1 = 24$$

$$\Rightarrow -8I_1 + 3I_2 + 5I_3 = 24 \quad \text{--- Eq ①}$$


Supermesh (i₃ + i₂),

$$5(I_3)$$


KVL in supermesh,

$$\therefore -24 + (5I_1 + 10I_2 - 15I_3) + 20I_2 = 0$$
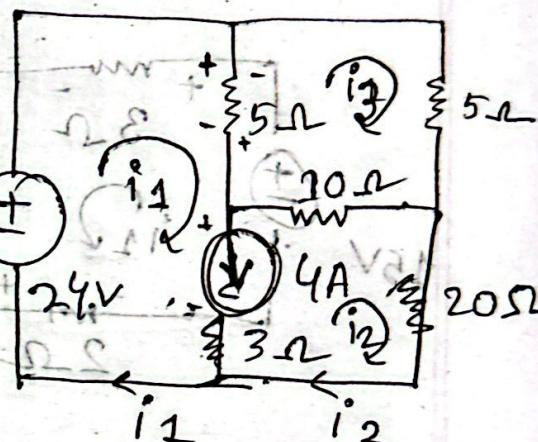
$$\therefore 5I_1 + 30I_2 - 15I_3 = 24 \quad \text{--- Eq ③}$$



Soln:

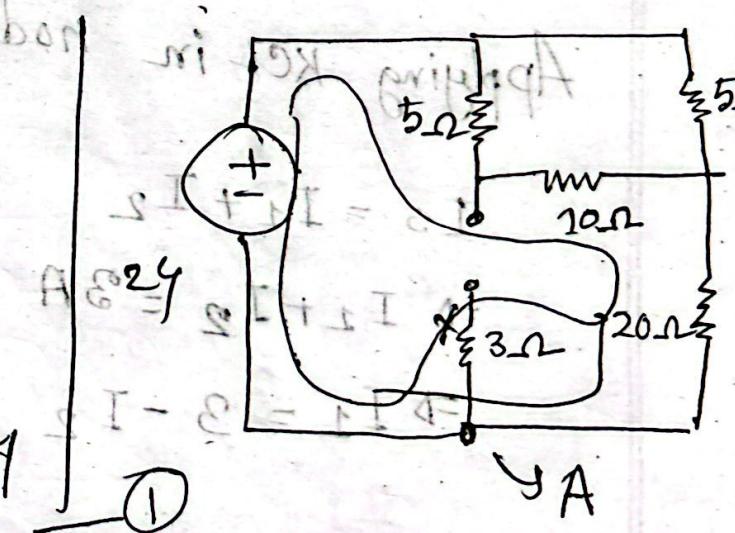

KVL, In mesh (3)

$$+5(I_3 - I_1) + 5I_3 + 10(I_3 - I_2) = 0$$

$$\Rightarrow 5I_3 - 5I_1 + 5I_3 + 10I_3 - 10I_2 = 0 \text{ ist.}$$

$$\Rightarrow 20I_3 - 5I_1 - 10I_2 = 0 \quad \text{III}$$

Applying KCL in node A;

$$\cancel{4+i_2+i_1}^{38} \quad 4+i_2 = i_1$$

$$20I_3 - 5(4+I_2) - 10I_2 = 0$$


$$\Rightarrow 20I_3 - 20 + 5I_2 = 10I_2 = 0 \quad | :10$$

$$\Rightarrow 20I_3 - 15I_2 = 20 \cdot 8 - 15 \cdot 8 \Rightarrow$$

$$\Rightarrow 4I_3 - 3I_2 = 1$$

$$\therefore I_2 = \frac{4 - 4I_3}{-3}$$
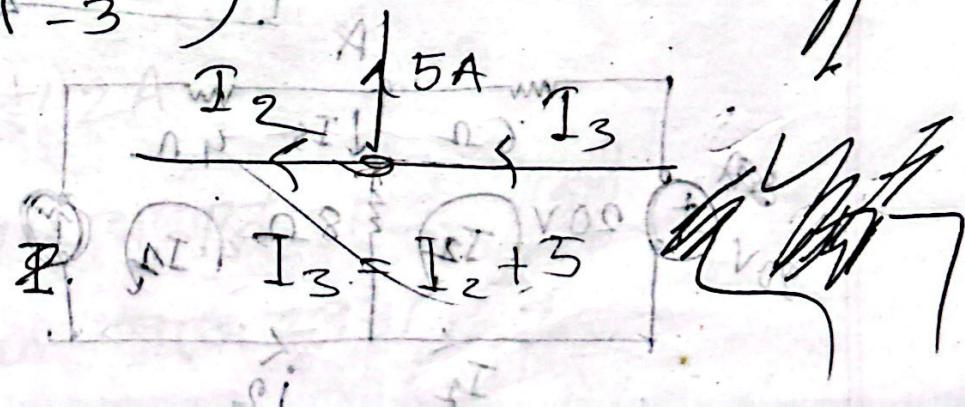
$$eq \textcircled{1} \quad 5I_1 + 30 \left(\frac{\cdot}{-3} \right)$$



15/07/29 - Quiz - Mesh Analysis পর্যবেক্ষণ

$$-15i_2 + 20i_3 = 20 \quad \textcircled{B}$$

$$35i_2 - 5i_3 = 4$$

$$\Rightarrow \cancel{-15} \quad I_2 = \frac{4 + 15I_3}{35}$$

$$-15\left(\frac{4 + 15I_3}{35}\right) + 20I_3 = 20$$



$$\Rightarrow -60 - 225I_3 + 20I_3 = 700 \quad \text{Wrong}$$

$$\Rightarrow -205I_3 = 760$$

$$\therefore I_3 = -3.7$$

$$i_2 =$$

Find mesh current

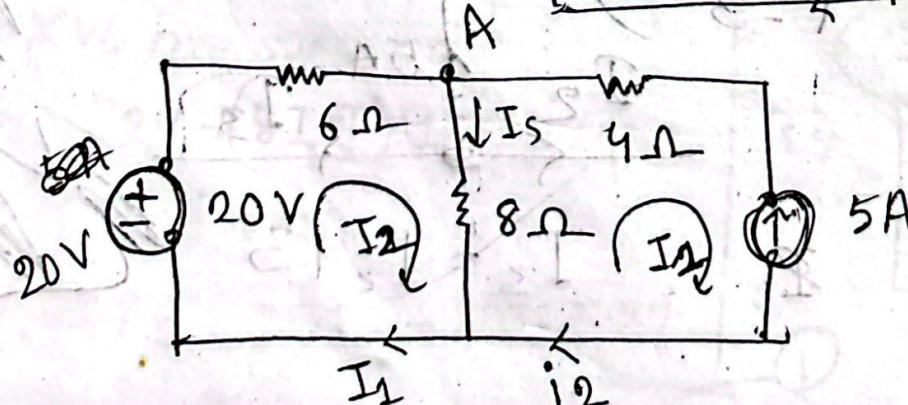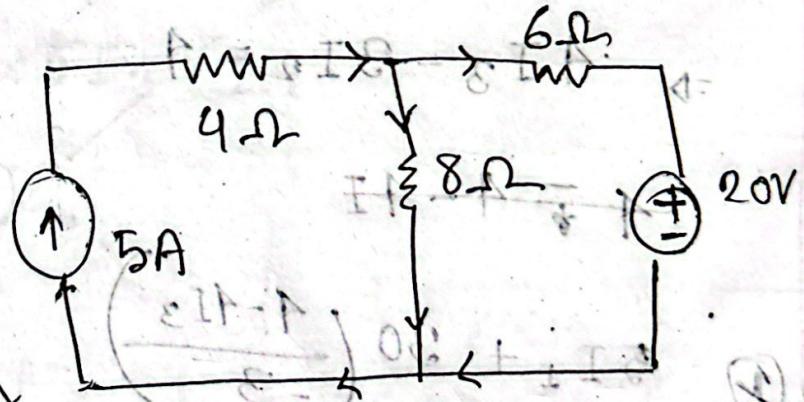

$$I_1 = 5A$$

KVL in mesh 1,

$$-20 + 6I_1 + 8(I_1 - I_2) = 0$$

$$\Rightarrow -20 + 6I_1 + 8I_1 - 8I_2 = 0$$

$$\Rightarrow -14I_1 - 8I_2 = 20 \quad \text{volt} \quad \text{Eqn 1}$$

KCL in node A,

$$I_1 = 5 + I_2$$

$$-14(5 + I_2) - 8I_2 = 20$$

$$\Rightarrow 70 + 14I_2 - 8I_2 = 20$$

$$\Rightarrow 6I_2 = -50$$

$$\therefore I_2 = -8.33 \text{ A}$$

$$I_1 = 5 + (-8.33) = -3.33 \text{ A}$$

KVL in mesh 2,

~~$$\text{Solt: } I_2 = 1 + 42A$$~~

I_s mesh এর মাধ্যমে ~~নেই~~ দ্বিতীয় circuit

open করতে হবে ~~না~~, $I_1 + I_2 = 0$

KVL in mesh 1,

$$-10 + 20I_1 + 10(I_1 - I_2) = 0$$

$$\Rightarrow -20I_1 + 10I_1 - 10I_2 = 10$$

$$\Rightarrow 30I_1 - 10I_2 = 10$$

$$\therefore 3I_1 - I_2 = 1 \quad \text{--- (1)}$$

KVL in mesh 2 and 3

Supermesh,

$$10(I_2 - I_1) + 30(I_2 - 3) + 10(I_3) = 0$$

$$\Rightarrow 10I_2 - 10I_1 + 30I_2 - 90 + 10I_3 = 0$$

$$\Rightarrow 40I_2 - 10I_1 + 10I_3 = 90$$

$$\Rightarrow -I_1 + 4I_2 + I_3 = 9$$


KCL in node A, $I_3 + I = i_2$

$$\Rightarrow I_3 + (-10) = i_2 \Rightarrow -10 = i_2$$


$$\Rightarrow I_3 = I_2 + 10 \quad \text{if } I_2 = -10$$

$$-I_1 + 4I_2 + (I_2 + 10) = 0 \quad \text{F.W. New}$$
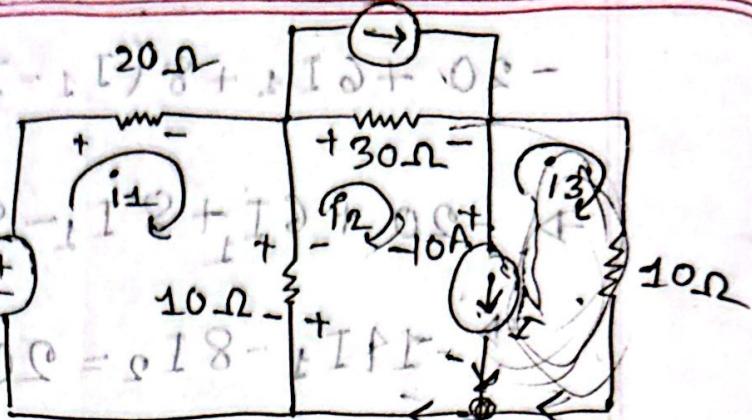
$$\Rightarrow -I_1 + 4I_2 + I_2 + 10 = 0 \quad \text{node}$$



(A) shown

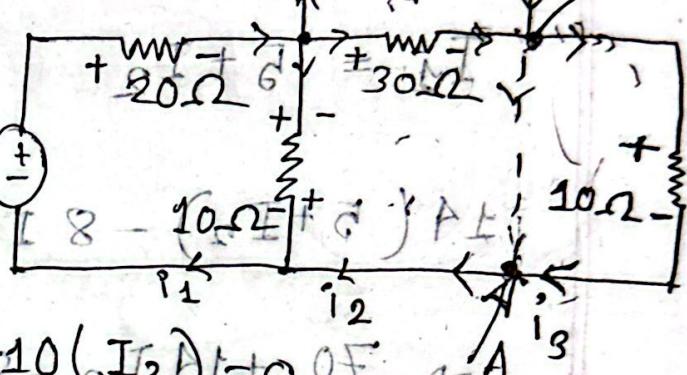

S' x s' z' z'

$$\Rightarrow 5I_2 + 10 = I_1$$

putting this value in eqn ①

$$3(5I_2 + 10) - I_2 = 1$$

$$\Rightarrow 15I_2 + 30 - I_2 = 1$$

$$\Rightarrow 14I_2 = 29$$

$$\therefore I_2 = 2.07 \text{ A}$$

$$3I_1 + 2.07 = 1$$

$$\therefore I_1 = 1.023 \text{ A}$$

$$\text{eqn ②, } I_1 - 1.023 + (4 \times 2.07) + I_3 = 9$$

$$\Rightarrow I_3 = 7.783 \text{ A}$$

$$+1 \quad -1 \quad -1$$

$$\begin{bmatrix} 3 & -1 & 0 \\ -1 & 4 & 1 \\ 0 & 1 & -1 \end{bmatrix}$$

$$-(-1)(1+4)$$

$$3(-4 + 1) - (-1)(1+4)$$

$$\Delta = 14$$


$$\Delta_1 = -4$$

$$\Delta_2 = 58$$

$$\Delta_3 = -39$$

$$1' 10^3$$

Lab 04

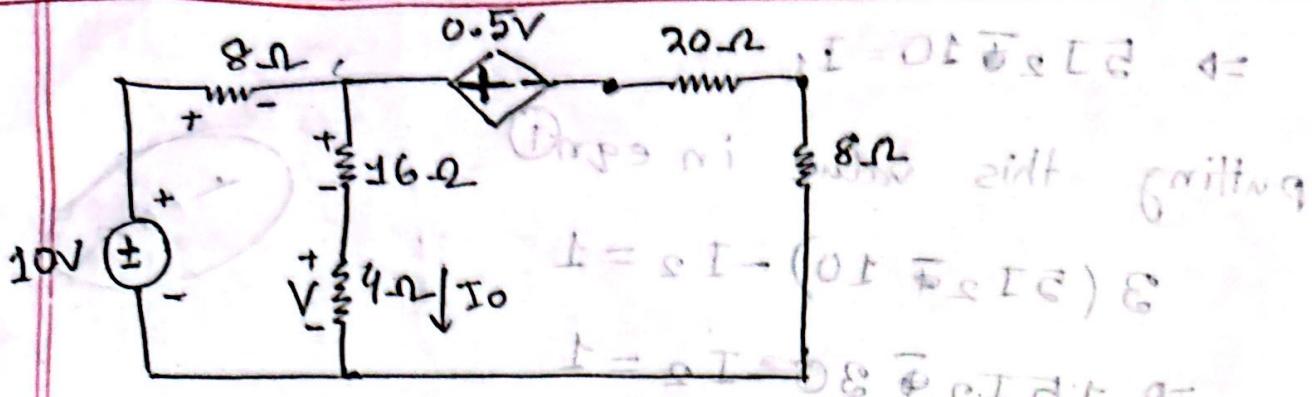

KVL in mesh 1,

$$-10 + 8I_1 + 16(I_1 - I_2) + 4(I_2 - I_1) = 0 \quad \therefore$$

$$\Rightarrow 8I_1 + 20I_1 - 20I_2 = 10$$

$$\Rightarrow 28I_1 - 20I_2 = 10 \quad \therefore \quad 14I_1 - 10I_2 = 5 \quad \text{Eqn 1}$$

KVL in mesh 2,


$$4(I_2 - I_1) + 16(I_2 - I_1) + 0.5 \times 4 + 20I_2 + 8I_2 = 0 \quad \text{Eqn 2}$$

$$\Rightarrow 4I_2 - 4I_1 + 16I_2 + 16I_1 + 28I_2 = -0.5 \quad \text{Eqn 2}$$

$$\Rightarrow -20I_1 + 48I_2 = 0 \quad \text{Eqn 2}$$

$$\Rightarrow 10I_1 + 24I_2 = \frac{0.5}{2} = 0.25 \quad \text{Eqn 1}$$
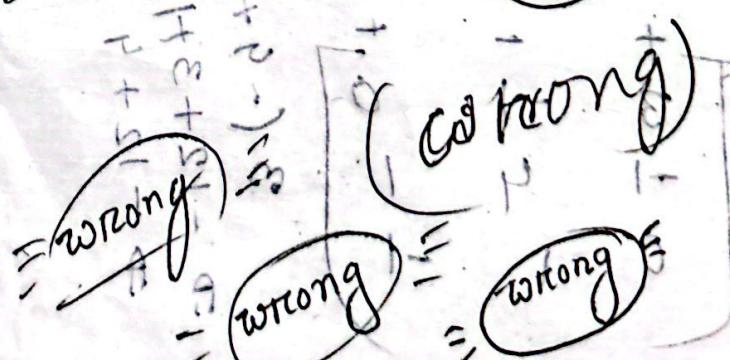
$$\Rightarrow 5I_1 + 12I_2 = 0.25 \quad \text{Eqn 1}$$



$$8 + 20 = 28 \Omega$$

$$16 + 4 \Omega = 20 \Omega$$

$$20 \parallel 28 = 11.67 \Omega = R'$$

~~$$V_{ab} = E - 11.67 + 8$$~~

$$\therefore R_{eq} \Rightarrow 19.67 \Omega$$

$$I = \frac{V_s}{R_{eq}} = \frac{10}{19.67} = 0.5 A$$

$$V_{ab} = IR' = 11.67 \times 0.5 = 5.835 V$$

~~KVL Applying KVL in mesh 1,~~

~~$$4I_1 - 10I_2 = 5$$~~

Applying KVL in mesh 2 ~~$0.5A(I_1 - I_2)$~~

~~$$4I_2 - 4I_1 + 16I_2 - 16I_1 + 0.5V_{ab} + 20I_2 + 8I_2 = 6$$~~


~~$$\Rightarrow -20I_1 + 48I_2 + (0.5 \times 5.835) = 0$$~~

~~$$\Rightarrow 20I_1 + 48I_2 = 2.9175$$~~

~~$$\Rightarrow 5I_1 + 12I_2 = 0.73$$~~

~~$$\Rightarrow -9I_1 + 23I_2 = 0$$~~
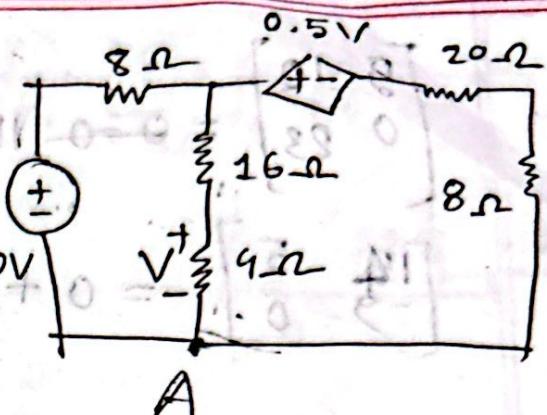
$$\begin{bmatrix} 14 & -10 \\ -5 & 23 \end{bmatrix} = 115 + 108 = 223$$



$$V_{ab} = 4I_0$$

$$= 4(I_1 - I_2)$$

KCL at node A

$$I_1 = I_0 + I_2$$

$$\therefore I_0 = I_1 - I_2$$

$$\begin{bmatrix} 3 & 10 \\ 0 & 23 \end{bmatrix} = 0 - 0 = 115$$

$$\begin{bmatrix} 14 & 5 \\ -5 & 0 \end{bmatrix} = 0 + 45 = 45$$

$$\therefore I_1 = \frac{\Delta_1}{\Delta} = \frac{10}{0.49} = 0.50A$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{0}{0.49} = 0.19A$$

$$V_{BE} = V_{CE} = 0.6 \times 10.1E = I_1 I = 0.50A$$

Pract

$$I_1 = \frac{10}{3+6} = 0.33A$$

$$I_2 = \frac{3.3 \times 10 \times 6}{3+6} = 6.67A$$

$$I_3 = \frac{16 \times 3}{6+3} = 0.111A$$

$$I_8 = I_1 + I_2 + I_3 = 0.33 + 6.67 + 0.111 = 7.01A$$


$$R_i = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$I_8 = I_1 + I_2 + I_3 = 0.33 + 6.67 + 0.111 = 7.01A$$

$$I_8 = I_1 + I_2 + I_3 = 0.33 + 6.67 + 0.111 = 7.01A$$

$$I_8 = I_1 + I_2 + I_3 = 0.33 + 6.67 + 0.111 = 7.01A$$

$$I_8 = 8.01A$$

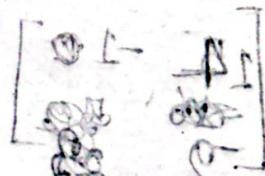

$$I_8 = 8.01A$$

c.w
15/07/2021

MID
24/7/24

(Quiz Ans)


$$R_2 \parallel R_3 = 2\ \Omega$$

$$R_5 \parallel R_6 = 4\ \Omega$$


$$1+2+3+4=22$$

V_A

①

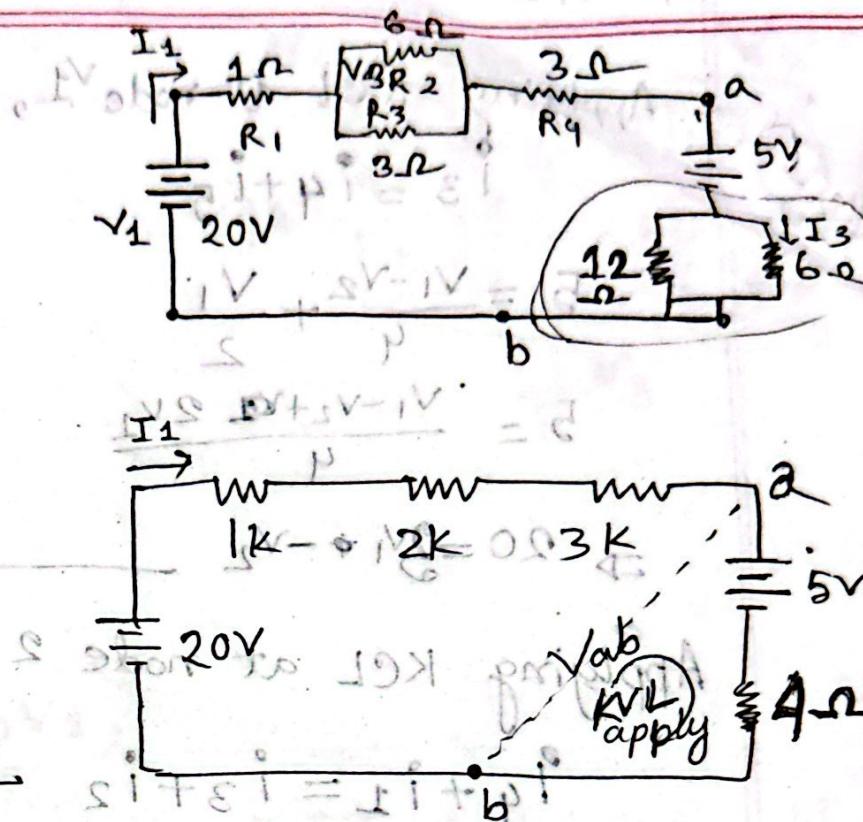

Nodal Analysis:

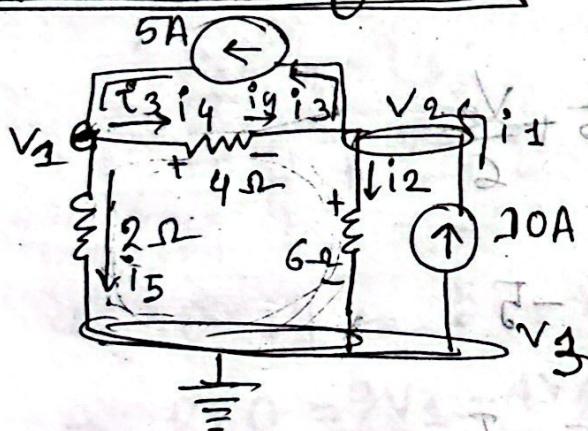

Applying Ohm's law,

$$i_1 = 10A$$

$$i_2 = \frac{V_2 - 0}{6} = \frac{V_2}{6}$$

$$i_3 = 5A$$

$$i_4 = \frac{V_1 - V_2}{4} = \frac{08}{4} = 2V$$

$$(i) V_{12}/i_5 = \frac{V_1 - 0}{9} = \frac{08}{9} = 0.8 + 0.8 = 1.6V$$

① node identification

② reference/ground node

③ Flow of current

$$i = \frac{V_{High} - V_{Low}}{R}$$

$$\begin{array}{l} \text{L4, b:} \\ \frac{2}{2,3} \\ 4x^2 = 12 \end{array}$$

Applying KCL at node V_1 ,

$$i_3 = i_4 + i_5$$

$$5 = \frac{V_1 - V_2}{4} + \frac{V_1}{2}$$

$$5 = \frac{V_1 - V_2 + 2V_1}{4}$$

$$\Rightarrow 20 = 3V_1 - V_2 \quad \boxed{1}$$

Applying KCL at node V_2 ,

$$i_4 + i_1 = i_3 + i_2$$

$$\Rightarrow \frac{V_1 - V_2}{4} + i_{10} = 5 + \frac{V_2}{6}$$

$$\Rightarrow \frac{V_1 - V_2}{4} - \frac{V_2}{6} = -5$$

$$\Rightarrow \frac{3V_1 - 3V_2 - 2V_2}{12} = -5$$

$$\Rightarrow 3V_1 - 5V_2 = -60$$

$$\boxed{1} \neq \boxed{11} \Rightarrow 20 + 60 = 3V_1 - V_2 - 3V_1 + 5V_2$$

$$\Rightarrow 80 = 4V_2$$

$$\Rightarrow V_2 = \frac{80}{4} = 20V \quad (\text{Ans})$$

$$3V_1 = 20 + 20 = 40 \quad \underline{\underline{V_1 = 13.33V \quad (\text{Ans})}}$$

Determine node voltage :-

Applying KCL


$$i_1 = 14A$$

$$i_2 = \frac{V_1}{4}$$

$$i_3 = \frac{V_1 - V_2}{5}$$

$$i_4 = \frac{V_2}{5}$$

$$i_5 = 7$$

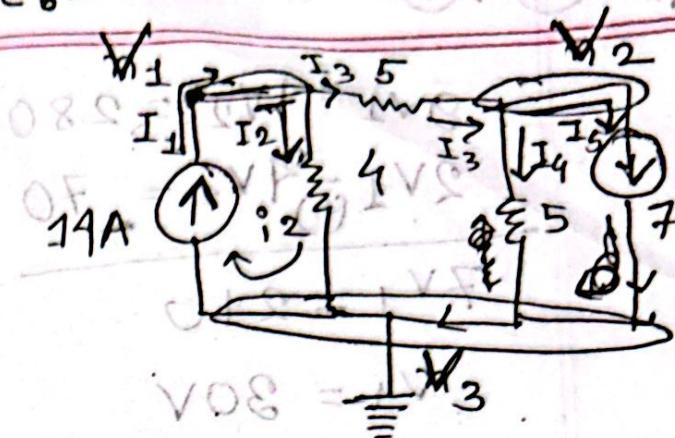

$$V_3 = 5V_2 - 5V$$

$$V_3 = 5V_2 - 4V$$

$$V_3 = 5V_2 - 5V$$

Applying KCL at V_1 ,

$$i_1 = i_2 + i_3$$

$$14 = \frac{V_1}{4} + \frac{V_1 - V_2}{5}$$

$$\Rightarrow 20 \times 14 = 5V_1 + 4V_1 - 4V_2$$

$$280 = 9V_1 - 4V_2$$

Applying KCL at V_2 ,

$$i_3 = i_4 + i_5$$

$$\Rightarrow \frac{V_1 - V_2}{5} = \frac{V_2}{5} + 7$$

$$V_1 - V_2 - V_2 = 35$$

$$\Rightarrow V_1 - 2V_2 = 35$$

$$\Rightarrow 2V_1 - 4V_2 = 70$$

$$AC = E$$

$$\frac{5V - 4V}{P} = C$$

$$\frac{V - 4V}{P} = C$$

$$\frac{5V - 5V}{P} = C$$

$$\frac{V - 5V}{P} = C$$

$$\frac{V - V}{P} = C$$

$$\frac{V - V}{P} = C$$

i - ii

$$9V_1 - 4V_2 = 280$$

$$-2V_1 - 4V_2 = -70$$

$$7V_1 = 210$$

$$V_1 = 30V$$

$$V_1 - 2V_2 = 35$$

$$\Rightarrow -2V_2 = 5$$

$$\therefore V_2 = -2.5V$$


 Determine node Voltages and ~~and~~ i_x .

$$i_1 = 3A$$

$$i_2 = \frac{V_1 - V_3}{4}$$

$$i_3 = \frac{V_2 - V_3}{4}$$

$$i_4 = \frac{V_2 - V_3}{8}$$

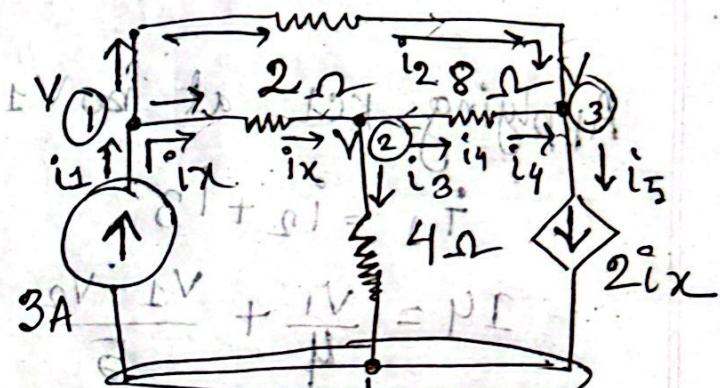

$$V_A - V_B + V_C = 1V + 1V = 2V$$

$$i_5 = 2i_x = 2 \frac{V_1 - V_2}{2} = V_1 - V_2$$

$$i_x = \frac{V_1 - V_2}{2} \text{ if } \pi = \sigma i$$

Apply KCL in node 1,

$$i_1 = i_2 + i_x$$

$$3 = \frac{V_1 - V_3}{4} + \frac{V_1 - V_2}{2}$$

$$12 = 2V_1 - 2V_2 + 2V_1 - 2V_2$$

$$F + \frac{2V}{6} = \frac{-2V - 1V}{3\sqrt{2}} - 2V_2 - V_3 = 12$$

$$5V_1 - 4V_2 - V_3 = 12 \quad (1)$$

Applying KCL in V_2 ,

$$i_x = i_3 + i_4$$

$$\Rightarrow \frac{v_1 - v_2}{2} = \frac{v_2}{4} - \frac{v_2 - v_3}{8}$$

$$\Rightarrow 8v_1 - 8v_2 = 2v_2 - v_2 + v_3$$

$$\Rightarrow -8v_1 - 9v_2 - v_3 = 0$$

$$4v_1 - 7v_2 + v_3 = 0 \quad \text{--- (II)}$$

Applying KCL at node 3,

$$i_2 + i_4 = i_5$$

$$\Rightarrow \frac{v_1 - v_3}{4} + \frac{v_2 - v_3}{8} = v_1 - v_2$$

$$2v_1 - 3v_2 + v_3 = 0 \quad \text{--- (III)}$$

$$\Delta = \begin{bmatrix} 3 & -2 & 1 \\ 4 & -7 & 1 \\ 2 & -3 & 1 \end{bmatrix} = 3(-7+3) + 2(4-2) - 1(-12+14) = -10$$

$$\Delta_1 = \begin{bmatrix} 12 & -2 & -1 \\ 0 & -7 & 1 \\ 0 & -3 & 1 \end{bmatrix} = 12(-7+3) = -48$$

$$\Delta_2 = \begin{bmatrix} 3 & 12 & -1 \\ 4 & 0 & 1 \\ 2 & 0 & 1 \end{bmatrix} = 3(0-0) + 12(4-2) - 1(0-0) = -24$$

$$\Delta_3 = \begin{bmatrix} 3 & -2 & 12 \\ 4 & -7 & 0 \\ 2 & -3 & 0 \end{bmatrix} = 12(-12+14) = 24$$



$V_S \rightarrow$ short circuit
 $I_S \rightarrow$ open "

$$V_1 = \frac{-48}{-10} = 4.8 V$$

$$V_2 = \frac{-24}{-10} = 2.4 V$$


$$V_3 = \frac{24}{-10} = -2.4 V$$

$$i_x = \frac{V_1 - V_2}{2} = 1.2 A$$

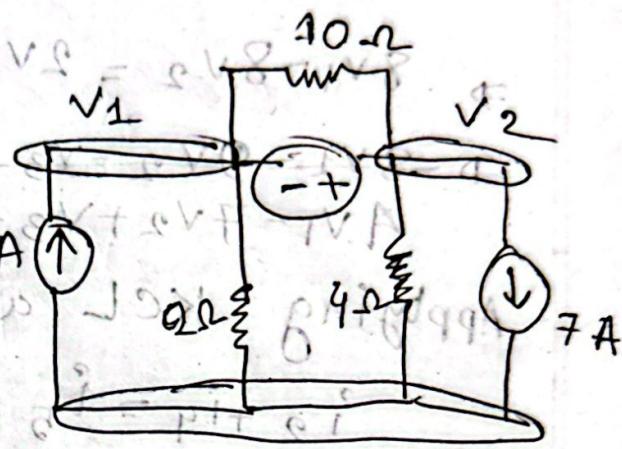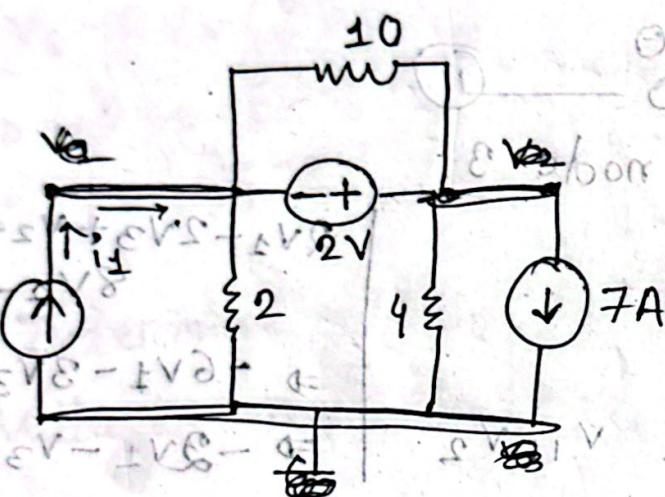

Step Solution:

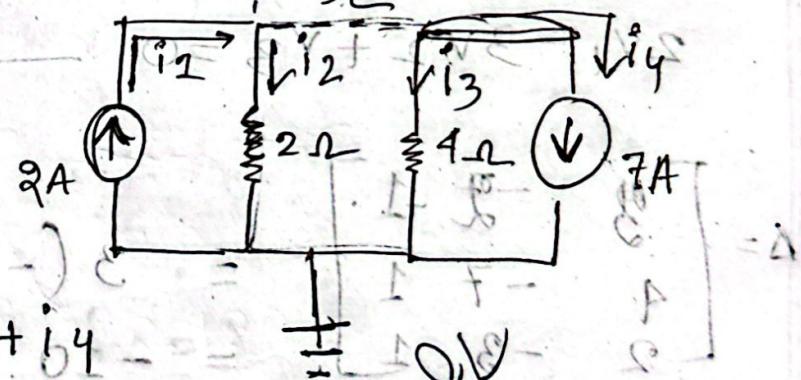Applying KCL in Supernode $\Rightarrow i_1 = i_2 + i_3 + i_4$



$$2 = i_2 + i_3 + 7$$

$$\Rightarrow \frac{i_1}{2} + \frac{\sqrt{2}}{4} = -5$$

$$\begin{bmatrix} 1 & 1 & 1 & 0 \\ 0 & 2 & 0 & 0 \\ 0 & 0 & 4 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} = 1 A$$

$$(0+0) \leftarrow (2V_1 + V_2) = -20 \begin{bmatrix} 1 & 1 & 1 & 0 \\ 0 & 2 & 0 & 0 \\ 0 & 0 & 4 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} \quad (1)$$

$$PS = (1E + 2E -) S r = \begin{bmatrix} 2E & 1E & 1E & 0 \\ 0 & 4E & 0 & 0 \\ 0 & 0 & 4E & 0 \\ 0 & 0 & 0 & 1E \end{bmatrix} = \varepsilon^A$$

Applying KVL in loop 1,

$$-V_1 - 2 + V_2 = 0$$

$$\Rightarrow -V_1 + V_2 = 2 = 0 \quad (1)$$

eq ① - eq ②,

$$2V_1 + V_2 = -20$$

$$(+) -V_1 + V_2 = -2$$

$$\cancel{V_1 + 2V_2 = -22}$$

$$3V_1 = -22$$

$$\therefore V_1 = -\frac{22}{3} = -7.33V$$

Putting $V_1 = -7.33V$ in eq (1)

$$-(-7.33) + V_2 = 2$$

$$\Rightarrow V_2 = 2 - 7.33 = -5.33V \text{ (Ans)}$$

* * *

২টি Node এর মাঝেরেন V_s হিসেবে Super node

* * *

২টি mesh এর মাঝের I হিসেবে Super mesh

AP. Q.

$\frac{E \times 2 - E}{E + E} = 1$

E



19/08/29
Revision

Determine I_1, I_2, I_3, I_4 & V_1, V_2

$$I_4 \text{ & } V_1, V_2$$

30x

4K

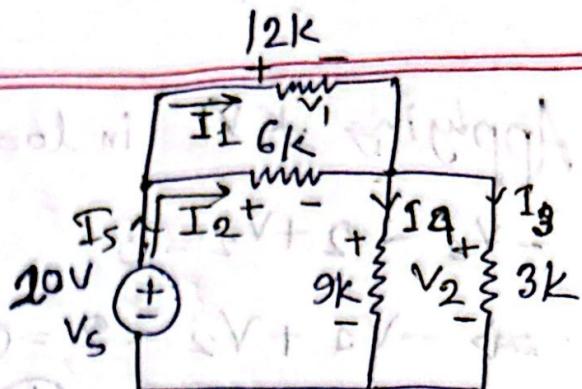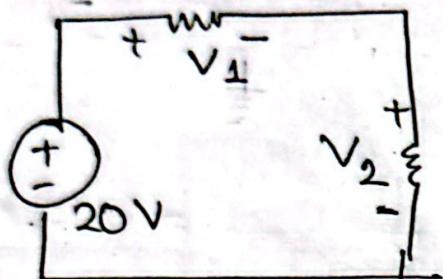

$$V_1 = \frac{20 \times 4}{4 + 2.25} = 12.8V$$

$$V_2 = \frac{20 \times 2.25}{4 + 2.25} = 7.2V$$

$$R_{eq} = 6.25K = \frac{20}{8} = 2.5V$$

$$I = \frac{20}{6.25} = 3.2A$$

$$(enA) V \in E. \vec{d} = E \cdot F - S = 5V$$



$$\checkmark I_1 = \frac{3.2 \times 6}{12+6} = 1.067A$$

$$\checkmark I_2 = \frac{3.2 \times 12}{12+6} = 2.13A$$

$$I_3 = \frac{3.2 \times 3}{3+9} = 0.8A$$

$$I_4 = \frac{3.2 \times 9}{3+9} = 2.4A$$

Determine, V_1, V_2, V_3 & I_1, I_2, I_3

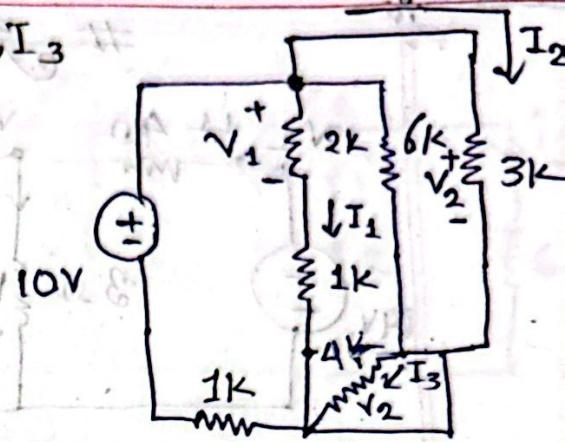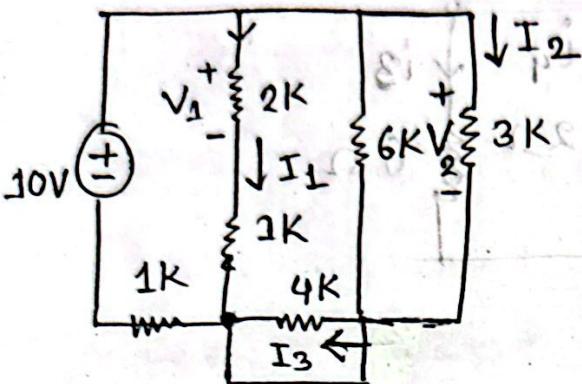


$$R_{eq} = 1 + ((2+1) \parallel (3 \parallel 2))$$

$$= 1 + (3 \parallel 2)$$


$$= 1 + 1 \cdot 2$$

$$= 2 \cdot 2 - 2$$
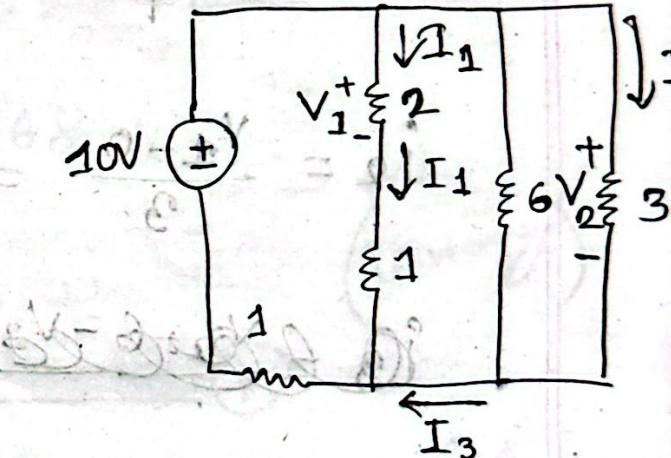
$$I_s = \frac{V_s}{R_{eq}} = \frac{10}{2 \cdot 2} = 4.54 A$$



$$V_1 = I_1 \times 2 = 3.6 A \text{ V}$$

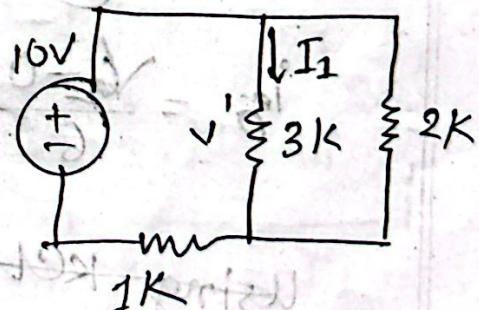


$$I_1 = \frac{4.54 \times 2}{3+2} = 1.816 A$$

$$I_2 = 2.724 A = \frac{4.54 \times}{6+}$$

$$V' = I_1 \times 3 = 5.4$$

10K hour

Determine V_1, V_2, V_3 & I_1, I_2, I_3

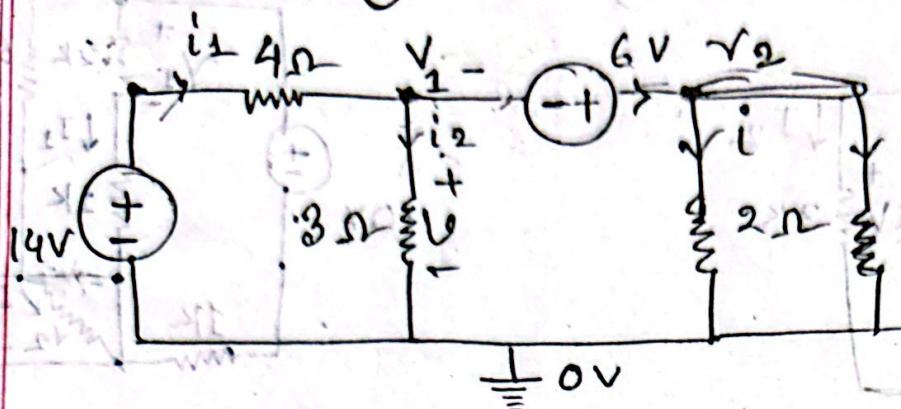

$$i_1 = \frac{14 - V_1}{4\Omega} = \frac{14 - V_1}{(4\Omega) \parallel (3\Omega) + 1} = \frac{14 - V_1}{5\Omega}$$

$$i_2 = \frac{V_1 - 0}{3\Omega} = \frac{V_1}{3\Omega}$$

~~$$i_3 = V_2 - 0$$~~

~~$$i = i_3 = \frac{V_2}{2\Omega}$$~~

~~$$i_3 = \frac{V_2 - 0}{6\Omega} = \frac{V_2}{6\Omega}$$~~

Using KCL at node 1: $i_1 + i_2 = i_3$

$$i_1 + i_2 = \frac{14 - V_1}{5\Omega} + \frac{V_1}{3\Omega} = \frac{V_1 + 42}{15\Omega}$$


$$\frac{V_1 + 42}{15\Omega} = \frac{V_2}{6\Omega} = \frac{V_2}{2\Omega}$$

3.13.6.2
1,2,2

KCL at supernodes,

$$i_1 = i_2 + i_3 + i$$
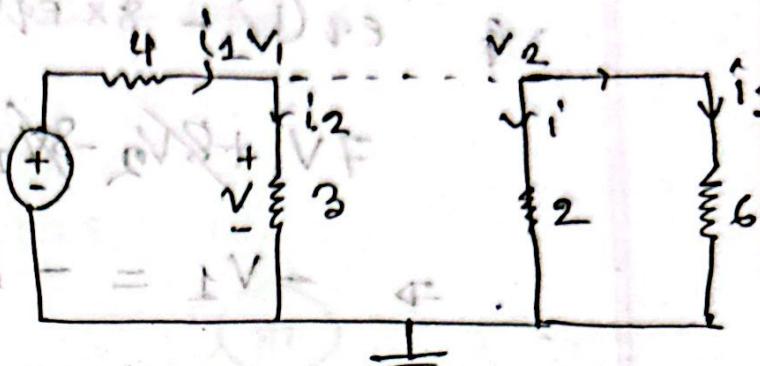
$$\Rightarrow \frac{14 - V_1}{4} = \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2}{2}$$



$$\Rightarrow \frac{14 - V_1}{4} = \frac{4V_1 + 2V_2 + 6V_3}{12}$$

$$\Rightarrow 168 - 12V_1 = 16V_1 + 8V_2 + 24V_3$$

$$\Rightarrow -28V_1 - 32V_2 = -168$$

$$\Rightarrow 14V_1 + 16V_2 = 84$$

(wrong)

$$\Rightarrow 7V_1 + 8V_2 = 42$$

$$\Rightarrow (i_1 - i_2) \cdot 4 + i_1 \cdot 3 + i_2 \cdot 6 = 42$$

KVL in loop 1,

$$= V_1 - 6 + 2I = 0$$

$$\Rightarrow -3I =$$

$$-V_1 - 6 + V_2 = 0$$

$$\Rightarrow V_2 - V_1 = 6$$

$$\Rightarrow (i_1 - i_2) \cdot 2 - 2(i_1 - i_2) \cdot 3 + (i_1 - i_2) \cdot 6 = 6$$


(R) V_8 (KVL)
current in +
out - } mesh analysis

$\Rightarrow \text{eq } ① - 8 \times \text{eq } ⑪$, add both equations to get

$$7\text{V}_1 + 8\text{V}_2 - 8\text{V}_2 - 8\text{V}_1 = 42 - 48 \Rightarrow -6$$

$$\Rightarrow -\text{V}_1 = -6 \quad \frac{\text{V}}{4} + \frac{\text{V}}{3} + \frac{\text{V}}{6} = \frac{\text{V} - 12}{3}$$
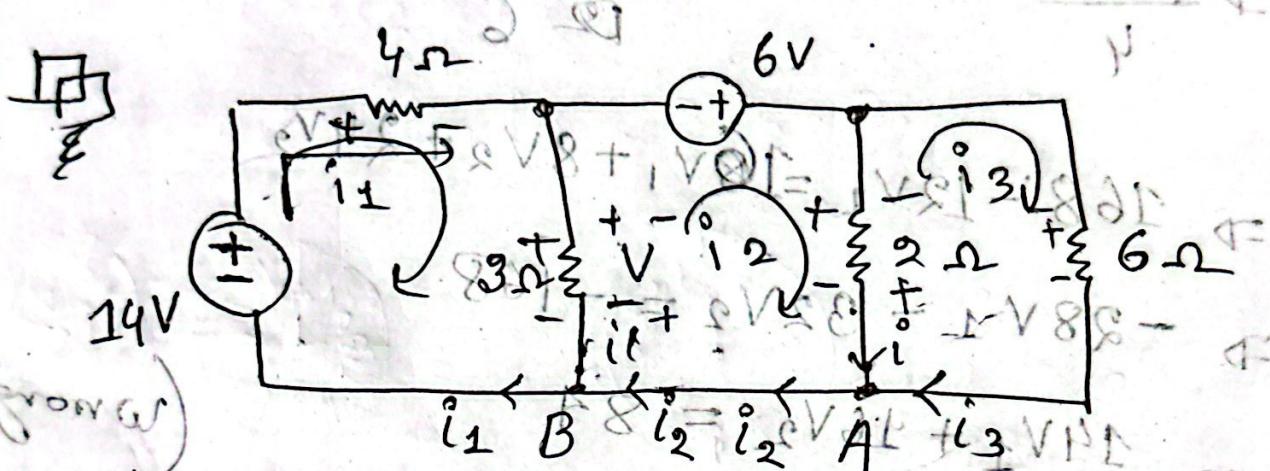
$$\therefore \text{V}_1 = 6 \quad \frac{\text{V}}{4} + \frac{\text{V}}{3} + \frac{\text{V}}{6} = \frac{\text{V} - 12}{3}$$



KVL in mesh 1,

$$-14 + 4i_1 + 3(i_1 - i_2) = 0$$

$$\Rightarrow -14 + 4i_1 + 3i_1 - 3i_2 = 0$$

$$\Rightarrow 7i_1 - 3i_2 = 14$$

KVL in mesh 2,

$$+ 3(i_2 - i_1) - 6 - 2(i_2 - i_3) = 0$$

$$\Rightarrow 3i_2 - 3i_1 + 2i_2 - 2i_3 = 6$$

$$\Rightarrow -3i_1 + 5i_2 + 2i_3 = 6 \quad \text{--- (11)}$$

KVL in mesh 3,

$$2i_3 - 2i_1 + 6i_3 - \cancel{2i_2} = 0$$

$$\Rightarrow 8i_3 - 2i_1 = 0 \quad \text{--- (11)}$$

$$\begin{bmatrix} 7 & -3 & 0 \\ -3 & 5 & -2 \\ -2 & 0 & 8 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 14 \\ 6 \\ 0 \end{bmatrix}$$

$$\Delta = 280 - 84 = 196$$

$$\Delta_1 = \begin{bmatrix} 14 & -3 & 0 \\ 6 & 5 & -2 \\ 0 & 0 & 8 \end{bmatrix} = 560 + 144 = 704$$

$$\Delta_2 = \begin{bmatrix} 7 & 14 & 0 \\ -3 & 6 & -2 \\ -2 & 0 & 8 \end{bmatrix} = 336 + 392 = 728$$

$$\Delta_3 = \begin{bmatrix} 7 & -3 & 14 \\ -3 & 5 & -2 \\ -2 & 0 & 8 \end{bmatrix} = 0 + 36 + 140 = 176$$

$I_1 = 3.6 A$	$I_2 = 3.7 A$	$I_3 = 0.89 A$
---------------	---------------	----------------

KCL in node A,

$$i_2 = i + i_3$$

$$i = i_2 - i_3 = 2.8A$$


② Apply KCL at node B

$$i^1 + i_2 = i^1$$

$$\Rightarrow i^1 = i_1 - i_2 = -3.6 - 3.7 = -0.13A$$



10:10

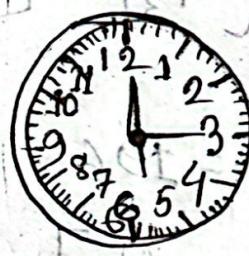

Clock

Wall Mounted Watch

Clock, Wall Clock

$$OF = PV_1 + QV_2 =$$

$$\begin{bmatrix} 0 & P_1 & F \\ S & 0 & 0 \end{bmatrix} = \Delta$$

$$SCE = SCE + QEE =$$

$$\begin{bmatrix} 0 & P_1 & F \\ S & 0 & E \\ 8 & 0 & 0 \end{bmatrix} = \Delta$$

$$QFI = QP_1 + QEE + 0 =$$



$$\begin{bmatrix} P_1 & E & F \\ 0 & 0 & E \\ 0 & 0 & 0 \end{bmatrix} = \Delta$$

$$AE8.0 = \epsilon I$$

$$AF.E = \epsilon I$$

$$AD.E = \epsilon I$$

Final

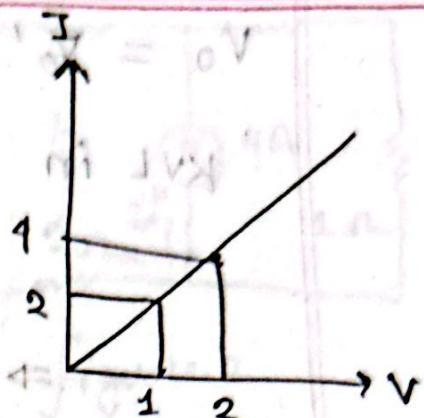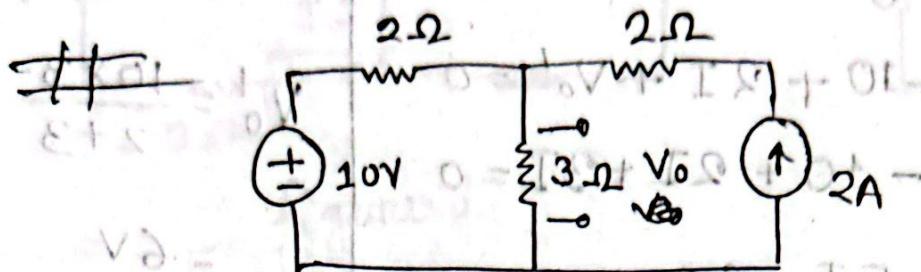Superposition (Theorem)(Only Applicable for) ***
Linear circuitDetermine V_o voltage: (using superposition)

প্রতিযানু একটি source নিয়ে কাজ করবে,

$$V_s \rightarrow \left\{ \begin{array}{l} \text{source} \\ \text{circuit} \end{array} \right.$$

$$I_s \rightarrow \left\{ \begin{array}{l} \text{source} \\ \text{circuit} \end{array} \right.$$

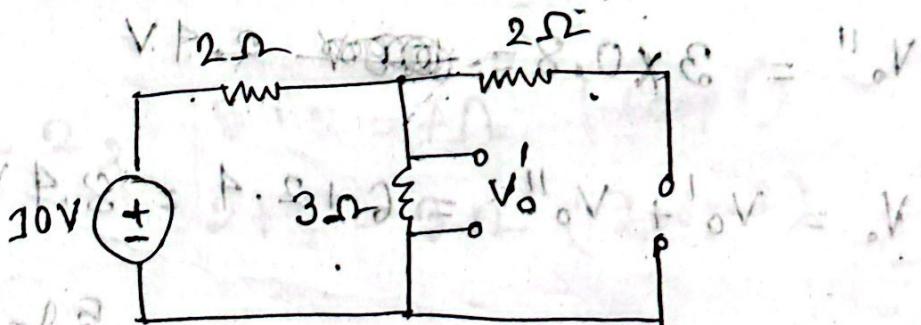
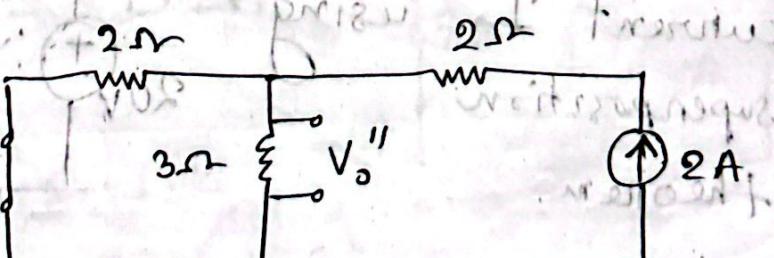
Step 1:
(only)Figure 11. ~~arrange~~Step 2:

Figure 9

PG09 | 80/85

(initial) voltage source

$$V_o = V_o' + V_o''$$

KVL in figure 1,

$$-10 + 2I + V_o' = 0$$

$$\Rightarrow -10 + 2I + 3I = 0$$

$$\Rightarrow 5I = 10$$

$$\therefore I = 2A$$

$$V_o' = 3 \times 2 = 6V$$


CDR in figure 2,

$$I_{o''} = \frac{2 \times 2}{2+3} = 0.8A$$

$$V_o'' = 3 \times 0.8 = 2.4V$$

$$\therefore V_o = V_o' + V_o'' = 6 + 2.4 = 8.4V \quad (\text{Ans})$$

Determine the current I_o using superposition theorem

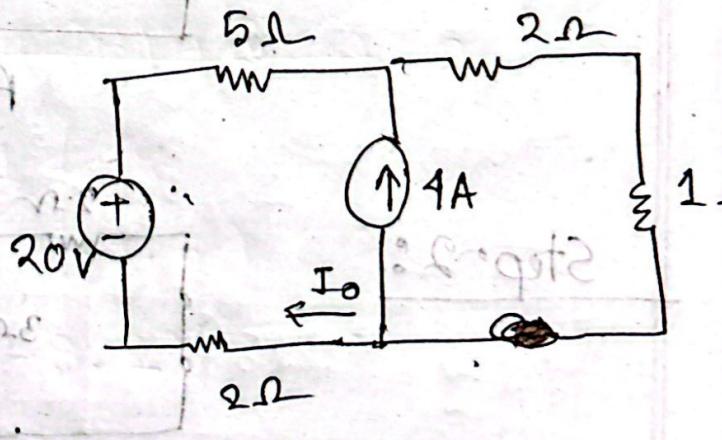

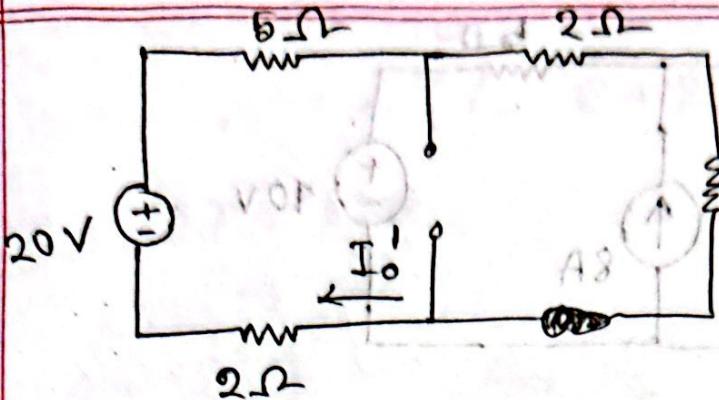


figure 1

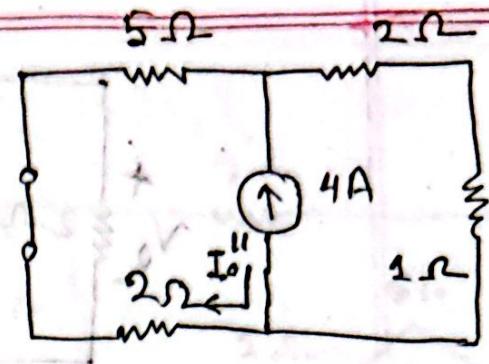


figure 2

$$I_o = \frac{V}{R}$$

$$\cancel{V_o} \times \cancel{R} \therefore V' = \frac{20 \times 2}{10}$$

$$= 4V$$

$$I_o' = \frac{V'}{R} = \frac{4}{2} = 2A$$


at fit in 8.0V

in figure 2,

$$5 + 2 = 7\Omega \text{ (loop 1)}$$

$$2 + 1 = 3\Omega \text{ (loop 2)}$$
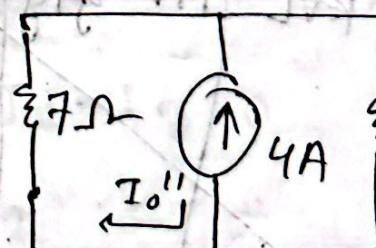
$$I_o'' = \frac{-4 \times 3}{7+3} = -1.2A$$



$$I_o = I_o' + I_o'' = 2 - 1.2$$

$$I_o = 0.8A \text{ (Ans)}$$

Using superposition theorem, find V_o

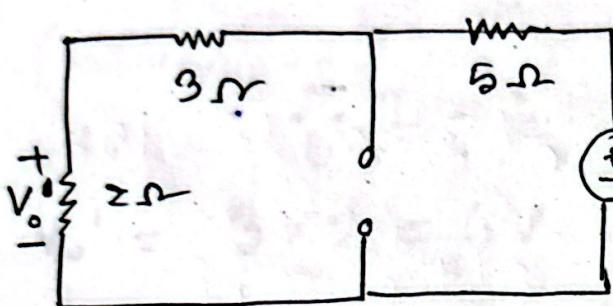
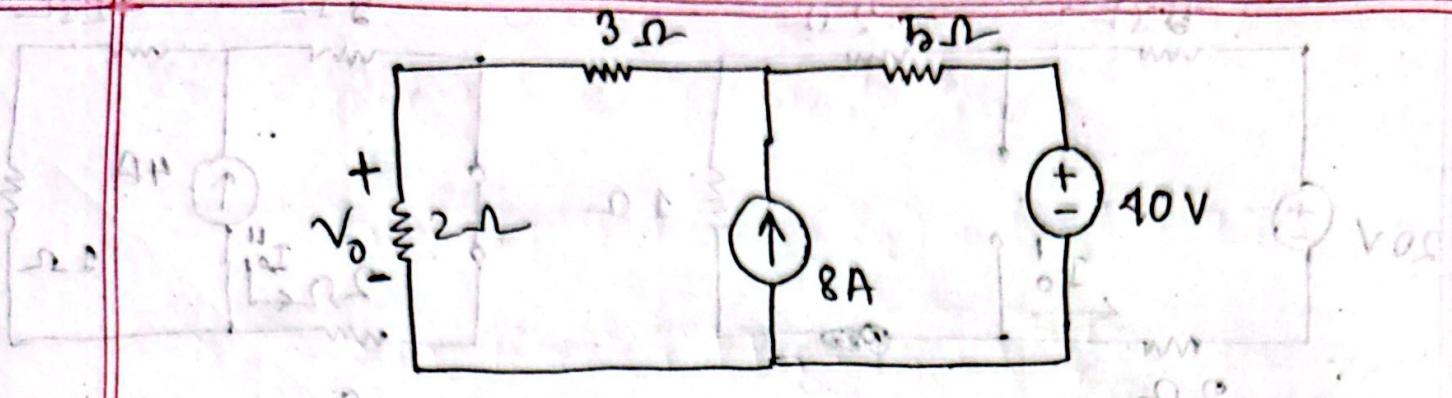


figure 1

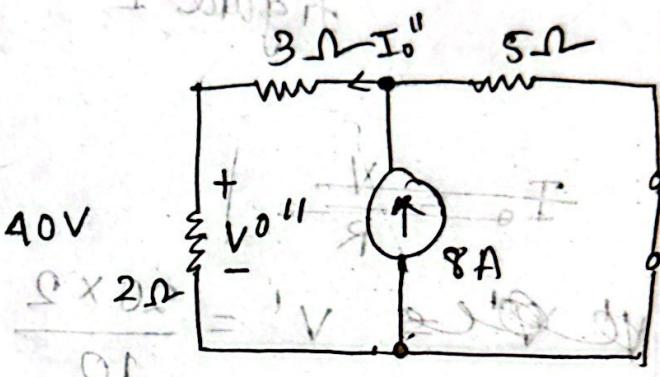


fig 2

@ VDR in fig 1,

$$V_o' = \frac{40 \times 2}{(1 + 5 + 3 + 2)}$$

$$(C = 8V) \quad R_o = 2\Omega$$

$$A_S = \frac{V_o''}{I_0} = \frac{8 \times 5}{5 + 5} = 4A$$

$$V_o'' = 2I = 4 \times 2 = 8V$$

RVL in fig 2,

$$2I + 3I + 8 = 0$$

$$\Rightarrow 5I = -8$$

$$\therefore I = -1.6A$$

$$V_o'' = 2 \times -1.6 = -3.2V$$

$$(Ans) A8.0 = I$$

$$V_o = V_o' + V_o''$$

$$\varepsilon = 8 + 8 = 16 \text{ V}$$

$$0 = \frac{8}{3+2} + (8I - \varepsilon) + \frac{8+8}{2} + (8I - \varepsilon)$$

$$= \frac{-4.8}{5} + 8I$$

Find I_o using
① Superposition theorem.


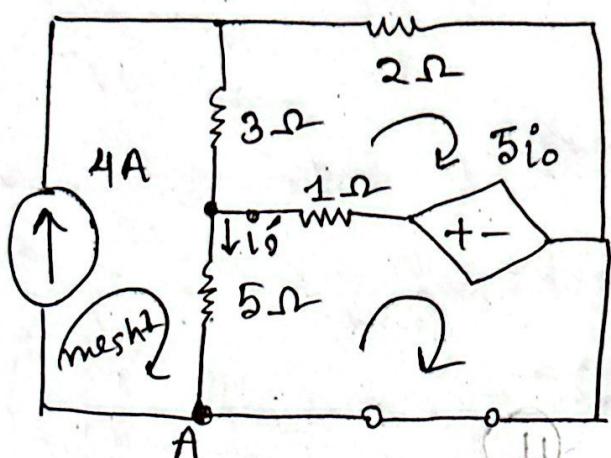


figure 1

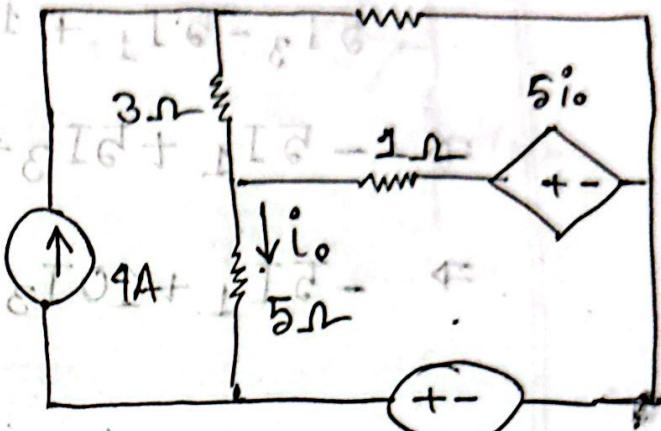

c A short to JCF 20V

$$\varepsilon^i + i_0^i = I^i$$

$$\varepsilon^i + i_0^i = A \cdot a =$$

$$\varepsilon^i - A = i_0^i$$

KVL in mesh 1,

$$I_1 = 4A$$

KVL in mesh 2,

$$3(I_2 - I_1) + 2(I_2) - 5i_0^i + 1(I_2 - I_3) = 0$$

$$\Rightarrow 3I_2 - 12 + 2I_2 - 5i_0^i + I_2 - I_3 = 0$$

$$\Rightarrow 6I_2 - I_3 - 5(4 - I_3) = 12$$

$$\Rightarrow 6I_2 + 4I_3 = 32$$

III

Applying KVL in mesh 3, $V_A + V_B = 0V$

$$5I_3 - 5I_1 + 1(I_3 - I_2) + 5i_0' + 4I_3 = 0$$

$$\Rightarrow -5I_1 + 5I_3 + 1I_3 - I_2 + 5i_0' + 4I_3 = 0,$$

$$\Rightarrow -5I_1 + 10I_3 - I_2 + 5i_0' = 0 \quad \text{--- (1)}$$

KCL at node A,

$$i_1 = i_0' + i_3$$

$$\Rightarrow A = i_0' + i_3$$

$$\therefore i_0' = A - i_3 \quad \text{--- (II)}$$



$$-5I_1 - 5(4) + 40I_3 - I_2 + 5(4 - i_3) = 0$$

$$\Rightarrow -20 + 10I_3 - I_2 + 20 - 5I_3 = 0 \quad \text{KVL}$$

$$\Rightarrow 5I_3 - I_2 = 0 \quad (I_1 = 4 - i_3)$$

$$0 = 8I - 2I + 10I - 5I \Rightarrow 9I_2 + 2I - 5I = 0 \quad \Leftarrow$$

$$i_3 = 0.95 \quad I_1 = (8I - 2I) / 10 = 13.05A$$


i_3 value in eq (II), $13.05 = 8I + 2I \Rightarrow$

KVL in mesh 1,

$$3(i_a) + 2(i_a) - 5i_o'' + 1(i_a - i_b) = 0$$

$$\Rightarrow 3i_a + 2i_a - 5i_o'' + i_a - i_b = 0$$
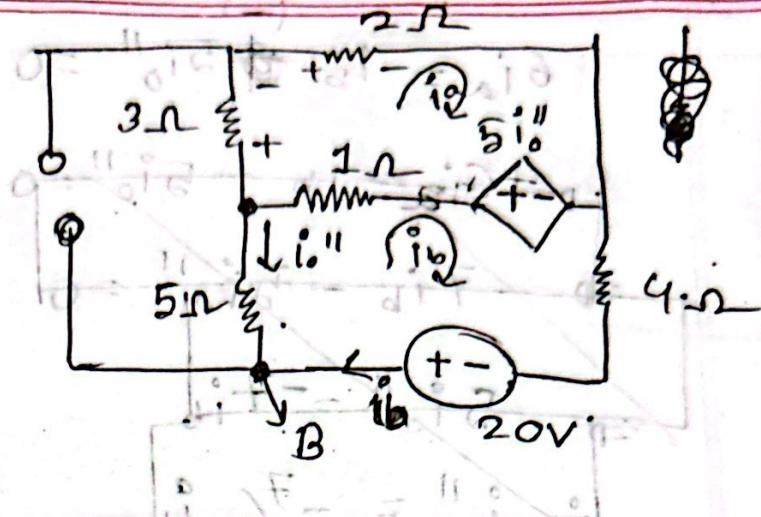
$$\Rightarrow 6i_a - i_b - 5i_o'' = 0 \quad \text{--- (1)}$$



KVL in mesh 2,

$$-20 + 5i_b + 1(i_b - i_a) + 5i_o'' + 4i_b = 0$$

$$\Rightarrow 5i_b + i_b - i_a + 5i_o'' + 4i_b = 20 \quad \text{--- (2)}$$

$$\Rightarrow 10i_b - i_a + 5i_o'' = 20 \quad \text{--- (2)}$$

(Add (1) + (2))

$$6i_a - i_b - 5i_o'' + 10i_b - i_a + 5i_o'' = +20$$

$$\Rightarrow 5i_a + 9i_b = 20$$

$$\Rightarrow 5i_a + 20 - 9i_b = 0$$

$$\therefore i_a - 20 - 9i_b = 0$$

Applying KCL at node B,

$$i_o'' + i_b = 0$$

$$\therefore i_o'' = -i_b$$

$$6i_a - i_b - 5i_o'' = 0 \rightarrow$$

$$+6i_a - i_b - 5i_o'' = 0$$

$$7i_b - 5i_o'' = 0$$

$$5i_o'' = -7i_b$$

$$\frac{i_o''}{i_b} = -\frac{7}{5}$$

$$6i_a - i_b - 5(-i_b) = 0$$

$$6i_a - i_b + 5i_b = 0$$

$$6i_a + 4i_b = 0$$

$$10i_b - i_a + 5i_o'' = 20$$

$$\Rightarrow 10i_b - i_a + 5(-i_b) = 20$$


$$\Rightarrow 5i_b - i_a = 20$$

$$i_o'' = i_o' + i_o'' = 3.05 + (-3.53)$$


$$= -0.48 \text{ (Ans)}$$

Source Transformation


Use source transformation to find V_o .

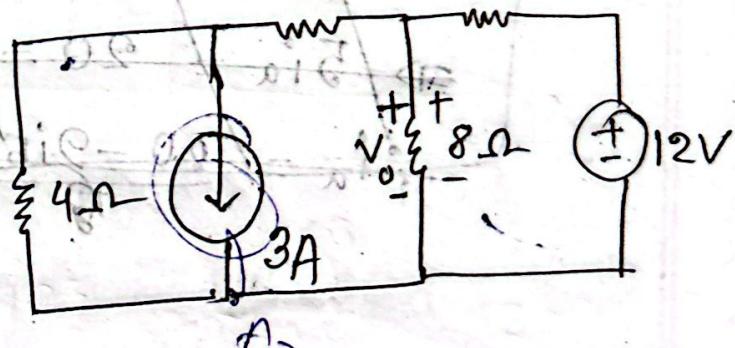




Theory:

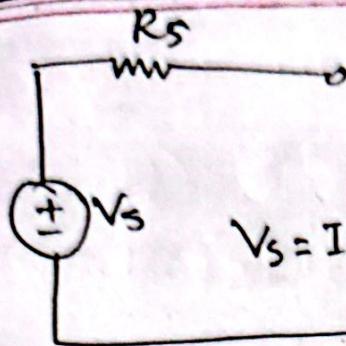

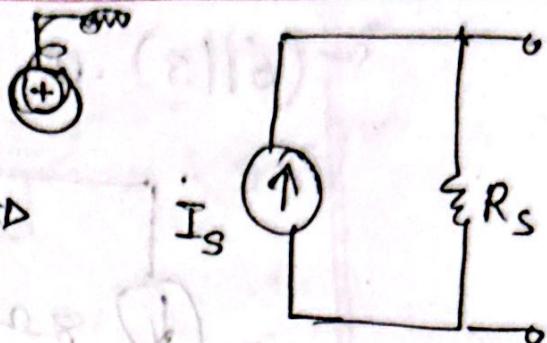
$$V_s = I_s R_s \Rightarrow I_s = \frac{V_s}{R_s} \Rightarrow$$




Ans:

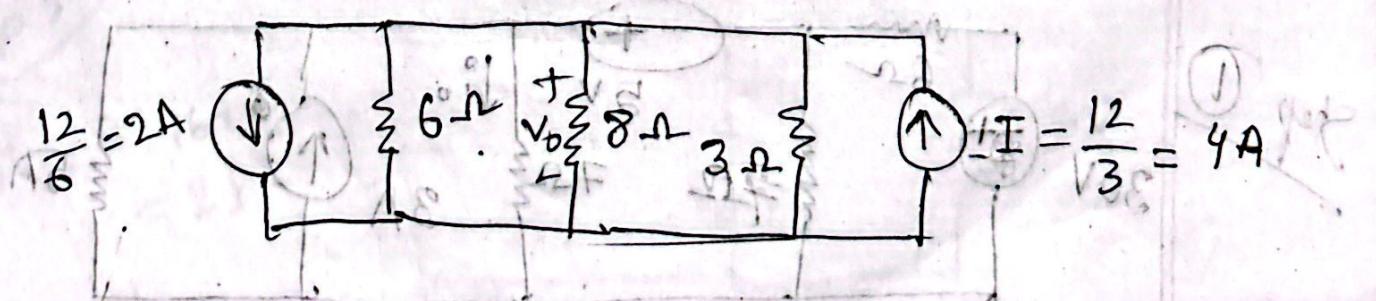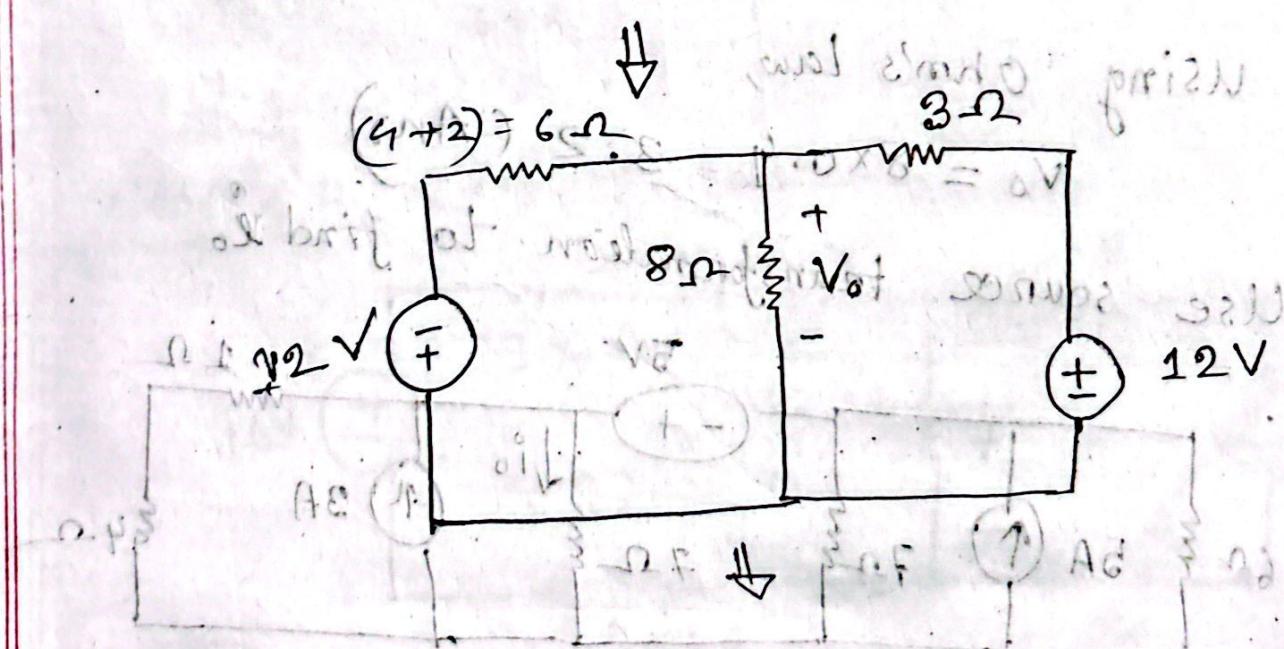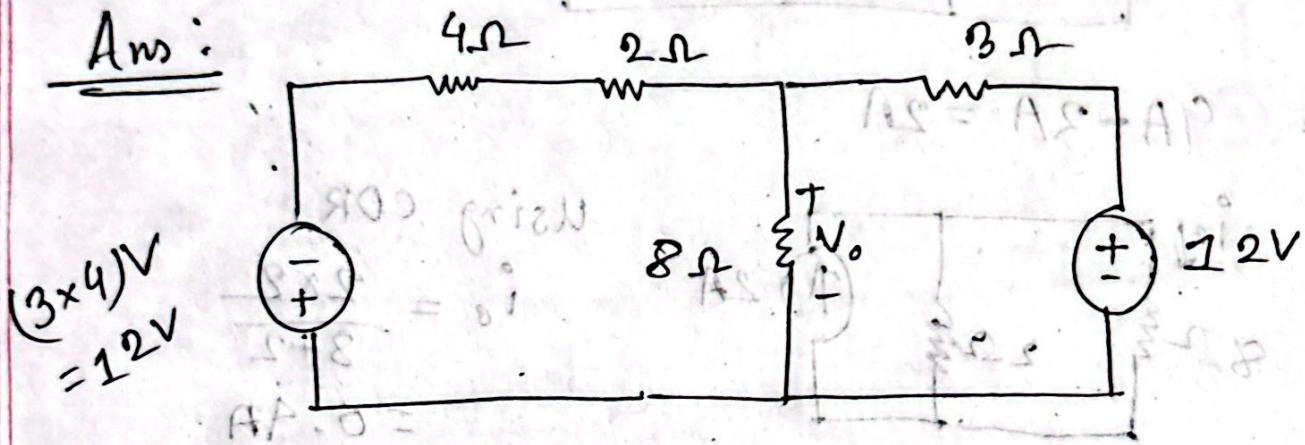
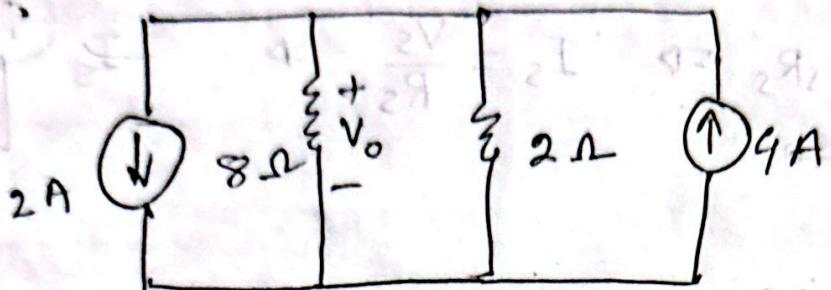
$$(6 \parallel 3) - R = \frac{6 \times 3}{6+3} = 2 \Omega$$



$$9A - 2A = 2A$$

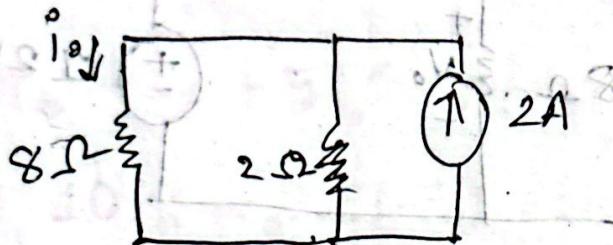


Using COR,

$$i_o = \frac{2 \times 2}{8+2} = 0.4A$$


using Ohm's law,

$$v_o = 8 \times 0.4 = 3.2 \text{ (Ans)}$$

Use source transformation to find i_o

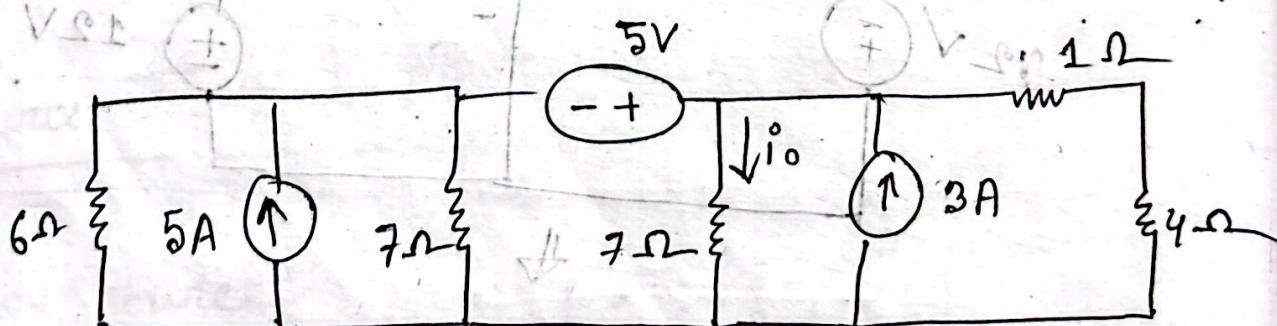


Step ①

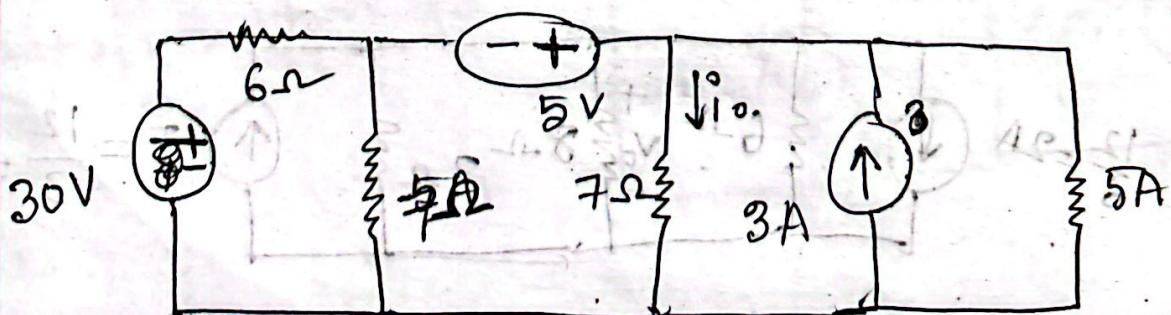


V_s = Series
 I_s = Parallel

Step

(2)

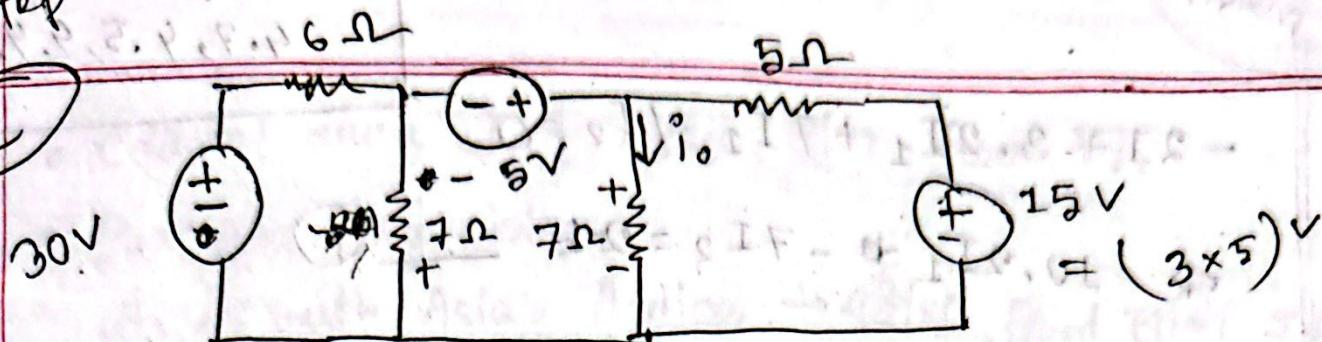


Step-3

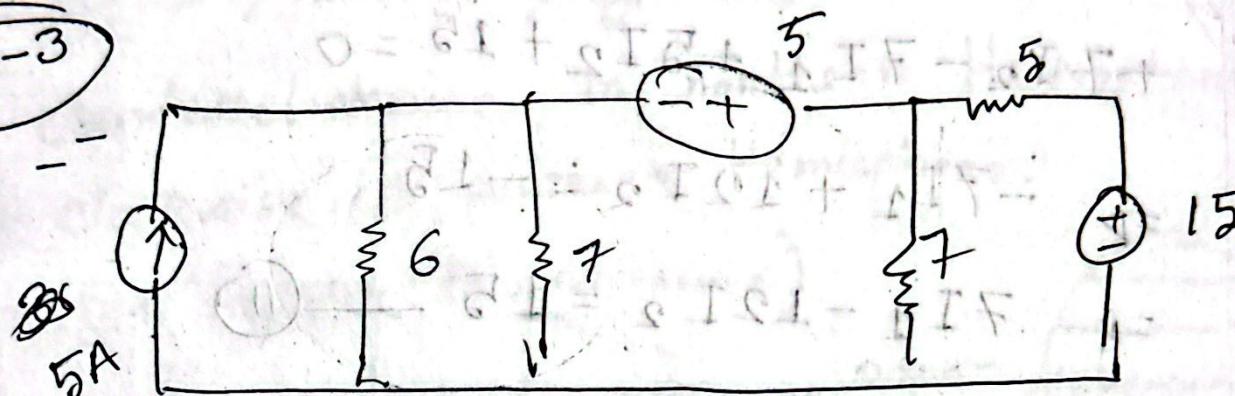

$$6 \parallel 7 = \frac{6 \times 7}{6 + 7} = 3.2 \Omega$$


Step 4

$$5 \times 3.2 = 16V$$

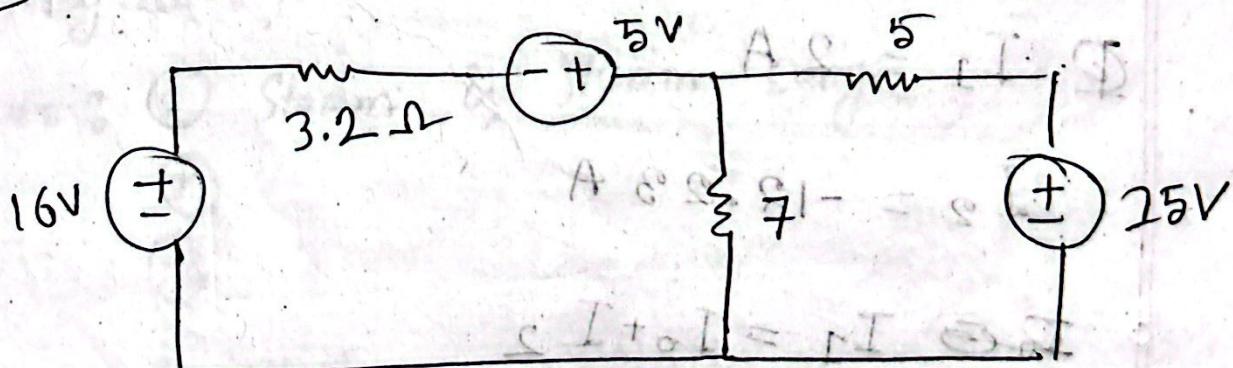

Step 5

$$\frac{16+5}{11} = 2\Omega$$

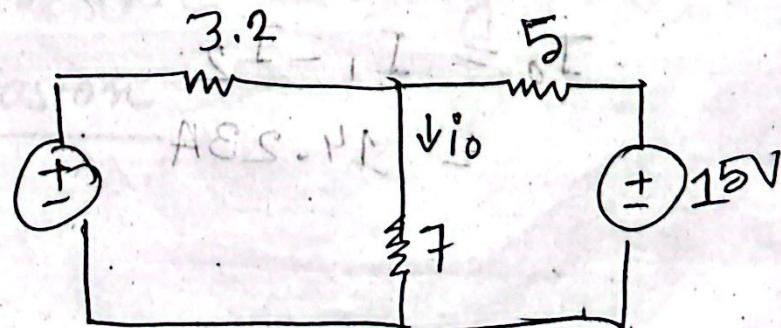

LX- 4.7, 4.8, 4.5

Prac prob -

4.7, 4.5, 4.4,

mesh 1

$$-21 + 3.2I_1 + 7I_1 - 7I_2 = 0$$

$$\Rightarrow 10.2I_1 - 7I_2 = 21 \quad \text{--- (1)}$$

mesh 2

$$+7I_2 - 7I_1 + 5I_2 + 15 = 0$$

$$\Rightarrow -7I_1 + 12I_2 = -15$$

$$\Rightarrow 7I_1 - 12I_2 = 15 \quad \text{--- (11)}$$

$$\begin{bmatrix} 10.2 & -7 \\ 7 & -12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 21 \\ 15 \end{bmatrix}$$

$$\Delta = -73.4$$

$$\Delta_1 = -147$$

$$\Delta_2 = 6$$

$$\textcircled{1} \quad I_1 = 2A$$

$$V_{01} \quad I_2 = -12.23A$$

$$\textcircled{2} \quad I_1 = I_o + I_2$$

$$I_o = I_1 - I_2$$

$$= 14.23A$$

MID





Assignment — 15

Class Test. — 15 (Next Monday)
02/09/2024
(mesh, Node Analysis)

28/08/2024

Thevenin's Theorem

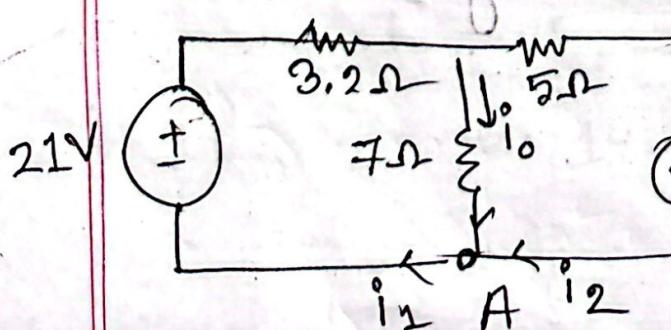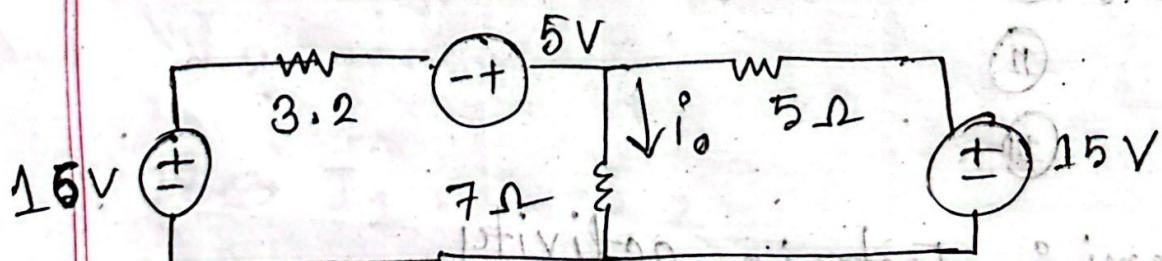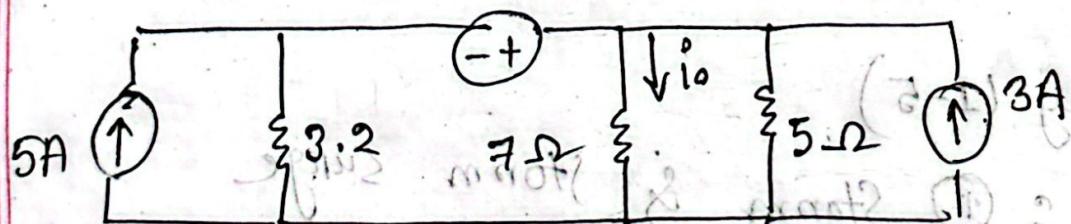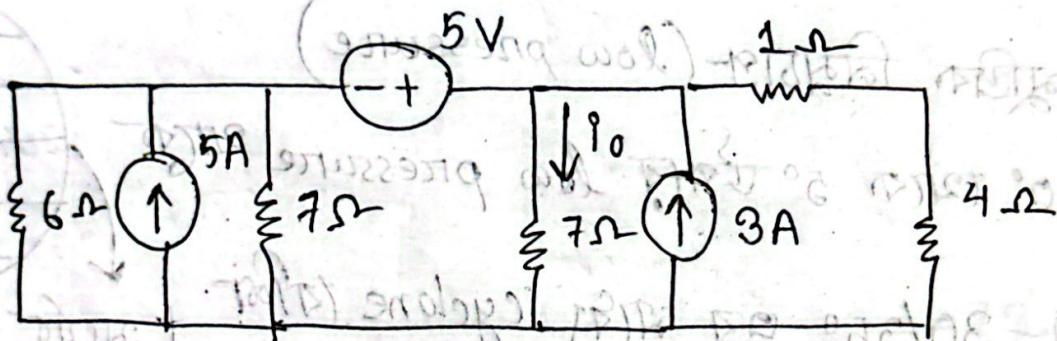finding
using
super source
transformation



KCL at node A,

$$i_0 + i_2 = i_1$$

$$\therefore i_0 = i_1 - i_2$$

Applying KVL in mesh 1,

$$-2i_1 + 3 \cdot 2i_1 + 7(i_1 - i_2) = 0$$

$$\Rightarrow 10.2i_1 - 7i_2 = 21$$

Applying KVL in mesh 2,

$$-7i_1 + 12i_2 = -15 \quad \text{--- (1)}$$

$$i_1 = 2A$$

$$i_2 = -0.081A$$

$$i_o = i_1 - i_2$$

$$= 2 - (-0.081)$$


$$= 2.081A \text{ (Ans)}$$

 Thevenin's Theorem

Find the Thevenin equivalent

circuit the following figure to the

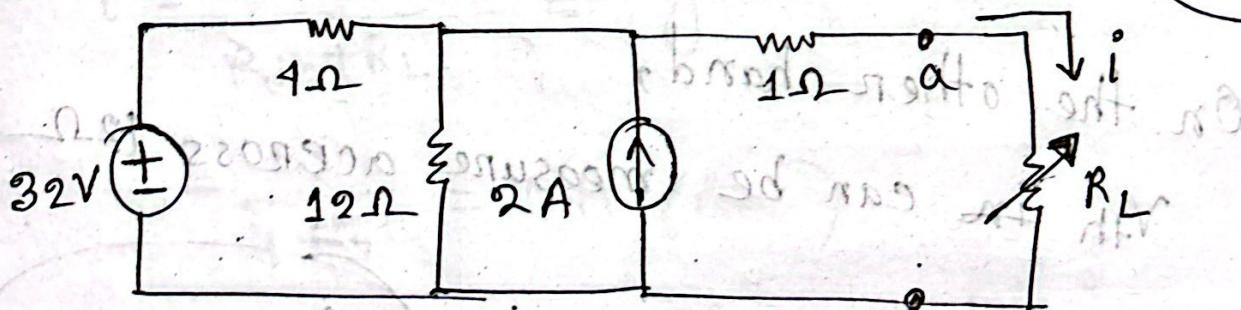
left of the terminal a-b then find i , ($R_L = 6\Omega, 76$)




R_{th} = Thevenin Equivalent Resistance

$V_{th} = 11$ Voltage

Step 1: Open R_L ,

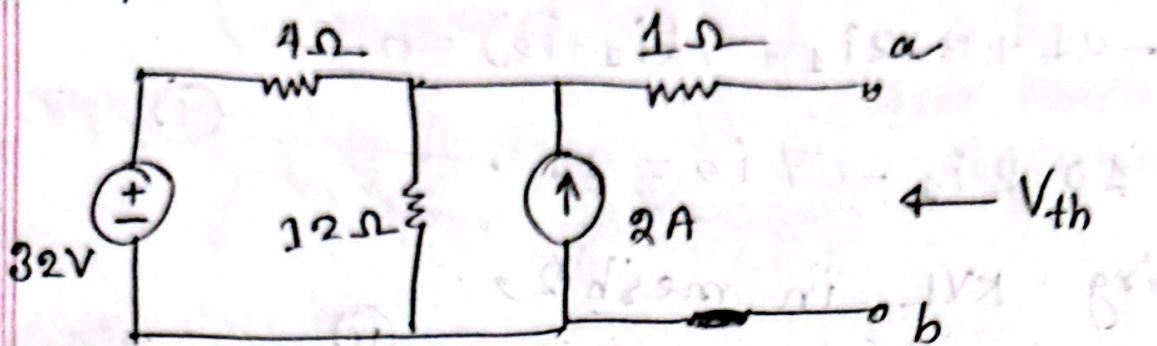


Step 2: Superposition formula,

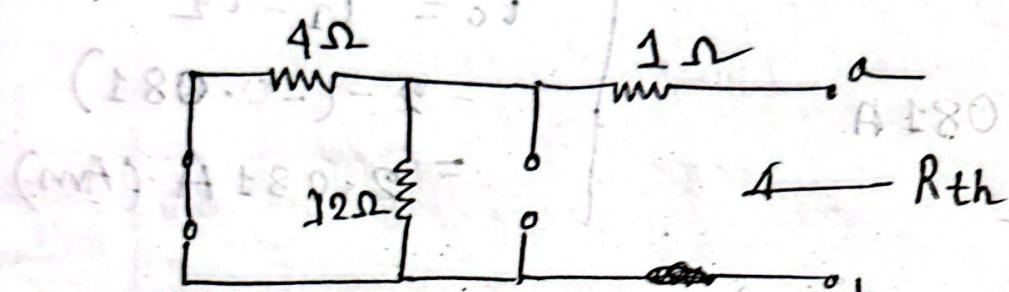

$$\therefore R_{th} = [(4 \parallel 12) + 1] \Omega \\ = (3 + 1) \Omega = 4 \Omega$$

On the other hand,

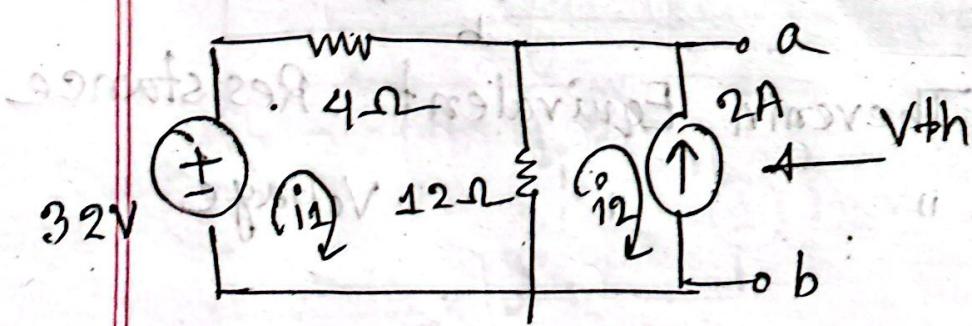V_{th} can be measured across $\frac{12\Omega}{12\Omega}$




$$i_2 = -2A$$

KVL in mesh 1, [4]
 around to + of left of loop $-32 + 4I_1 + 12I_1 - 12 \times (-2) = 0$ left
 $\therefore I_1 = 0.5 \text{ A}$

$$\therefore V_{th} = 12(I_1 - I_2) = 12(0.5 - (-2)) = 30 \text{ V}$$

∴ Thévenin Equivalent circuit,

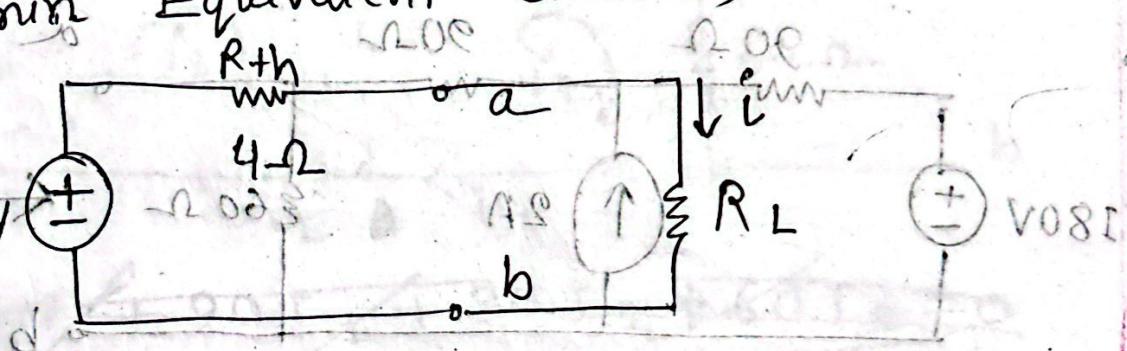

$$i = \frac{V_{th}}{R_{th} + R_L} \quad [\text{Using Ohm's Law}]$$

$$\Rightarrow \frac{30}{4+16} = 3 \text{ A (Ans)}$$


$$\text{On } i = \frac{30}{4+16} = 1.5 \text{ A. (Ans)}$$

$$0.11(0\Omega + 0\Omega) = 0.11$$


$$-2 \text{ J} =$$

B

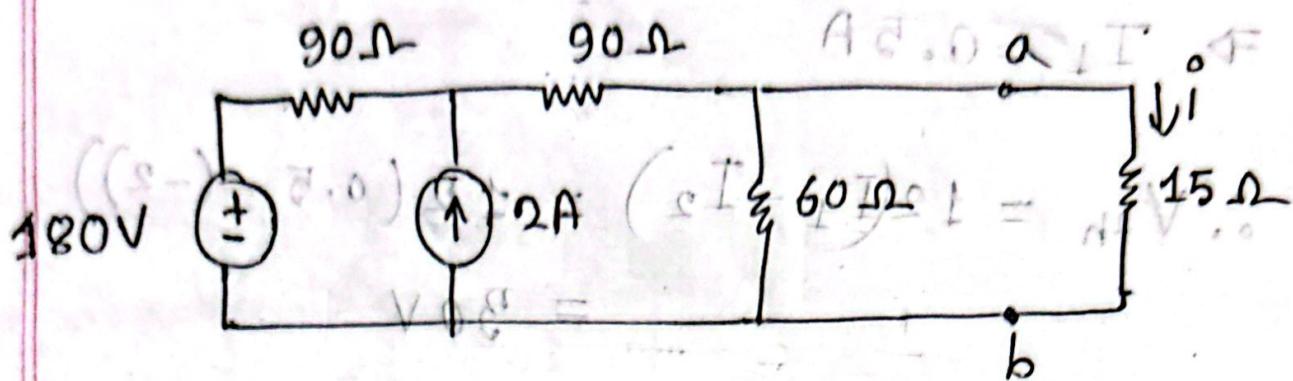
Find the Thvenin equivalent circuit for the following figure to the left of terminals a-b.



$\underline{V_{th}}$

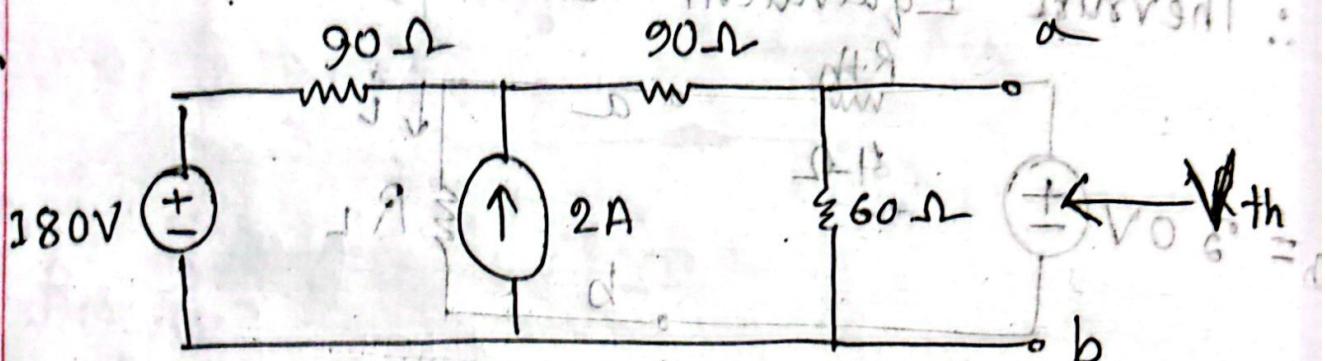


$\underline{R_{th}}$

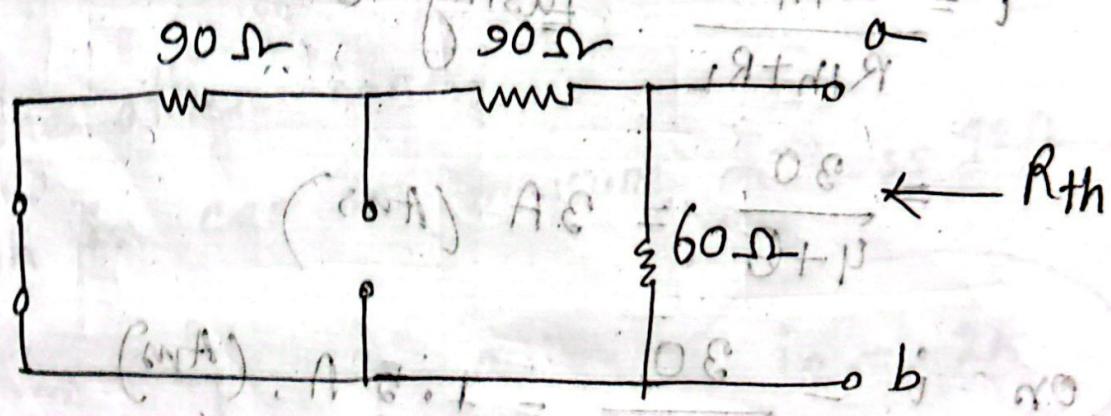

$$R_{th} = (90 + 90) \parallel 60 \\ = 15\Omega$$

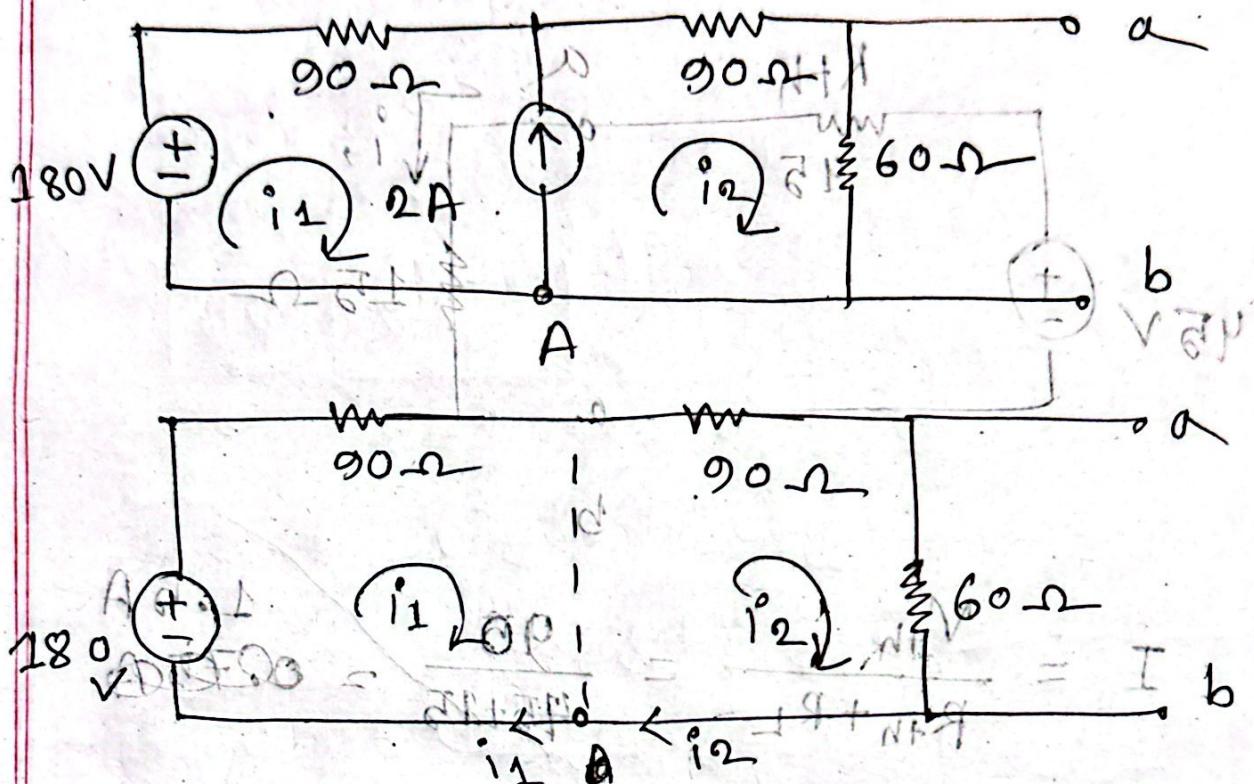V_{th} (trans) be measured across 60Ω , following circuit



~~$$180V + 90I_1 + 90I_2 + 60I_2 = 0$$~~

(This equation is crossed out)

$\therefore V_3 = \frac{180 \times 60}{90 + 90 + 60}$

$V_{th} = 45V$

$i_2 = i_1 + i_s$


$V_{AB} = i_1 \cdot 90$

$i_1 = \frac{180 - 45}{90 + 90 + 60}$

$i_1 = 0.833A$

$i_2 = 0.833 + 0.833 = 1.666A$

Thevenin Equivalent Circuit

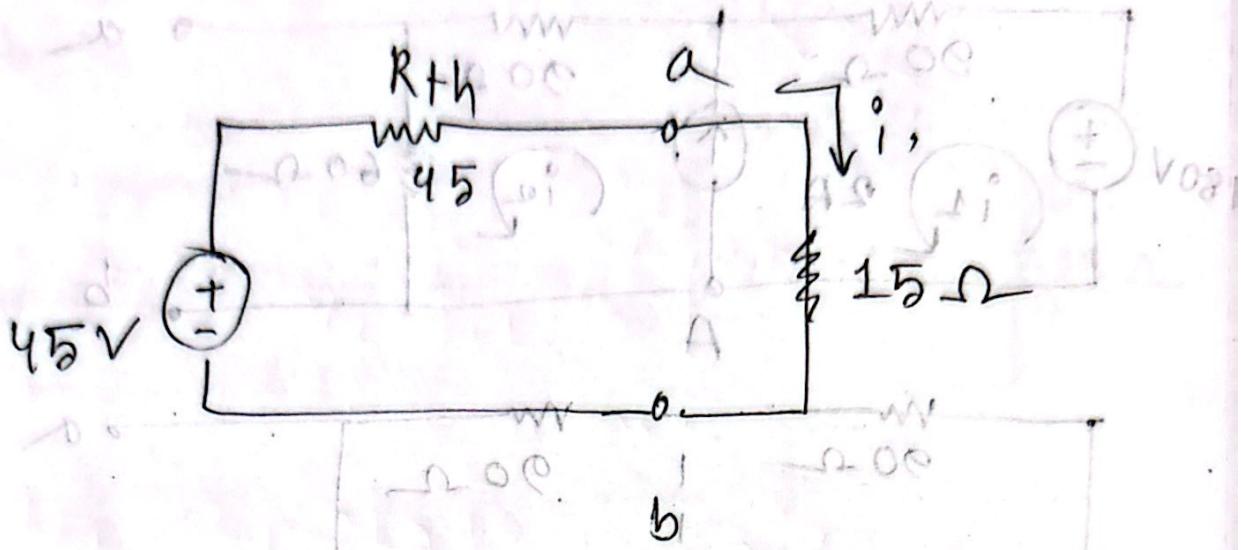

$$I = \frac{V_{th}}{R_{th} + R_L} = \frac{90}{90 + 15} = 0.75A$$

with superposition

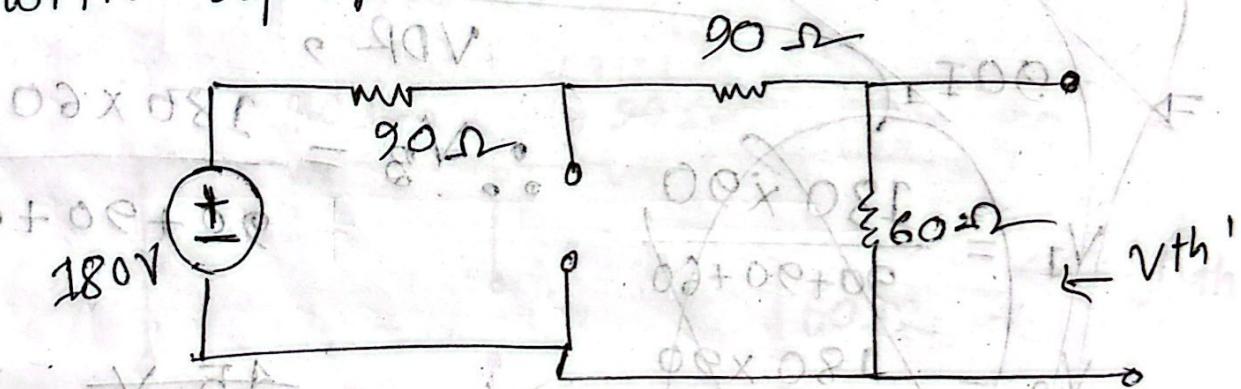


Fig 1

$$i_1 + i_2 = I$$


$$-180 + 90i_1 + 90i_2 + 60i_2 = 0$$

$$\therefore 90i_1 + 150i_2 = 180$$

$$V_{th}' = 45V$$

CDR,

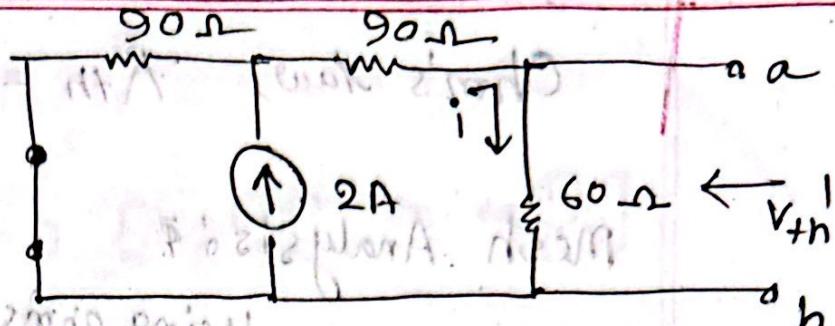
$$i = \frac{2 \times 90}{90 + (90 + 60)} = 0.75 \text{ A}$$



Using Ohm's law,

$$V_{th}'' = 60 i = 60 \times 0.75 = 45 \text{ V}$$
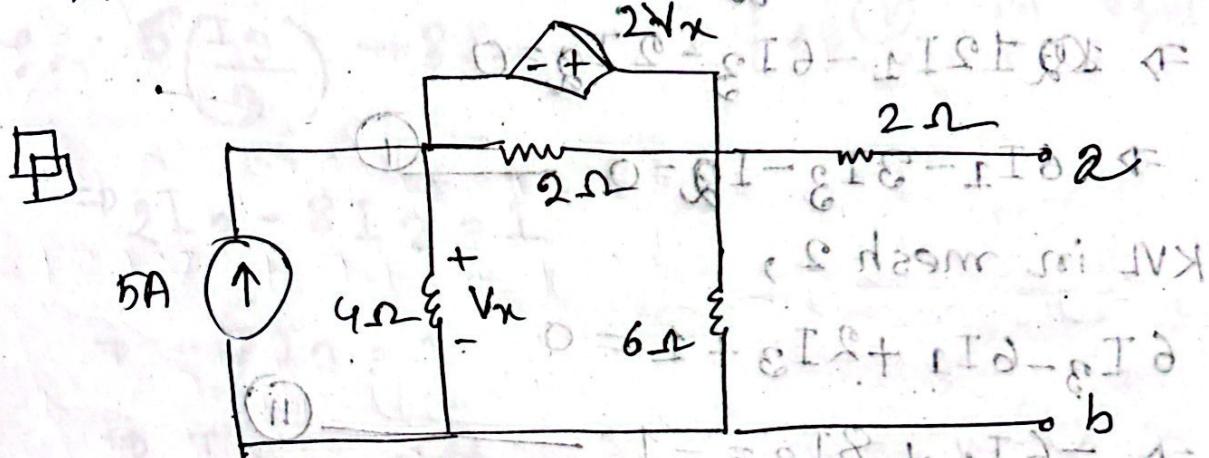
$$V_{th} = V_{th}' + V_{th}'' = 45 + 45 = 90 \text{ V}$$




Find the Thvenin equivalent circuit at terminal a-b:-

~~aff dependent source এর জন্যে~~

মাত্র terminal এবং মাত্র

R parallel ২৭৪৮ ১A এর জন্যে

R series ২৭৩৮ ১V এর জন্যে

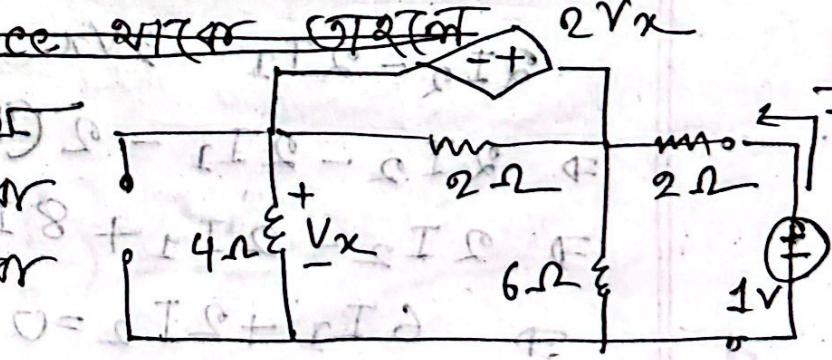


$$\text{Ohm's law, } R_{th} = \frac{V}{I} = \frac{1}{I}$$

Mesh Analysis;

Using Ohm's law,

$$V_x = 4I_1$$

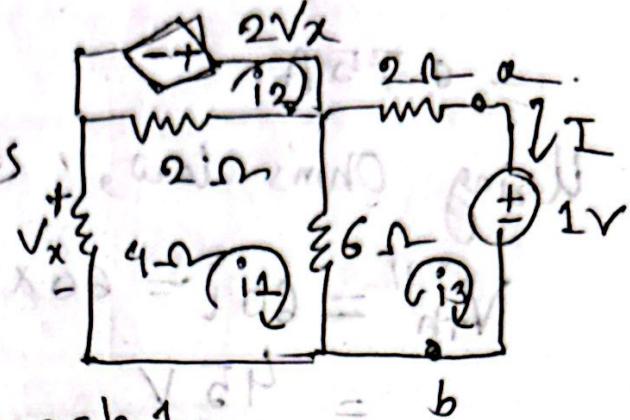

~~+Vx - Vx~~ KVL in mesh 1,

$$4I_1 + 2I_1 - 2I_2 + 6I_1 - 6I_3 = 0$$

$$\Rightarrow 12I_1 - 6I_3 - 2I_2 = 0$$

$$\Rightarrow 6I_1 - 3I_3 - I_2 = 0 \quad \text{--- (1)}$$

KVL in mesh 2,

$$6I_3 - 6I_1 + 2I_3 + 1 = 0$$

$$\Rightarrow -6I_1 + 8I_3 = -1 \quad \text{--- (2)}$$

~~$$3I_1 - 4I_3 = 1 \quad \text{--- (3)}$$~~

KVL in mesh 2,

$$2I_2 - 2I_1 - 2V_x = 0$$

$$\Rightarrow 2I_2 - 2I_1 - 2(4I_1) = 0$$

$$\Rightarrow 2I_2 - 2I_1 + 8I_1 = 0$$

$$\Rightarrow 6I_1 + 2I_2 = 0$$

$$\therefore 3I_1 + I_2 = 0 \quad \text{--- (3)}$$

$$\Rightarrow I_2 = 2I_1 \quad \text{--- (IV)}$$

$$\therefore 6I_1 - 3I_3 + 3I_1 = 0 \quad [\text{eq (IV) in eq (I)}]$$

$$\Rightarrow 9I_1 - 3I_3 = 0$$

$$\Rightarrow 3I_1 - I_3 = 0$$

$$\Rightarrow I_1 = \frac{I_3}{3} \quad \text{--- (V)}$$

$$\therefore 6\left(\frac{I_3}{3}\right) - 8I_3 = 1 \quad [\text{eq (V) in eq (II)}]$$

$$\Rightarrow 2I_3 - 8I_3 = 1$$

$$\Rightarrow -6I_3 = 1$$

$$\Rightarrow I_3 = -\frac{1}{6}$$


Applying KCL at node 'a',

$$I_3 + I = 0$$

$$\Rightarrow I = I_3$$

$$\Rightarrow I = -\left(-\frac{1}{6}\right) = \frac{1}{6}$$
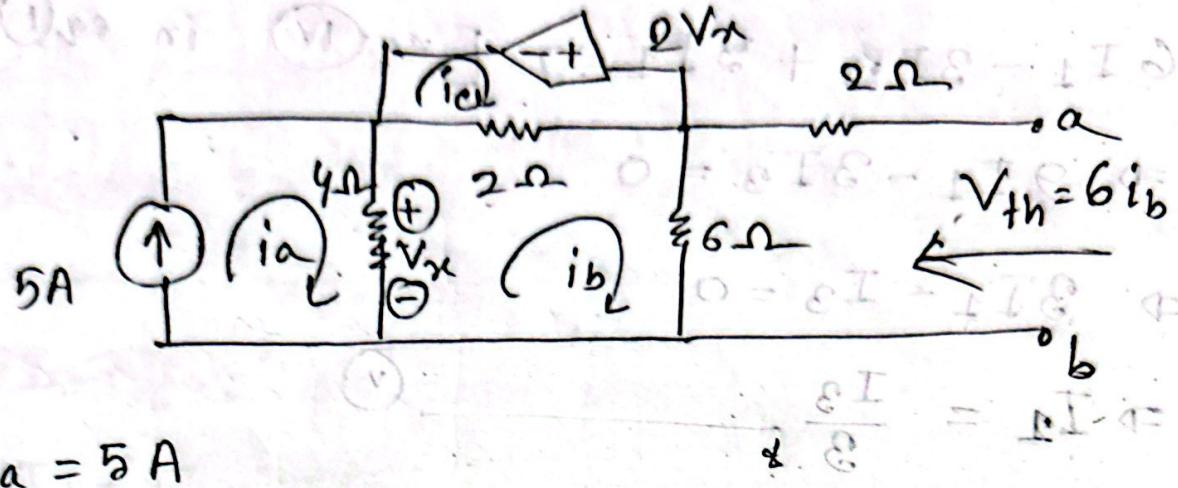
$$R_{th} = \frac{V}{I} = \frac{1}{\frac{1}{6}} = 6\Omega$$



$$i_a = 5A$$

KVL in mesh b,

$$4I_b - 4I_a + 2I_b - 2I_c + 6I_b = 0$$

$$\Rightarrow \cancel{\frac{19}{10}} I_b - 20 - 2I_c = 0$$

$$\Rightarrow 6I_b - I_c = 10 \quad \text{--- (1)}$$

KVL in mesh c,

$$2I_c - 2I_b - 2V_x = 0$$

$$\therefore V_x = I_c - I_b$$

~~$$= 0I_c - 2I_b - 2V_x = 4(5 - I_b)$$~~

~~$$\therefore V_x = 4I_b - 20 = 20 - 4I_b$$~~

$$I_c - I_b = 4I_b - 20 \quad \text{---} \quad ①$$

$$\Rightarrow I_c - 4I_b = 20 \quad \text{---} \quad ②$$

$$\begin{bmatrix} 5 & -1 \\ -5 & 1 \end{bmatrix} \begin{bmatrix} I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 10 \\ 20 \end{bmatrix}$$

$$I_b = 1A$$

$$I_c = 5A$$

$$25 - I_c = 10$$

$$5I_b - 5 = 10$$

$$\Rightarrow I_b = 1$$

$$I_c - I_b = V_x = 20 - 4I_b$$

$$\Rightarrow I_c = 20 \quad \text{Def.} \quad -3I_b - I_c = -20$$

$$I_b = -3.333$$

$$\therefore I_b - I_c = 20$$

$$6I_b - I_c = 10$$

$$3I_b + I_c = 20$$


$$9I_b = 30$$

$$\therefore I_b = 3.333$$

$$V_{th} = 6I_b$$

$$= 6 \times 3.333$$

$$\approx 20V$$

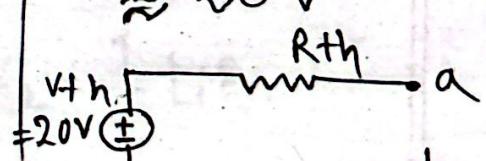


Norton Theorem

$$I_N = \text{Norton Current} = \frac{V_{th}}{R_{th}}$$

$$R_N = \text{Norton Resistance} = R_{th}$$

Norton equivalent circuit,

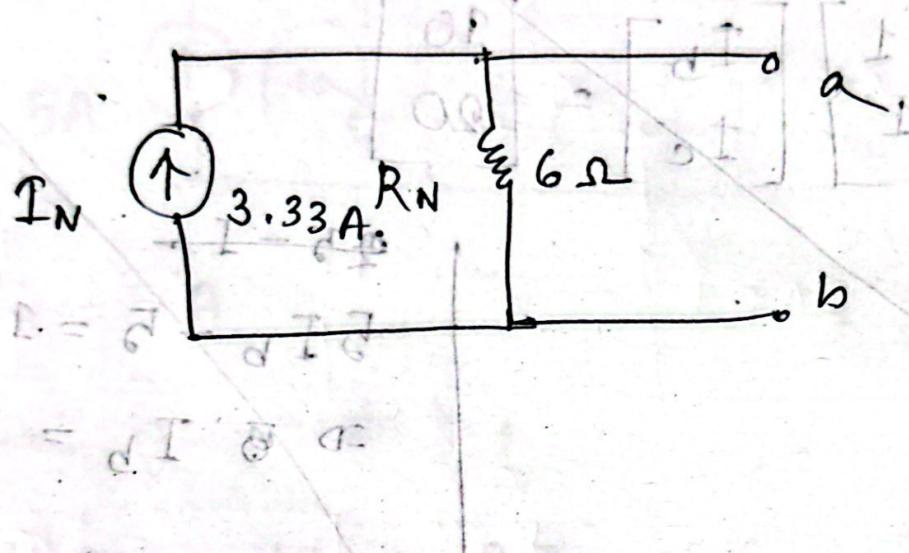

$$\alpha I - 0.2 = x v = \alpha I - 0.2$$


$$0.2 = 0.2I - 0.16 \rightarrow 0.2 = 0.2I \rightarrow I = 1$$


$$0.2 = 0.2I - 0.16$$

$$0.2 = 0.2I + 0.16$$


$$0.2 = 0.2I$$

$$0.2 = 0.2I$$

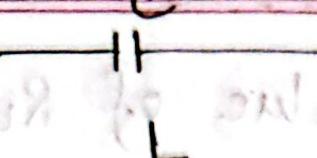Capacitor 


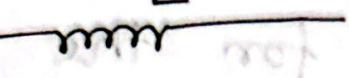
Inductor 

(S)

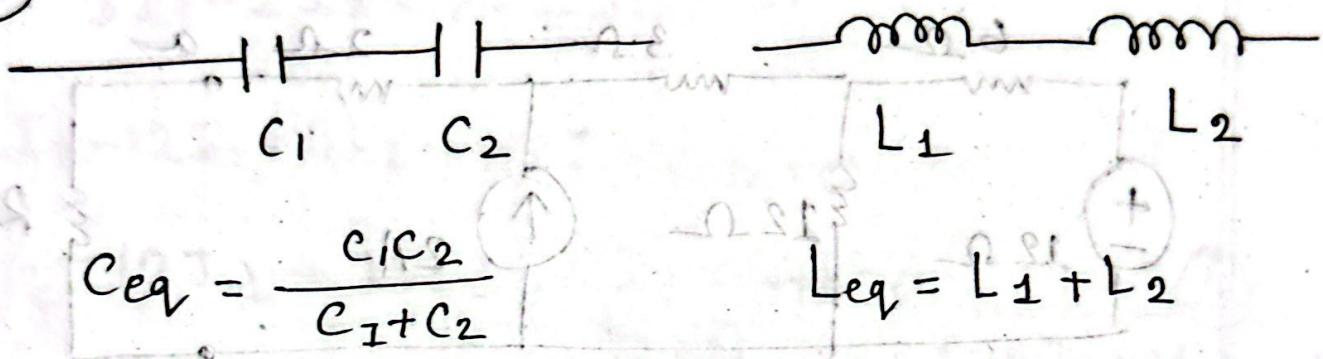

Energy: $W_C = \frac{1}{2} C V_C^2$

(P)

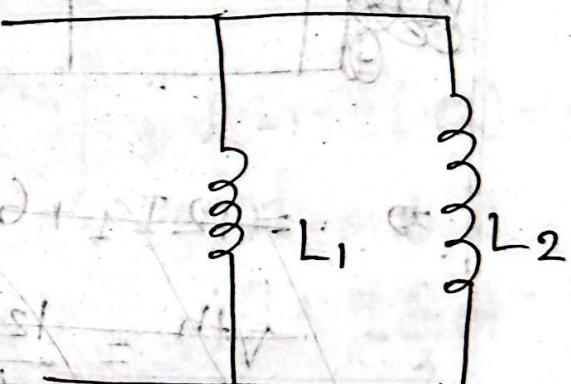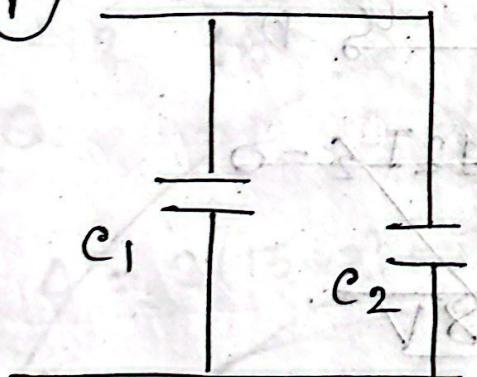



$$C_{eq} = C_1 + C_2$$

$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

Energy: $W_L = \frac{1}{2} L i^2$

~~Maximum Power Transfer Theorem~~

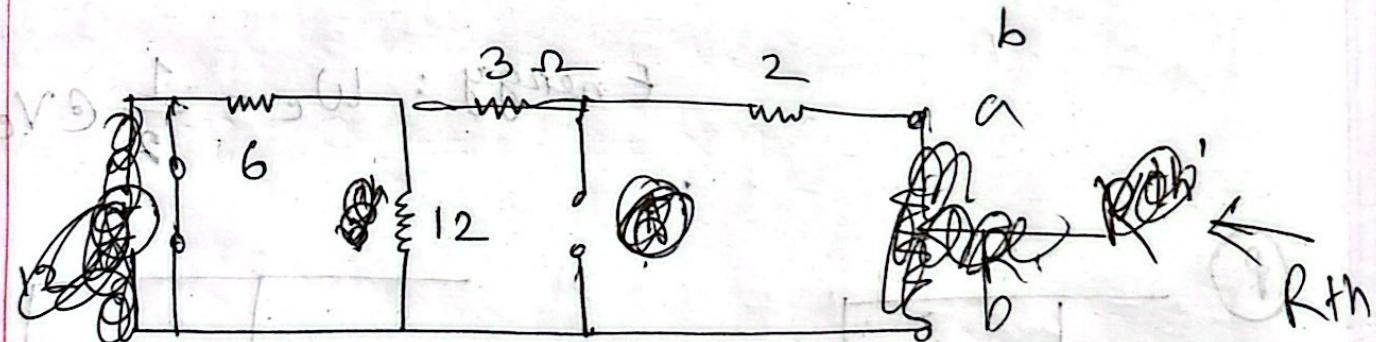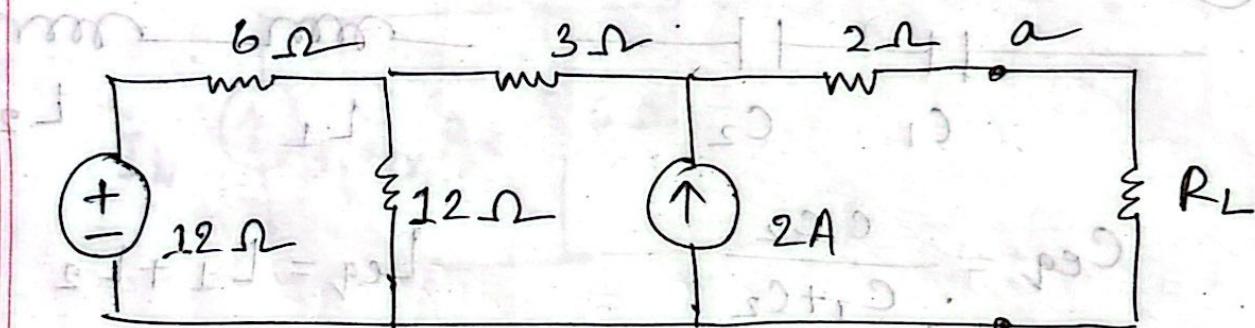Find the value of R_L for maximum power transfer for the following circuit, find the maximum power.



~~$$12I_1 + 6I_1 + 12I_2 - 12I_3 = 0$$~~

~~$$V_{Th} = \frac{12 \times 12}{6+12} = 8V$$~~

~~$$R_{Th} = 3+2+12+6 = 23\Omega$$~~

$$R_{Th} = (6 \parallel 12) + 3 + 2$$


$$= 4 + 3 + 2 = 9\Omega$$

$$-12 + 6I_1 + 12I_1 - 12I_2 = 0$$

$$\Rightarrow 18I_1 - 12I_2 = 12$$

$$\Rightarrow 9I_1 - 6I_2 = 6 \quad \text{--- (i)}$$
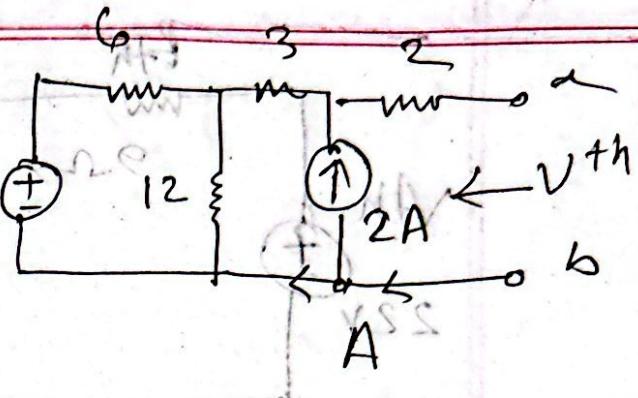
$$\Rightarrow 3I_1 - 2I_2 = 2 \quad \text{--- (ii)}$$



$$12I_2 - 12I_1 + 3I_2 + 2I_3 + V_{th} = 0$$

$$\Rightarrow -12I_1 + 15I_2 + 2I_3 = -V_{th} = 0 \quad \text{--- (iii)}$$

KCL at node A, $I_3 = 2 + I_2$

$$\begin{bmatrix} 3 & -2 & 0 \\ -12 & 15 & 2 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 2 \\ -V_{th} \\ 2 \end{bmatrix}$$

$$\Rightarrow I_2 = -2$$

$$3I_1 - 2(-2) = 2$$

$$\Rightarrow 3I_1 = 6 \quad \text{--- (iv)}$$

$$\therefore I_1 = \frac{2}{3} A$$

$$\Delta = 3(15+2) + 2(-12-0) =$$


$$\left(-12 \times \frac{2}{3} \right) + (15 \times -2) + V_{th} = 0$$

$$\Delta_1 =$$

$$\Delta_2 =$$

$$\Delta_3 =$$

$$\therefore V_{th} = 22 V$$

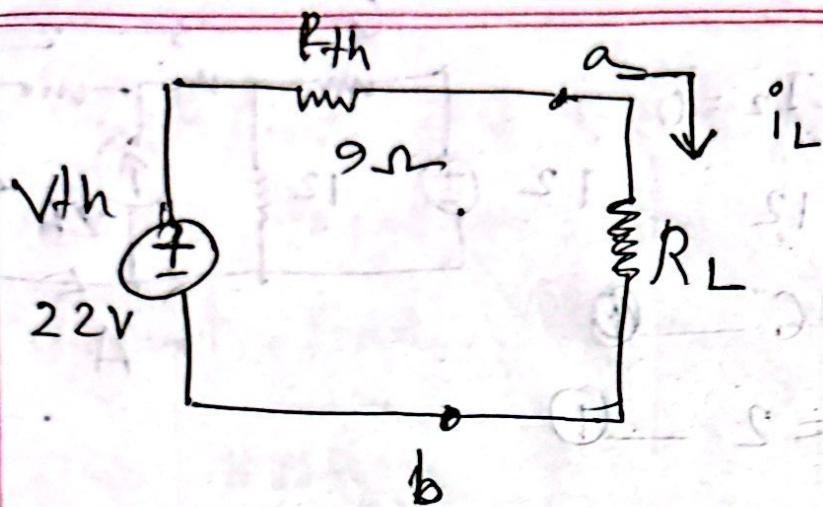

For maximum power transfer

$$R_L = R_{th} = 9 \Omega$$

$$P = i_L^2 R_L = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 \times R_L$$

$$= \left(\frac{V_{th}}{R_{th} + R_{th}} \right)^2 \times R_{th}$$


$$[R_L = R_{th}]$$

$$= \frac{V_{th}^2}{4R_{th}} = \frac{(22)^2}{4 \times 9} = 13.4 \text{ W} \quad (\text{Ans})$$


D) (Farad) Capacitors → Resistor → open
 (Henry) Inductors = Resistance to input → short circuit
 low to high

~~#~~ Under (dc) conditions, find (a) i , v_c , i_L .

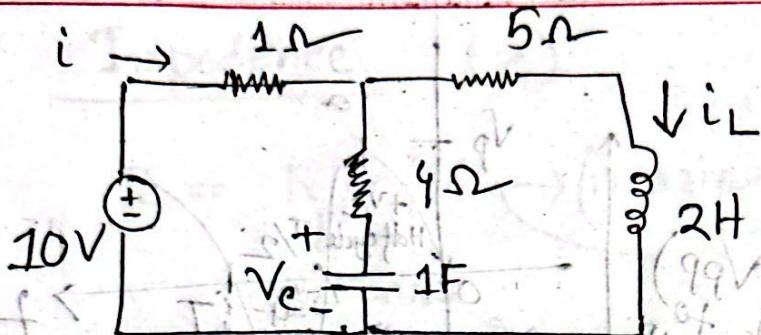(b) The energy stored in capacitor and Inductor.



Soln : @

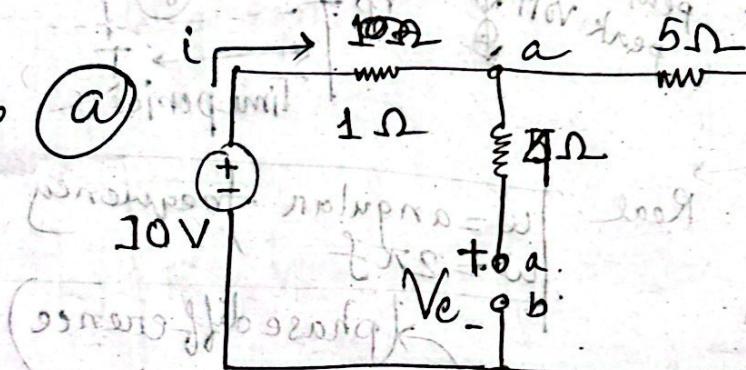

$$i = i_L = \frac{12}{(1+5)} = 2A$$

$$V_c = 5i_L = 5 \times 2 = 10V$$

$$(b) W_C = \frac{1}{2} C V_c^2 = \frac{1}{2} \times 1 \times 10^2 = 50 J$$


$$W_L = \frac{1}{2} L i_L^2 = \frac{1}{2} \times 2 \times 2^2 = 4 J$$

Amplitude

AC

V_p = Peak Voltage

T = Period

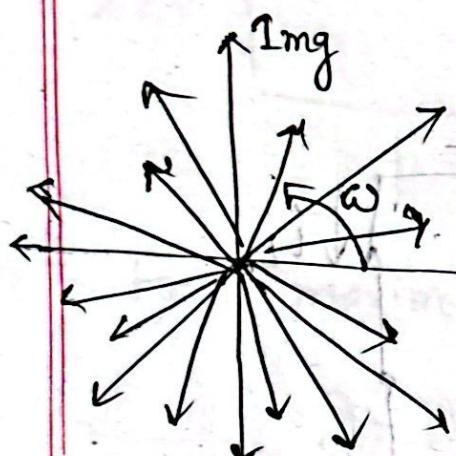


(V_{pp})
peak to
peak volt

Real

ω = angular frequency


$$\omega = 2\pi f$$

phase difference

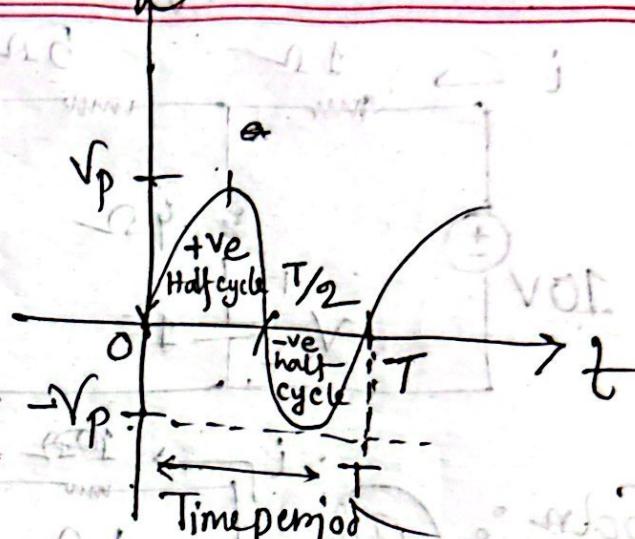


$$V(t) = \text{Amp} \sin(\omega t + \theta)$$

$$= V_p \sin(\omega t + \theta)$$

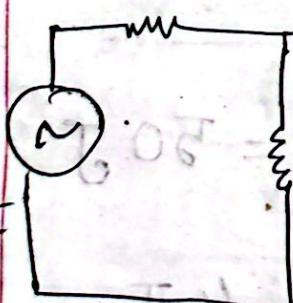

$$20 \sin 4t$$


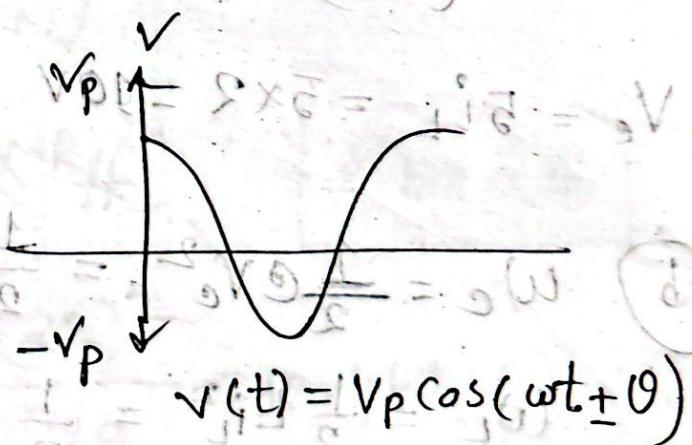


01/09/2024

Impedance (Z)


$$Z = R + j\omega L \rightarrow \text{imaginary part / reactance part}$$

Real part
(Resistance) depends on L, C

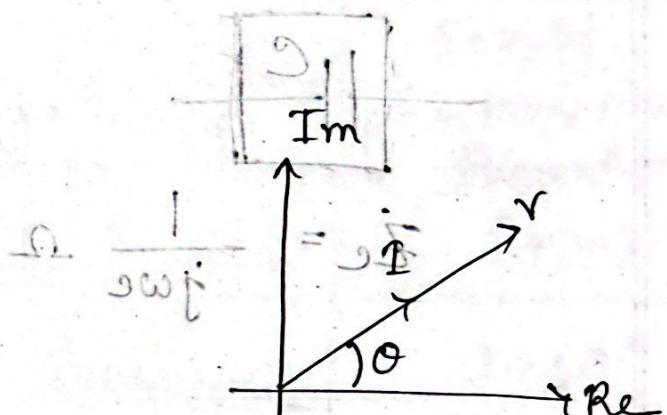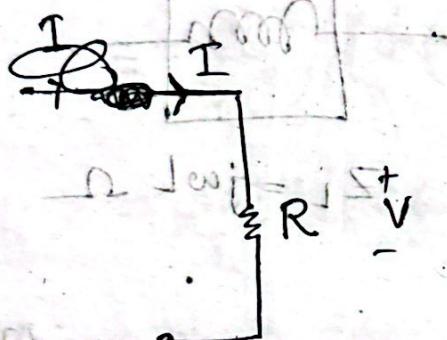

(f) I leads (f) V behind


Here, Resistance is a linear property

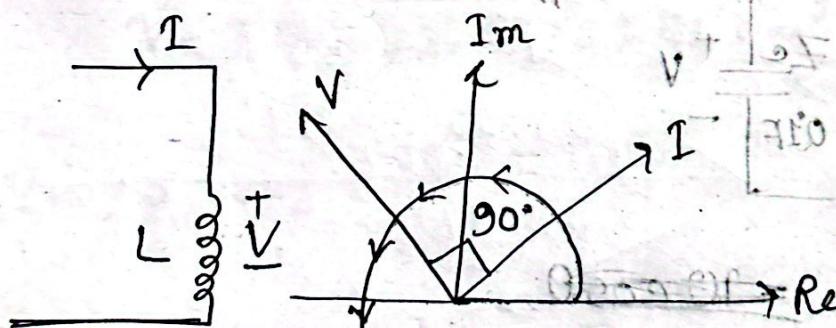


[Inductance is a property of current]

V leads I

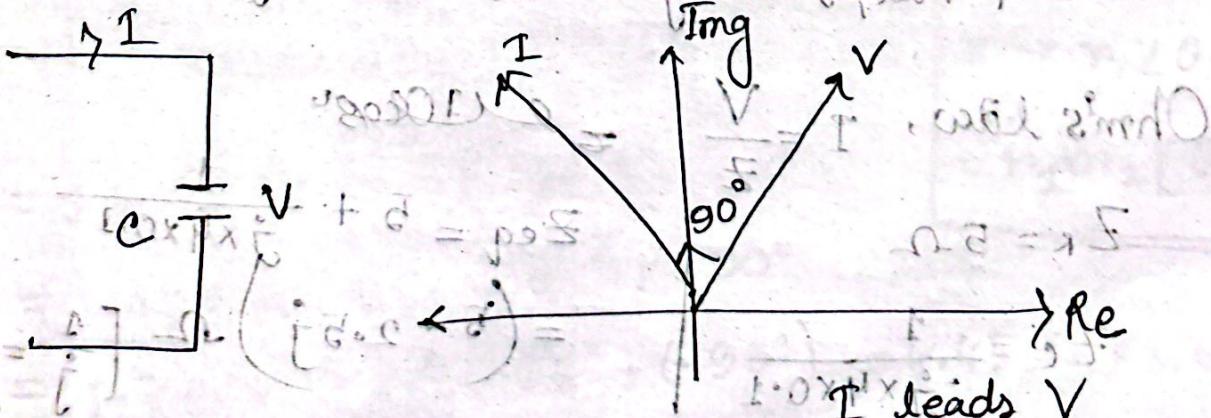
current always lags voltage = ωL where $\omega = \omega$



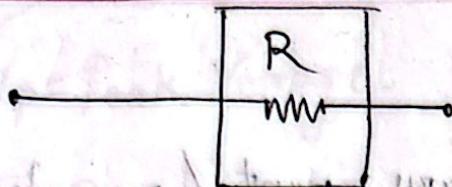


(S)

$$Z_R = R + 0 = R \Omega$$

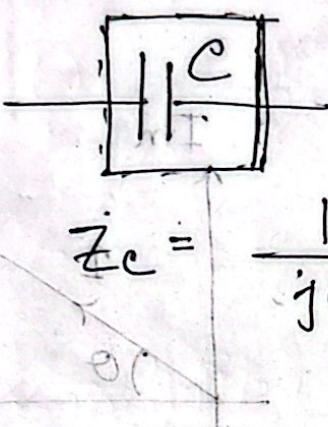


$$Z_C = \frac{1}{j\omega C} \Omega$$

Resultant
(capacitive)

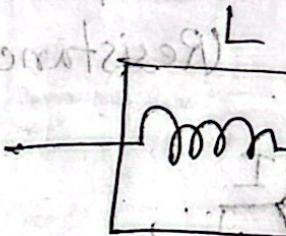

$$Z_L = j\omega L \Omega$$

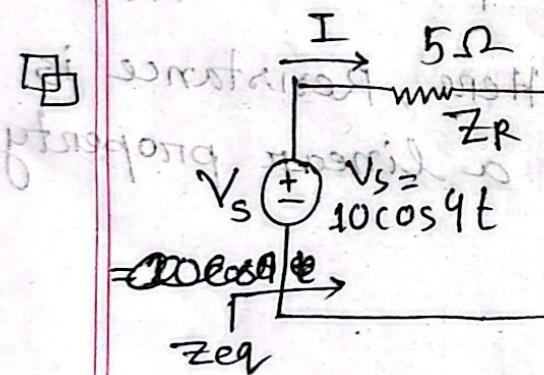

Find $v(t)$ and $I(t)$

$$V_s = 10\cos 4t$$

$$= 10\angle 0^\circ V \quad [\text{phasor representation}]$$

$\omega = 4 \text{ rad/s}$ = angular frequency

$$\text{Ohm's law, } I = \frac{V}{Z}$$

$$Z_R = 5 \Omega$$

$$Z_C = \frac{1}{j\omega \times 4 \times 0.1}$$

$$= 10\angle 4t$$

$$Z_{eq} = 5 + \frac{1}{j \times 4 \times 0.1}$$

$$= (5 - 2.5j) \Omega \quad \left[\frac{1}{j} = -j \right]$$

~~Per → pol (shift +)~~

angle - polar form

j - rectang form

$$I = \frac{V_s}{Z_{eq}} = \left(\frac{10 \cos 4t}{5 - 2.5j} \right) A = \left(\frac{10 \angle 0^\circ}{5 - 2.5j} \right) A = 2V$$

$$= \frac{10 \angle 0^\circ}{5.59 \angle -26.56^\circ}$$

$$= \frac{10}{5.59} \angle (0^\circ - (-26.56^\circ))$$

$$= 1.78 \angle 26.56^\circ A$$

Using Ohm's law,

$$V = I Z_C = 1.78 \angle 26.56^\circ \times \left(\frac{1}{j\omega C} \right)$$

$$V = I Z_C = I \times \left(\frac{1}{j\omega C} \right)$$

$$= 1.78 \angle 26.56^\circ \times \frac{1}{j \times 4 \times 10^{-9}}$$

$$= \frac{1.78 \angle 26.56^\circ}{0.4f}$$

$$= 1.78 \angle 26.56^\circ \times (-j2.5)$$

$$= 1.78 \angle 26.56^\circ \times 2.5 \angle -90^\circ$$

$$= (1.78 \times 2.5) \angle (26.56^\circ + (-90^\circ)) = 4.45 \angle -63.44^\circ V$$

$5 - 2.5j$

(Rectangular formation)

$\equiv (+/-)$

$10 \angle 0^\circ$

(polar formation)

(\div/x)

$$\div \rightarrow \frac{r_1 \angle \theta_1}{r_2 \angle \theta_2}$$

$$= \frac{r_1}{r_2} (\theta_1 - \theta_2)$$

$$x \rightarrow r_1 \angle \theta_1 \times r_2 \angle \theta_2$$

$$= r_1 r_2 (\theta_1 + \theta_2)$$

(+) right) ~~phasor~~
current \rightarrow voltage
~~voltage~~ - i

$$V_s = 10 \cos(4t) = A \left(\frac{+1320.01}{\sqrt{3}} \right) = \frac{eV}{\sqrt{3}} = E$$

$$V(t) = 4.45 \cos(4t - 63.44^\circ) V$$

=

$$\frac{0.102}{0.2638 - j0.2638}$$

(inductance not shown)

$$I(t) = (1.78 \cos(4t + 26.56)) A$$

$$(-V) =$$


$$A^{\circ} 22.38 + j8 F \cdot L =$$

(without phasor)
(x \div)

Phason

Diagram,

Img

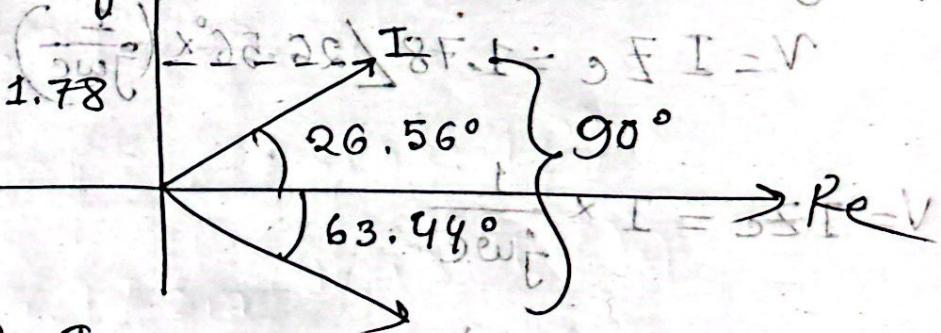

V leads I

This circuit behaves like an inductor.

$$(53.18^\circ + j0) \times e^{j4t} =$$

$$(53.18^\circ + j0) \times e^{j4t} =$$

$$V = 1.78 \cos(4t - 63.44^\circ) = (0^\circ) + j22.38 \times (53.18^\circ + j0) =$$

$$V(t) \cdot \& I(t)$$

Soln:

$$V_s = 20 \sin(10t + 30^\circ)$$

$$= 20 \angle 30^\circ V$$

$$I = \frac{V}{Z}$$

$$Z_R = 4 \Omega$$

$$Z_L = j\omega L = 0.2 \times 10 j = 2 j$$

$$Z_{eq} = (4+2j)\Omega$$

$$I = \frac{V_s}{Z_{eq}} = \frac{(20 \sin(10t + 30^\circ))}{4+2j} A$$

$$= \frac{20 \angle 30^\circ}{4+2j} = \frac{20 \angle 30^\circ}{4.47 \angle 26.56^\circ}$$

$$= \frac{20}{4.47} \angle (30^\circ - 26.56^\circ)$$

$$= 4.47 \angle 3.44^\circ$$

Using Ohm's law,

$$(f) E = 8 \cdot (f) V$$

$$\cancel{V - IZ_L} = 4.47 \angle 56.56^\circ \times 2j \cancel{(10 \angle 2^\circ)}$$

$$V(+) = IZ_L \quad (0.08 + j0.08) \sin 0.08 = 2V$$

$$= 4.47 \angle 3.44^\circ \times -j\omega$$


$$= 4.47 \angle 3.44^\circ \times j \times 10 \times 0.2$$

$$= 4.47 \angle 3.44^\circ \times 2j$$

$$= 4.47 \angle 3.44^\circ \times 2 \angle 90^\circ$$


$$= 4.47 \times 2 \angle 3.44^\circ + 90^\circ$$

$$= 8.94 \angle 93.44^\circ$$

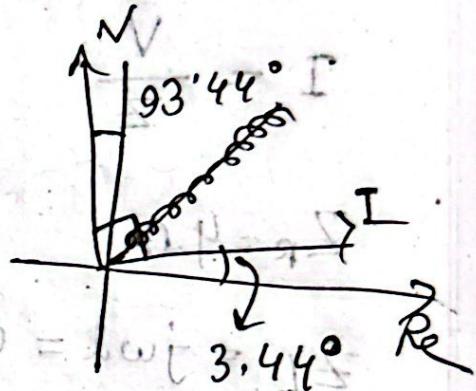

$$v(t) = 8.94 \sin(10 + 93.44^\circ) V$$

$$I(t) = 4.47 \sin(10 + 3.44^\circ) A$$

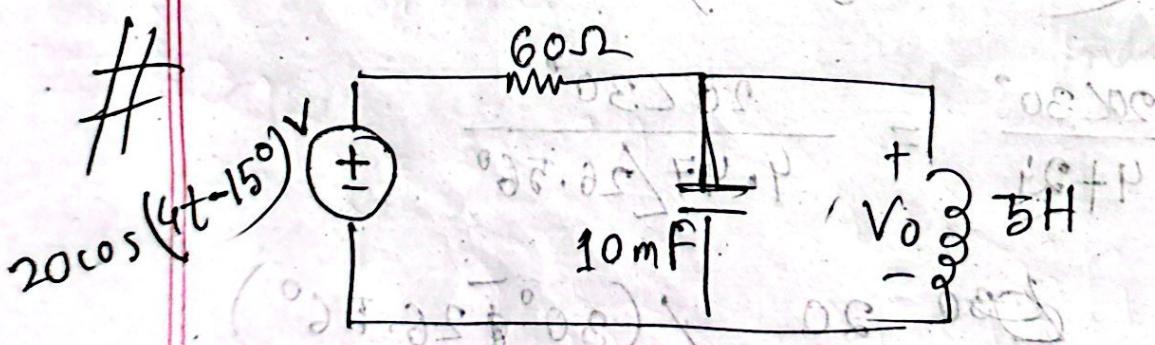

$$v_s = 20 \cos(4t - 15^\circ) V \quad | \quad \omega = 4 \text{ rad/s}$$

$$Z_R = 60 \Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{4j \times 10 \times 10^{-3}} = -j 25 \Omega$$

$$Z_L = j\omega L = j 4 \times 5 = 20j \Omega$$

$$Z_C \parallel Z_L = (-j 25 \parallel j 20)$$

$$V = \frac{-j 25 \times j 20}{-j 25 + j 20}$$

$$= \frac{25 \angle -90^\circ \times 20 \angle 90^\circ}{-j 5}$$

$$= \frac{25 \times 20 (\angle -90^\circ + 90^\circ)}{5 \angle -90^\circ}$$


$$= \frac{25 \times 20}{5} \angle 0 - 90^\circ$$

$$= 100 \angle 90^\circ \Omega$$

$$Z_{eq} = Z_R + Z_C \parallel Z_L$$

$$= 60 + j 100 \Omega$$


$$= 116.61 \angle 59.03^\circ$$

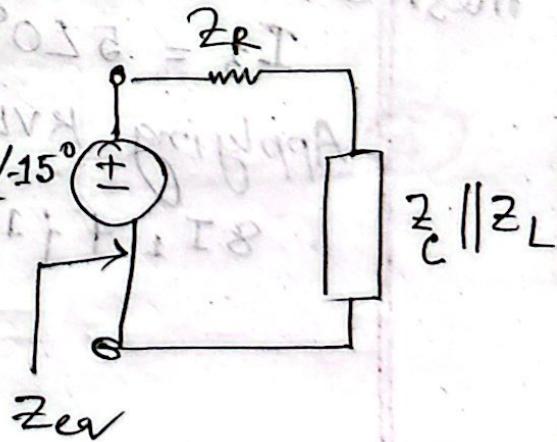

Applying VDR,

$$V_o = \frac{20 \angle -15^\circ \times 100 \angle 90^\circ}{60 + j100}$$
$$= \frac{20 \times 100 \angle -15^\circ + 90^\circ}{116.61 \angle 59.03^\circ}$$
$$= 17.15 \angle 15.96^\circ \text{ V}$$
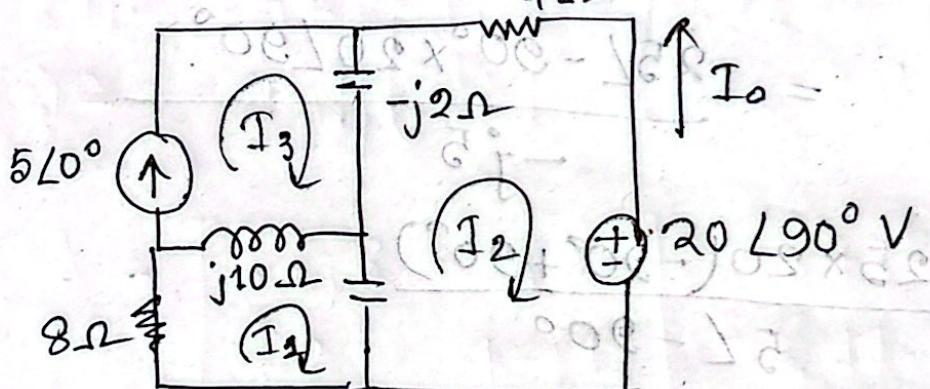
$$v_o(t) = 17.15 \cos(4t + 15.96^\circ) \text{ V}$$



Determine current I_o using mesh analysis.

Sum of
mesh 3,

$$I_3 = 5 \angle 0^\circ \text{ A}$$

Applying KVL in mesh 1,

$$8I_1 + j10(I_1 - I_3) + (-j2)(I_1 - I_2) = 0$$

$$\Rightarrow 8I_1 + j10I_1 + j10I_3 - j2I_1 + j2I_2 = 0$$

$$\Rightarrow (8+j8)I_1 + 12I_2 - j10I_3 = 0 \quad (11)$$

Applying KVL in mesh 2,

$$+ (j2)(I_2 - I_1) + (-j2)(I_2 - I_3 + 4I_2 + 20\angle 90^\circ = 0$$

$$\Rightarrow -j2I_1 + j2I_1 - j2I_2 + j2I_3 + 4I_2 + 20\angle 90^\circ = 0$$

$$\Rightarrow j2I_1 + 4I_2 - j4I_2 + j2I_3 + j20 = 0$$

$$\Rightarrow j2I_1 + (4-j4)I_2 + j2I_3 = -j20$$

$$\Rightarrow j2I_1 + (4-j4)I_2 + j2I_3 + j2I_3 = 20\angle -90^\circ \quad (11)$$

In equation (ii) & (iii) substituting $I_3 = 5\angle 0^\circ A$

$$I_1(8+j8) + j2I_2 - j10 \times 5\angle 0^\circ = 0$$

$$\Rightarrow I_1(8+j8) + 12I_2 - 50\angle 0^\circ \times 5\angle 0^\circ = 0$$

$$\Rightarrow I_1(8+j8) + j2I_2 - 50\angle 0^\circ = 0$$

$$\Rightarrow I_1(8+j8) + j2I_2 = 50\angle 0^\circ \quad (A)$$

$$A^2 8F \xrightarrow{\text{PHE}} S.C.D. = \frac{S.A.}{A} = S.F. = 0.1$$

$$j2I_1 + (4 - j4)I_2 + j2 \times 5 \angle 0^\circ = 20 \angle -90^\circ$$

$$\Rightarrow j2I_1 + (4 - j4)I_2 + 2 \angle 90^\circ \times 5 \angle 0^\circ = 20 \angle -90^\circ$$

$$\Rightarrow j2I_1 + (4 - j4)I_2 + \underbrace{10 \angle 90^\circ}_{j10} = 20 \angle -90^\circ$$

$$\Rightarrow j2I_1 + (4 - j4)I_2 = j20 - j10$$

$$\Rightarrow j2I_1 + (4 - j4)I_2 = -j30 = 30 \angle -90^\circ \quad \text{(B)}$$

$$\begin{bmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 30 \angle 90^\circ \\ -j30 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{bmatrix} = (8 + j8)(4 - j4) - j2 \times j2$$

$$\Delta_1 = \begin{bmatrix} 50 \angle 90^\circ & j2 \\ 30 \angle -90^\circ & 4 - j4 \end{bmatrix} = 63.90 \angle 144^\circ - (-4)$$

$$\Delta_2 = \begin{bmatrix} 8 + j8 & 50 \angle 90^\circ \\ j2 & 30 \angle -90^\circ \end{bmatrix} = 67.90^\circ = \Delta$$

$$I_0 = -I_2 = \frac{-\Delta_2}{\Delta} = 6.12 \angle 144^\circ \angle 78^\circ A$$