

\*\*\* Page 39 (Exercise) Odd numbers




### Ohm's Law

$$I = \frac{V}{R}$$

$$V = IR = A E$$

$$R = \frac{V}{I}$$

### Passive elements

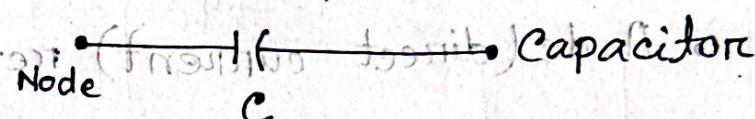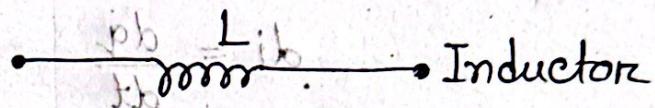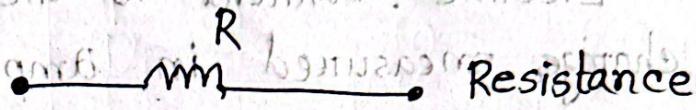

### Circuit


#### I Series

(1st start = 2nd start)

#### II Parallel


(1st start = 2nd start)

(1st end = 2nd end)

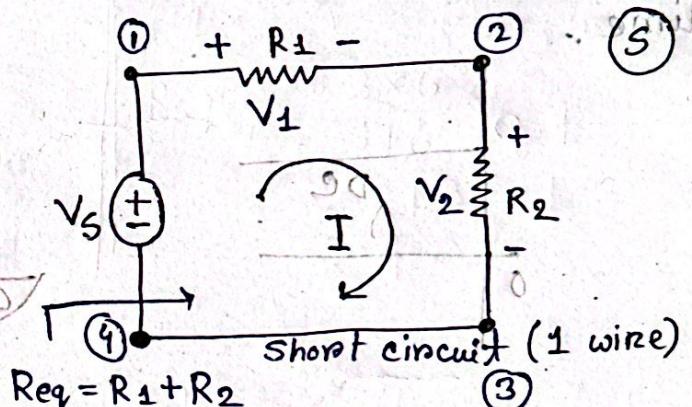

Series circuit

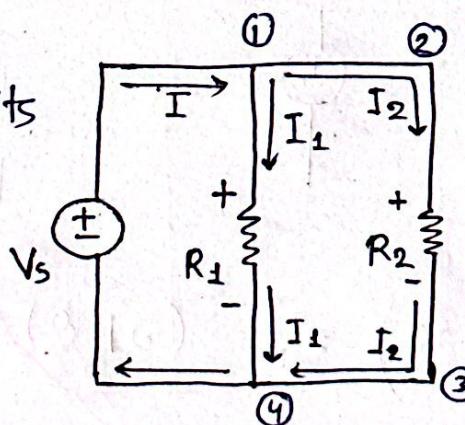\* Here both series and parallel circuits are close loop circle




$$V = V_1 = V_2$$

$$R_{eq} = \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{R_1 R_2}{R_1 + R_2}$$

Parallel circuit

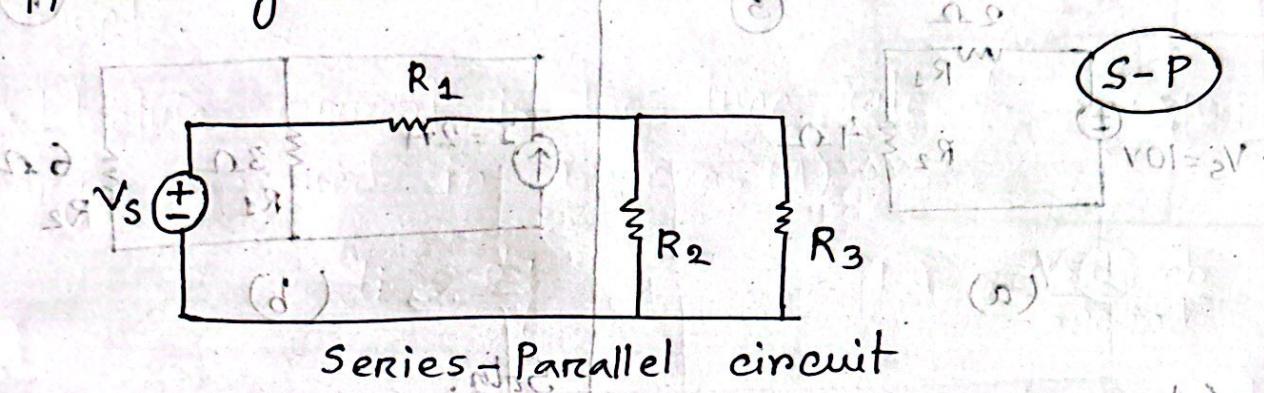- Short circuit is a circuit element with resistance approaching zero.



	Series	Parallel
V	Divided Voltage	Same Voltage
I	Same Current	Divided Current


### Open circuit:

$$V = \text{max}, I(=0 \Omega) = \text{no}$$

$$\text{Short circuit: } I = \text{max}; V = 0$$


	Voltage Source	Current Source
Independent		
Dependent	$\frac{\partial V_o}{\partial S} = 1 + \frac{1}{R_o}$	$\frac{\partial I_o}{\partial S} = 1 + \frac{1}{R_o}$

Determine the equivalent resistance

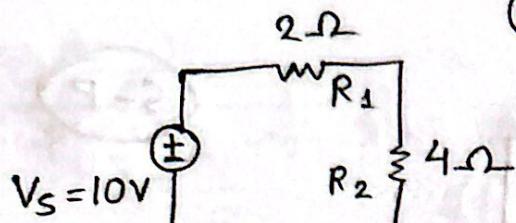

(a)


⑤

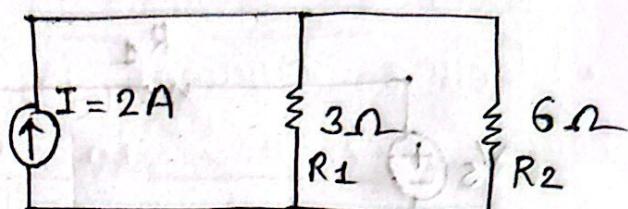

(b)

P


Soln:

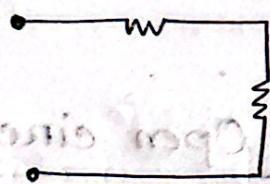

$$R_{eq} = (2 + 4) \Omega$$

$$= 6 \Omega$$

Soln:


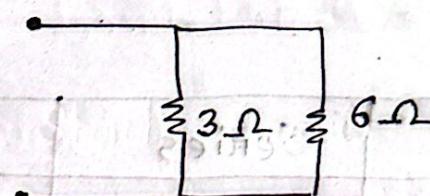


$$R_{eq} = \frac{3 \times 6}{3+6} \Omega$$

$$= 2 \Omega$$

Find  $R_{eq}$ :

Step 1: Open Source

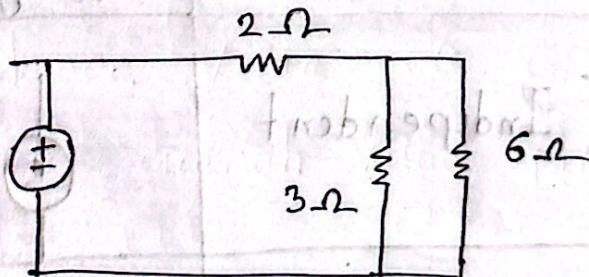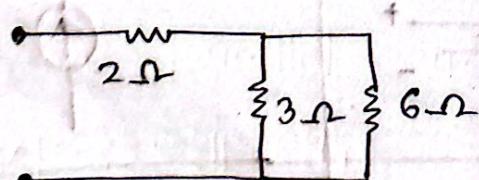



$$R_{eq} : 2 + (3||6)$$

$$I = \left( 2 + \frac{3 \times 6}{3+6} \right) \Omega$$

$$\therefore R_{eq} = 2 + 2 = 4 \Omega$$

Determine the equivalent resistance and current


• Step 1:

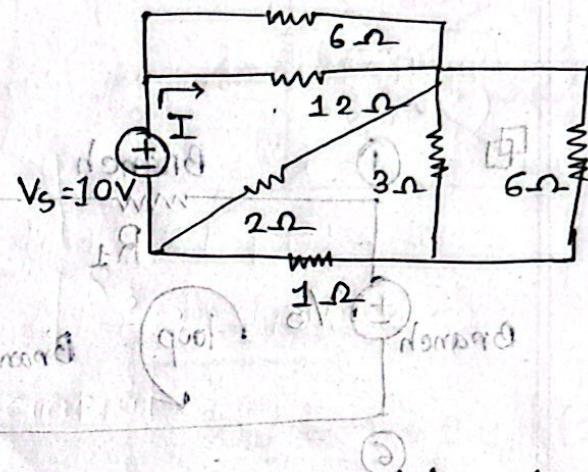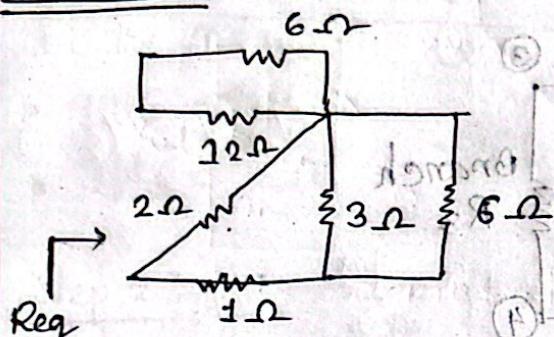

• Step 2: if source is from left to right then solve from right to left.  $\Gamma = d \text{ demand}$

• Step 3:  $(n+1) = d \text{ min}$

$$I - (E + \Sigma) =$$

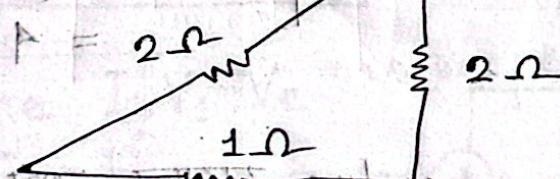


$$\Sigma = 1, e = 90\Omega$$

$$E = n \mid 6 \parallel 12 \parallel 4 \Omega$$


$$3 \parallel 6 = 2 \Omega$$

• Step 4:

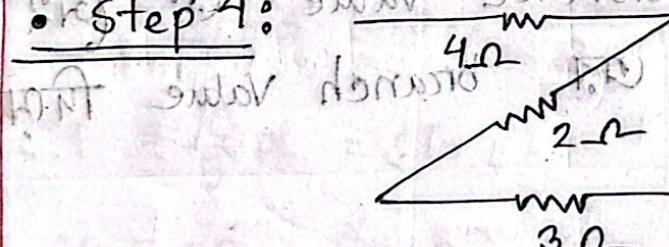

$$1 + 2 = 3 \Omega$$


• Step 5:

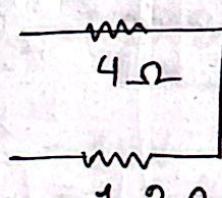

Step 6:  $4 + 1.2 = 5.2 \Omega$

$$\therefore R_{eq} = 5.2 \Omega$$

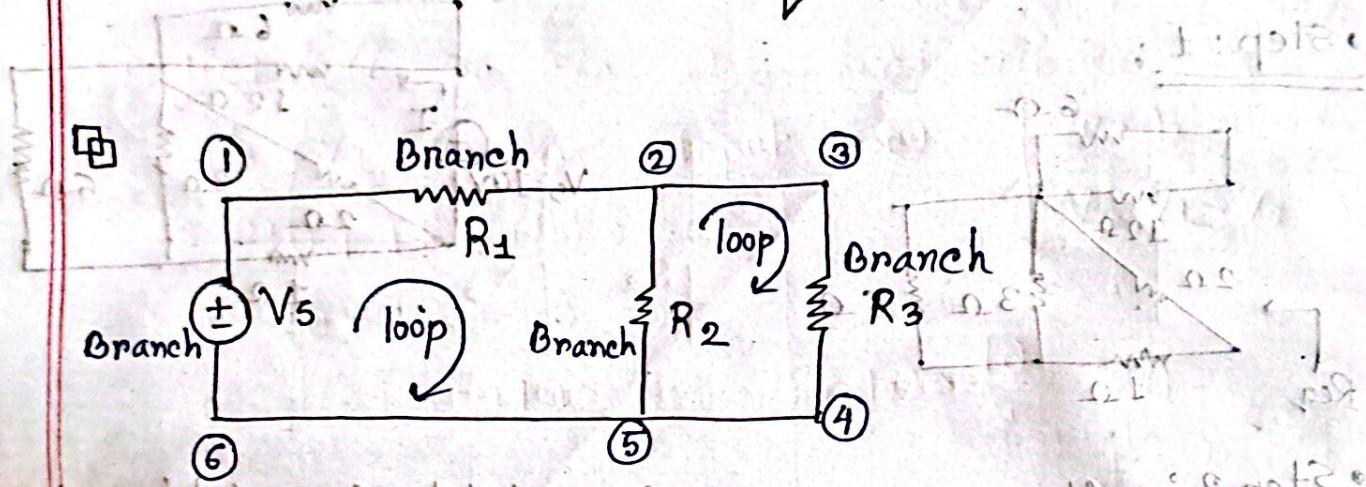Using Ohm's Law:  $I = \frac{V_s}{R_{eq}} = \frac{10}{5.2} = 1.92A$



(2, 3) Short circuit

Branch, b = 4

Loop, l = 2

Nodes, n = 3

$\Omega_f = 2||8$

$$\therefore b = (l+n) - 1 \\ = (2+3) - 1 \\ = 4$$

\* যদি Resistance value অমান হয় parallel circuit  
এবং ক্ষেত্রে তাহলে Resistance Value : কে অর  
branch parallel circuit এর branch value দিয়ে  
আগ জুড়ে হয়,

$$\Omega_f = \Omega_1 + \Omega_2 + \dots$$


no branch.

$$\Omega_f = p \Omega_1$$

Exercise (2) prof. Abdallahs

# Determine the equivalent resistance:


Step 1:

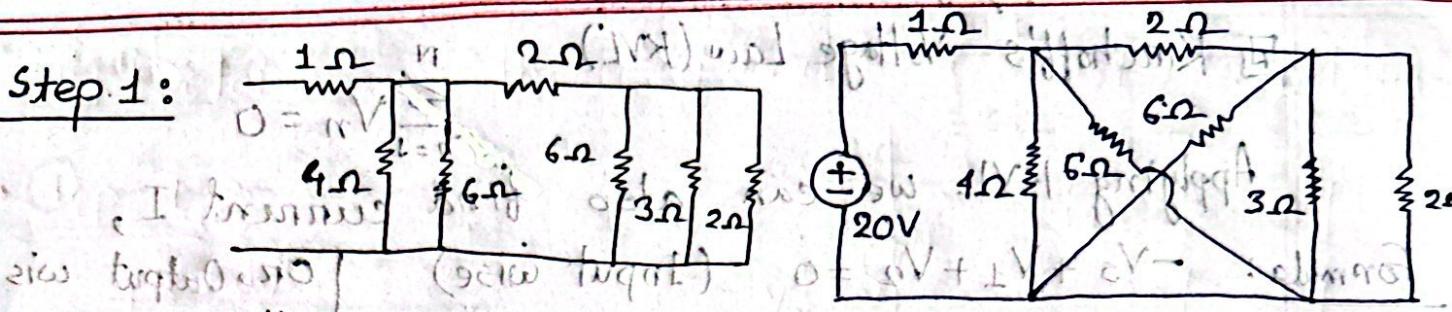

$$\bullet 4 \parallel 6 = 2.4 \Omega$$

$$\bullet 3 \parallel 2 = 1.2 \Omega$$

Step 2:

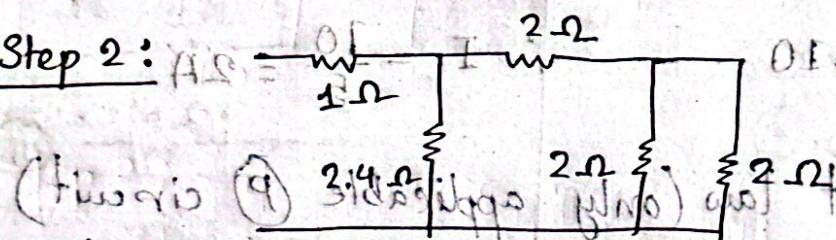


Step 4:

$$R_{eq} = 1 + 2.4 \parallel 3$$

$$= 1 + 2.4 \parallel 3 \\ = 2.33 \Omega$$

Step 3:

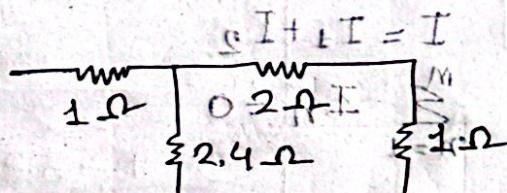


$$I = \frac{20}{1 + 2.4 + 1.2} = I \quad (\text{Ans})$$

# Determine  $I$ ,  $V_1$ ,  $V_2$

$$Req = R_1 + R_2 = 2 + 3 = 5$$

Using Ohm's law,  $I = \frac{V_s}{Req}$

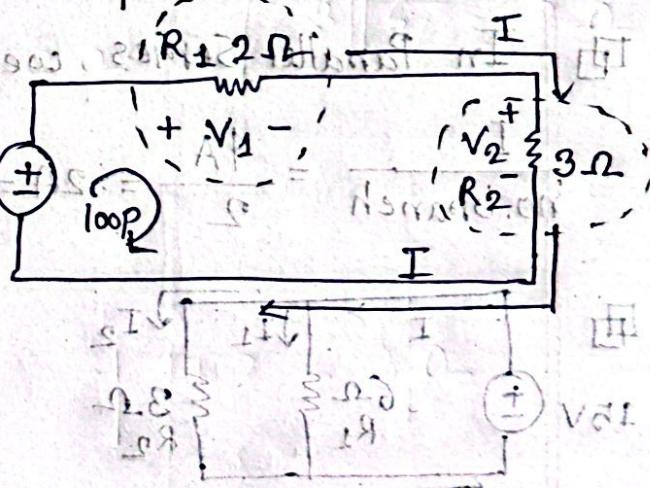

$$V_1 = IR_1 = (2 \times 2) = 4V$$

$$V_2 = IR_2 = (2 \times 3) = 6V$$

$$V_s = 4 + 6 = 10V \quad (\text{source Voltage})$$

Distributed Voltage

$$V_{EL} = 4V - 2V = 2V$$

only applicable for  $\textcircled{S}$  circuit

symmetric topologies with symmetric  $\text{LL}$

### Q) Kirchoff's Voltage Law (KVL)

$$\sum_{n=1}^N V_n = 0$$

Applying KVL we can also find current  $I$ ,


Formula:  $-V_s + V_1 + V_2 = 0$  (Input wise) | Or, Output wise

$$\Rightarrow -10 + IR_1 + IR_2 = 0 \quad | V_s - V_1 - V_2 = 0$$

$$\Rightarrow -10 + I_2 + I_3 = 0$$

$$\Rightarrow I(2+3) = 10 \quad | I = \frac{10}{5} = 2A$$
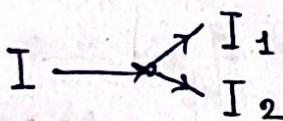
### Q) Kirchoff's Current Law (only applicable $\textcircled{P}$ circuit)





$$I = I_1 + I_2$$

$$\sum_{n=1}^N I_n = 0$$

In Parallel Series we can use
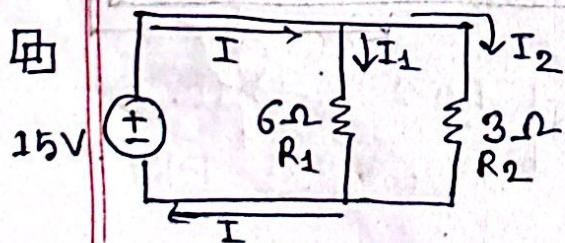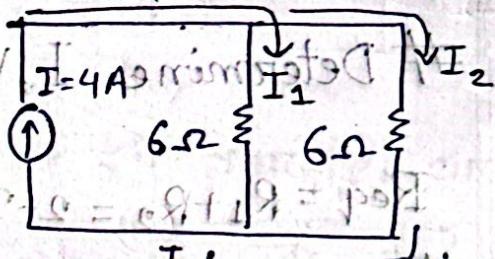
$$\frac{I}{\text{no. branch}} = \frac{4A}{2} = 2A = I_1 = I_2$$



Since Source  $\parallel R_1 \parallel R_2$

$$V_1 = V_2 = V_s = 15V$$

$$I_1 = \frac{V_1}{R_1} = \frac{15}{6} = 2.5A$$

$$I_2 = 5A$$

Using KCL we can find  $I$

$$I = I_1 + I_2 = 2.5 + 5 = 7.5A \quad (\text{Ans})$$

Another way to find  $I$

$$R_{\text{eq}} = \frac{6 \times 3}{6 + 3} = 2\Omega$$




$$\text{Ohm's law } I = \frac{V_s}{R_{\text{eq}}} = \frac{15V}{2\Omega}$$

$$\therefore I = 7.5A \quad (\text{Ans})$$






## Practise

Ans:  $10\ \Omega$

Prac. Prob. 2.9

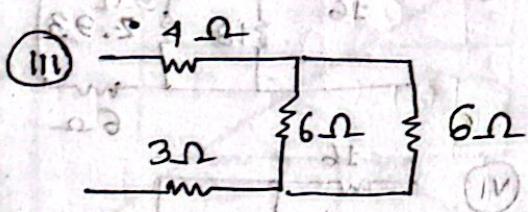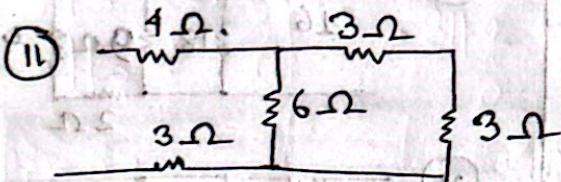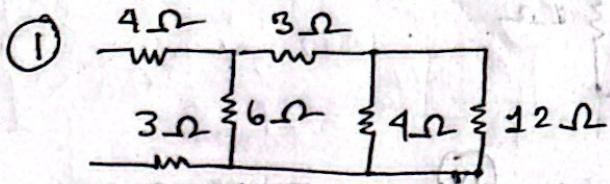


Prob. 2.9

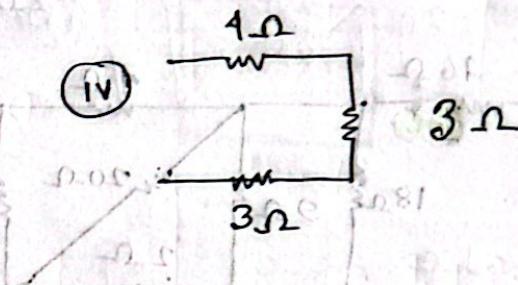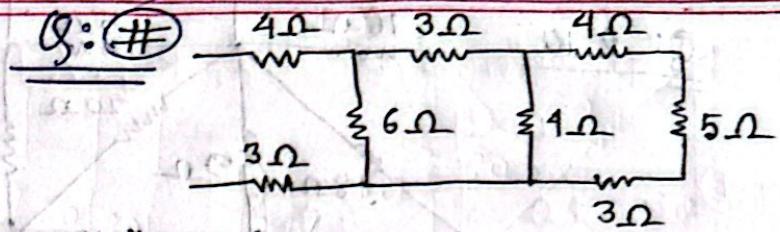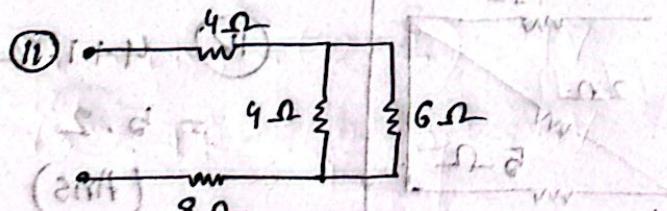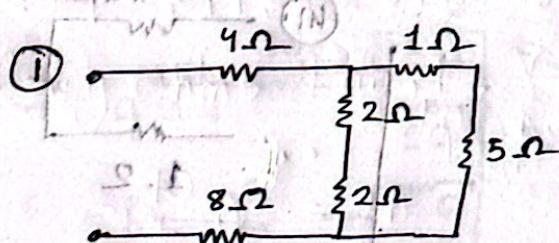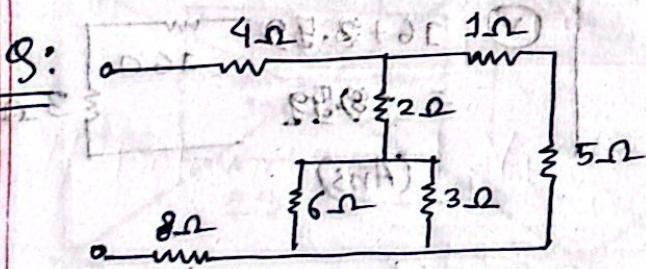


V
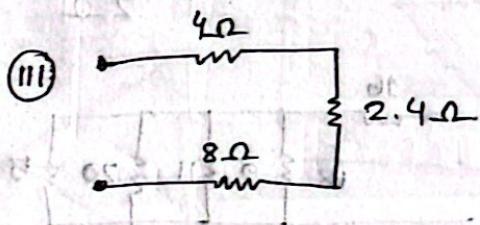
$$4 + 3 + 3 = 10\ \Omega \quad (\text{Ans})$$








N




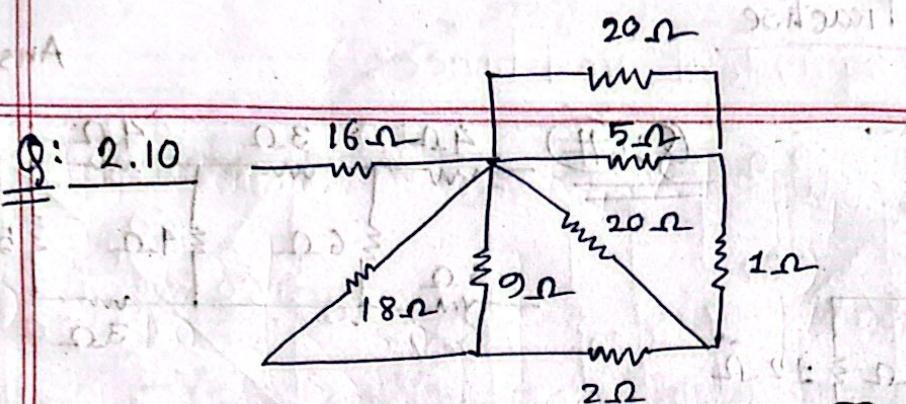
$$2.4 + 4 + 8 = 14.4\ \Omega \quad (\text{Ans})$$



Ans: 19

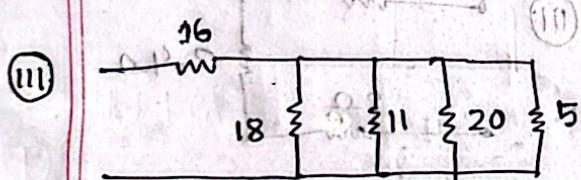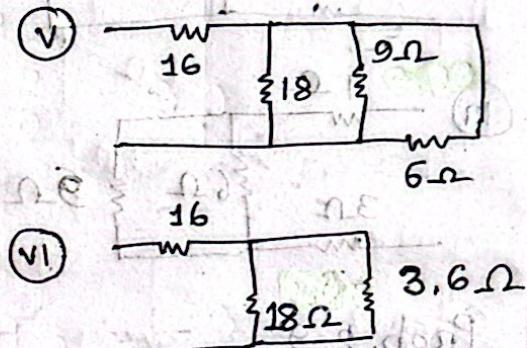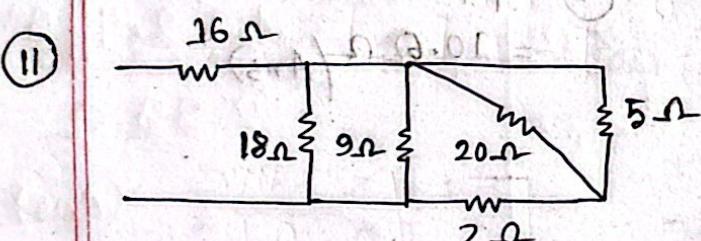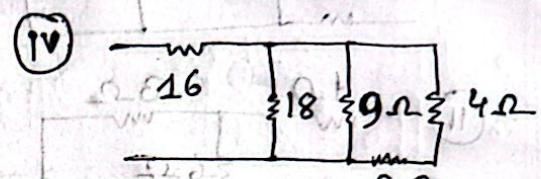
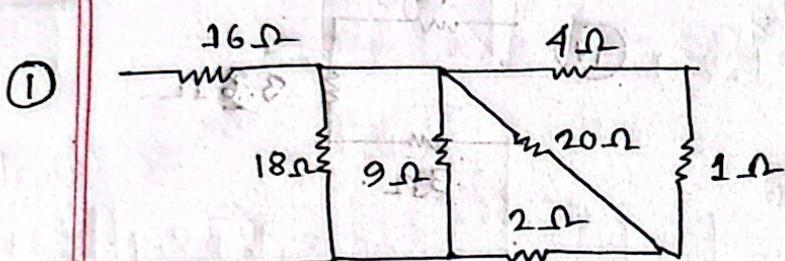

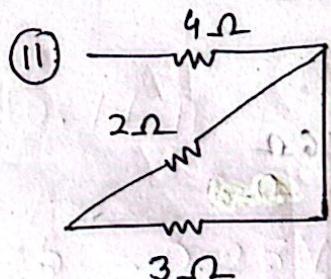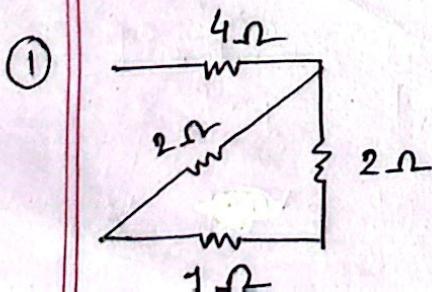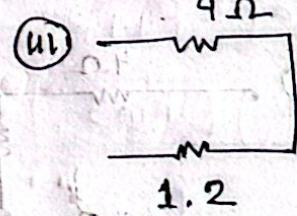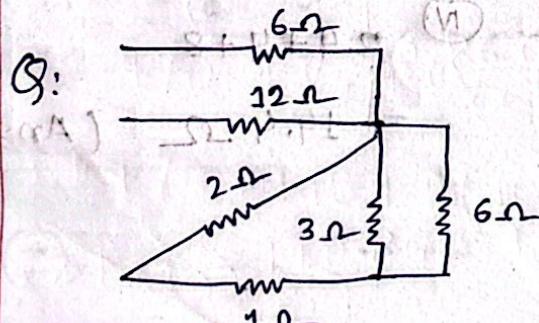
$$\text{⑤ } 16 + 3 = 19 \Omega \quad (\text{Ans})$$




$$\text{⑦ } 4 + 1.2 = 5.2 \quad (\text{Ans})$$


Q: 2.39

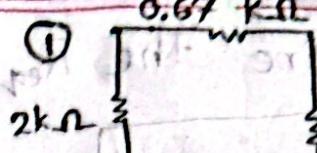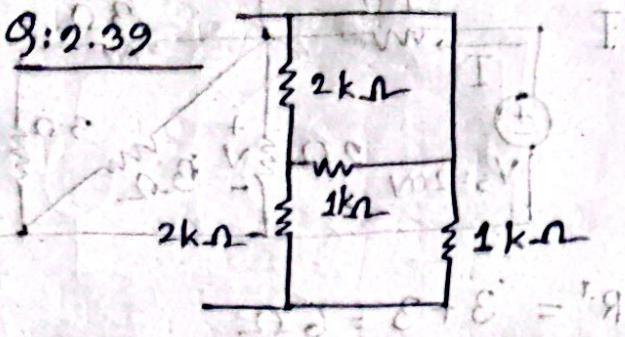




②

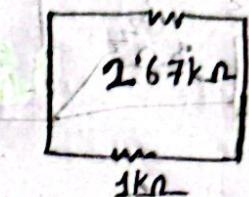

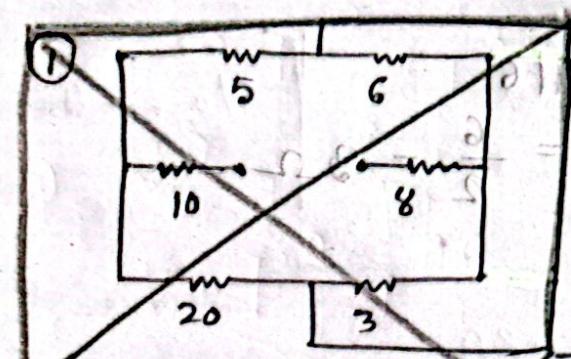
$$\text{③ } \frac{2.67 \times 1}{2.67 + 1} k\Omega = 0.727 k\Omega = 727.5 \Omega \quad (\text{Ans})$$



Q: 2.47

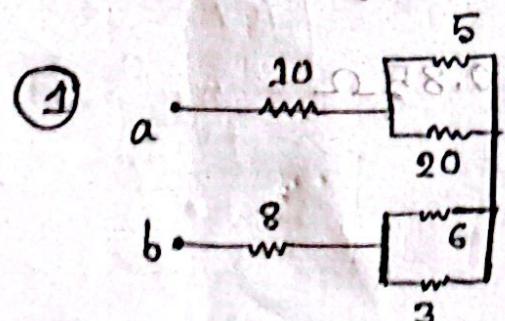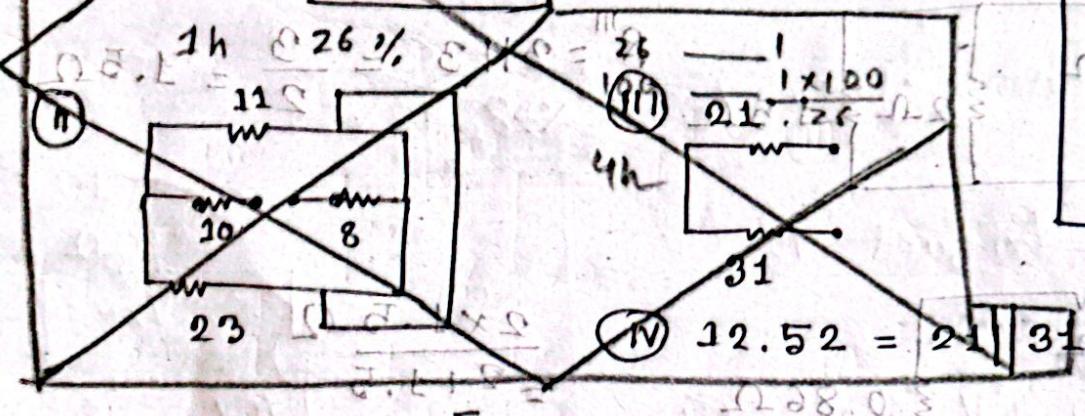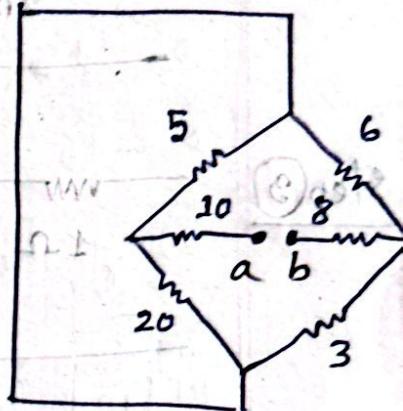

⑤

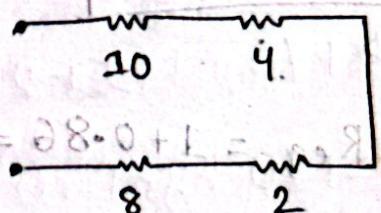



$$\text{⑥ } 10 + 4 + 8 + 2 = 24 \quad (\text{Ans})$$

$$V_{D.C.E} = 28.0 \times 78.0 = 2184 \text{ mV}$$

C.W  
03/07/2A


Determine the  $R_{eq}$ ,  $V$ ,  $I$

Step ①

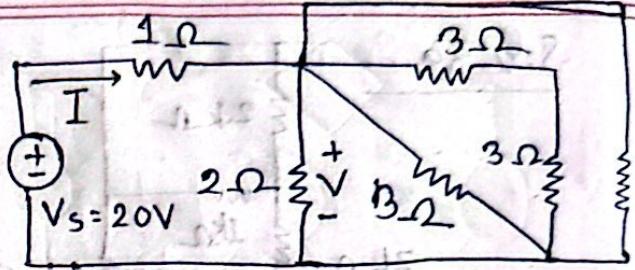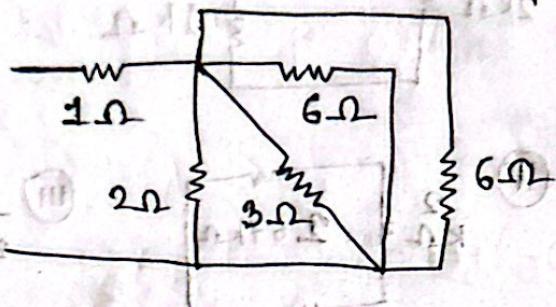

$$R' = 3 + 3 = 6\Omega$$


Step ②

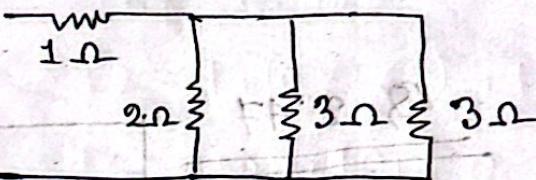

$$6 \parallel 6$$


$$R'' = \frac{6}{2} = 3\Omega$$

Step ③

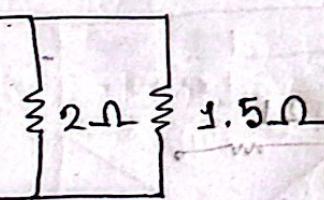

$$R''' = 3 \parallel 3 = \frac{3}{2} = 1.5\Omega$$

Step ④

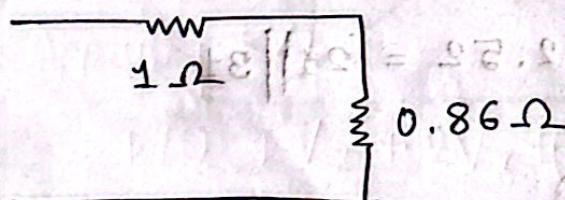

$$\frac{2 \times 1.5\Omega}{2 + 1.5}$$

$$R^IV = 0.85\Omega$$

Step ⑤

$$\therefore R_{eq} = 1 + 0.86 = 1.86\Omega$$

$$\therefore I = \frac{20}{R_{eq}} = \frac{20}{1.86\Omega} = 10.77\text{ A}$$


$$\therefore V = IR^{IV} = 10.77 \times 0.85 = 9.25\text{ V}$$

■ Determine  $V_{ab}$

$$\text{KVL: } -V_s + 2I + 3I + 5I = 0$$

$$\Rightarrow -20 + 10I = 0$$
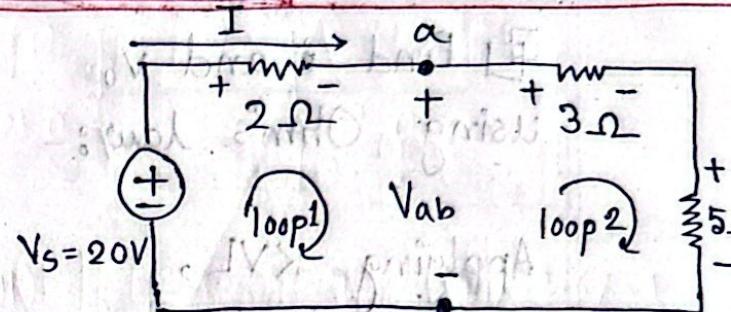
$$\Rightarrow 10I = 20 \quad \therefore I = 2A$$



Applying KVL in loop 1,  $-20 + 2I + V_{ab} = 0$

$$\therefore V_{ab} = 20 - 2 \times 2 = 16V$$

Applying KVL in loop 2,  $-V_{ab} + 3I + 5I = 0$

$$\Rightarrow -V_{ab} = -8I$$

$$\therefore V_{ab} = 8 \times 2 = 16V$$

■ Find  $V_1, V_2$

Using KVL,

$$-32 + V_1 - (-8) - V_2 = 0$$


$$\Rightarrow -32 + 8 + IR_1 - (-I2) = 0$$

$$\Rightarrow -24 + 4I + 2I = 0$$

$$\Rightarrow -24 + 6I = 0$$

$$\Rightarrow 6I = 24$$

$$\therefore I = 4A$$

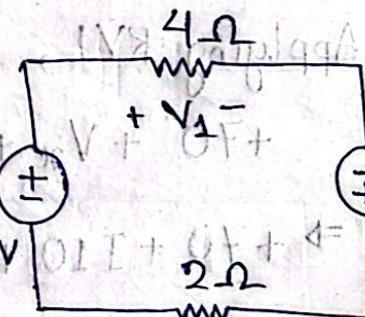


$$V_1 = IR_1 = 4 \times 4 = 16V$$

$$V_2 = -IR_2 = -4 \times 2 = -8V$$

Find  $i$  and  $v_o$  using Ohm's law :-

Applying KVL,

$$-12 + 4i + 2v_o - 4 - (-6i) = 0$$

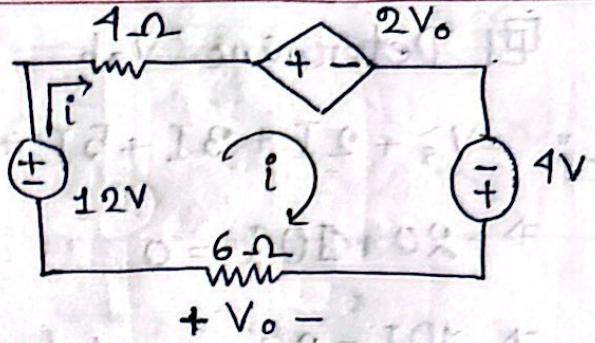

$$\Rightarrow -12 - 4 + 2v_o + 10i = 0$$

$$v_o = -6i$$

$$\Rightarrow -12 - 4 + (2 \times -6i) + 10i = 0$$

$$\Rightarrow -16 - 12i + 10i = 0$$


$$\Rightarrow -16 - 2i = 0 \quad \therefore i = -8A$$

$$\text{using Ohm's law, } v_o = -6 \times -8 = 48V$$

Find  $v_x$  and  $v_o$

Applying KVL,

$$+70 + v_x + 2v_x - (-v_o) = 0$$

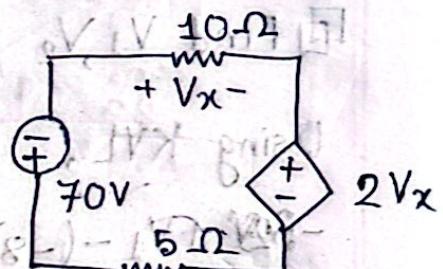

$$\Rightarrow +70 + 10I + 2(10I) + 5I = 0$$

$$\Rightarrow +70 + 35I = 0$$

$$\Rightarrow I = -2A$$

$$\therefore v_x = 10 \times -2 = -20V$$

$$\therefore v_o = -5 \times -2 = 40V$$

Find  $V_o$  and  $i_o$ .

Applying KCL at node A,

$$15 = i_o + \frac{V_o}{4} + i_1$$

$$\Rightarrow 15 = \frac{V_o}{2} + \frac{V_o}{4} + \frac{V_o}{12}$$


$$\Rightarrow 15 = \frac{17V_o}{24}$$

$$\therefore V_o = \frac{24 \times 15}{17} = 21.176$$

$$i_o = \frac{V_o}{2} = \frac{21.176}{2} = 10.58A \quad (\text{Ohm's Law})$$

Voltage divider rule


(S) circuit

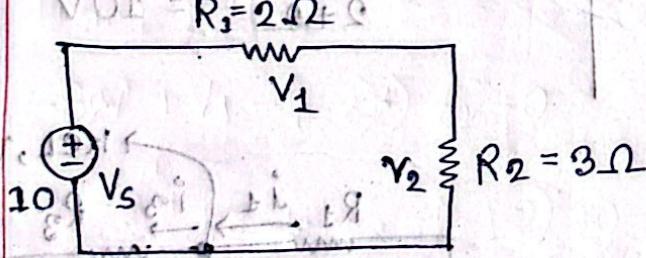

$$+V_1 = \frac{V_s R_1}{R_1 + R_2} = \frac{10 \times 2}{5} = 4V$$

$$+V_2 = \frac{V_s R_2}{R_1 + R_2} = \frac{10 \times 3}{5} = 6V$$


e.I. e.I. I. 6V 4V 12Ω A

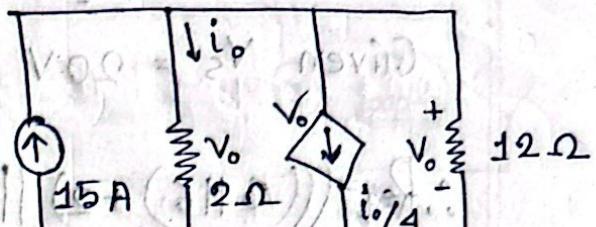

e.I. e.I. I. 6V 4V 12Ω

Current divider rule

(P) circuit

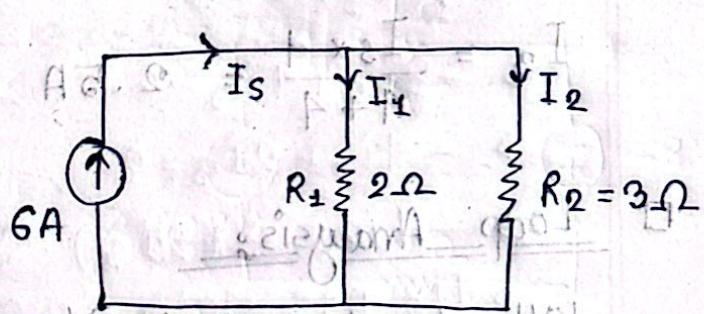

$$I_1 = \frac{I_s R_1}{R_1 + R_2} \quad \text{যদি } 3 \text{টা থাকে}$$

$$I_2 = \frac{I_s R_2}{R_1 + R_2}$$

Find  $V_1, V_2, I_1, I_2, I_3$

Given  $V_s = 20V$

$$\therefore R_{eq} = ((3 \parallel 6) + 2) \parallel 4 + 2$$

$$= (2 + 2 \parallel 4) + 2$$


$$= (4 \parallel 4) + 2 = 2 + 2 = 4\Omega$$

$$\therefore I_s = \frac{V_s}{R_{eq}} = \frac{20}{4} = 5A$$

$$I_1 = \frac{I_s \times 4}{4+4} = 2.5A$$


$$I_2 = \frac{I_1 \times 6}{3+6} = 1.6A$$
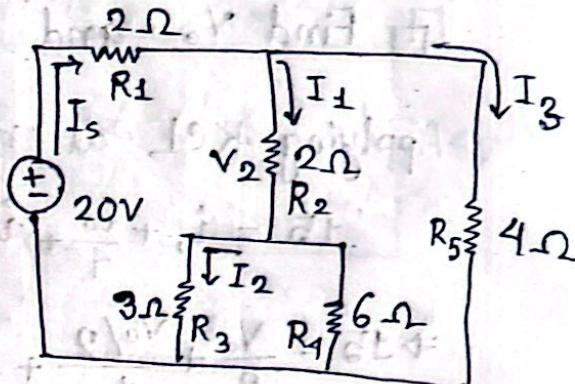
$$I_3 = \frac{I_s \times 1}{4+4} = 2.5A$$



$$V_1 = \frac{20 \times 2}{2+2} = 10V$$

$$V_2 = \frac{20 \times 2}{2+2} = 10V$$

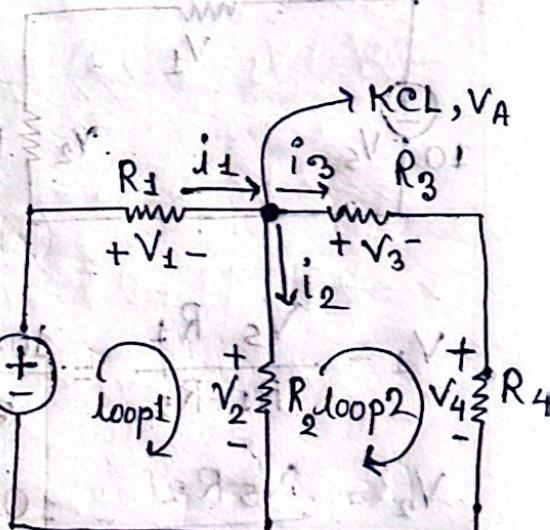

### Loop Analysis:

$$KVL \text{ loop } 1, -V_s + V_1 + V_2 = 0$$

$$\text{for loop 2, } -V_2 + V_3 + V_1 = 0$$

Applying KCL in node A,

$$i_1 = i_2 + i_3$$

$$\text{Ohm's Law apply, } i_1 = \frac{V_1}{R_1}, i_2 = \frac{V_2}{R_2}, \dots$$

$$V_s - V_A = V_1$$

# Practise


6 - omni tool  
F2021T0180

v? i<sub>x</sub>?

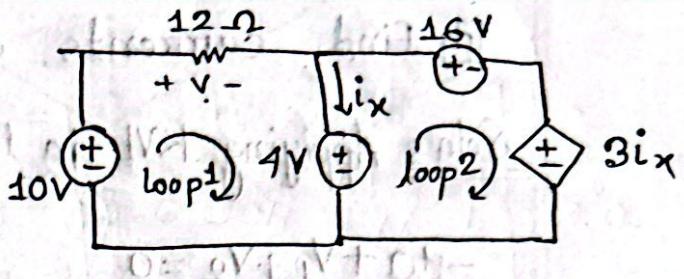2.15 Applying KV L,

$$\text{loop 1}, -10 + v + 4 = 0$$

$$\Rightarrow -6 + v = 0 \quad \therefore v = 6 \text{ V}$$



$$\text{loop 2}, -4 + 16 + 3i_x = 0$$

$$\Rightarrow +12 + 3i_x = 0$$

$$\Rightarrow 3i_x = -12 \quad \therefore i_x = \frac{-12}{3} = -4 \text{ A}$$

2.19  $-12 + 10 - (-3I) - (-8) = 0$

$$\Rightarrow 6 + 3I = 0$$

$$\therefore I = -2 \text{ A}$$

$$P_1 = 12 \times 2 = -24 \text{ W}$$

$$P_2 = 10 \times 2 = -20 \text{ W}$$

$$P_3 = -3 \times 2 = -6 \text{ W (wrong)}$$


$$P_4 = -8 \times 2 = 16 \text{ W}$$

$$\frac{\partial \Omega E - \partial I + \mathcal{E}}{F^-} = \frac{(i_1 \mathcal{E} - i_2) \Omega + 3 \mathcal{E}}{F^-} = \frac{i_1 (\mathcal{E} + 6) + i_2 (-8)}{F^-} = i_1 \Omega + i_2 F^-$$

$$\mathcal{E} + \mathcal{E} = i_1 \Omega$$

$$A \mathcal{E} + \mathcal{E} = i_1 \Omega$$

(cont)

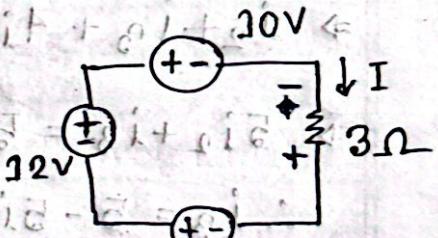

Lecture - 3  
08/07/2024

Find currents and voltage

Soln: Applying KVL in loop 1,

$$-10 + V_1 + V_2 = 0$$

$$\Rightarrow V_1 + V_2 = 10$$

$$\Rightarrow 2i_1 + 8i_2 = 10$$

$$\Rightarrow i_1 + 4i_2 = 5$$

$$\Rightarrow i_2 + i_3 + 4i_2 = 5$$

$$\Rightarrow 5i_2 + i_3 = 5 \quad \dots \dots \dots \textcircled{1}$$

$$\therefore i_3 = 5 - 5i_2$$

Applying KVL in loop 2,

$$-V_2 + V_3 - 6 = 0$$

$$\Rightarrow -8i_2 + 4i_3 = 6$$

$$\Rightarrow -4i_2 + 2i_3 = 3$$

$$\Rightarrow -4i_2 + 2(5 - 5i_2) = 3$$


$$\Rightarrow -4i_2 + 10 - 10i_2 = 3$$

$$\Rightarrow -14i_2 = -7$$

$$\Rightarrow i_2 = \frac{-7}{-14} = 0.5 \text{ (Ans)}$$

$$\text{putting value } i_2 = (5 \times 0.5) + i_3 = 5$$

$$\therefore i_3 = 2.5 \text{ A (Ans)}$$

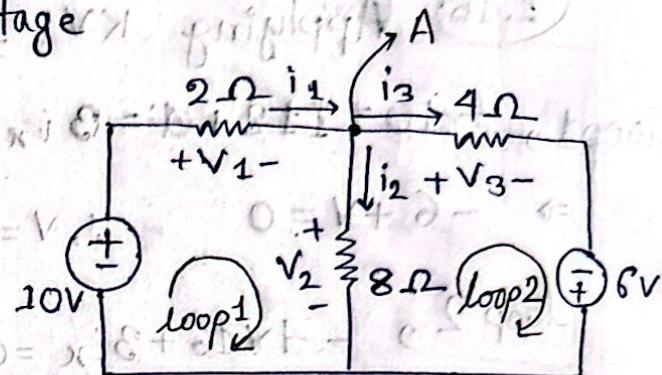

Applying KCL in node A

$$i_1 = i_2 + i_3$$

$$\therefore i_1 - i_2 - i_3 = 0$$

Using Ohm's law,

$$V_1 = 2i_1$$

$$V_2 = 8i_2$$

$$V_3 = 4i_3$$

$$\therefore i_1 = 0.5 + 2.5$$

$$\therefore i_1 = 3 \text{ A (Ans)}$$


$$V_1 = 2i_1 = 2 \times 3 = 6V \quad (\text{Ans})$$

$$V_2 = 8i_2 = 8 \times 0.5 = 4V \quad (\text{Ans})$$

$$V_3 = 4i_3 = 4 \times 2.5 = 10V \quad (\text{Ans})$$

$$\begin{aligned} 5i_2 &= 5 - 3.18 \\ \Rightarrow 5i_2 &= 1.82 \\ \therefore i_2 &= 0.36A \end{aligned}$$

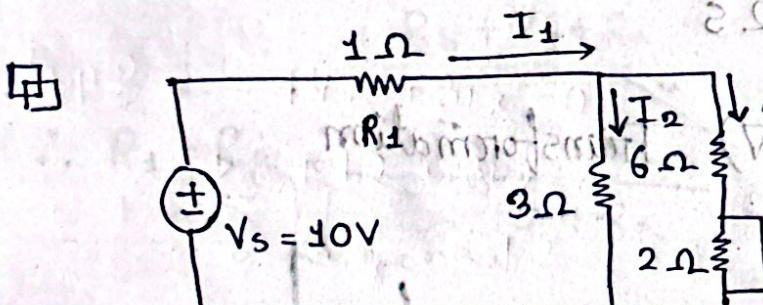
$$\begin{aligned} i_1 &= i_2 + i_3 \\ &= 0.36 + 3.18 \\ &= 3.54A \end{aligned}$$



Find  $I_1, I_2, I_3$  &  $V$ .

$$I_1 = \frac{V_s}{R_1} = \frac{10}{3} = 3.33A$$
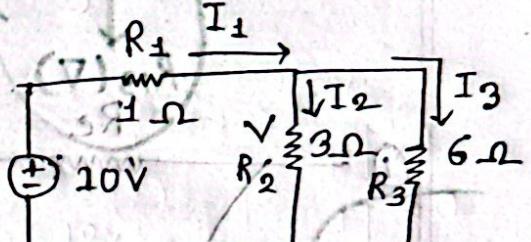
$$\text{CDR, } I_2 = \frac{I_1 \times R_3}{R_2 + R_3} = 2.22A$$



$$\text{Req} = 1 + R' = 1 + 2 = 3\Omega$$

$$\text{CDR, } I_3 = \frac{I_1 \times R_2}{R_2 + R_3} = 1.11A$$

$$R' = R_2 \parallel R_3 = \frac{3 \times 6}{3+6} = 2\Omega \quad \therefore V = 2.22 \times 2 = 4.44V$$

Another way to solve : Applying KVL ;  $-10 + 1I_1 + 3I_2 = 0$  (loop 1)  
again KVL ;  $-3I_2 + 6I_3 = 0$  (loop 2)


KCL in node A,  $I_1 = I_2 + I_3$

conductance,  $G = \frac{1}{R}$  ( $\text{A/V}$ )

□  $R_{eq} = 2 + 3 \Omega$


$$G_1 = \frac{1}{2} S, G_2 = \frac{1}{3} S$$
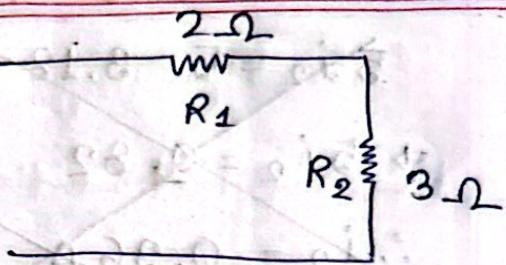
$$G_{eq} = \frac{2 \times 3}{2+3} = 1.2 S$$




□ WYE-DELTA ( $\Delta$ - $\gamma$ ) Transformation

(T- $\pi$ )

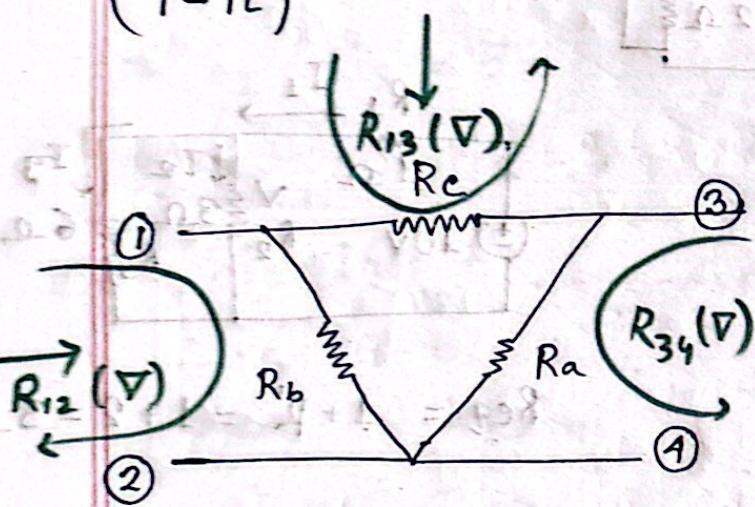

$\Delta$  connection

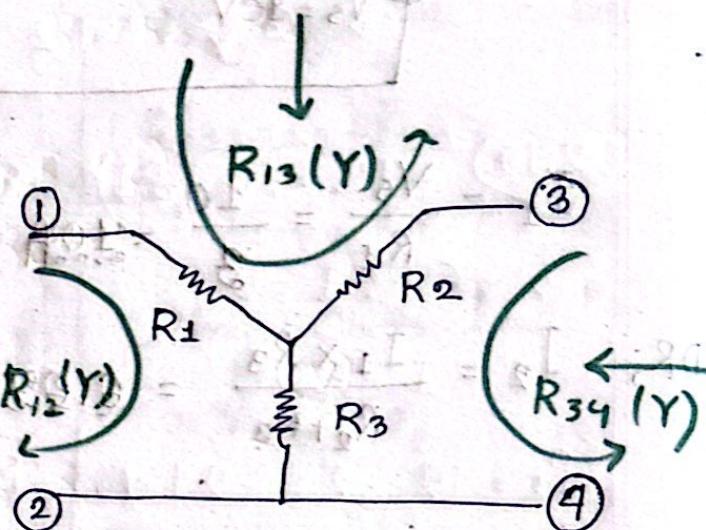

$\gamma$  connection

$$R_{12}(\Delta) = R_b \parallel (R_c + R_a)$$

$$R_{13}(\Delta) = R_c \parallel (R_a + R_b)$$

$$R_{34}(\Delta) = R_a \parallel (R_b + R_c)$$

$$R_{12}(Y) = R_1 + R_3$$

$$R_{13}(Y) = R_1 + R_2$$

$$R_{34}(Y) = R_2 + R_3$$

$$\therefore R_{12}(Y) = R_{12}(\nabla)$$

$$R_1 + R_3 = R_b \parallel (R_c + R_a)$$

$$\Rightarrow R_1 + R_3 = \frac{R_b \times (R_c + R_a)}{R_b + R_c + R_a}$$

$$\therefore R_1 + R_3 = \frac{R_b R_c + R_b R_a}{R_b + R_c + R_a} \quad \text{--- (I)}$$

$$\therefore R_{13}(Y) = R_{13}(\nabla)$$

$$\Rightarrow R_1 + R_2 = \frac{R_c \times (R_a + R_b)}{R_a + R_b + R_c}$$

$$\Rightarrow R_1 + R_2 = \frac{R_a R_c + R_c R_b}{R_a + R_b + R_c} \quad \text{--- (II)}$$

$$\therefore R_{34}(Y) = R_{34}(\nabla)$$

$$\Rightarrow R_2 + R_3 = R_a \parallel (R_b + R_c)$$

$$\Rightarrow R_2 + R_3 = \frac{R_a \times (R_b + R_c)}{R_a + R_b + R_c}$$

$$\therefore R_2 + R_3 = \frac{R_a R_b + R_a R_c}{R_a + R_b + R_c} \quad \text{--- (III)}$$

eq ① - eq ③ ,

$$R_1 - R_2 = \frac{R_b R_c - R_a R_c}{R_a + R_b + R_c} \quad \text{--- (IV)}$$

eq ② + eq ④ ,

$$R_1 + R_2 + R_1 - R_2 = \frac{2 R_b R_c + 2 R_a R_c}{R_a + R_b + R_c}$$

$$\Rightarrow 2 R_1 = \frac{2 (R_b R_c)}{R_a + R_b + R_c} \quad \text{--- (V)}$$

$$\therefore R_1 = \frac{R_b R_c}{R_a + R_b + R_c} \quad \text{--- (V)}$$

Substituting  $R_1$  in eq ② ,

$$R_2 = \frac{R_a R_c + R_c R_b}{R_a + R_b + R_c} - \frac{R_b R_c}{R_a + R_b + R_c}$$

$$\therefore R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$


So, Similarly,

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$\Delta$  to Y  
conversion

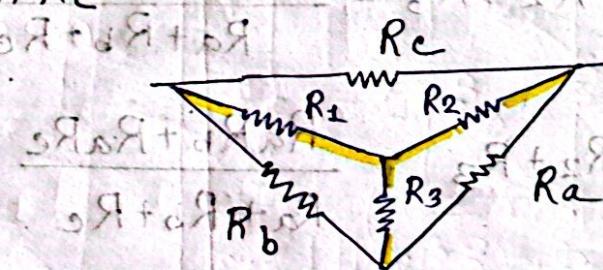

$$\begin{aligned}
 R_1 R_2 + R_2 R_3 + R_3 R_1 &= \frac{R_b R_c (R_c R_a)}{(R_a + R_b + R_c)^2} + \frac{(R_c R_a)(R_a R_b)}{(R_a + R_b + R_c)^2} + \frac{(R_b R_c)(R_a R_b)}{(R_a + R_b + R_c)^2} \\
 &= \frac{R_a R_b R_c^2 + R_a^2 R_b R_c + R_a R_b^2 R_c}{(R_a + R_b + R_c)^2} \\
 &= \frac{R_a R_b R_c (R_a + R_b + R_c)}{(R_a + R_b + R_c)^2} \\
 \therefore R_1 R_2 + R_2 R_3 + R_3 R_1 &= \frac{R_a R_b R_c}{R_a + R_b + R_c}, \quad \text{--- (A)}
 \end{aligned}$$

eqn (A) ÷ eqn ①,

$$\frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{\cancel{R_a R_b R_c}}{\cancel{R_a + R_b + R_c}} = R_c$$

So, similarly

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$



$\Delta$  to  $\nabla$  conversion

$$(e.m.f) A.E.B = \frac{0.5}{0.5} = \frac{eV}{joule} = I \quad \therefore$$




Find  $I$  using  
WYE - DELTA Transformation.

$\Delta$  to  $\nabla$ :

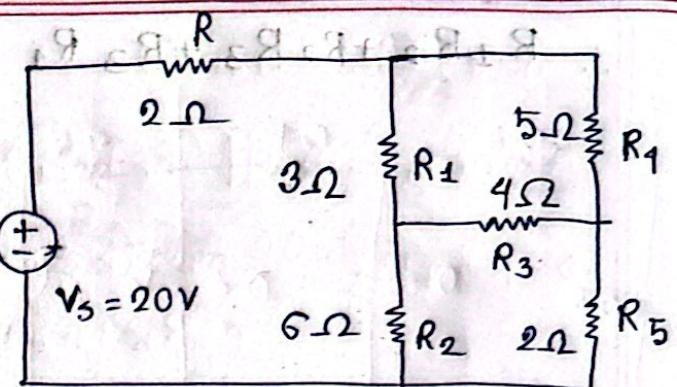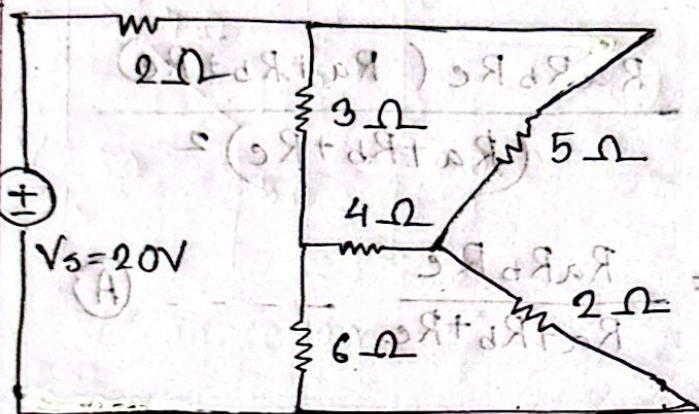

1 mpa ÷ 10 mpa

Step 2:

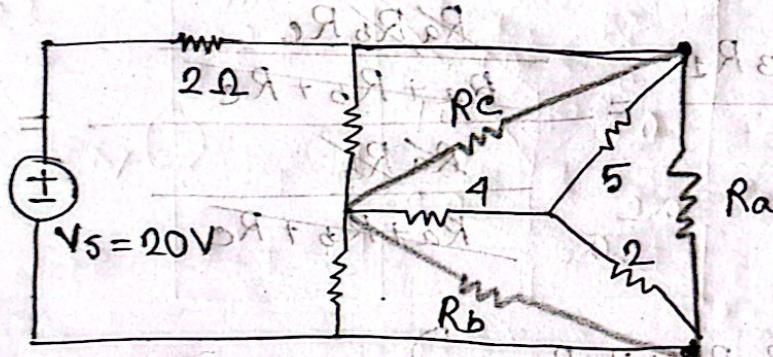


$$R_a = \frac{(4 \times 5) + (5 \times 2) + (2 \times 4)}{5} = 9.5 \Omega$$

$$R_b = \frac{(4 \times 5) + (5 \times 2) + (2 \times 4)}{5} = 7.6 \Omega$$

$$R_c = \frac{(4 \times 5) + (5 \times 2) + (2 \times 4)}{2} = 19 \Omega$$


$$\begin{aligned} R_{eq} &= (19 + 9.5) \parallel 7.6 \parallel (3 + 4) \\ &= (6 \parallel 9) + 2 \\ R_{eq} &= 3.6 + 2 = 5.6 \end{aligned}$$
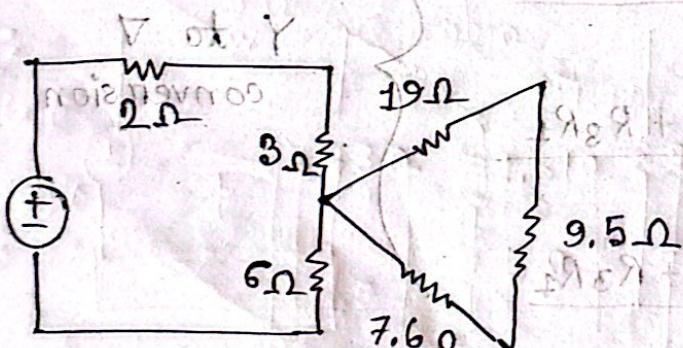
$$\therefore I = \frac{V_s}{R_{eq}} = \frac{20}{5.6} = 3.5 A \quad (\text{Ans})$$




We can also solve this by  $\Delta$  to  $\Gamma$  conversion:

Step 1:

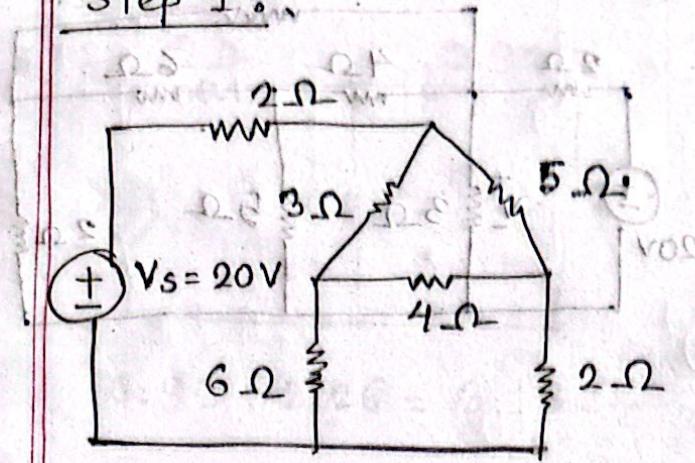

Step 2:

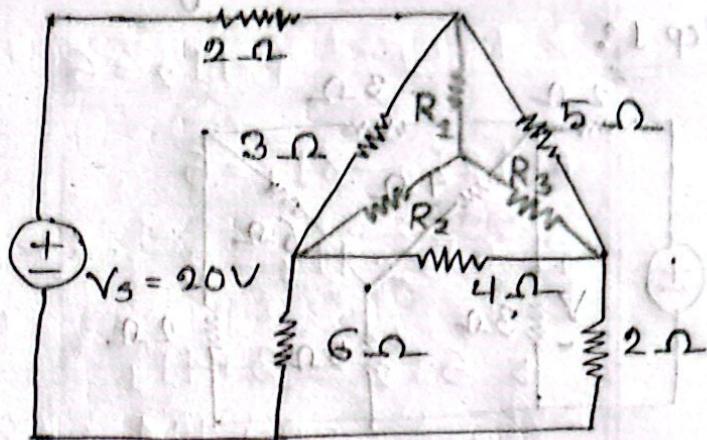

$$R_1 = \frac{5 \times 3}{3 + 4 + 5} = 1.25\Omega$$


$$R_2 = \frac{3 \times 1}{3 + 4 + 5} = 1\Omega$$

$$R_3 = \frac{5 \times 1}{3 + 4 + 5} = 1.67\Omega$$

$$\begin{aligned} R_{eq} &= ((1+6) \parallel (1.67+2)) + 1.25 + 2 \\ &= 2.40 + 1.25 + 2 \\ &= 5.65\Omega \end{aligned}$$

$$I = \frac{V_s}{R_{eq}} = \frac{20}{5.65} = 3.54\text{ A (Ans)}$$

Step 3:


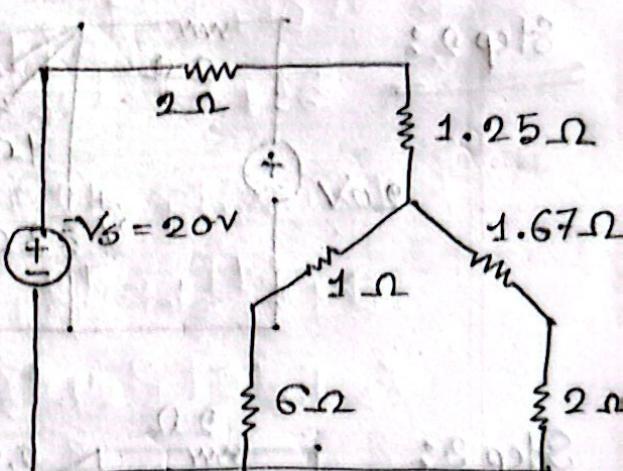


09/07/2024

#Determine the current I

and the voltage V.


Step 1:

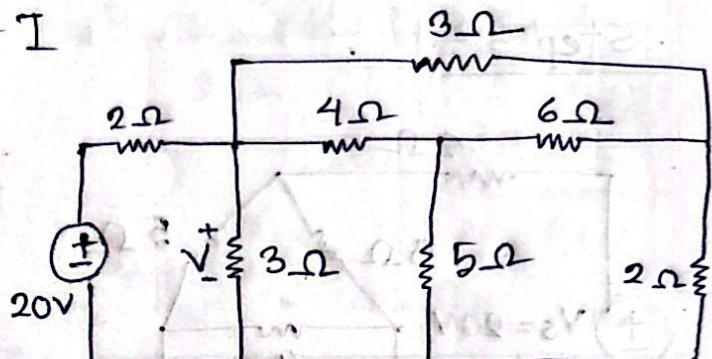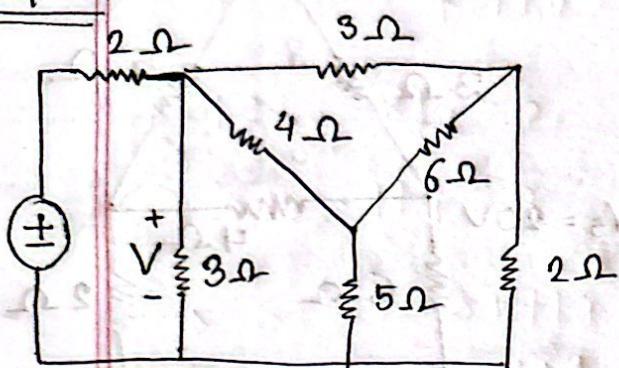

▽ connection

$$R_1 = \frac{4 \times 3}{3+4+6} = 0.92\Omega$$


Step 2:

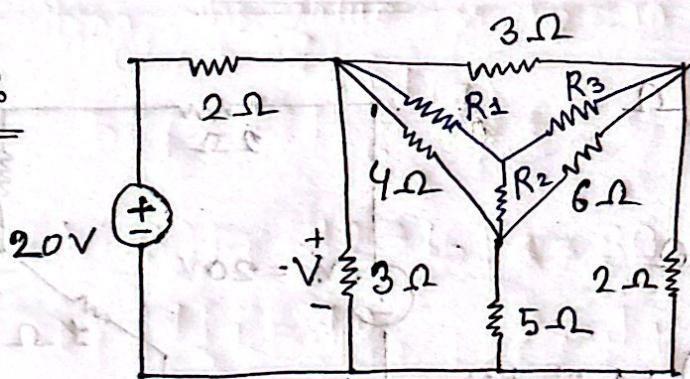

$$R_2 = \frac{6 \times 4}{3+4+6} = 1.81\Omega$$

$$R_3 = \frac{3 \times 6}{3+4+6} = 1.38\Omega$$


Step 3:

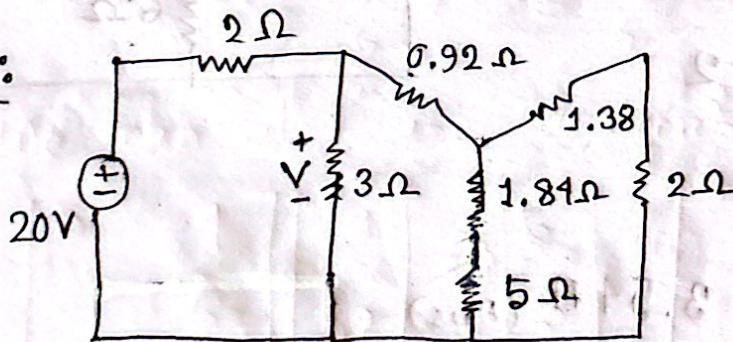

$$1.81 + 5 = 6.81\Omega$$


$$1.38 + 2 = 3.38\Omega$$

Step 4:

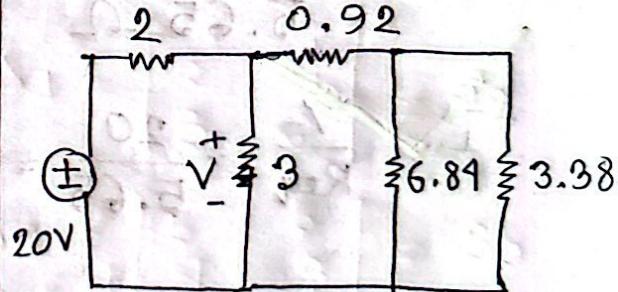


$$6.81 || 3.38 = 2.26\Omega$$

### Step 5:

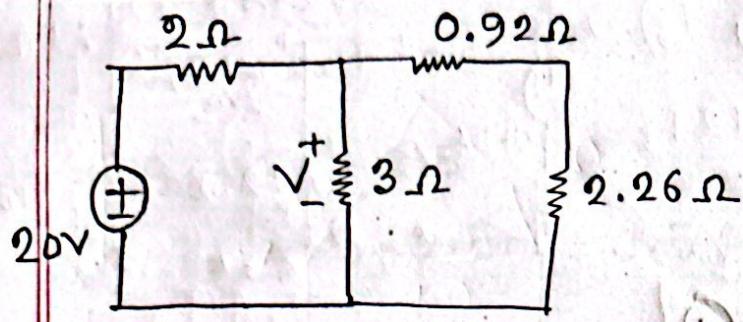

$$0.92 + 2.26 = 3.18 \Omega$$

### Step 6:

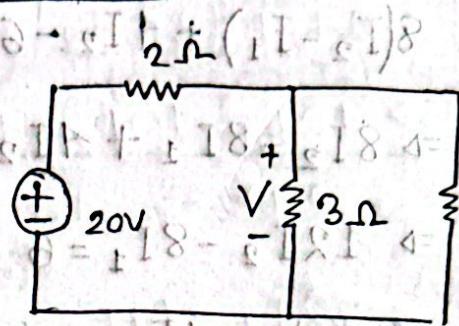


$$3 || 3.18 = 1.54 \Omega$$

$$I_1 + I_2 + I_3 = 2 \text{ A}$$

$$I_1 + I_2 + I_3 = 2 \text{ A}$$

### Step 7:

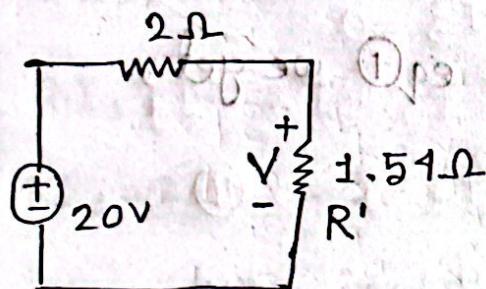

$$\therefore \text{Req.} = 2 + 1.54 \Omega$$

$$= 3.54 \Omega$$

$$\therefore I = \frac{V_s}{\text{Req.}} = \frac{20}{3.54} = 5.65 \text{ A}$$

$$\therefore V = IR' = 5.65 \times 1.54 = 8.7 \text{ V}$$

### Mesh Analysis

Find  $I_1, I_2, I_3$ .


KVL in mesh 1,

$$-10 + 2I_1 + 8(I_1 - I_2) = 0$$

$$\Rightarrow 2I_1 + 8I_1 - 8I_2 = 10$$

$$\Rightarrow 10I_1 + 8I_2 = 10$$
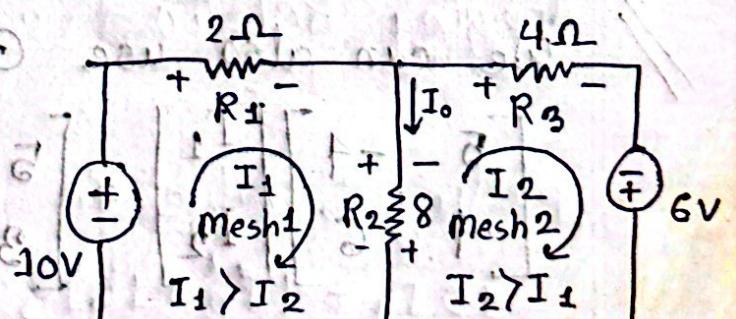
$$\therefore 5I_1 - 4I_2 = 5 \quad \dots \dots \textcircled{1}$$



$$R_1 = 2 \Omega$$

$$R_2 = 8 \Omega$$

$$R_3 = 4 \Omega$$

KVL in mesh 2,

$$8(I_2 - I_1) + 4I_2 - 6 = 0$$

$$\Rightarrow 8I_2 - 8I_1 + 4I_2 = 6$$

$$\Rightarrow 12I_2 - 8I_1 = 6$$

$$\therefore 6I_2 - 4I_1 = 3 \quad \text{--- --- ---} \quad \text{②}$$

$$\Rightarrow 6I_2 = 3 + 4I_1$$

$$\therefore I_2 = \frac{3 + 4I_1}{6}$$

putting the value of  $I_2$  in eq ① we get,

$$5I_1 - 4\left(\frac{3 + 4I_1}{6}\right) = 5$$

$$\Rightarrow 30I_1 - 12 - 16I_1 = 30$$

$$\Rightarrow 14I_1 = 42 \quad \therefore I_1 = 3A \quad (\text{Ans})$$

$$\therefore I_2 = \frac{3 + (4 \times 3)}{6} = \frac{15}{6} = 2.5A \quad (\text{Ans})$$

// We can also use Cramer's Rule to find  $I_1, I_2$

$$\begin{vmatrix} 5 & -4 \\ -4 & 6 \end{vmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 3 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 5 & -4 \\ -4 & 6 \end{vmatrix} = 14$$

$$\Delta_1 = \begin{bmatrix} 5 & -4 \\ 3 & 6 \end{bmatrix} = 42$$

$$\Delta_2 = \begin{bmatrix} 5 & 5 \\ -4 & 3 \end{bmatrix} = 35$$


$$I_1 = \frac{\Delta_1}{\Delta} = 3A ; \quad I_2 = \frac{\Delta_2}{\Delta} = 2.5A$$

Applying KCL in node A,

$$I_1 = I_o + I_2$$

$$\Rightarrow 3 = I_o + 2.5$$
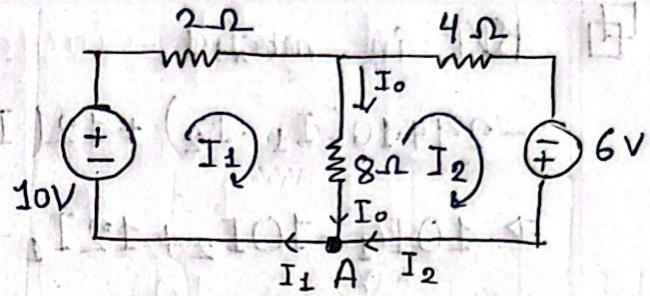
$$\therefore I_o = 3 - 2.5 = 0.5 \text{ A. (Ans)}$$




Find the mesh currents.

Applying KVL in mesh 1,

$$-10 + 2I_1 + 2(I_1 - I_2) + 5 = 0$$

$$\Rightarrow 2I_1 + 2I_1 - 2I_2 = 10 - 5$$
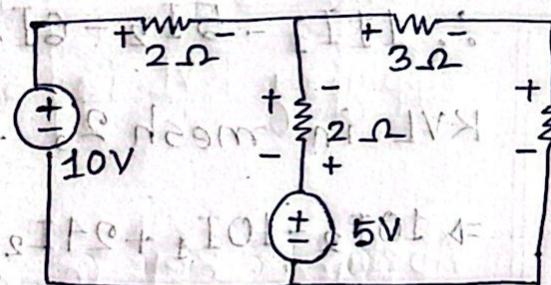
$$\Rightarrow 4I_1 - 2I_2 = 5 \quad \text{(1)}$$



Applying KVL in mesh 2,  $-5 + 2(I_2 - I_1) + 3I_2 + 4I_2 = 0$

$$\Rightarrow 2I_2 - 2I_1 + 3I_2 + 4I_2 = 5$$

$$\Rightarrow -2I_1 + 9I_2 = 5 \quad \text{(II)}$$

$$\begin{bmatrix} 4 & -2 \\ -2 & 9 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 5 \end{bmatrix}$$

$$\Delta_2 = \begin{bmatrix} 4 & 5 \\ -2 & 5 \end{bmatrix} = 20 - (-10) = 30$$

$$\Delta = \begin{bmatrix} 4 & -2 \\ -2 & 9 \end{bmatrix} = 36 - (4) = 32$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{55}{32} = 1.7 \text{ A (Ans)}$$


$$\Delta_1 = \begin{bmatrix} 5 & -2 \\ 5 & 9 \end{bmatrix} = 45 - (-10) = 55$$

$$I_2 = \frac{\Delta_2}{\Delta} = 0.93 \text{ A (Ans)}$$

KVL in mesh 1,

$$-24 + 10(I_1 - I_2) + 12(I_1 - I_3) = 0$$
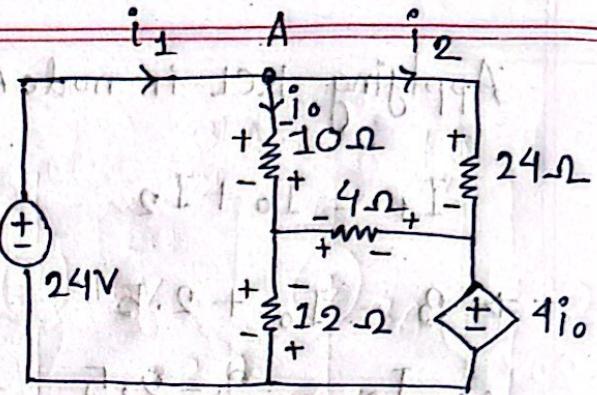
$$\Rightarrow 10I_1 - 10I_2 + 12I_1 - 12I_3 = 24$$



$$\Rightarrow 22I_1 - 10I_2 - 12I_3 = 24$$

$$\therefore 11I_1 - 5I_2 - 6I_3 = 12 \quad \text{--- (1)}$$

KVL in mesh 2,  $+10(I_2 - I_1) + 24I_2 + 4(I_2 - I_3) = 0$

$$\Rightarrow 10I_2 - 10I_1 + 24I_2 + 4I_2 - 4I_3 = 0$$

$$\Rightarrow -10I_1 + 38I_2 - 4I_3 = 0$$

$$\therefore -5I_1 + 19I_2 - 2I_3 = 0 \quad \text{--- (II)}$$

KVL in mesh 3,  $12(I_3 - I_1) + 4(I_3 - I_2) + 4i_o = 0$

$$\Rightarrow 12I_3 - 12I_1 + 4I_3 - 4I_2 + 4i_o = 0$$

$$\Rightarrow -12I_1 - 4I_2 + 16I_3 + 4i_o = 0 \quad \text{--- (III)}$$

Applying KCL in node A,  $I_1 = I_2 + i_o$   
 $\therefore i_o = I_1 - I_2$

putting  $i_o$  value in eq (III),

$$-12I_1 - 4I_2 + 16I_3 + 4(I_1 - I_2) = 0$$

$$\Rightarrow -12I_1 - 4I_2 + 16I_3 + 4I_1 - 4I_2 = 0$$

$$\Rightarrow -8I_1 - 8I_2 + 16I_3 = 0 \quad \therefore -I_1 - I_2 + 2I_3 = 0$$

दोनों दोनों फॉर्मूला वाले एक से दूसरे को घटा दें  
 (एक दूसरी दूसरे) = दोनों का

$$\begin{bmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix} \quad \text{दोनों बहुपदी}$$

$$\Delta = \begin{bmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{bmatrix} = 11(38-2) - (-5)(-10+2) - 6(5+19)$$

$$\textcircled{1} \quad \Delta_1 = \begin{bmatrix} 12 & -5 & -6 \\ 0 & 19 & -2 \\ 0 & -1 & 2 \end{bmatrix} = 12(38-2) - 0 + 0$$

$$\Delta_2 = \begin{bmatrix} 11 & 12 & -6 \\ -5 & 0 & -2 \\ -1 & 0 & 2 \end{bmatrix} = 11(0-0) - 12(-10+2) - 6(0-0)$$

$$= (-12 \times -8) = 96$$

$$\textcircled{2} \quad \Delta_3 = \begin{bmatrix} 11 & -5 & 12 \\ -5 & 19 & 0 \\ -1 & 1 & 0 \end{bmatrix} = 11(0-0) + 5(0-0) + 12(-5+19)$$

$$= 168$$

$$I_{1A} = \frac{\Delta_1}{\Delta} = 2.25 A$$

$$I_{2A} = \frac{\Delta_2}{\Delta} = \frac{96}{192} = 0.5 A$$

$$I_{3A} = \frac{\Delta_3}{\Delta} = \frac{168}{192} = 0.875 A$$

$$(ii) I_o = I_1 - I_2$$



$$= 2.25 - 0.5$$

$$= 2.20 A$$

যদি দুটি mesh এর মধ্যে current source থাকে তাহলে  
 Supermesh = (mesh1 + mesh2) ধরে নিতে হবে

Find mesh currents :-

Soln:-

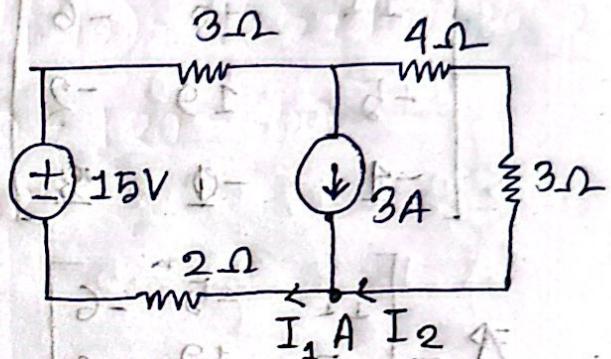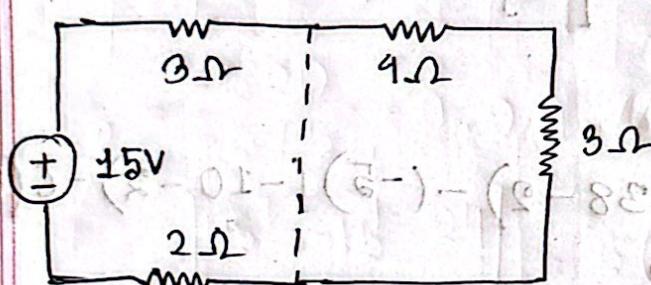

Applying KVL in supermesh,  $-15 + 3I_1 + 1I_2 + 3I_2 + 2I_1 = 0 \Rightarrow 5I_1 + 7I_2 = 15 \quad \text{--- (1)}$

Applying KCL in node A,  $I_3 + I_2 = I_1$

$$\Rightarrow I_1 - I_2 = 3$$

$$\therefore I_1 = I_2 + 3 \quad \text{--- (ii)}$$

Putting eq(ii) in eq(i),

$$5(I_2 + 3) + 7I_2 = 15$$

$$\Rightarrow 5I_2 + 15 + 7I_2 = 15$$


$$\Rightarrow 12I_2 = 0$$

$$\therefore I_2 = 0 \text{ A} \quad (\text{Ans})$$

$$I_1 = 0 + 3$$


$$\therefore I_1 = 3 \text{ A} \quad (\text{Ans})$$

Find mesh currents.

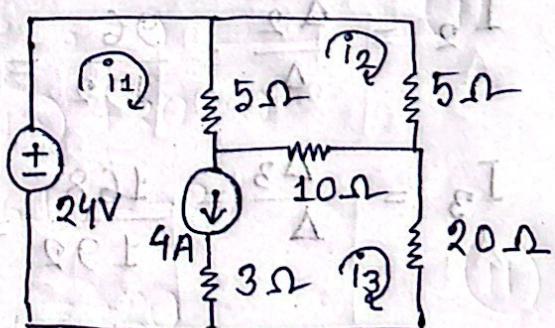

KVL in Supermesh (mesh 1 + mesh 3);
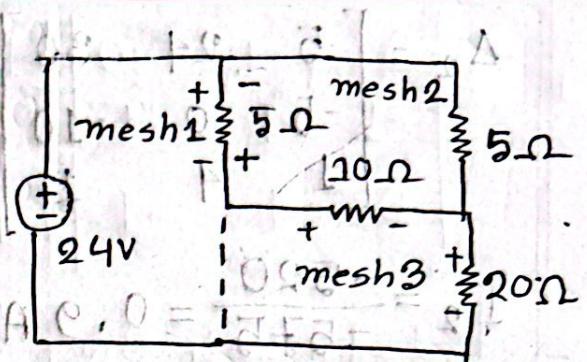
$$-24 + 5(I_1 - I_2) + 10(I_3 - I_2) + 20I_3 = 0$$



$$\Rightarrow 5I_1 - 5I_2 + 10I_3 - 10I_2 + 20I_3 = 24$$

$$\Rightarrow 5I_1 - 15I_2 + 30I_3 = 24 \quad \text{--- (I)}$$


KVL in mesh 2,  $5(I_2 - I_1) + 5I_2 + 10(I_2 - I_3) = 0$

$$\Rightarrow 5I_2 - 5I_1 + 5I_2 + 10I_2 - 10I_3 = 0$$

$$\Rightarrow 20I_2 - 5I_1 - 10I_3 = 0 \quad \text{--- (II)}$$

Apply KCL in node A,  $I_1 = 4 + I_3 \quad \text{--- (III)}$
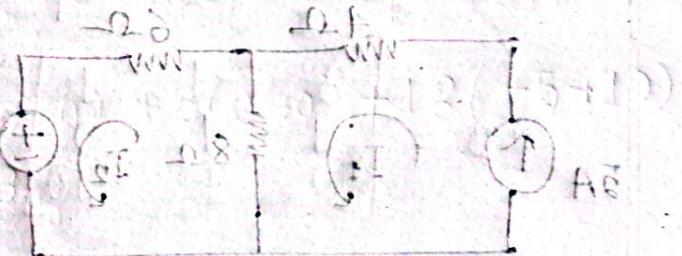
$$\begin{bmatrix} 5 & -15 & 30 \\ -5 & 20 & -10 \\ 1 & 0 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 24 \\ 0 \\ 4 \end{bmatrix}$$



$$\Delta = 5(20-0) - (-15)(-5+10) + 30(0-20)$$

$$\Delta = 100 - 75 - 600 = -575$$

$$\Delta_1 = \begin{vmatrix} 24 & -15 & 30 \\ 0 & 20 & -10 \\ 4 & 0 & 1 \end{vmatrix} = +2520 \quad | \quad I_1 = \frac{-2520}{-575}$$

$$\Delta_1 = 24(20-0) + 15(0-40) + 30(0-80) = 480 + (-600) + (-2400) = -2520 \quad | \quad = 4.38 \text{ A} \quad (\text{Ans})$$


$$\Delta_2 = \begin{bmatrix} 5 & -24 & 30 \\ -5 & 0 & -10 \\ 1 & 4 & 1 \end{bmatrix} = 5(0+40) - 24(-5+10) + 30(-20) \\ = 200 - 120 - 600 \\ = -520$$

$$I_2 = \frac{-520}{-575} = 0.9 \text{ A} \quad (\text{Ans})$$

$$\Delta_3 = \begin{bmatrix} 5 & -15 & 24 \\ -5 & 20 & 0 \\ 1 & 0 & 4 \end{bmatrix} = 5(80-0) + 15(-20+0) + 24(0-20) \\ = 400 - 300 - 480 \\ = -380$$

$$I_3 = \frac{-380}{-575} = 0.66 \text{ A} \quad (\text{Ans})$$

Find mesh currents about in loop B

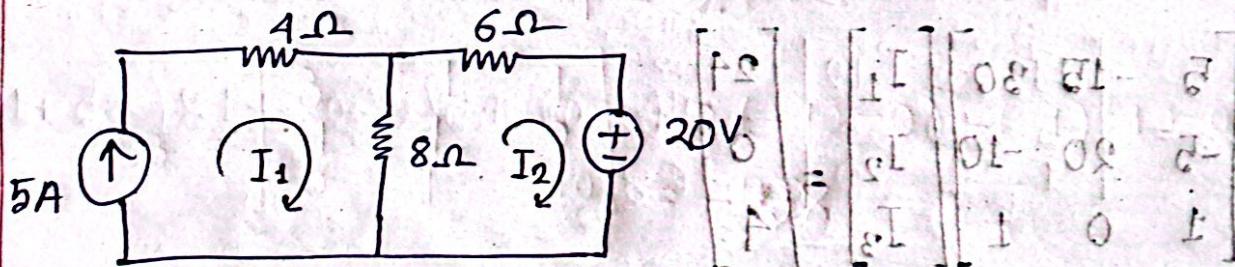

$$\text{KVL in mesh 1: } 4I_1 + 8(I_1 - I_2) = 0$$

$$\Rightarrow 4I_1 + 8I_1 - 8I_2 = 0$$

$$\Rightarrow 12I_1 - 8I_2 = 0 \quad (1)$$

$$\text{KVL in mesh 2: } 8(I_2 - I_1) + 6I_2 + 20 = 0$$

$$\Rightarrow 8I_2 - 8I_1 + 6I_2 = -20$$

$$\Rightarrow 14I_2 - 8I_1 = -20 \quad (II)$$

Applying KCL in node A,  $I_1$ . For mesh 1,

$$\text{We can say } I_1 = 5 \text{ A} \quad (\text{Ans})$$

putting this value in eq ⑪,

$$14I_2 - (8 \times 5) = -20$$


$$\Rightarrow I_2 = \frac{-20 + 40}{14} = 1.42 \text{ A} \quad (\text{Ans})$$

Lab

KVL in mesh 1,

$$-10 + 20I_1 + 10(I_1 - I_2) = 0$$
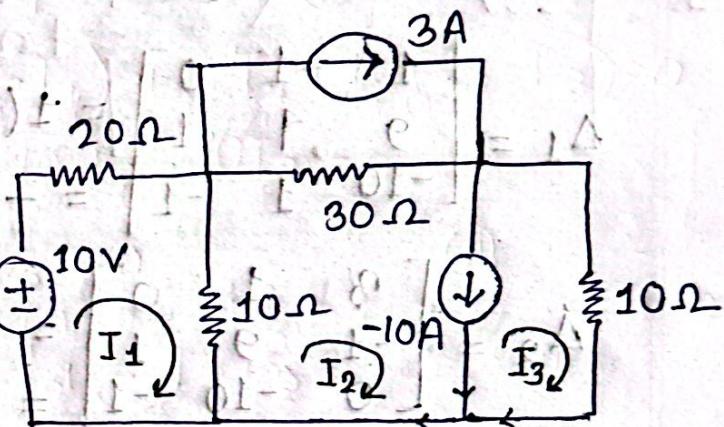
$$\Rightarrow 20I_1 + 10I_1 - 10I_2 = 0$$



$$\Rightarrow 30I_1 - 10I_2 = 10$$

$$\therefore 3I_1 - I_2 = 1 \quad \text{--- } ①$$

KVL in (mesh 2 + mesh 3) = Supermesh,

$$10(I_2 - I_1) + 30(I_2 - 3) + 10(I_3 - 3) = 0$$

$$\Rightarrow 10I_2 - 10I_1 + 30I_2 - 90 + 10I_3 - 10I_2 = 0$$

$$\Rightarrow -10I_1 + 40I_2 + 10I_3 = 90$$

$$\Rightarrow -I_1 + 4I_2 + I_3 = 9 \quad \text{--- } ⑪$$

KVL in node A,  $I_2 = -10 + I_3$

$$I_2 - I_3 = -10 \quad \text{--- } ⑬$$

$$\begin{bmatrix} 3 & -1 & 0 \\ -1 & 4 & 1 \\ 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 9 \\ -10 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 3 & -1 & 0 \\ -1 & 4 & 1 \\ 0 & 1 & -1 \end{bmatrix} = 3(-4-1) - (-1)(1-0) + 0 = -14$$

$$\Delta_1 = \begin{bmatrix} 1 & -1 & 0 \\ 9 & 1 & 1 \\ -10 & 1 & -1 \end{bmatrix} = 1(-4-1) - (-1)(-9+10) + 0 = -1$$

$$\Delta_2 = \begin{bmatrix} 3 & 1 & 0 \\ -1 & 9 & 1 \\ 0 & -10 & -1 \end{bmatrix} = 3(-9+10) - 1(1-0) + 0 = 2$$

$$\Delta_3 = \begin{bmatrix} 3 & -1 & 1 \\ -1 & 4 & 9 \\ 0 & 1 & -10 \end{bmatrix} = 3(-40-9) - (-1)(40-0) + 1(-1-0) = -138$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{-4}{-14} = 0.285 \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{2}{-14} = 0.142 \text{ A}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{-138}{-14} = 9.85 \text{ A}$$

(iii)

$\text{ot} = 0.15 \text{ A}$

## Lab 2


KVL in mesh 1,

$$-10 + 8I_1 + 16(I_1 - I_2) + 4(I_1 - I_2) = 0$$

$$\Rightarrow 8I_1 + 20I_1 - 20I_2 = 10$$

$$\Rightarrow 28I_1 - 20I_2 = 10$$
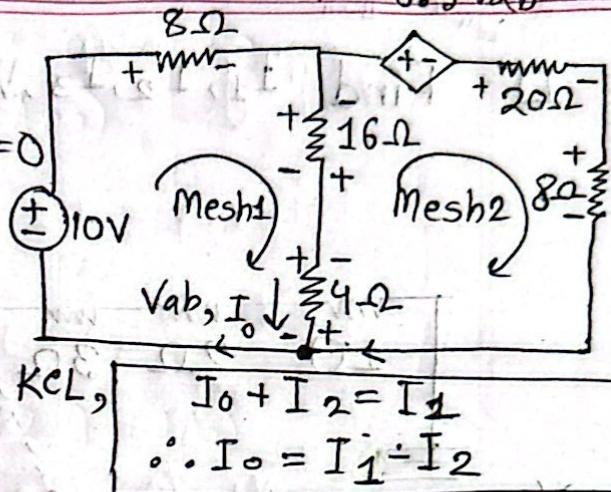
$$\Rightarrow 14I_1 - 10I_2 = 5 \quad \text{--- (1)}$$



KVL in mesh 2,  $4(I_2 + I_1) + 16(I_2 - I_1) + 0.5 Vab$

$$+ 20I_2 + 8I_2 = 0$$

$$\Rightarrow 4I_2 - 4I_1 + 16I_2 - 16I_1 + 0.5 Vab (4I_1 - 4I_2) + 28I_2 = 0$$

$$\Rightarrow 20I_2 - 4I_1 + 2I_1 - 2I_2 + 28I_2 = 0$$

$$\Rightarrow -18I_1 + 46I_2 = 0$$

$$\Rightarrow -9I_1 + 23I_2 = 0 \quad , \quad 9I_1 - 23I_2 = 0$$

$$\begin{bmatrix} 14 & -10 \\ 9 & -23 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \end{bmatrix}$$

$$\Delta (-322 + 90) = -232$$

$$\Delta_1 = \begin{bmatrix} 5 & -10 \\ 0 & -23 \end{bmatrix} = -115$$

$$\Delta_2 = \begin{bmatrix} 14 & 5 \\ 9 & 0 \end{bmatrix} = (0 - 45) = -45$$

$$I_1 = \frac{-115}{-232} = 0.19A$$

$$I_2 = \frac{-45}{-232} = 0.19A$$


## □ Nodal Analysis

Steps : ① Node identification

② Reference/ground node ( $\frac{1}{\infty}$ )

③ Flow of current
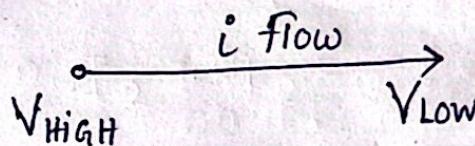
$$\text{Current, } i = \frac{V_{\text{HIGH}} - V_{\text{LOW}}}{R} \quad \begin{array}{l} \text{Current (i) द्यावान} \\ \text{यद्यपि pass रूप्त्वा start} \\ \text{इस द्यावान } V_{\text{HIGH}} \end{array}$$



□ Applying Ohm's law,


$$i_1 = 10 \text{ A}$$

$$i_2 = \frac{V_2 - 0}{6} = \frac{V_2}{6}$$

$$i_3 = 5 \text{ A}$$

$$i_4 = \frac{V_1 - V_2}{4}$$
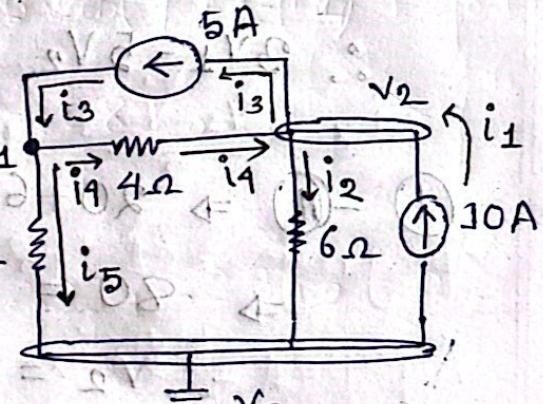
$$i_5 = \frac{V_1 - 0}{2} = \frac{V_1}{2}$$



Applying KCL at node  $V_1$ ,  $i_3 = i_4 + i_5$

$$\Rightarrow 5 \times 4 = \frac{V_1 - V_2}{4} + \frac{V_1}{2}$$

$$\Rightarrow 5 \times 4 = V_1 - V_2 + 2V_1$$

$$\therefore 20 = 3V_1 - V_2 \quad \dots \quad (1)$$

Node 2

Applying KCL at node  $V_2$ ,

(+)  $i_1 + i_4 = i_2 + i_3$

$$\Rightarrow \frac{V_1 - V_2}{4} + 10 = 5 + \frac{V_2}{6}$$

$$\Rightarrow \frac{V_1 - V_2}{4} - \frac{V_2}{6} = -5$$

$$\Rightarrow \frac{3V_1 - 3V_2 - 2V_2}{12} = -5$$

$$\therefore 3V_1 - 5V_2 = -60 \quad \text{--- (II)}$$

$$(I) - (II) \Rightarrow 20 + 60 = 3V_1 - V_2 - 3V_1 + 5V_2$$

$$\Rightarrow 80 = 4V_2$$

$$\therefore V_2 = 20V$$

putting  $V_2$  in eq (I),  $3V_1 - 20 = 20$

$$\Rightarrow 3V_1 = 40$$

$$\therefore V_1 = \frac{40}{3} = 1.33V$$

$$i_2 = \frac{V_2}{6} = 3.33V$$

$$i_4 = \frac{V_1 - V_2}{4} = -4.66V$$

$$i_5 = \frac{V_1}{2} = 0.66V$$

Q

Determine node voltage:


$$i_1 = 14 \text{ A}$$

$$i_2 = \frac{V_1 - 0}{4\Omega} = \frac{V_1}{4}$$

$$i_3 = \frac{V_1 - V_2}{5\Omega}$$

$$i_4 = \frac{V_2}{5\Omega}$$

$$i_5 = 7 \text{ A}$$

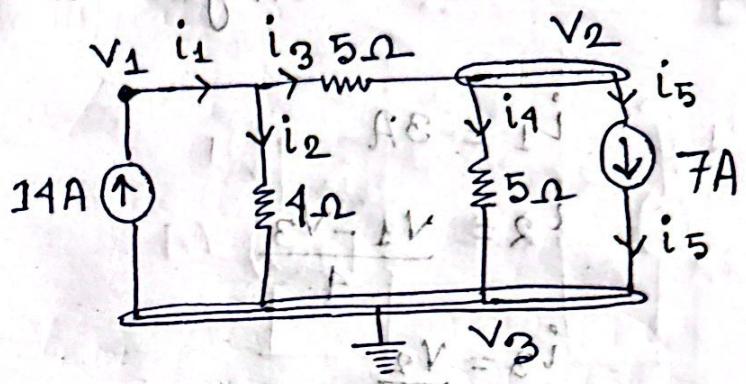

Applying KCL at  $V_1$ ,

$$i_1 = i_2 + i_3$$

$$\Rightarrow 14 = \frac{V_1}{4} + \frac{V_1 - V_2}{5}$$

$$\Rightarrow 20 \times 14 = 5V_1 + 4V_1 - 4V_2$$

$$\Rightarrow 280 = 9V_1 - 4V_2 \quad \text{(i)}$$

Applying KCL at node  $V_2$ ,

$$i_3 = i_1 + i_5$$

$$\Rightarrow \frac{V_1 - V_2}{5} = \frac{V_2}{5} + 7$$

$$\Rightarrow \frac{V_1 - V_2 - V_2}{5} = 7$$

$$\Rightarrow V_1 - 2V_2 = 35 \quad \text{(ii)}$$

$$(i) - (2 \times ii)$$

$$280 - 70 = 9V_1 - 4V_2 - 2V_1 + 4V_2$$

$$\Rightarrow 210 = 7V_1$$



$$(i) \Rightarrow V_1 = \frac{210}{7} = 30 \text{ V}$$

putting the value in eq(ii),

$$30 - 2V_2 = 35$$

$$\Rightarrow -2V_2 = 5 \quad \therefore V_2 = \frac{5}{-2} = -2.5 \text{ V}$$

④ Determine Voltages and  $i_x$ .

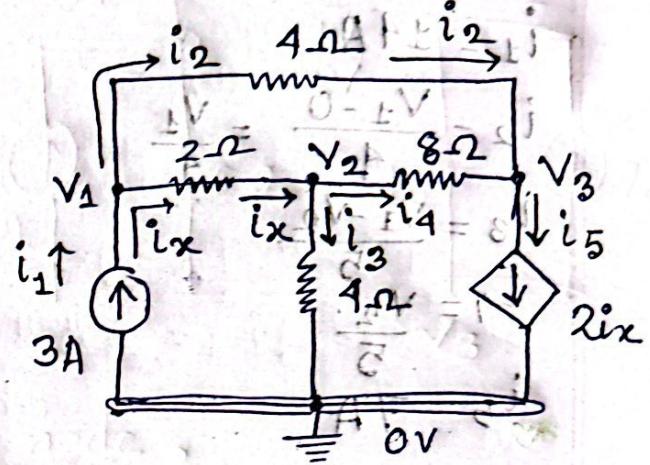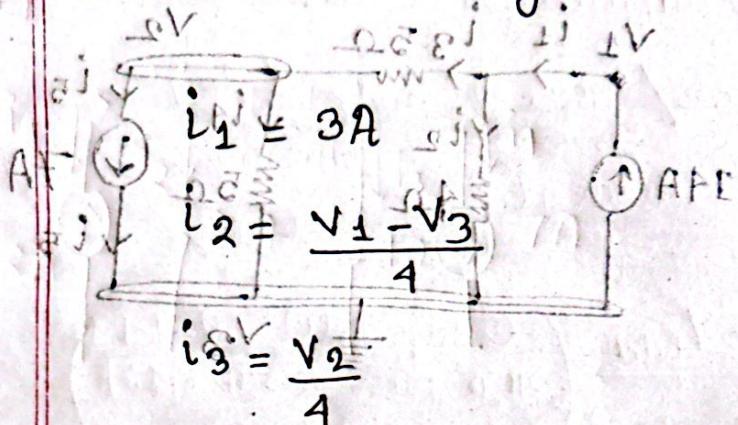

$$i_1 = i_2 + i_x$$

$$\Rightarrow 3 = \frac{V_1 - V_3}{4} + \frac{V_1 - V_2}{2}$$

$$\Rightarrow 12 = 2V_1 - 2V_3 + 2V_1 - 2V_2$$

$$\therefore 3V_1 - 2V_2 - 2V_3 = 12$$

Applying KCL in node 1,  $i_x = i_3 + i_4$

$$\Rightarrow \frac{V_1 - V_2}{2} = \frac{V_2 - V_3}{4} + \frac{V_2 - V_3}{8}$$

$$\Rightarrow \frac{V_1 - V_2}{2} = \frac{2V_2 + V_2 - V_3}{8}$$

$$\Rightarrow 8V_1 - 8V_2 = 4V_2 + 2V_2 - 2V_3$$

$$\therefore 4V_1 - 7V_2 + V_3 = 0 \quad (ii)$$

Applying KCL at node 3,

$$i_2 + i_4 = i_5$$

$$\Rightarrow \frac{V_1 - V_3}{4} + \frac{V_2 - V_3}{8} = V_1 - V_2$$

$$\Rightarrow 2V_1 - 2V_3 + V_2 - V_3 = 8V_1 - 8V_2$$

$$\therefore 2V_1 - 3V_2 + V_3 = 0 \quad (iii)$$

$$\Delta = \begin{vmatrix} 3 & -2 & -1 \\ 4 & -7 & 1 \\ 2 & -3 & 1 \end{vmatrix}$$

$$= 2V_1 + 1V_2 - 1V_3$$

$$= -10$$

$$\Delta_1 = \begin{vmatrix} 12 & -2 & -1 \\ 0 & -7 & 1 \\ 0 & -3 & 1 \end{vmatrix}$$

$$= -48$$

$$V_1 = \frac{-48}{-10} = 4.8 V$$

$$V_2 = \frac{-24}{-10} = 2.4 V$$

$$V_3 = \frac{24}{-10} = -2.4 V$$



$$\Delta_2 = \begin{vmatrix} 3 & 12 & -1 \\ 4 & 0 & 1 \\ 2 & 0 & 1 \end{vmatrix} = -24$$

$$i_x = \frac{V_1 - V_2}{2} = 1.2 A$$

$$\Delta_3 = \begin{vmatrix} 3 & -2 & 12 \\ 4 & -7 & 0 \\ 2 & -3 & 0 \end{vmatrix} = 24$$

Q

Solution :

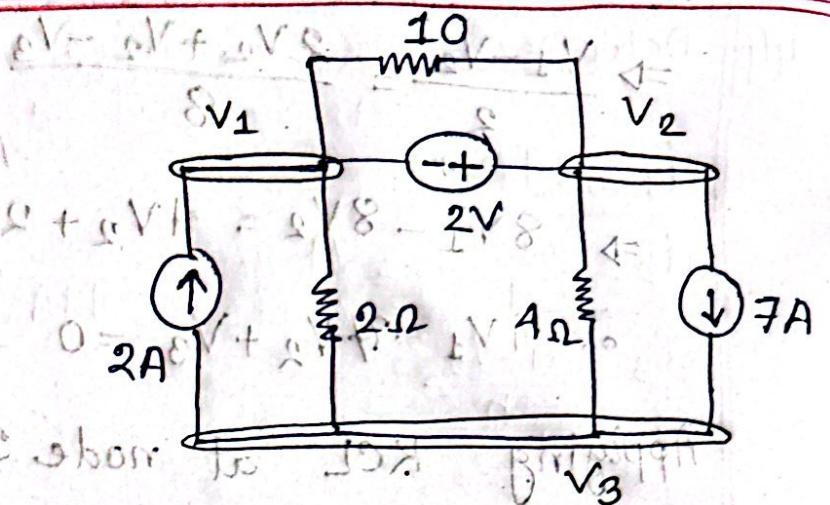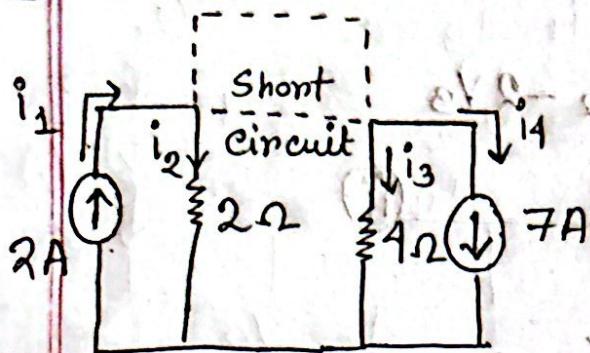

Applying KCL in Super node,  $i = i_1 + i_2 + i_3 + i_4$

$$i_1 = i_2 + i_3 + i_4 = \frac{eV - eV}{8} + \frac{eV - eV}{4} = 0$$

$$\Rightarrow 2 = i_2 + i_3 + 7 = eV - eV + eV - 1V \therefore$$

$$\Rightarrow \frac{V_1}{2} + \frac{V_2}{4} = -5 = eV + eV - 1V \therefore$$

$$\therefore 2V_1 + V_2 = -20$$


Applying KVL in loop 1,

$$-V_1 - 2 + V_2 = 0$$

$$\Rightarrow V_2 - V_1 = 2 \quad \text{--- (II)}$$

$$\text{eq (I) - eq (II), } 2V_1 + V_2 - V_2 + V_1 = -20 - 2$$

$$\Rightarrow 3V_1 = -22$$

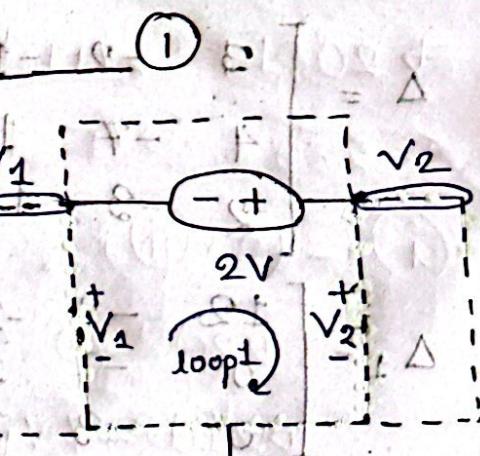

$$\therefore V_1 = \frac{-22}{3} = -7.33V$$

putting in eq (II),

$$\therefore V_2 = 2 + V_1 = 2 - 7.33 = -5.33V$$