



# East West University

## Assignment

**Semester:** Summer-2024

**Course Title:** Electrical Circuits

**Course Code:** CSE209

**Sec:** 01

### Submitted by-

Name: Sheikh Sarafat Hossain

Id: 2022-3-60-109

### Submitted to-

Dr. Sarwar Jahan

Associate Professor


Department of Computer Science & Engineering

East West University


**Date of Submission:** 4-September-2024

Ans to the Q: NO: 1


Last Digit of my id = 9

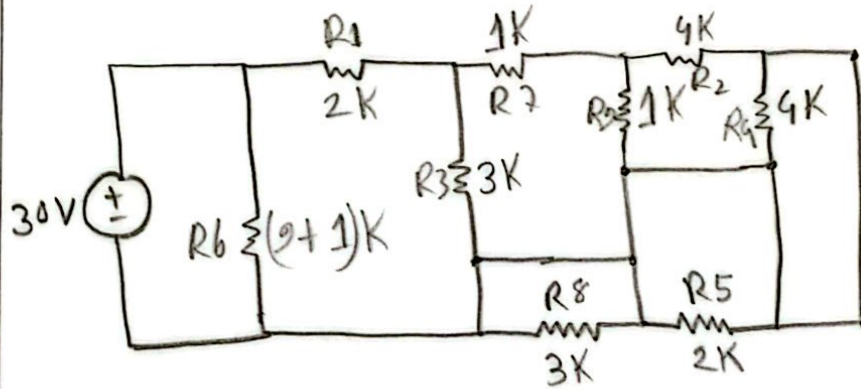

Soln:

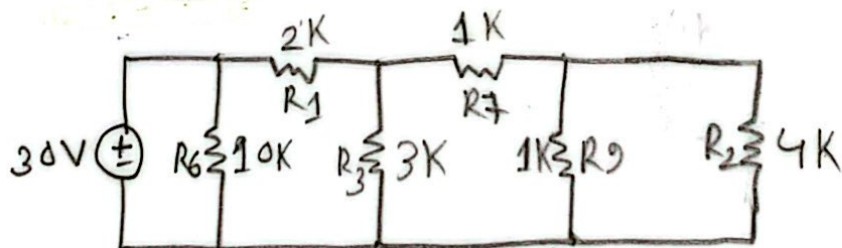

$$(R_9 || R_2) = (1 || 4) \overset{\text{fig-1}}{=} R' = 0.8K$$

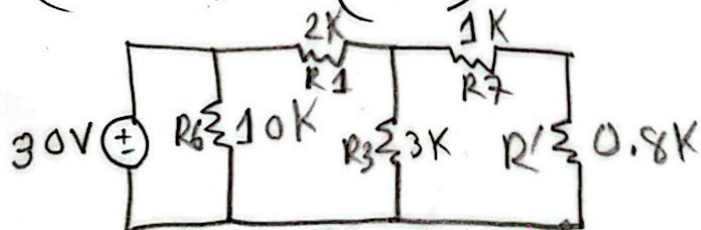

$$(R_7 + R') || R_3 \overset{\text{fig-2}}{=} (1 + 0.8) || 3 = 1.125K = R''$$



fig-3

$$R_1 + R'' = 2 + 1.125 \text{ K} = 3.125 \text{ K} = R'''$$

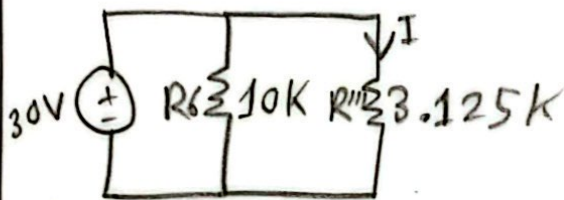


Fig-4

$$\therefore R_{eq} = R_6 \parallel R''' = \frac{10 \times 3.125}{10 + 3.125} = 2.38 \text{ K}$$

$$\therefore I_s = \frac{V_s}{R_{eq}} = \frac{30}{2.38} = 12.6 \text{ A}$$

From Fig-4, we can get \$I\$ using  
CDR Method,

$$\therefore I = \frac{I_s \times R_6}{R_6 + R'''} = \frac{12.6 \times 10}{10 + 3.125} = 9.6 \text{ A}$$

Applying VDR, in figure 3,


$$V_{R_3} = \frac{30 \times 1.125}{2 + 1.125} = 10.8 \text{ V}$$

$$\therefore V_{R_3} = 10.8 \text{ V}$$

Ans to the Q: No. 2

Last digit of my id is 9

$$R_2 = (3+9) = 12\Omega$$

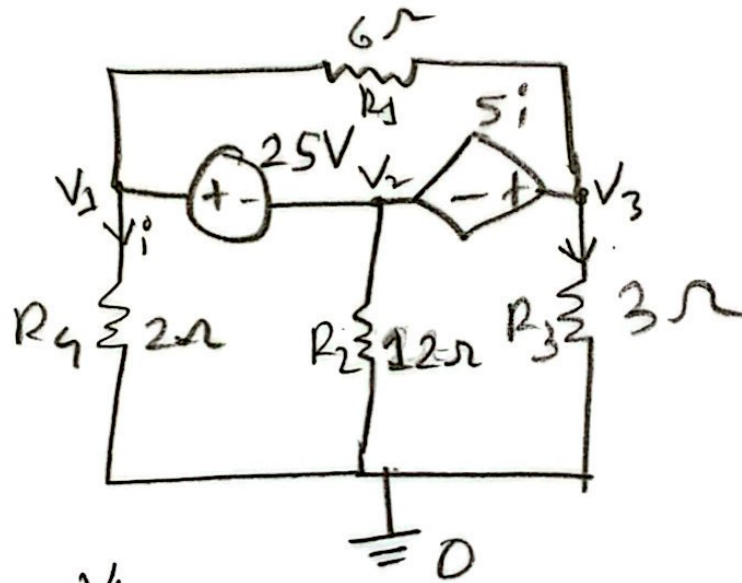


$$i_1 = \frac{V_1}{2}$$

$$i_2 = \frac{V_2}{3}$$

$$i_3 = \frac{V_1 - V_2}{6}$$

$$i_1 = \frac{V_1}{12}$$

$$i_4 = 5i = 5 \frac{V_2}{2}$$

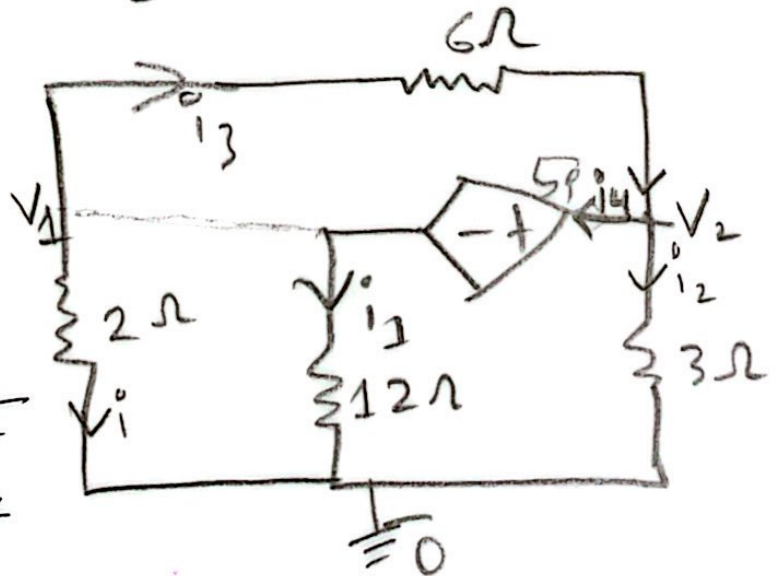

Applying KCL at V2,

$$i_3 = i_2 + i_4$$


$$\Rightarrow \frac{V_1 - V_2}{6} = \frac{V_2}{3} + \frac{5V_1}{2}$$

$$\Rightarrow \frac{V_1 - V_2}{6} - \frac{V_2}{3} - \frac{5V_1}{2} = 0$$

$$\Rightarrow \frac{V_1 - V_2 - 2V_2 - 15V_1}{6} = 0$$

$$\Rightarrow \frac{-14V_1 - 3V_2}{6} = 0$$
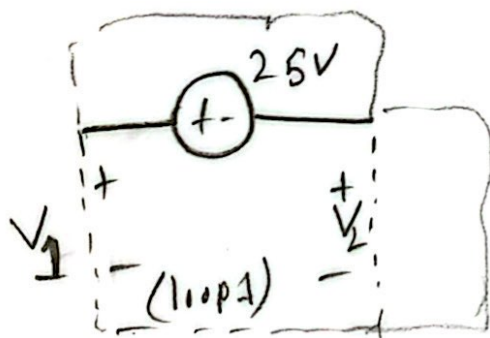
$$\Rightarrow \therefore 14V_1 + 3V_2 = 0 \quad \text{--- (I)}$$



Applying KVL in loop 1,

$$-V_1 + 25 + V_2 = 0$$

$$\Rightarrow V_2 - V_1 = -25$$

$$\therefore V_1 - V_2 = 25 \quad \text{--- (II)}$$



Using Cramer's rule,

$$\begin{bmatrix} 14 & 3 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 25 \end{bmatrix}$$

$$\Delta = -11$$

$$\Delta_1 = -25$$

$$\Delta_2 = 350$$

$$V_1 = \frac{-25}{-11} = 6.81V$$

$$V_2 = 31.8V$$


$$\therefore i = \frac{V_1}{2} = \frac{6.85}{2} = 3.41A$$

$$\therefore i = 3.41A.$$

3


Ans to the Q: No: 3

Last digit of my id is 9.

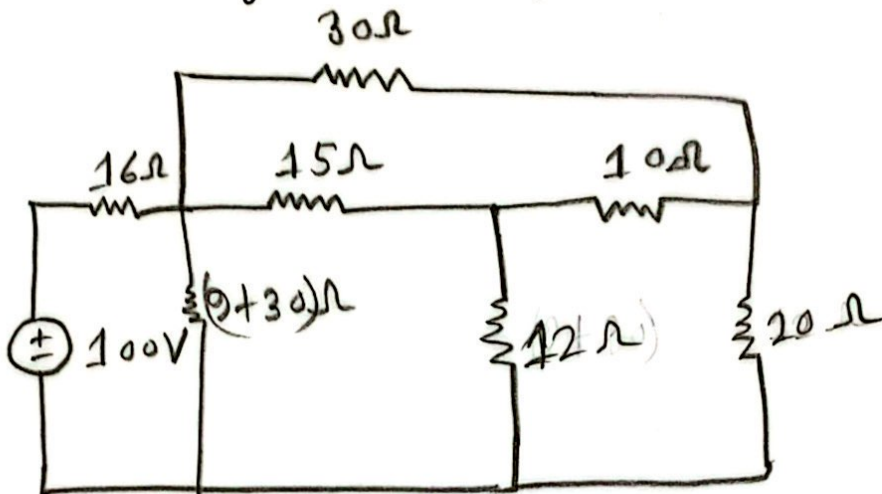

Sol<sup>n</sup>:

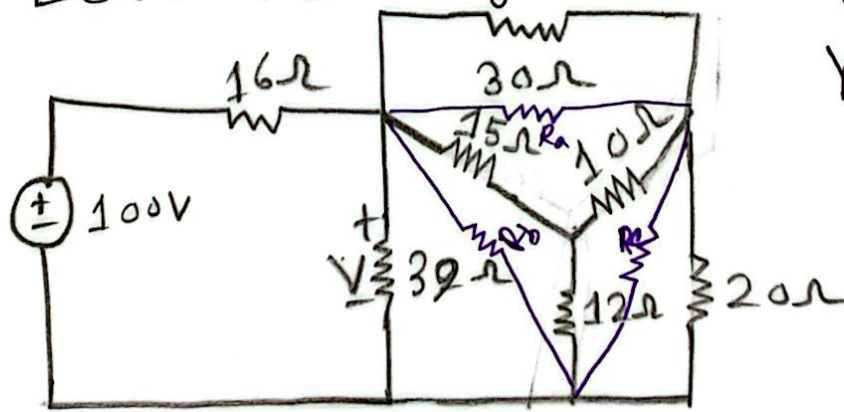Let's rearranged the circuits, and apply  $\Delta$  to  $Y$  conversion.



Assuming,  $R_1 = 15\Omega$

$R_2 = 10\Omega$

$R_3 = 12\Omega$

3

$$R_a = \frac{(R_1 \times R_2) + (R_1 \times R_3) + (R_2 \times R_3)}{12}$$

$$= \frac{(15 \times 10) + (15 \times 12) + (15 \times 12)}{12}$$


$$= 32.5 \Omega$$

$$R_b = \frac{450}{10}$$

$$= 45 \Omega$$

$$R_c = \frac{450}{15}$$

$$= 30 \Omega$$

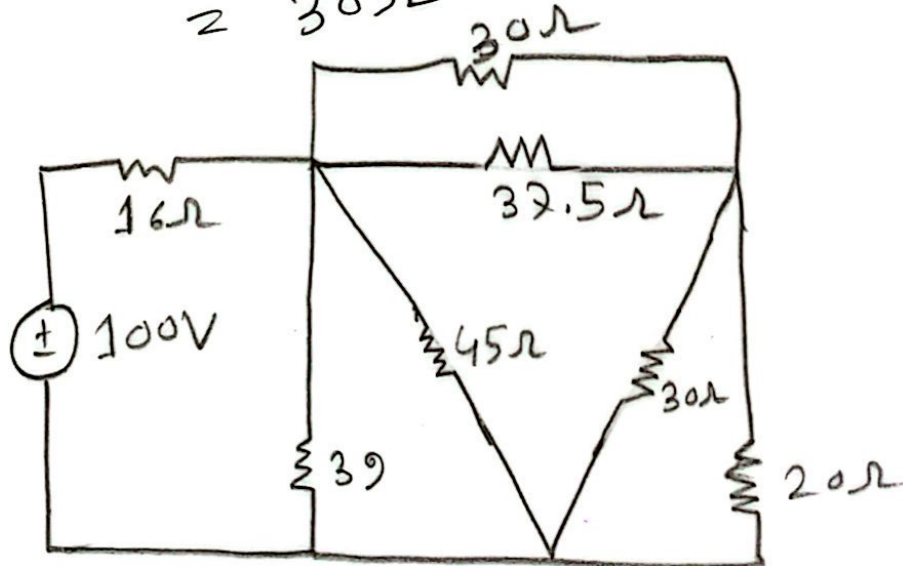


$$(30 \parallel 32.5) = 16.67 \Omega$$

$$(30 \parallel 20) = 12 \Omega$$


$$(39 \parallel 45) = 20.89 \Omega$$



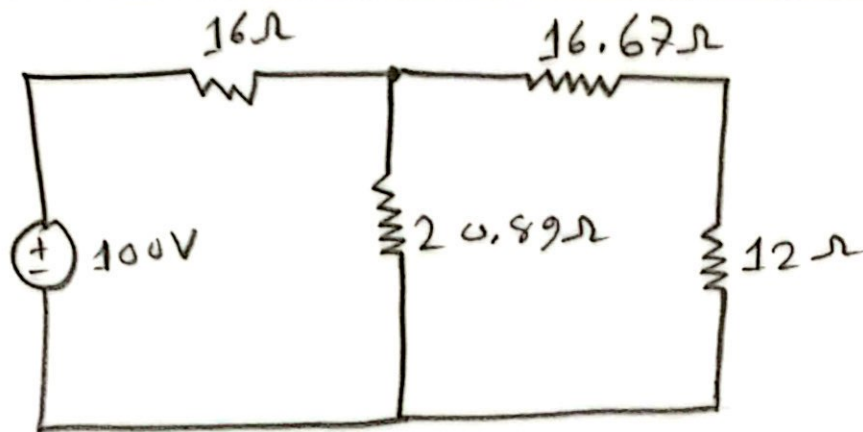

$$16.67 + 12 = 28.67 \Omega = R'$$
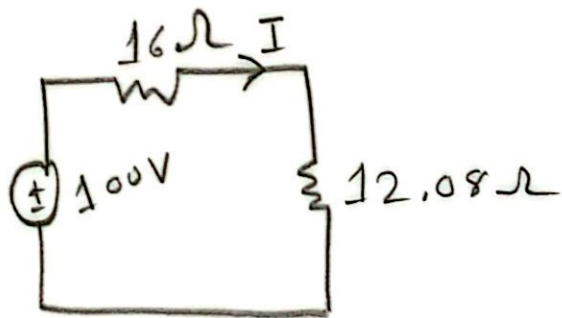
$$R' \parallel 20.89 = 28.67 \parallel 20.89 = 12.08 \Omega$$




$$\therefore R_{eq} = 16 + 12.08 \Omega = 28.08 \Omega$$

Using Ohm's law,


$$I = \frac{V_s}{R_{eq}} = \frac{100}{28.08} = 3.56 A$$

Ans to the Q: NO: 4

Last digit of my id is 9.

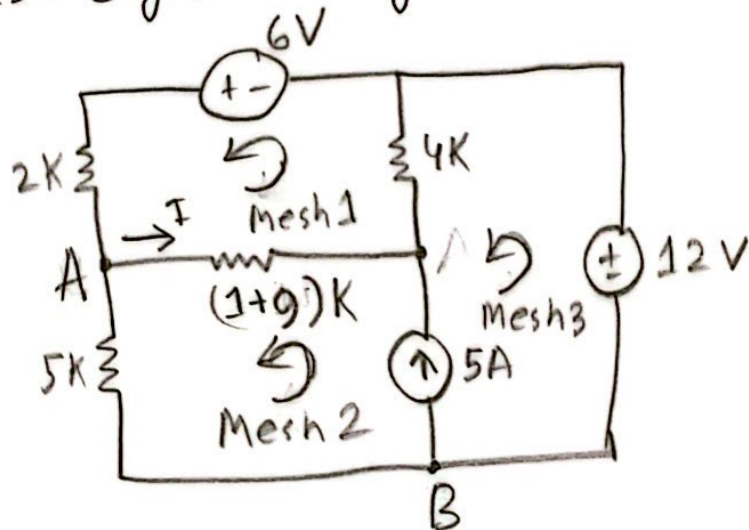

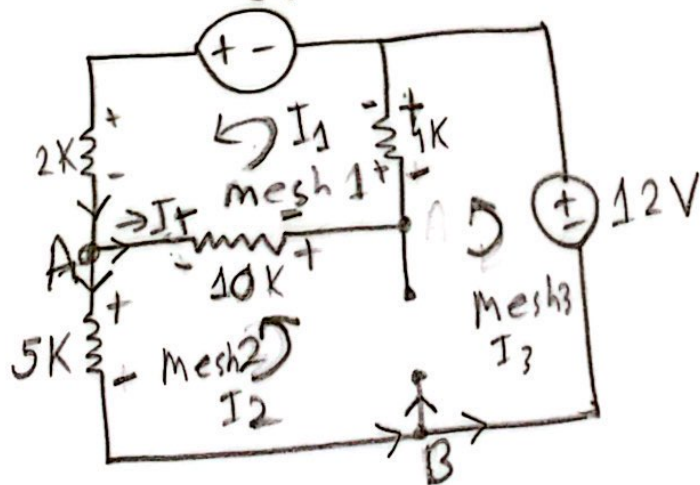Since the current source is in between two mesh, so we have to apply super-mesh. 6V



Applying KVL in Supermesh,

$$-12 + 4I_3 + 4I_1 + 10I_2 - 10I_1 + 5I_2 = 0$$

$$\Rightarrow -14I_1 + 15I_2 + 4I_3 = 12 \quad \text{--- (1)}$$

(u)

Applying KVL in mesh 1,

$$\Rightarrow -6 + 2I_1 + 10I_1 - 10I_2 + 4I_1 - 4I_3 = 0$$

$$\Rightarrow 16I_1 - 10I_2 - 4I_3 = 6$$

$$\Rightarrow 8I_1 - 5I_2 - 2I_3 = 3 \quad \text{--- (iii) [Divided by 2]}$$

Now, let's apply KCL at node B,

$$I_2 = 5 + I_3$$

$$\Rightarrow I_2 - I_3 = 5 \quad \text{--- (iv)}$$

Applying Cramer's rule,

$$\begin{bmatrix} -14 & 15 & 4 \\ 8 & -5 & -2 \\ 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 3 \\ 5 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} -14 & 15 & 4 \\ 8 & -5 & -2 \\ 0 & 1 & -1 \end{vmatrix} = 110$$

$$\Delta_1 = \begin{vmatrix} 12 & 15 & 4 \\ 3 & -5 & -2 \\ 5 & 1 & -1 \end{vmatrix} = 343$$

$$\Delta_2 = \begin{vmatrix} -14 & 12 & 4 \\ 8 & 3 & -2 \\ 0 & 5 & -1 \end{vmatrix} = 438$$

$$\Delta_3 = \begin{vmatrix} -14 & 15 & 12 \\ 8 & -5 & 3 \\ 0 & 1 & 5 \end{vmatrix} = -112$$

(3)

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{393}{110} = 3.11 \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{438}{110} = 3.89 \text{ A}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{-112}{110} = -1.018 \text{ A}$$

Applying KCL at node A,

$$I_1 = I + I_2$$

$$\Rightarrow I = I_1 - I_2$$

$$= 3.11 - 3.89$$

$$= -0.78 \text{ A}$$