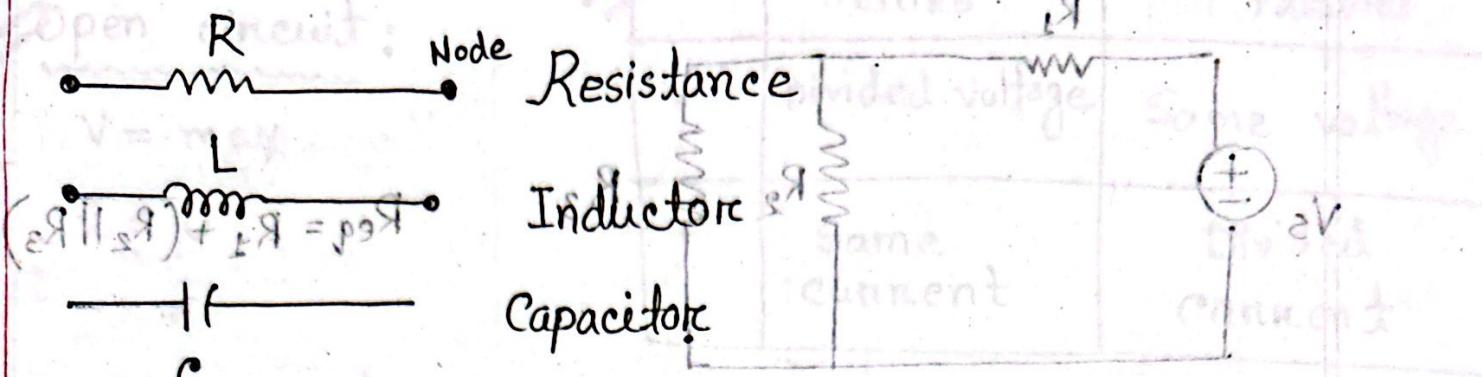


Passive elements:



Ohm's Law:


$$I = \frac{V}{R} ; R = \frac{V}{I} ; V = IR$$

V_s = Voltage source

Circuit:

① Series

② Parallel

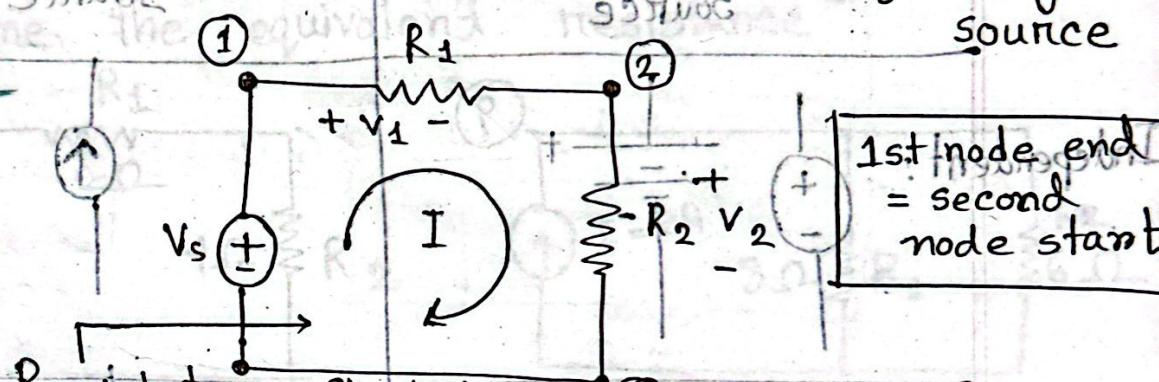


$$= R_1 + R_2$$

(Both are close loop circle)

1st node end = 2nd end

2nd node start = 1st start

③ Series circuit

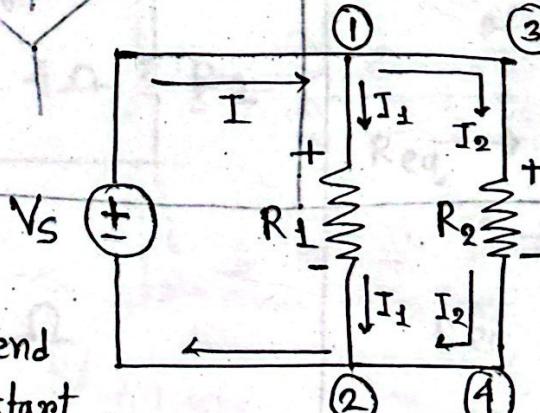

$$V = V_1 = V_2$$


∴ Equivalent Resistance

(Equivalent)


$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 R_2}{R_1 + R_2}$$

④ Parallel circuit

Ex 10

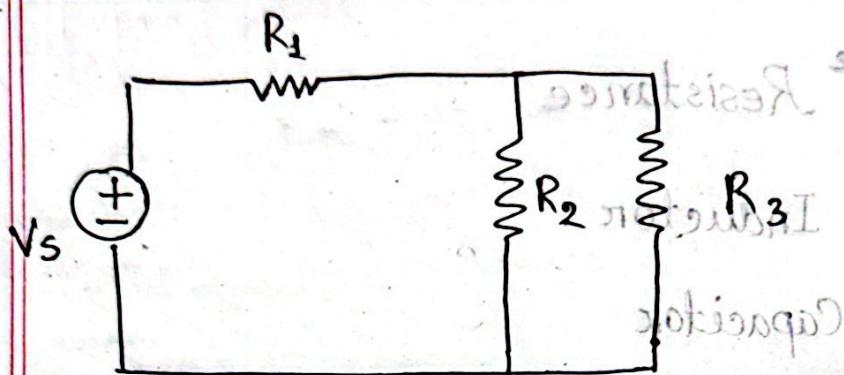

S-P (Series- Parallel)

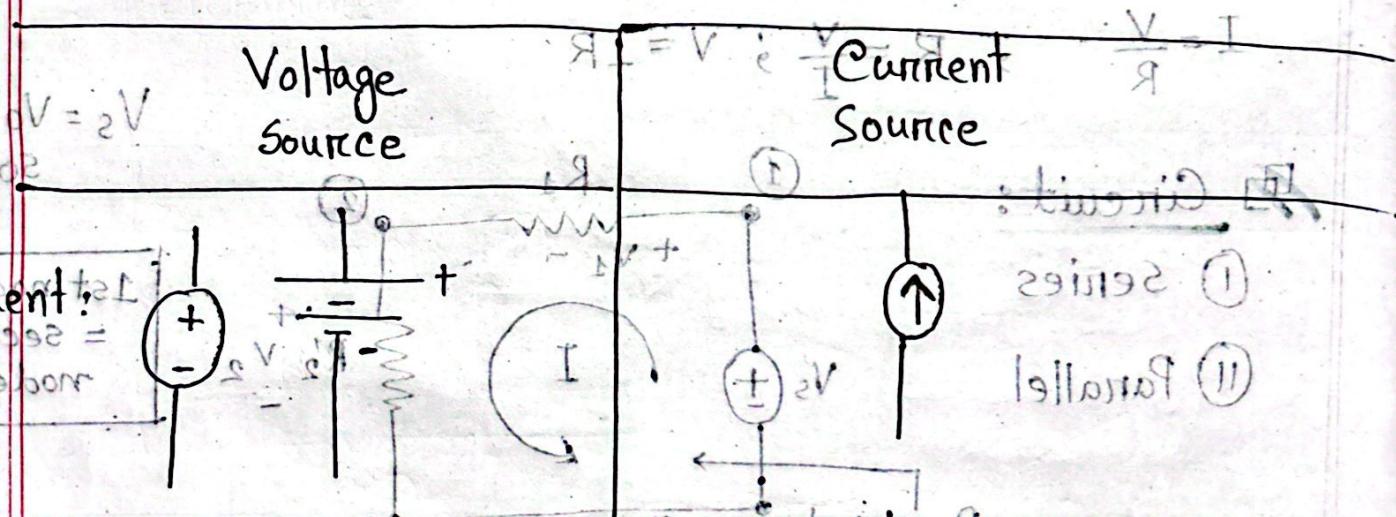


Independent:

voltage source

current source

Dependent:

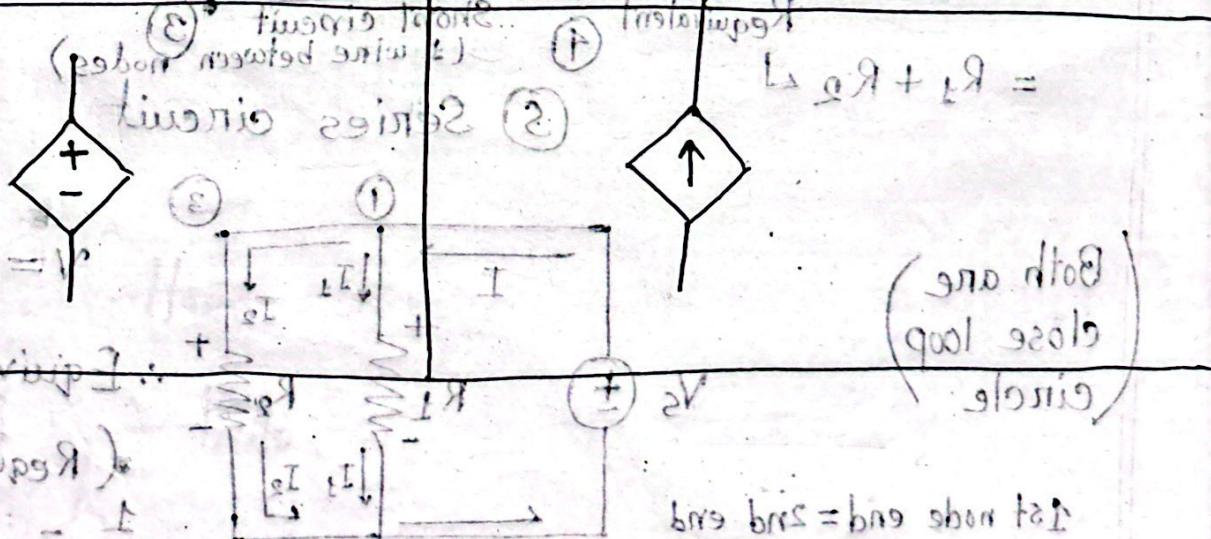

$$\frac{V}{R_s} = \frac{I}{R_s} + \frac{I}{R_s} = \frac{1}{R_s} + \frac{1}{R_s}$$

basis basis = basis short basis

basis basis = basis short basis

Solution

Step 1: Identify series/parallel combination
Step 2: Go left to right & right to left solve

Open circuit:

$$V = \text{max} = 9V$$

$$I = 0$$



	Series	Parallel
V	Divided voltage	Same voltage
I	Same current	Divided current

Short circuit:


$$I = \text{max}$$

Determine the equivalent resistance

Determine the equivalent resistance

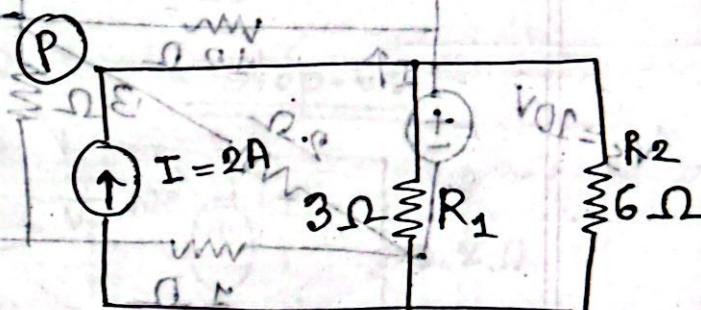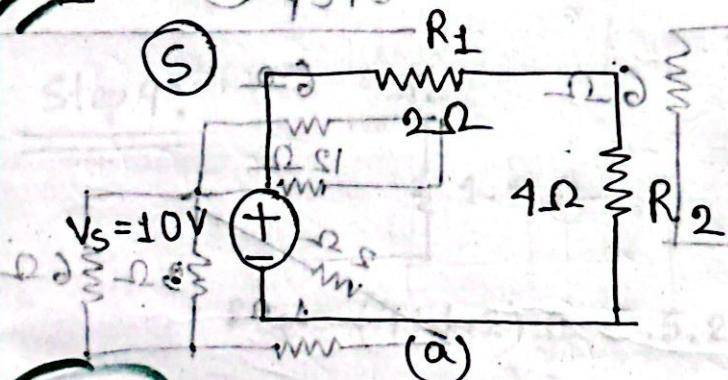

Soln:

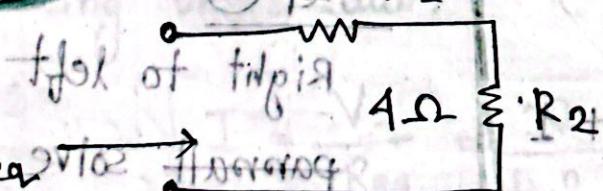

$$R_{eq} = R_1 + R_2$$

$$= (2+4)\Omega$$

$$= 6\Omega$$


$$R_{eq} = \frac{2 \times 4}{2+4} + 3\Omega$$

$$R_{eq} = \frac{8}{6} + 3\Omega = 6\Omega$$

$$R_{eq} = \frac{3 \times 6}{3+6}\Omega$$

$$= 2\Omega$$

Find Req:

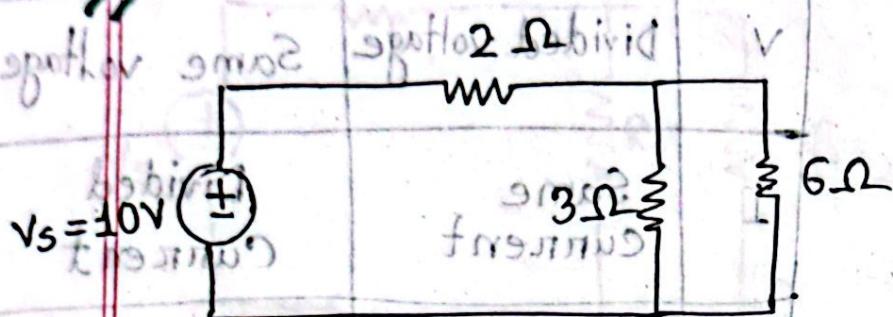



$$\text{Req} = [2 + (3 \parallel 6)] \Omega$$

$$= \left[2 + \frac{3 \times 6}{3+6} \right] \Omega$$

$$= \frac{12}{2+3} \Omega$$

$$= 4 \Omega$$

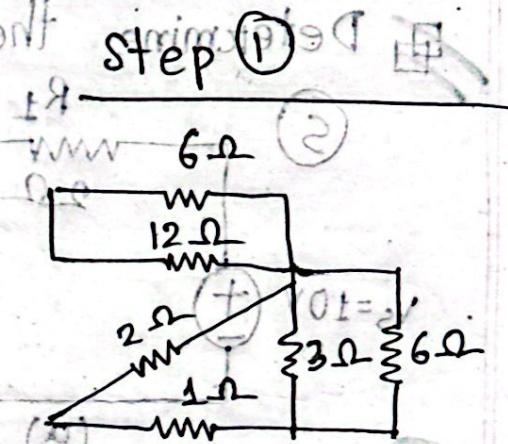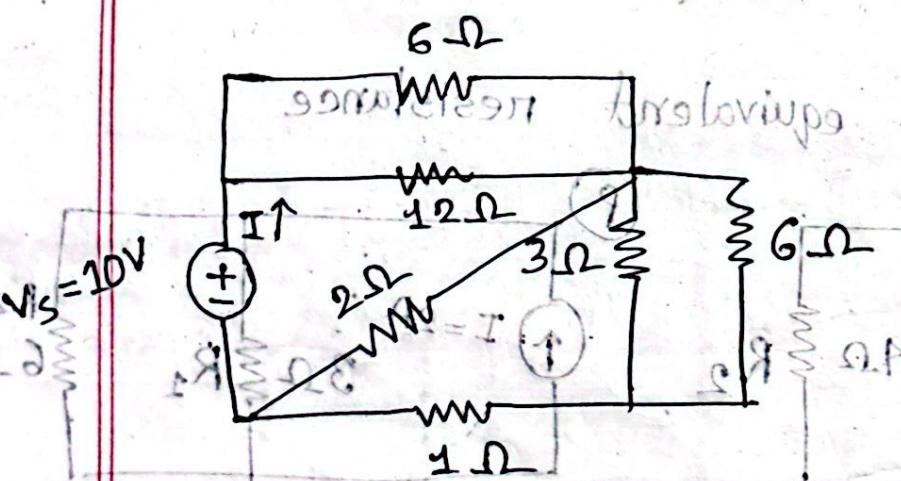Determine the equivalent resistance and current



$$2 + (6 \parallel 12) + (3 \parallel 6) + 1$$

$$\Rightarrow 2 + \frac{6 \times 12}{6+12} + \frac{3 \times 6}{3+6} + 1$$

$$\Rightarrow 2 + 4 + 2 + 1$$

$$\Rightarrow 9 \Omega$$


Step ②

Right to left
parallel solve parallel


Step ③

Wrong Answer


Solution %

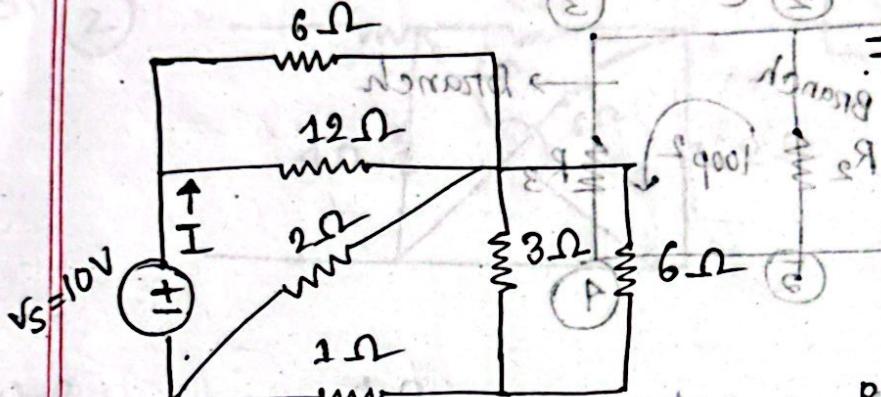


Step 1:

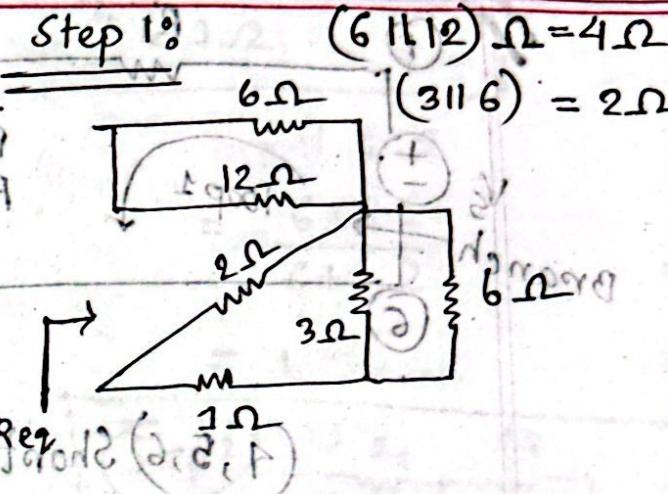


Step 2:

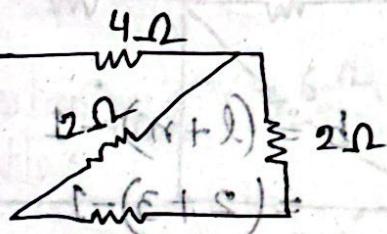


Step 3:

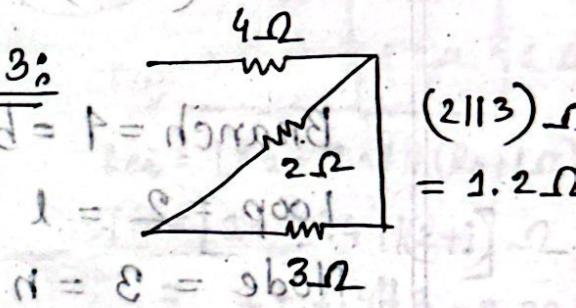

Step 4:

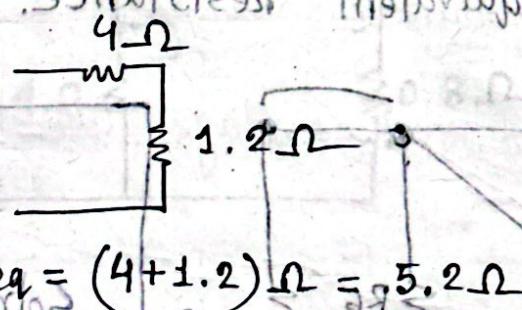

Step 6:

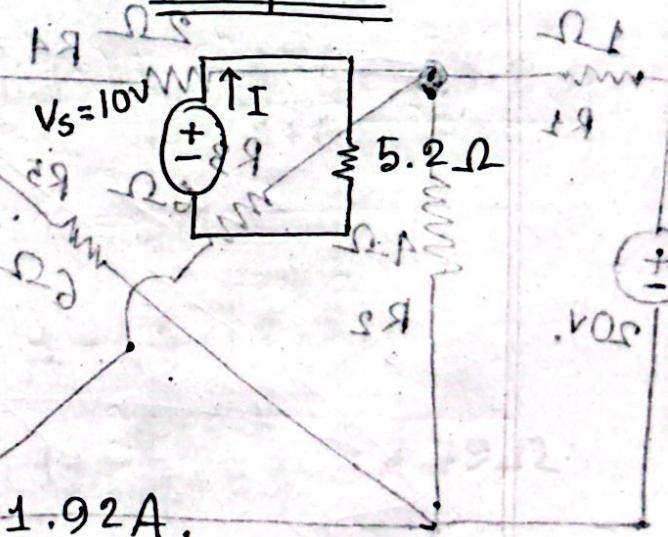


Using Ohm's law:


$$I = \frac{V_s}{R_{eq}}$$

$$I = \frac{10}{5.2} = 1.92A$$

$\Sigma R_s = 2\Omega$

$$I = \frac{V_s \times R_s}{R_s + R_p}$$

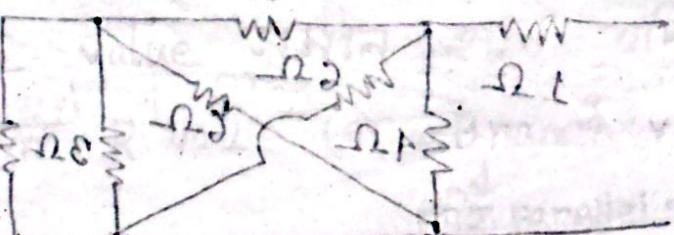

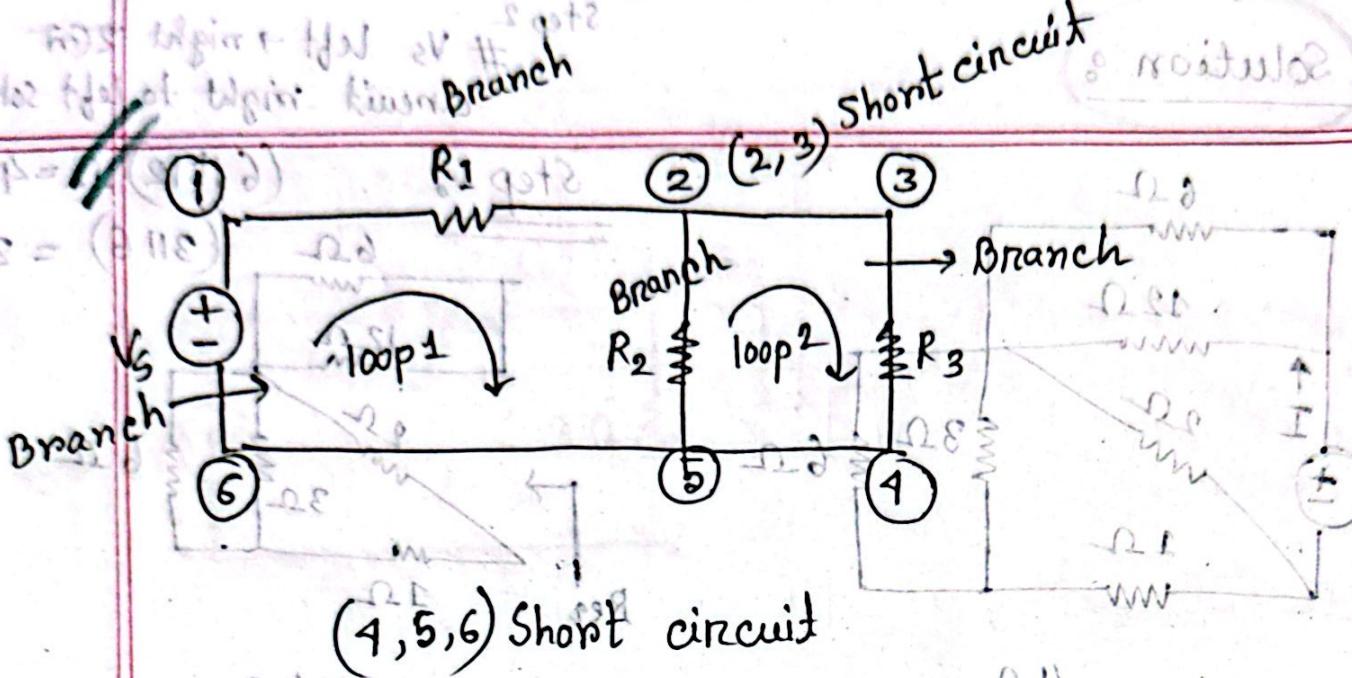

$$\text{Branch} = 4 = b$$


$$\text{Loop} = 2 = l$$

$$\text{Node} = 3 = n$$



$$b = (l+n)-1$$

$$= (2+3)-1$$

Determine the equivalent resistance.

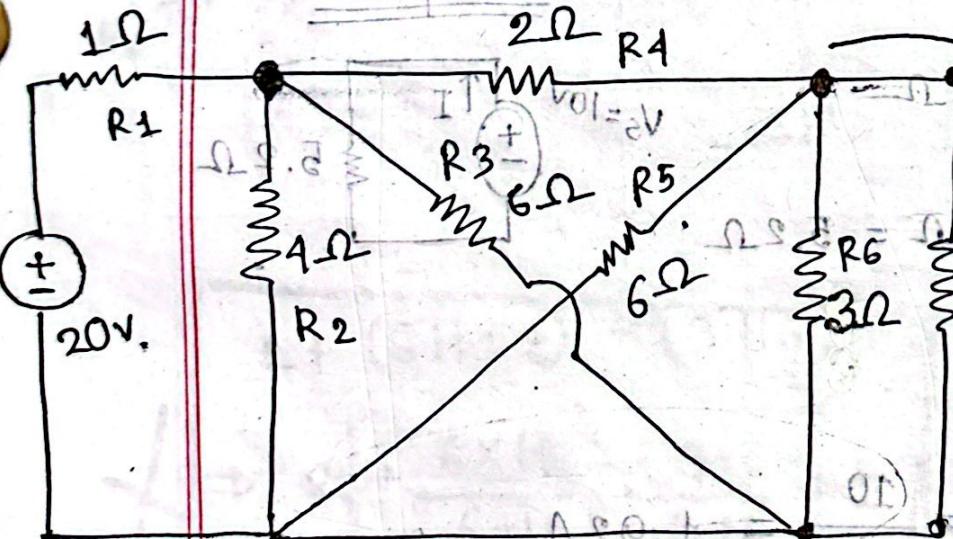


Step 1: Open Source

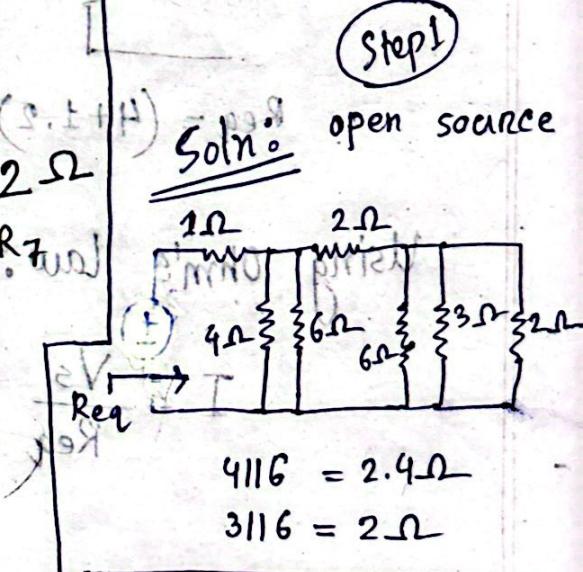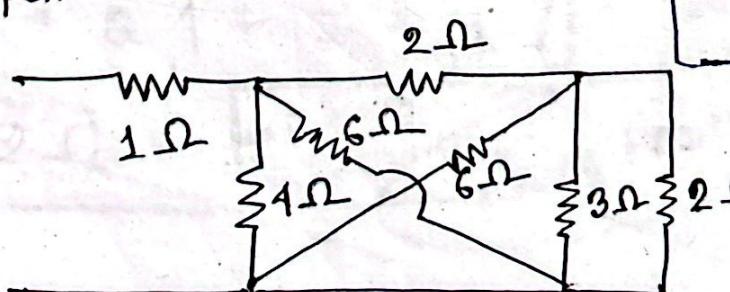

$$\therefore 3 \parallel 2 = \frac{3 \times 2}{3+2} = 1.2$$

Determine I, V_1, V_2

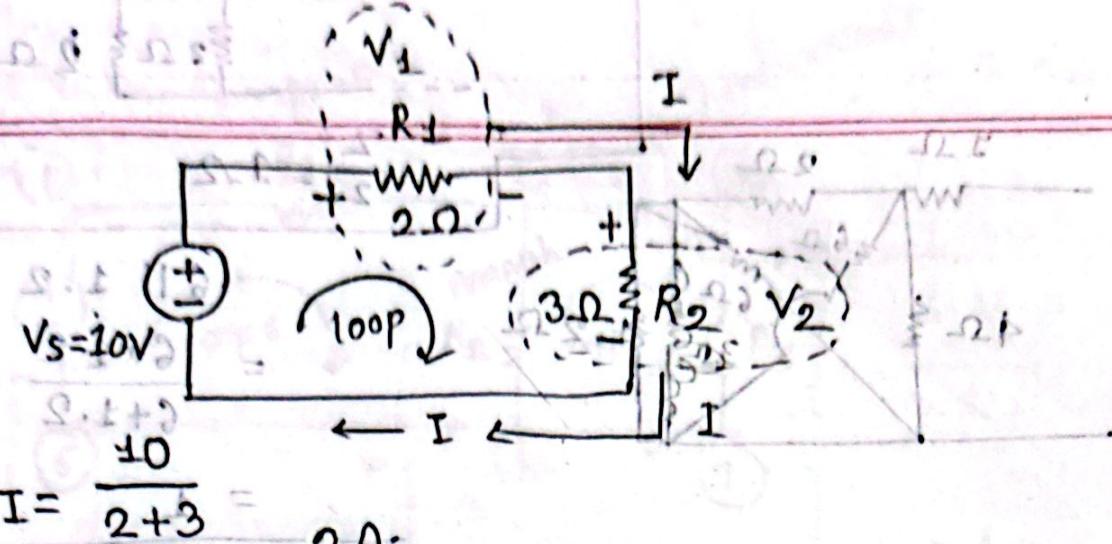

$$V_1 = IR_1 = (2 \times 2)V = 4V$$

} Distributed voltage

$$V_2 = IR_2 = (2 \times 3)V = 6V$$

$$V_s = 4 + 6 = 10V = \text{Source voltage}$$

This is called Kirchoff's voltage law (KVL)

$$\sum_{n=1}^N V_n = 0 \quad [V_s - V_1 - V_2 \dots = 0]$$

and every

To find KVL: use clockwise method in each loop.

$$\text{Applying KVL; } -V_s + V_1 + V_2 = 0 \quad (\text{Input wise})$$

$$V_s - V_1 - V_2 = 0 \quad (\text{Output wise})$$

$$10 - 4 - 6 = 0$$


$$\text{OR } -V_s + IR_1 + IR_2 = 0$$

parallel series

~~Practise -
odd number exercise
Alexander Book~~

To Verify KVL: $V_s - V_1 - V_2 = 0$ or Formula $V_s = V_1 + V_2$

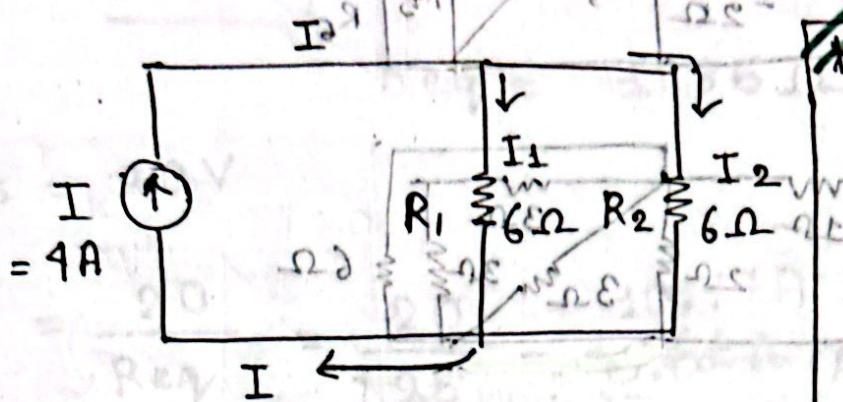
* KVL is only applicable for series circuit.



* Parallel applicable
Kirchoff current Law:
 $I = I_1 + I_2$

$$\frac{I}{\text{no. of branch}} = \frac{4A}{2} = 2A = I_1 = I_2$$

$$\sum_{n=1}^m I_n = 0$$

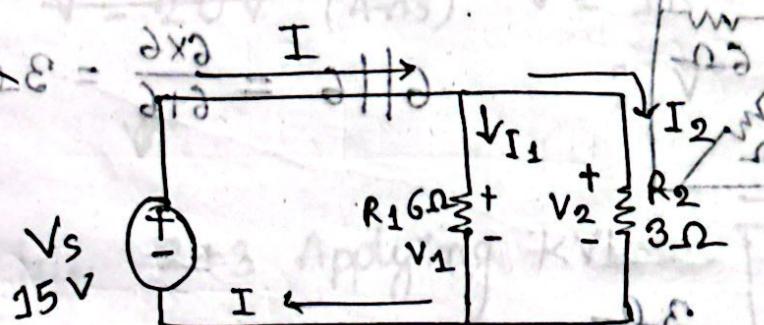

Since [Source || R_1 || R_2]

$$V_1 = V_2 = V_s = 15V$$

$$I_1 = \frac{V_s}{R_1} = \frac{15}{6} = 2.5A$$

$$I_2 = \frac{V_s}{R_2} = \frac{15}{3} = 5A$$

Another way to find I

$$\therefore \text{Req} = \frac{6 \times 3}{6+3} = 2\Omega$$

Ohm's law,

$$I_s = \frac{V_s}{\text{Req}} = \frac{15V}{2\Omega}$$


$$I = 7.5A$$

Using KCL at node A


$$I = I_1 + I_2 = 2.5 + 5 = 7.5A$$

03/07/21

Determine the Req.

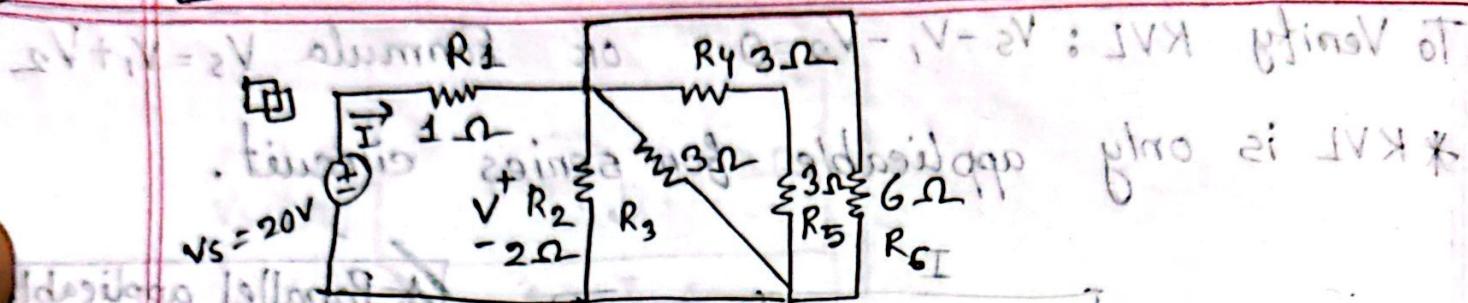


Step 1

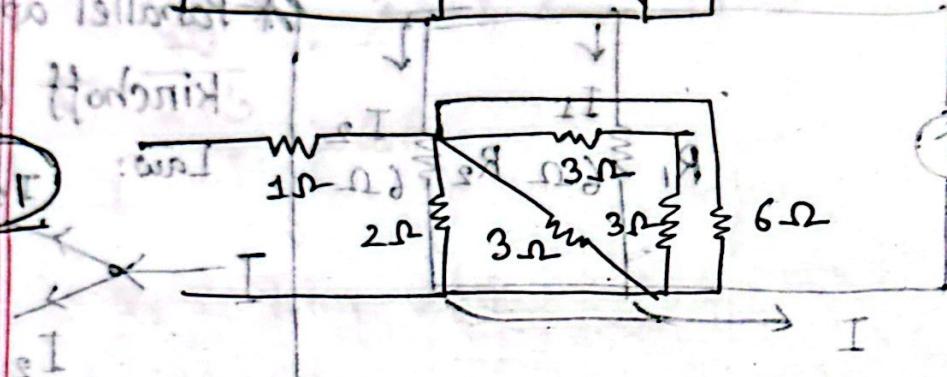

$$+I \Rightarrow IR_4 + R_5 = 3 + 3 = 6 \Omega$$

$$I = \frac{A_F}{\Omega} = \frac{6}{6} = 1$$


Step 2

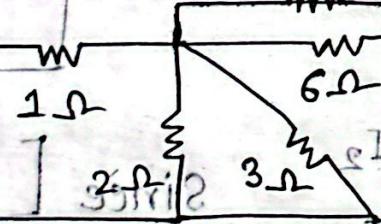

$$6//6 = \frac{6 \times 6}{6+6} = 3 \Omega$$

$$V_{21} = 2V = 1V$$


Step 3

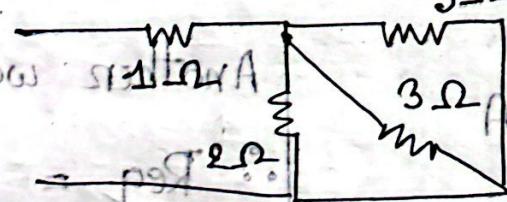

$$\Omega = \frac{3 \times 3}{3+3} = 1.5$$

$$A_F = \frac{1.5}{1.5} = 1$$

Step 4

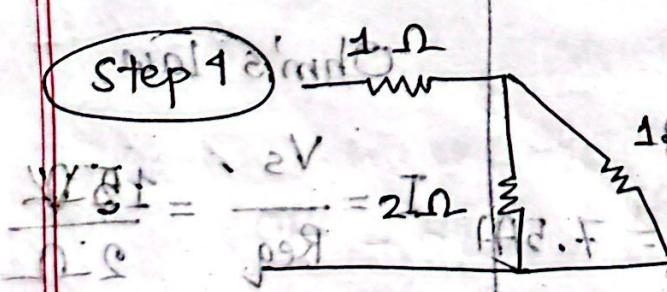


$$1.5 \Omega \text{ becomes } 2||1.5 \Omega$$

$$\frac{2 \times 1.5}{3.5} = \frac{1}{0.85} = 1.17$$

$$A_F = 1$$

Step 5

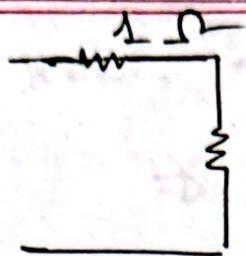


$$V_s = I_1 R + I_2 R \quad \text{where } I_1 = 0.85 \text{ A}$$

$$0 = 2 \times 8 + 0.85 \times 2 \quad \text{Rearranging}$$

$$R_{eq} = 4.85 \Omega \therefore \text{(Ans)}$$

$$V_s = 20V$$

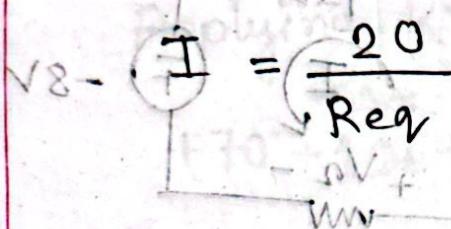

$$I = 10.77A$$

$$= 10.77A \quad \text{(Ans)}$$

$$V_s = V \quad \text{Since } (V_s || R_2)$$

$$V = 20V \quad \text{(Ans)} \quad V = IR = 10.77 \times 0.86 \Omega$$


$$\therefore V = 9.25V$$

Q

2+3 Applying KVL

$$-V_s + I_2 + I_3 + I_5 = 0$$

$$\Rightarrow -20 + I(2 + 3 + 5) = 0$$

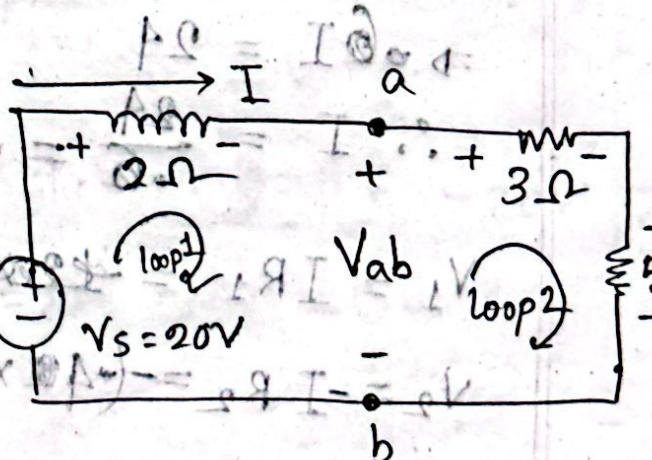

$$\therefore I(10) = 20$$

$$\therefore I = \frac{20}{10} = 2A$$

Applying KVL in loop 1,

$$-20 + I_2 + V_{ab} = 0$$

$$\Rightarrow -20 + 2 \times 2 + V_{ab} = 0$$

$$\therefore V_{ab} = 16V$$

Applying KVL in loop 2,

$$-V_{ab} + 3I + 5I = 0$$

$$\Rightarrow -V_{ab} + 8 \times 2 = 0$$

$$\therefore V_{ab} = 16V$$

Find V_1, V_2

Using KVL, $-V_2$

$$-32 + IR_1 - (-8)(-I) = 0$$

$$\Rightarrow -32 + 8 + I(4+2) = 0$$

$$\Rightarrow -24 + 6I = 0$$

$$\Rightarrow 6I = 24$$

$$\therefore I = \frac{24}{6} = 4A$$

$$V_1 = IR_1 = 4 \times 4 = 16V$$



$$V_2 = -IR_2 = -(4 \times 2) = -8V$$

find i and V_o

Using Ohm's law :

$$V_o = 12V + 6i + 0.2 - 4$$

$$= 12V + 6i - 4$$

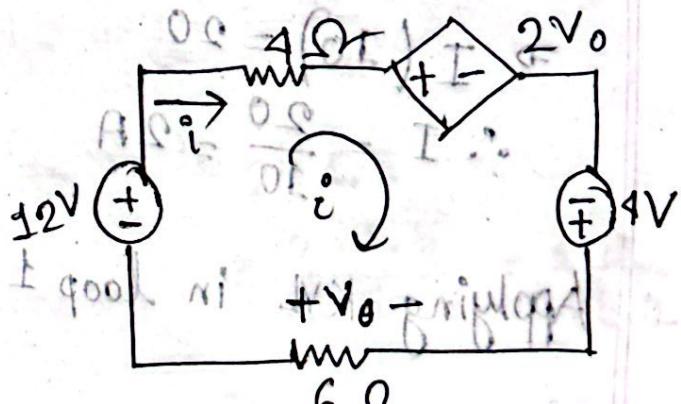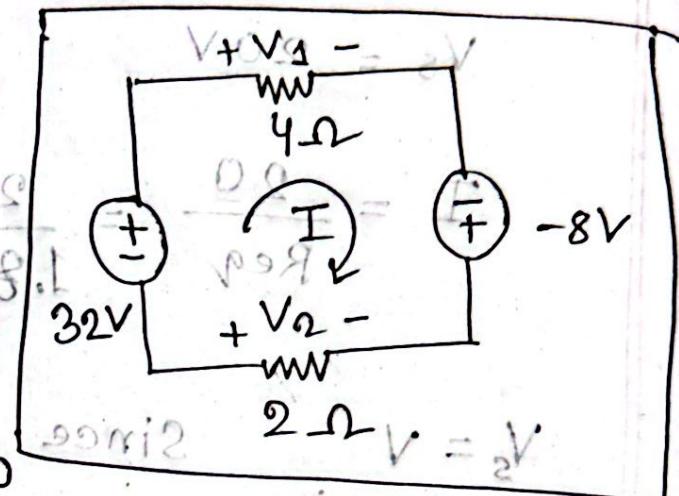

Applying KVL, $-12 + 4i + 2V_o - 4 + 6i = 0$

$$\Rightarrow -12 + 4i + 2 \times (-6i) - 4 + 6i = 0$$

$$\Rightarrow i = -8A$$

Q Find V_x and V_o .

Applying KVL,

$$+70 + 10I + 2 - V_o + (2 \times 10I) \Rightarrow 70 + 10I + 20 - (-5I) = 0$$


$$\Rightarrow 70 + 10I + 20 - (-5I) = 0$$

$$\Rightarrow 70 + 15I = 0 \quad 35I = -70 \quad I = -2A$$

$$\Rightarrow I = -2A$$

$$V_x = 10I = -2 \times 10 = -20V$$

$$V_o = 5I = -5 \times -2 = 10V$$

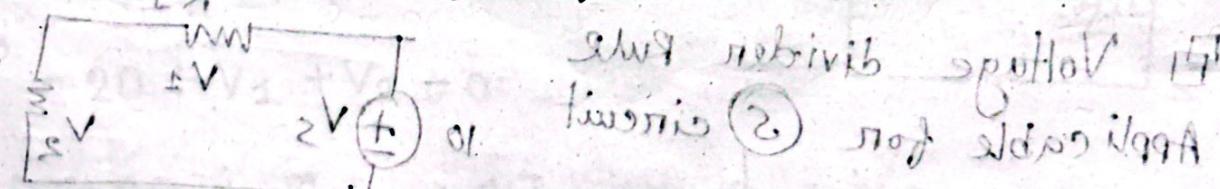


$$\frac{2V}{5\Omega + R_s} = V_o$$

$$\frac{2V}{R_s + 5\Omega} = V_o$$

$$V_o = \frac{2 \times 10}{15} = 2V \quad V_o = \frac{2 \times 10}{5} = 4V$$

I { + enter
- out }

Find V_o and i_o .

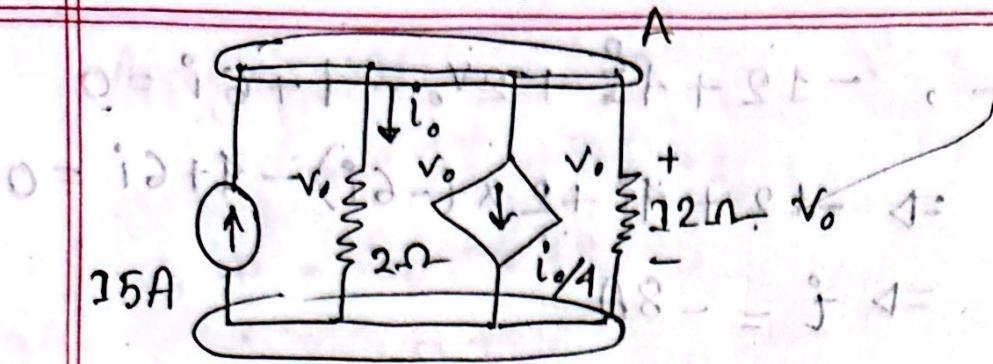

Applying KCL at node A

$$15 = i_o + \frac{i_o}{4} + i_1$$

$$\Rightarrow 15 = \frac{V_o}{2} + \frac{V_o}{4} + \frac{V_o}{12}$$


$$\Rightarrow 15 = \frac{V_o}{2} + \frac{V_o}{8} + \left(\frac{V_o}{12} - 10 \right) + 10 + OF$$

$$\Rightarrow 15 = \frac{6V_o + 1.5V_o + V_o}{24} = \frac{8.5V}{24}$$

$$\therefore V = \frac{15 \times 12}{8.5} = \frac{15 \times 24}{17} = 21.176 V$$

$$\text{Ohm's law, } i_o = \frac{V_o}{2} = \frac{21.17}{2} = 10.58 A$$

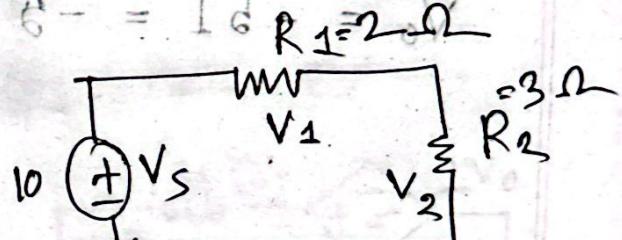Voltage divider Rule
Applicable for circuit



$$V_1 = \frac{V_s R_1}{R_1 + R_2}$$

$$V_2 = \frac{V_s R_2}{R_1 + R_2}$$

$$V_1 = \frac{10 \times 2}{5} = 4 V$$

$$V_2 = \frac{10 \times 3}{5} = 6 V$$


यदि node A द्वारा 6A का Source Current

Current Divider Rule:

$$I_1 = \frac{I_s \times R_2}{R_1 + R_2} = \frac{6 \times 3}{5} = 3.6A$$

$$I_2 = \frac{I_s \times R_1}{R_1 + R_2} = \frac{6 \times 2}{5} = 2.4A$$

यदि यही थाएं $I_1 = \frac{I_s \times (R_2 || R_3)}{R_1 + R_3 + R_2}$

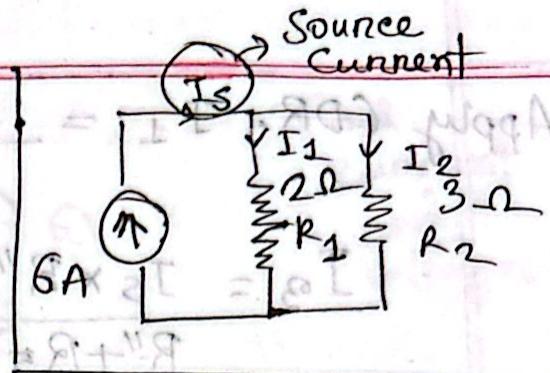

Find $V_1, V_2, I, I_2 \text{ & } I_3$

$$R_3 || R_4 = 2\Omega$$

$$\begin{aligned} R_{eq} &= 2 + (2+2) || 4 \\ &= 2 + 4 || 4 \\ &= 2 + 2 = 4\Omega \end{aligned}$$

$$\therefore I_s = \frac{20}{4} = 5A \quad (\text{Ans})$$



another
way, KVL,

$$-20 + V_1 + V_2 = 0$$

$$\Rightarrow -20 + 2I_s + 2I_s = 0$$

$$\Rightarrow -20 + 4I_s = 0$$

$$\Rightarrow I_s = 5A$$

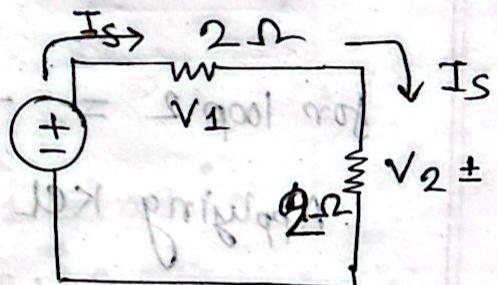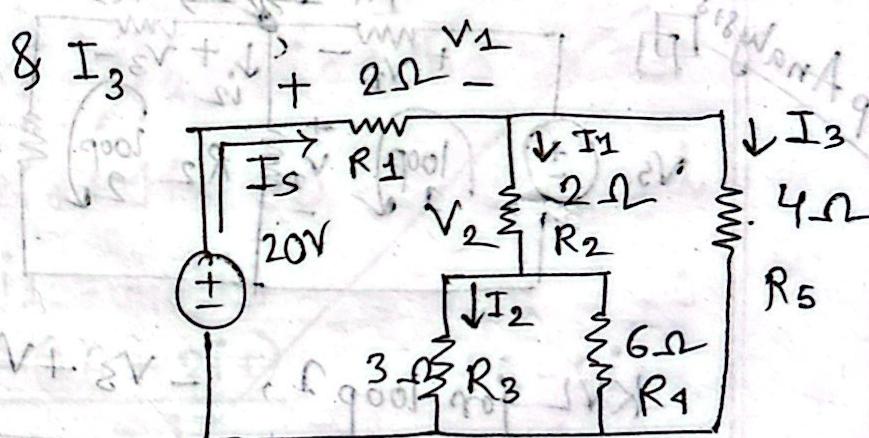

$$V_1 = 2I_s = 10V \quad (\text{Ans})$$

$$V_2 = 4I_s = 20V \quad (\text{Ans})$$


$$\text{CDR, } \therefore I_1 = I_2 = I_s = \frac{I_s \times R_2}{2+2} = \frac{5 \times 2}{4} = 2.5A$$

$$\text{Apply (DR), } I_1 = \frac{I_s \times R_5}{R'' + R_5} = \frac{5 \times 4}{4+4} = 2.5 \text{ A (Ans)}$$

$$I_3 = \frac{I_s \times R''}{R'' + R_5} = \frac{5 \times 4}{4+4} = 2.5 \text{ A (Ans)}$$

$$I_2 = \frac{I_1 \times R_4}{R_3 + R_4} = \frac{2.5 \times 6}{3+6} = 1.66 \text{ A (Ans)}$$

loop Analysis

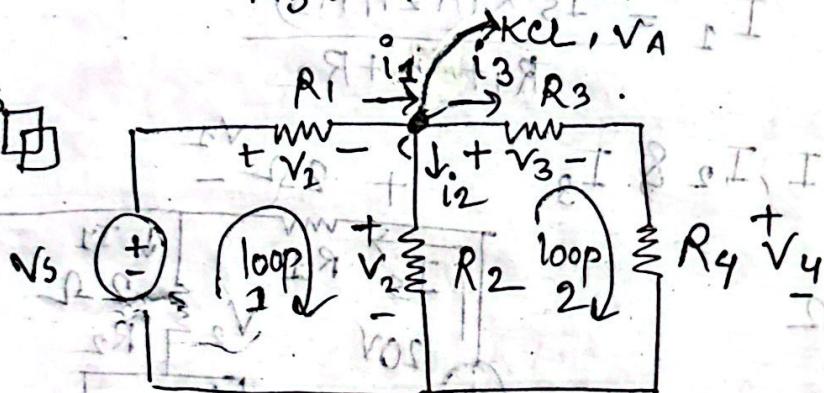

$$\text{KVL for loop 1, } -V_s + V_1 + V_2 = 0 \quad (1)$$

$$\text{for loop 2, } -V_2 + V_3 + V_4 = 0 \quad (2)$$

Applying KCL in node A,


$$i_1 = i_2 + i_3 \quad (3)$$

(Ans) Ohm's law ~~is~~ \rightarrow Apply ~~is~~ solve করা

$$(Ans) V_o = I R_1 \Rightarrow I = \frac{V_1}{R_1} \quad i_2 = \frac{V_1}{R_1} \quad i_3 = \frac{V_3}{R_3} \quad V_3 = V_s - V_A$$

$$i_2 = \frac{V_2}{R_2} \quad i_4 = \frac{V_4}{R_4} \quad A.D. = I = \frac{V_1}{R_1}$$

C.W
08/07/2021

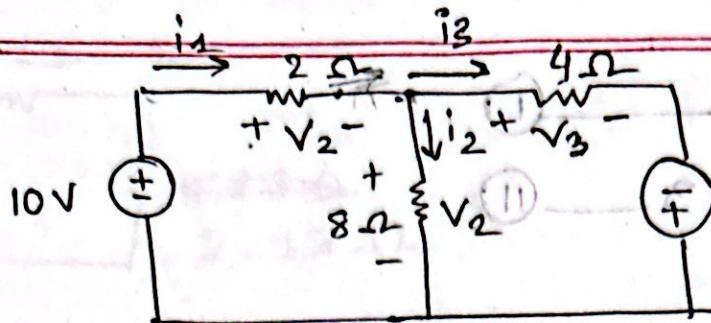

Find current and voltage

KVL,

$$10 + 2i_1 + 8i_2 = 0 \quad \text{--- (I)}$$

$$-8i_2 + 4i_3 - 6 = 0 \quad \text{--- (II)}$$

$$(I) + (II) \Rightarrow -10 + 2i_1 + 8i_2 - 8i_2 + 4i_3 - 6 = 0$$

$$\Rightarrow -16 + 2i_1 + 4i_3 = 0 \quad (= 0 \times 6) - 6 = 6i_3$$

$$\Rightarrow -16 + 2i_1 = -4i_3 \quad = 6i_1 + 6i_3 = 12i_1$$

$$i_3 = \frac{-(16 - 2i_1)}{4} = \frac{16 - 2i_1}{4}$$

$$-8i_2 - 16 + 2i_1 = -4 \cdot \frac{16 - 2i_1}{4}$$

Applying KCL at node A, $i_1 = i_3 + i_2$

$$V \cdot i_1 - i_2 - i_3 = 0 \quad \text{for both}$$

Using ohms law,

$$V_1 = 2i_1 = 2 \times 3 = 6V$$

$$V_2 = 2 \times 3 = 6V \quad 8i_2 = 4V$$

$$V_3 = 4i_3 = 4 \times 2.5 = 10V$$

Quiz - I

25/7/24

Monday

10.40 am

$5i_2 + i_3 = 5 \quad \text{--- (I)}$
 $-4i_2 + 2i_3 = 3 \quad \text{--- (II)}$
 $i_3 = 5 - 5i_2$

(I) $-4i_2 + 2(5 - 5i_2) = 3$


$\Rightarrow -4i_2 + 10 - 10i_2 = 3$

$\Rightarrow -14i_2 = -7 \quad \therefore i_2 = \frac{-7}{-14} = \frac{1}{2} = 0.5$

$i_3 = 5 - (5 \times 0.5) = 2.5$


$i_1 = i_3 + i_2 = 2.5 + 0.5 = 3$


$\therefore i_1 = 3$

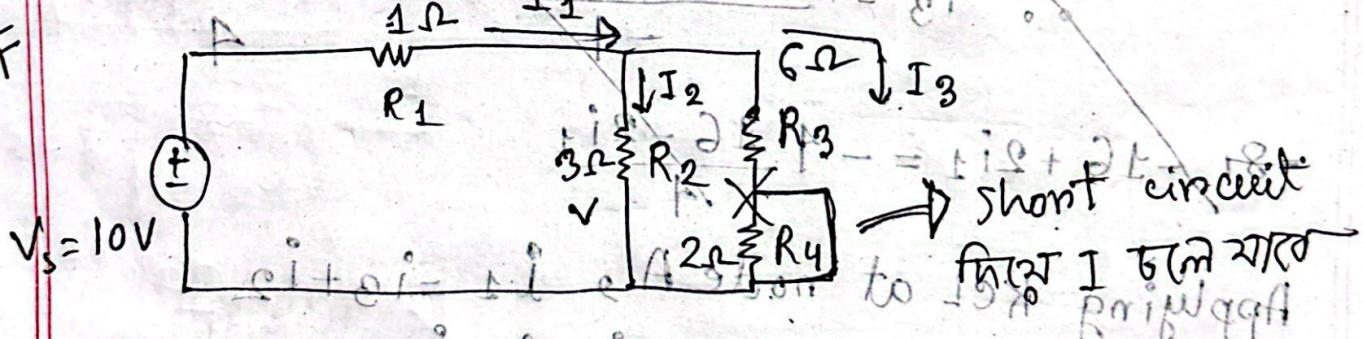

find I_1, I_2, I_3 & V .

Ans:

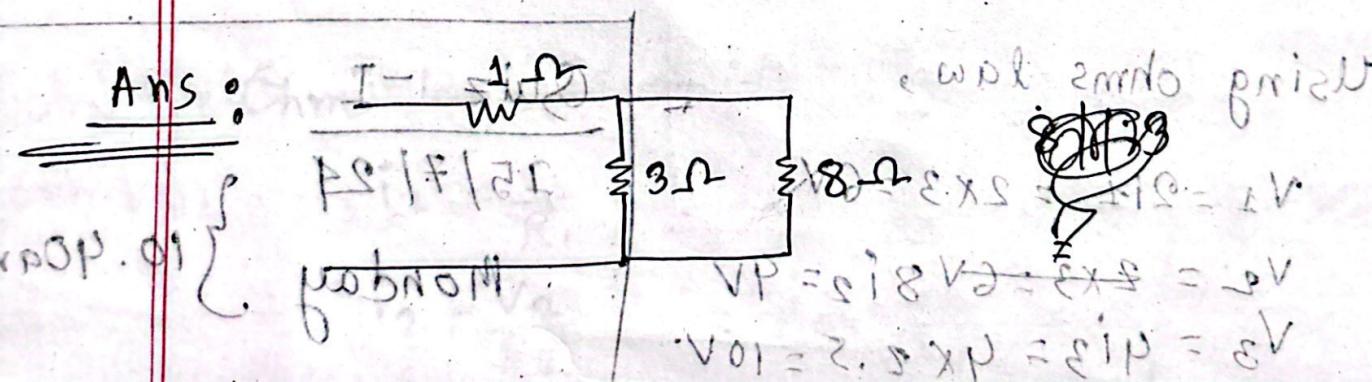

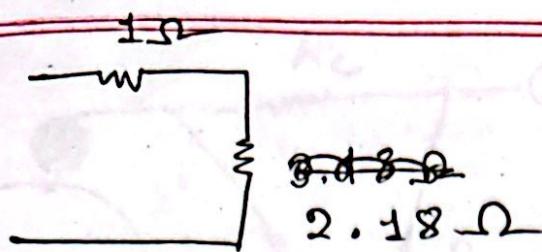

$$8 \parallel 3 = 2.18 \Omega$$

$$Req = 1 + 2.18 \Omega$$

$$= 3.18 \Omega$$

$$V = I \times 3.18$$

$$= 3.18 \times 0.31 A$$

$$= 0.98 V$$

$$I_1 = \frac{V_s}{Req}$$

$$= \frac{10}{3.18}$$


$$= 0.31 A$$

$$3.14 A$$

$$I_2 = \frac{I_1 \times (R_3 + R_4)}{3 + 2} = \frac{0.31 A}{5} = 0.496$$

$$I_3 = \frac{I_s (R_2)}{3 + 2} = 0.186 A$$

Soln

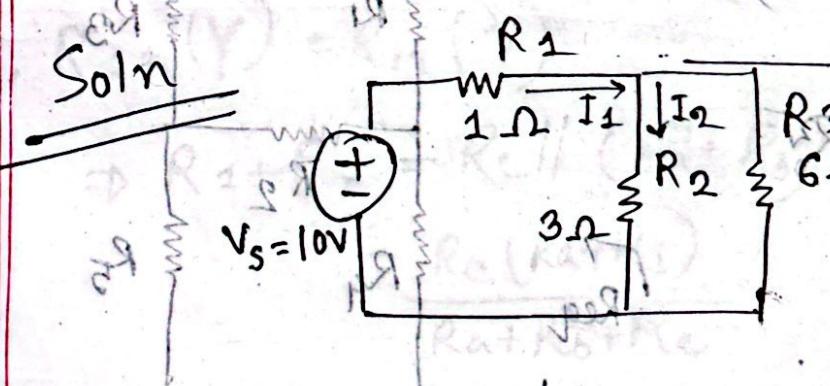

$$3 \parallel 6 = \frac{3 \times 6}{3 + 6} = 2 \Omega$$

$$Req = 1 + 2 = 3 \Omega$$

$$I_1 = \frac{10}{3} = 3.33 A$$

$$I_2 = 2.22 A \quad I_3 = 1.11 A$$

~~We can also use~~

Applying KVL, loop 1

$$-V_s + I_1 1 + I_2 3 = 0$$

$$I_1 1 + I_2 3 = 10$$


Loop 2

$$-3I_2 + 6I_3 = 0$$

$$\Rightarrow -I_2 + 2I_3 = 0 \quad \text{--- (II)}$$

KCL,

$$\text{Node A} \quad I_1 = I_2 + I_3$$

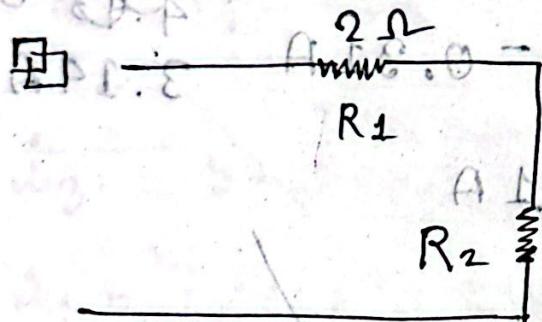

Conductance = $\frac{1}{R}$

$$G_1 = \frac{1}{2} \text{ S}, \quad G_2 = \frac{1}{3} \text{ S}$$

~~$$R_{eq} = 2 + 3 = 5 \Omega$$~~

$$G_1 = \frac{1}{2}, \quad G_2 = \frac{1}{3}, \quad G_{eq} = \frac{2 \times 3}{3 + 2} = 1.2 \text{ S}$$




WYE DELTA (Δ -Y)


Transformation

$$T - \pi \quad \text{or} \quad \Delta - Y$$

$$A_{EE} = \frac{01}{E} = \frac{1}{E} I$$
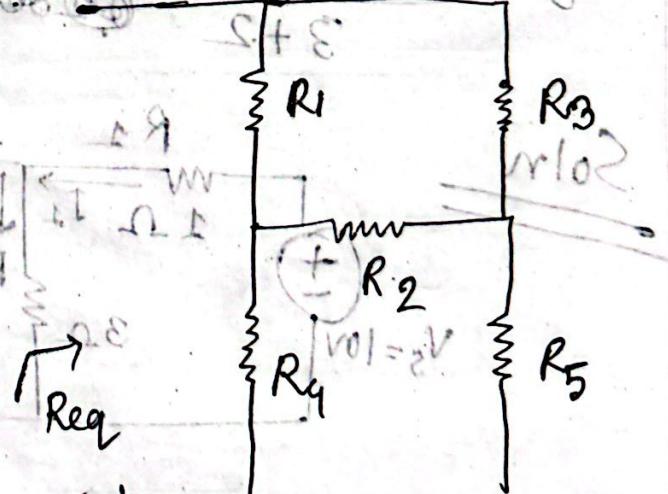
$$A_{II} = E + A_{EE} = E + \frac{1}{E} I$$



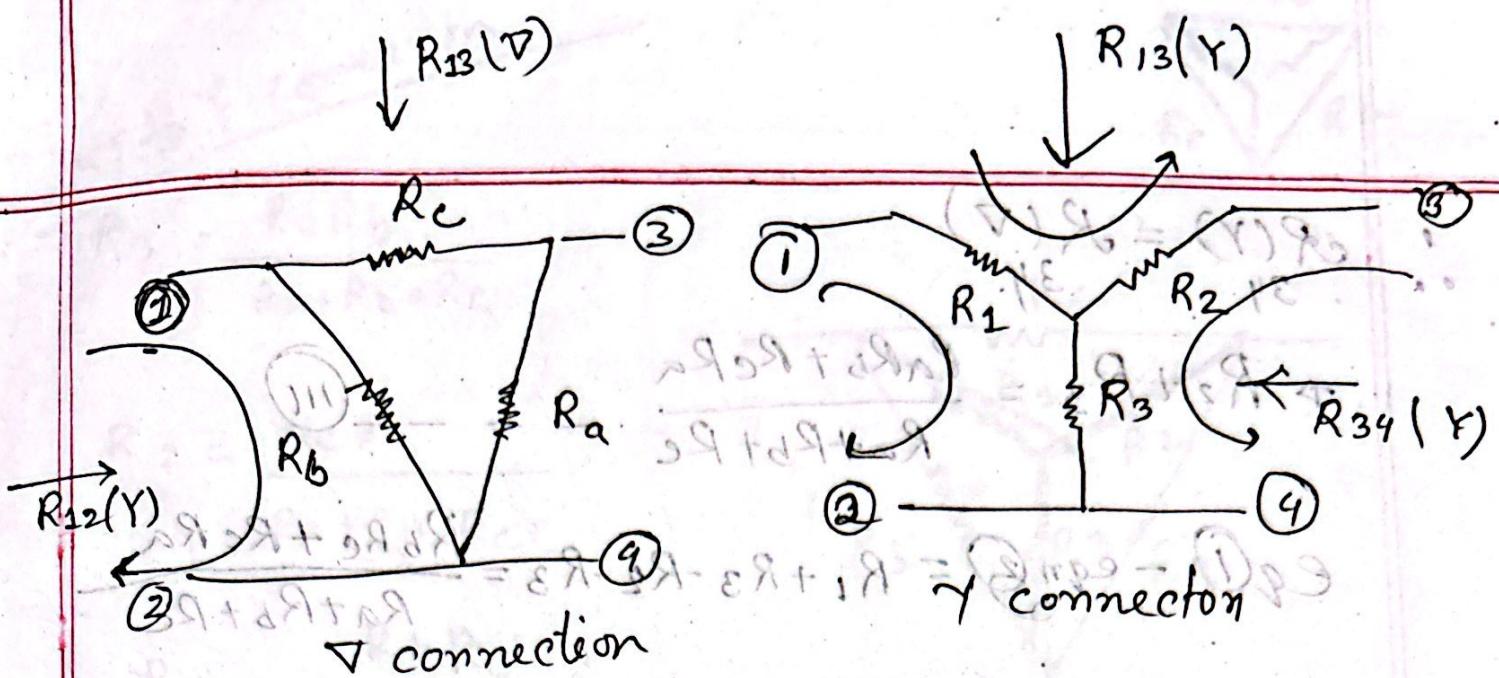

$$\text{V1} - R_{12}(Y) = R_{12} \cdot \frac{1}{(R_c + R_a)} \quad R_{12}(Y) = R_1 + R_3$$

$$R_{13}(Y) = R_c \parallel (R_a + R_b)$$

$$R_{13}(Y) = R_1 + R_2$$

$$R_{34}(Y) = R_a \parallel (R_b + R_c)$$

$$R_{34}(Y) = R_2 + R_3$$

$$R_{12}(Y) = R_{12}(Y)$$

$$\Rightarrow R_1 + R_3 = R_b \parallel (R_c + R_a)$$

$$\frac{R_1 + R_3}{R_a + R_b + R_c} = \frac{R_b(R_c + R_a)}{R_a + R_b + R_c} = \frac{R_b R_c + R_b R_a}{R_a + R_b + R_c} \quad \text{--- (1)}$$

$$\therefore R_{13}(Y) = R_{13}(Y)$$

$$\Rightarrow R_1 + R_2 = R_c \parallel (R_a + R_b)$$

$$= \frac{R_c(R_a + R_b)}{R_a + R_b + R_c}$$

primitived

$$\therefore R_1 + R_2 = \frac{R_c R_a + R_c R_b}{R_a + R_b + R_c}$$

$$\therefore \text{eq}(Y) = \text{eq}(\nabla)$$

$$\Rightarrow R_2 + R_3 = \frac{R_a R_b + R_c R_a}{R_a + R_b + R_c}$$

$$\text{eq}(\textcircled{1}) - \text{eq}(\textcircled{3}) = R_1 + R_3 - R_2 - R_3 = \frac{R_b R_c + R_c R_a}{R_a + R_b + R_c}$$

$$R_1 - R_2 = \frac{R_b R_c + R_c R_a}{R_a + R_b + R_c}$$

~~$$\text{eq}(\textcircled{1}) - \text{eq}(\textcircled{4}) = R_1 + R_3 - R_2 - R_3 = 0$$~~


$$\begin{aligned}\text{eq}(\textcircled{2}) + \text{eq}(\textcircled{4}) &= R_1 + R_2 + R_1 - R_2 = \frac{2 R_b R_c}{R_a + R_b + R_c} \\ &= 2 R_1 = \frac{2 R_b R_c}{R_a + R_b + R_c} \\ &= \text{eq}(\textcircled{1}) = \frac{2 R_b}{R_a + R_b + R_c}\end{aligned}$$

~~$$\text{eq}(\textcircled{4}) \text{ in } \text{eq}(\textcircled{1})$$~~

$$R_2 = R_b - \frac{R_b R_c + R_c R_a}{R_a + R_b + R_c}$$

Substituting R_1 in eq $(\textcircled{1})$
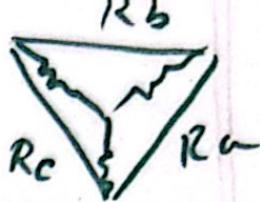
$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c} = \text{eq}(\textcircled{V})$$




Δ to Y conversion

$$R_3 = \frac{RaR_b}{Ra+R_b+R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$
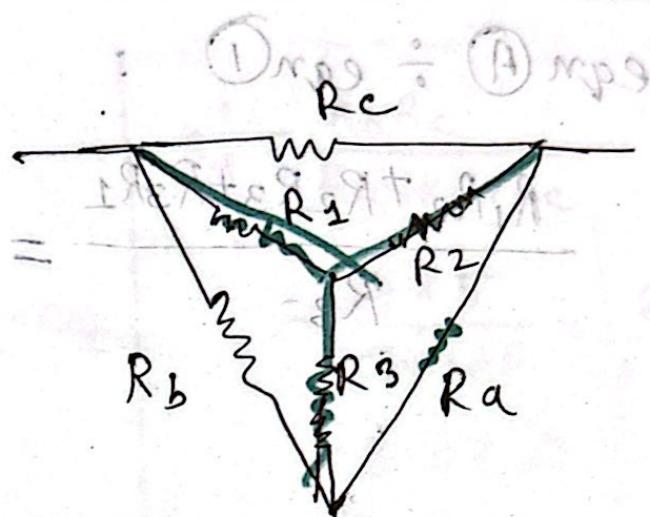
$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$



Δ conversion

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_b R_c (R_c R_a)}{(R_a + R_b + R_c)^2} + \frac{(R_c R_a)(R_a R_b)}{(R_a + R_b + R_c)^2} + \frac{(R_b R_c)(R_a)}{(R_a + R_b + R_c)}$$

$$= \frac{R_a R_b R_c^2 + R_a^2 R_b R_c + R_a R_b^2 R_c}{(R_a + R_b + R_c)^2}$$

$$= \frac{R_a R_b R_c (R_a + R_b + R_c)}{(R_a + R_b + R_c)^2}$$

$$= \frac{R_a R_b R_c}{R_a + R_b + R_c}$$

$$\therefore R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_a R_b R_c}{R_a + R_b + R_c}$$


eqn ① ÷ eqn ① :

$$\frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{\frac{R_a R_b R_c}{R_a + R_b + R_c}}{\frac{R_a R_b}{R_a + R_b + R_c}}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$


+ Similarly, $R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{(R_a + R_c)}$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1 + R_2 + R_3}$$

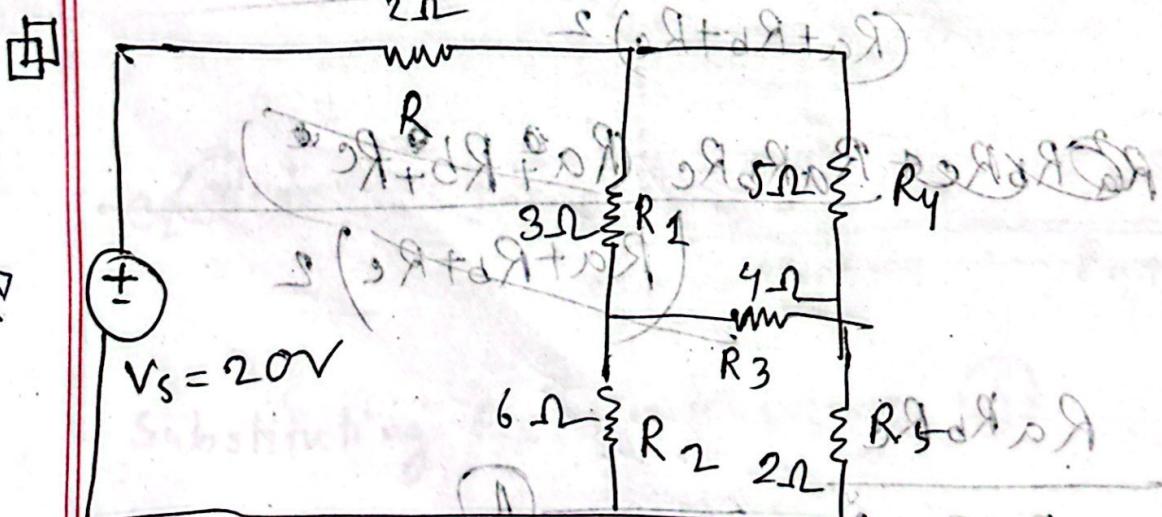

find I

In Δ format,

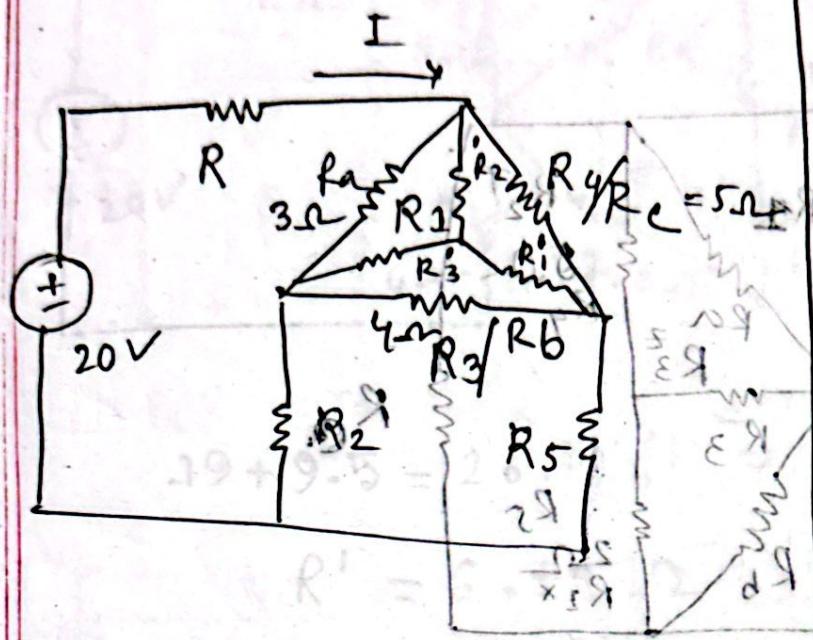

$$R_1' = \frac{R_b R_c}{R_a + R_b + R_c}$$


$$= \frac{4 \times 5}{3+4+5} = \frac{20}{12}$$

$$= 1.67 \Omega$$

$$R_2' = \frac{R_a + R_c}{R_a + R_b + R_c} = \frac{15}{12} = 1.25 \Omega$$

$$R_3' = \frac{12}{12} = 1 \Omega$$

Erase

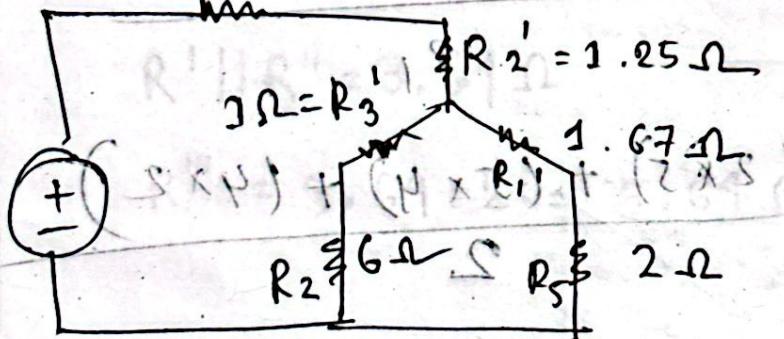

$$R'' = R_2 + R_3' = 6 + 1 = 7 \Omega$$

$$R''' = R_5 + R_1' = 2 + 1.67 = 3.67 \Omega$$

$$R^N = R_2 \cdot R'' \parallel R''' = \frac{7 \times 3.67}{7 + 3.67} = 2.407 \Omega$$

$$R^V = R^N + R_2' = 3.65 \Omega$$

$$R^W = 2 + 3.65 = 5.65 \Omega$$

$$I = \frac{V_s}{R_{eq}} = \frac{20}{5.65} = 3.53 A$$

Form of V RL

Y Equivalent Network,

$$sA_{AB} = I_R$$

$$\frac{V_0}{sI} = \frac{2\Omega^2}{s + R_1 + R_2}$$

$$sE = \frac{R_1 + R_2 + R_3}{s + R_1 + R_2 + R_3}$$

$$sI = \frac{2\Omega^2}{s + R_1 + R_2 + R_3}$$

$$Ra = \frac{R_1^2 + R_2^2 + R_3^2 + R_4^2}{sI}$$

$$= \frac{(2 \times 5) + (5 \times 4) + (4 \times 2)}{2\Omega^2} = 19 \Omega$$

$$= \frac{10 + 20 + 8}{2\Omega^2} = + \frac{38}{2} = 19 \Omega$$

$$R_b = \frac{38}{R_2} = \frac{38}{5} = 7.6 \Omega$$

$$sE = \frac{7.6 \times 8}{7.6 + 8} = 4.8 \Omega$$


$$R_{bc} = \frac{38}{4} = 9.5 \Omega$$

$$sE = \frac{3V}{20} = E$$

$$sE = 20.8 + 5 = 25.8 \Omega$$

$$sE = R_1 + R_2 = 19 \Omega$$

The Re Time

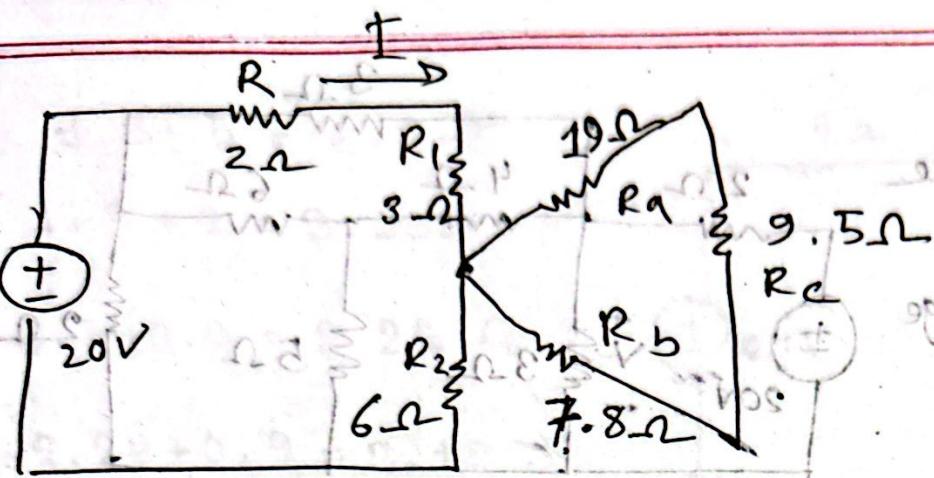


$$19 + 9.5 = 28.5 \parallel 7.8$$

$$R' = 6.12 \Omega$$

$$R'' = R_1 + R_2 = 9 \Omega$$

$$R' \parallel R'' = 3.61 \Omega$$

$$R''' = 3.64 + 2 = 5.64 \Omega$$

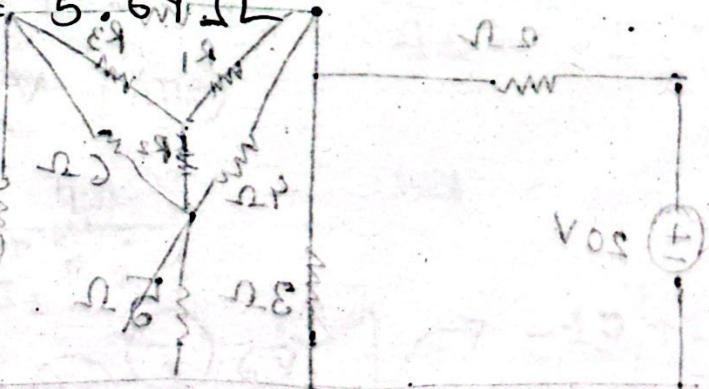

$$\Delta E.R = \frac{2 \times \delta}{\delta + p + \epsilon} = 89$$

$$\Delta E.0 = \frac{\delta \times \epsilon}{\delta + p + \epsilon} = 19$$


$$\Delta E.P = \frac{\delta \times p}{\delta + p + \epsilon} = 9$$

2.W
19/07/2024


Module III
Population and Environment

Mod 3

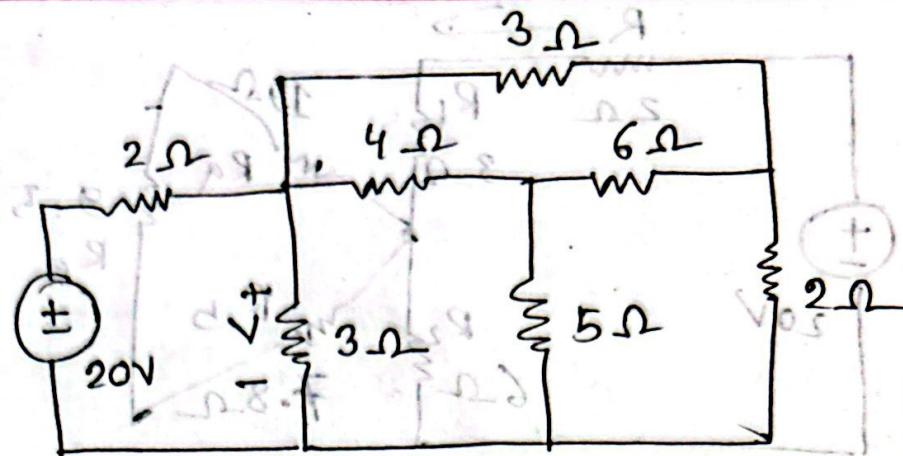Determine the current I and the voltage V.



Soln:

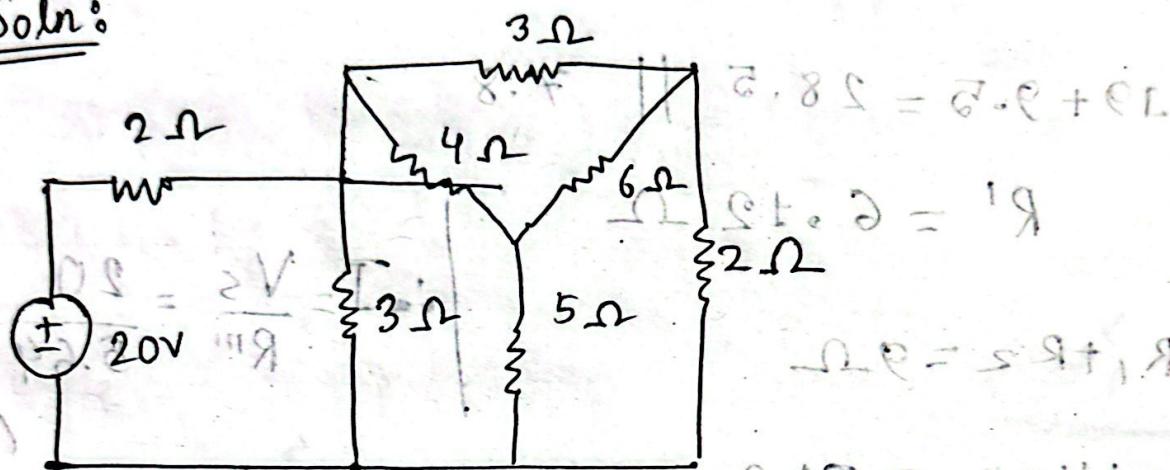


$$E \cdot 8\Omega = E \cdot R + E \cdot L$$

$$8V = 8\Omega \cdot I + 2\Omega \cdot I$$

$$8V = 10\Omega \cdot I + 2\Omega \cdot I$$

$$8V = 12\Omega \cdot I$$

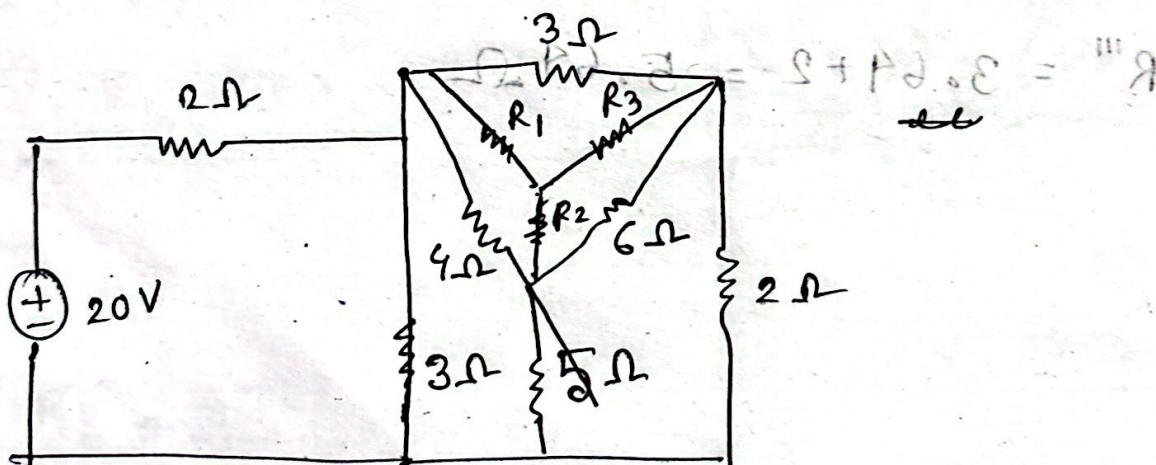

$$E \cdot 8\Omega = E \cdot R + E \cdot L = 12\Omega \cdot I$$

$$R_1 = \frac{3 \times 4}{3+4+6} = 0.9\Omega$$

$$R_2 = \frac{4 \times 6}{3+4+6} = 1.8\Omega$$

$$R_3 = \frac{3 \times 6}{3+4+6} = 1.3\Omega$$




$$1.8 + 5 = 6.8 \Omega$$

$$1.3 + 2 = 3.3 \Omega$$

$$6.8 \parallel 3.3 = 2.22 \Omega$$

$$2.22 + 0.9 = 3.12 \Omega$$

$$R' = 3.12 \parallel 3 = 1.53 \Omega$$

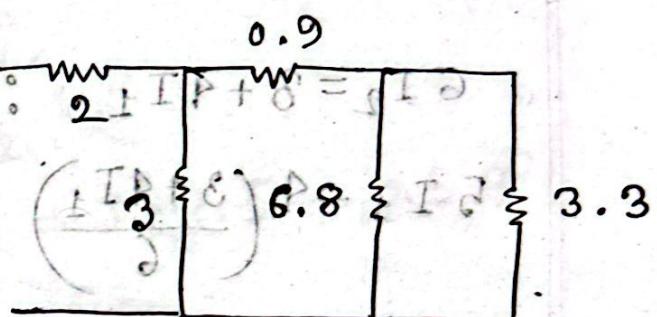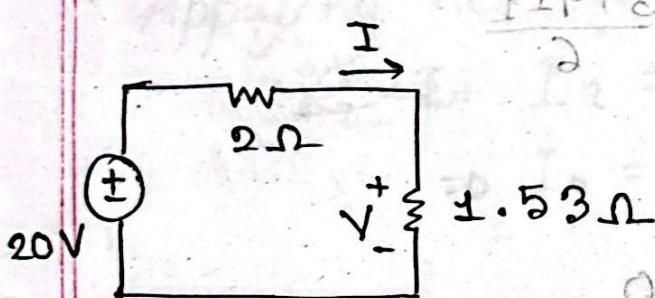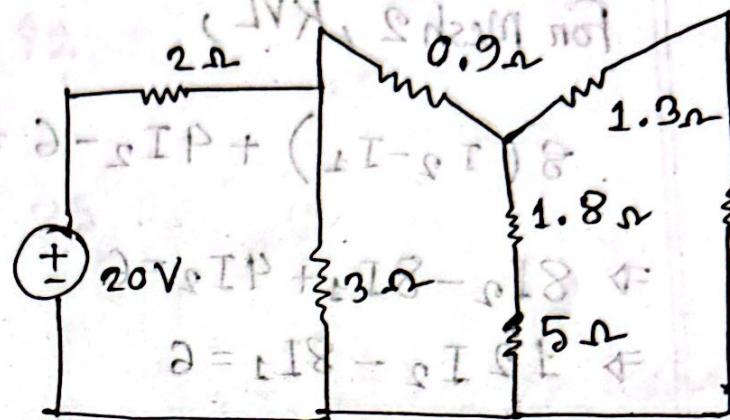


$$I = \frac{V_s}{R_{eq}} = \frac{20}{3.53} = 5.6 \text{ A (Ans)}$$

$$V = I R' = 5.6 \times 1.53$$

$$\text{Ans. } V = 8.5 \text{ V (Ans)}$$

Mesh Analysis

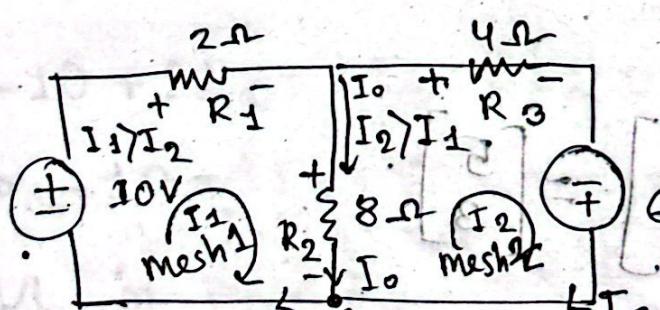

KVL in mesh 1,

$$-10 + 2I_1 + 8(I_1 - I_2) = 0$$

shared in both mesh

$$\begin{aligned} & -10 + 2I_1 + 8(I_1 - I_2) = 0 \\ & \Rightarrow -10 + 10I_1 - 8I_2 = 0 \\ & \Rightarrow 10I_1 - 8I_2 = 10 \\ & \therefore 5I_1 - 4I_2 = 5 \end{aligned}$$

(1)

For Mesh 2, KVL,

$$8(I_2 - I_1) + 4I_2 - 6 = 0$$

$$\Rightarrow 8I_2 - 8I_1 + 4I_2 = 6 \quad \text{Eq. 1}$$

$$\Rightarrow 12I_2 - 8I_1 = 6$$

$$6I_2 - 4I_1 = 3 \quad \text{Eq. 2}$$

$$5I_1 - 4I_2 = 5 \quad \text{Eq. 3}$$

$$6I_2 = 3 + 4I_1 \quad \therefore I_2 = \frac{3 + 4I_1}{6}$$

$$5I_1 - 4\left(\frac{3 + 4I_1}{6}\right) = 5$$

$$\Rightarrow 30I_1 - 12 - 16I_1 = 30$$

$$(errA) A2.6 = \frac{0.6}{8.8} = \frac{2V}{80\Omega} = 1A$$

$$\Rightarrow 14I_1 = 42$$

$$(errA) \therefore (5 \times 3) - 14I_2 = 5$$

$$\therefore I_1 = 3A$$

$$(errA) V6.5 \therefore I_2 = 2.5A$$

Another way, Cramer's Rule,

$$0 = \begin{vmatrix} 5 & -4 \\ -4 & 6 \end{vmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 3 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 5 & -4 \\ -4 & 6 \end{bmatrix}$$

$$0 = 30 - 16 \div 14 \neq 0$$

ribonade
new tool

$$\Delta_1 = \begin{bmatrix} 5 & -4 \\ 3 & 6 \end{bmatrix} = 42$$

$$\Delta_2 = \begin{bmatrix} 5 & 5 \\ -4 & 3 \end{bmatrix} = 35$$

$$I_1 = \frac{\Delta_1}{\Delta} = 3 A \quad (\text{Ans})$$

$$I_2 = \frac{\Delta_2}{\Delta} = 2.5 A \quad (\text{Ans})$$

Applying KCL in node A,

~~$I_1 = I_o + I_2$~~

~~$I_o = I_1 - I_2 = 3 - 2.5 = 0.5 A$~~

Find the mesh current

KVL in Mesh 1,

$$-10 + 2I_1 + 2(I_1 - I_2) = 0$$

$$\Rightarrow -10 + 2I_1 + 2I_1 - 2I_2 = 0$$

$$\Rightarrow -10 + 4I_1 - 2I_2 = 0$$

KVL in mesh 2,

$$-5 + 2(I_2 - I_1) + 3I_2 + 4I_2 = 0$$

$$\Rightarrow -5 + 2I_2 - 2I_1 + 3I_2 + 4I_2 = 0$$

$$\therefore 5I_2 - 2I_1 + 9I_2 = 5$$

5

$$9I_1 = 10 + 2I_2$$


$$\therefore I_1 = \frac{10 + 2I_2}{9}$$

$$9I_2 - 2\left(\frac{50 + 2I_2}{9}\right) = 5$$

$$\Rightarrow 38I_2 - 50 - 2I_2 = 45$$

$$\Rightarrow 16I_2 = 32 \quad I_2 = \frac{32}{16} = 2.25A$$

$$\therefore I_2 = 2.25A$$

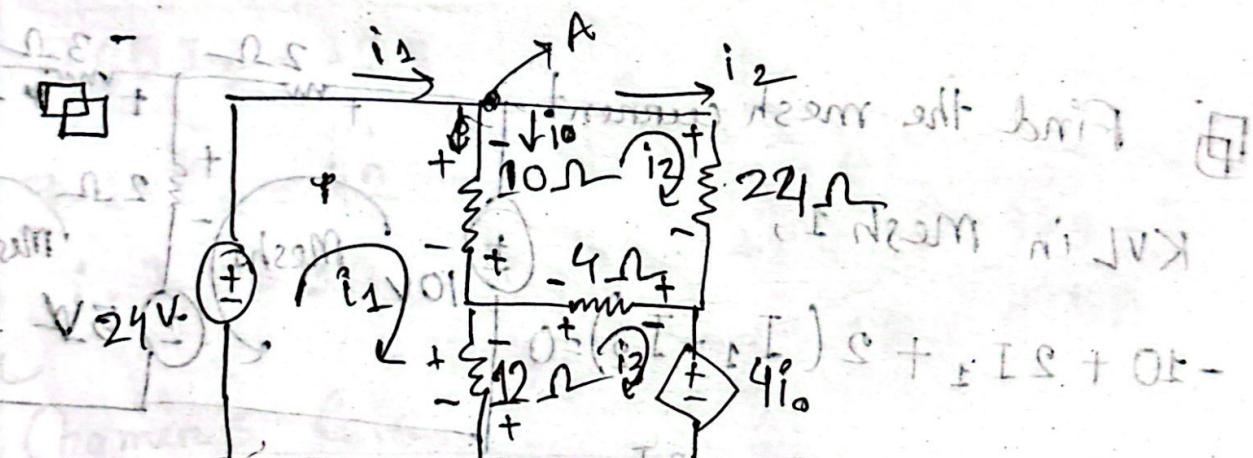

KVL in Mesh 1,

$$-24 + 10(I_1 - I_2) + 12(I_1 - I_3) = 0$$

$$\Rightarrow -24 + 10I_1 - 10I_2 + 12I_1 - 12I_3 = 0$$

$$\Rightarrow 22I_1 - 10I_2 - 12I_3 = 24$$

~~= Δ~~
KVL in Mesh 2,

$$+10(I_2 - I_4) + 24I_2 + 4I_0 = 0 \quad (I_2 - I_3)$$

$$\Rightarrow +10I_2 - 10I_1 + 24I_2 + 4I_2 - 4I_3 = 0$$

$$\Rightarrow -10I_1 + 38I_2 - 4I_3 = 0 \quad \therefore -5I_1 + 19I_2 - 2I_3 = 0$$

KVL in Mesh 3,

$$-12(I_3 - I_1) + 4(I_3 - I_2) + 4I_0 = 0$$

$$\Rightarrow 12I_3 - 12I_1 + 4I_3 - 4I_2 + 4I_0 = 0$$

$$\Rightarrow -12I_1 + 16I_3 - 4I_2 + 4I_0 = 0$$

$$\therefore -6I_3 + 20I_3 - 2I_2 + 4I_0 = 0$$

Applying KCL in node A

$$i_1 = i_0 + i_2$$

$$i_0 = i_1 - i_2$$

Putting i_0 ,

$$2I_3 - 2I_2 + 4(I_1 - I_2) = 0$$

$$\Rightarrow 2I_3 - 2I_2 + 4I_1 - 4I_2 = 0$$

$$\therefore 4I_1 - 6I_2 + 2I_3 = 0$$

$$2I_1 - 8I_2 + I_3 = 0$$

$$-i_1 - i_2 + 2i_3 = 0$$

$$\Delta =$$

$$\begin{bmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & 1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta_1 = \begin{bmatrix} 12 & -5 & -6 \\ 0 & 19 & -2 \\ 0 & -1 & 2 \end{bmatrix} = 12(38 - 2)$$

$$\Delta_2 = \begin{bmatrix} 12 & 11 & 12 & -6 \\ 0 & -5 & 0 & -2 \\ 0 & 0 & 2 \end{bmatrix}$$

$$\Delta_3 = \begin{bmatrix} 11 & -5 & 12 \\ -5 & 19 & 0 \\ -1 & 1 & 0 \end{bmatrix} =$$

$$\Delta = I_1 = \frac{\Delta_1}{\Delta} = 2i - 1i = i$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{(2i - 1i)(19 - 0) - (-5)(1 - 0)}{2i + 1i - 1} =$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{(2i - 1i)(-5 - 0) - (11)(1 - 0)}{2i + 1i - 1} =$$

Find mesh currents

$$\text{mesh 1}, -15 + 3I_1 + 2I_2 = 0$$


$$\Rightarrow 5I_1 = 15 \therefore I_1 = 3A$$

KVL in mesh 2,

$$4I_2 + 3I_2 = 0$$

$$\Delta E = 0 \Rightarrow 7I_2 = 0 \therefore$$

~~∴~~

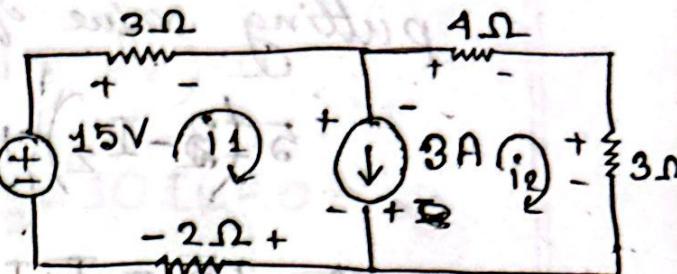

যদি mesh এর


মাঝখানে current

source থাকে

তোরলে supernode

(পুরো circuit) mesh
এর দ্বারা solve

ব্যবহা

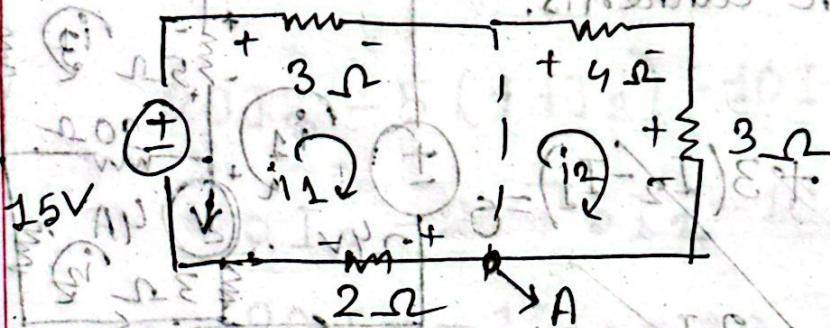

$$\begin{aligned} \text{KVL in Supermesh} & \left\{ -15 + 3I_1 + 4I_2 + 3I_2 + 2I_1 = 0 \right. \\ & \Rightarrow 5I_1 + 7I_2 = 15 \end{aligned} \quad \textcircled{1}$$

Applying KCL in node A,

$$I_S = I_1 + I_2$$

$$\Rightarrow I_1 + I_2 = 3A$$

$$\Rightarrow I_1 = 3 - I_2$$

AK

\textcircled{1}

\textcircled{111}

Putting value of eq (III) in eq (II).

$$5(3 - I_2) + 7I_2 = 15$$

$$\Rightarrow 15 - 5I_2 + 7I_2 = 15$$

$$\Rightarrow 2I_2 = 0$$

$$\therefore I_2 = 0 \text{ A}$$

$$\therefore I_1 = 3 - 0 = 3 \text{ A}$$

Find mesh currents.

Supermesh

$$-24 + 5(I_3 - I_1) + 3(I_2 - I_1) = 0$$

$$\Rightarrow 5I_3 - 5I_1 + 3I_2 - 3I_1 = 24$$

$$\Rightarrow -8I_1 + 3I_2 + 5I_3 = 24$$


Supermesh ($i_3 + i_2$),

~~i_3~~


KVL in supermesh,

$$\begin{aligned} \therefore -24 + (5I_1 - I_3) + 10(I_2 - I_3) \\ + 20I_2 = 0 \end{aligned}$$

$$\therefore 5I_1 + 30I_2 - 15I_3 = 24$$

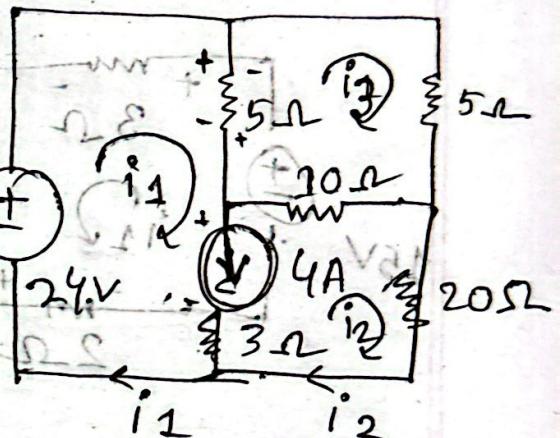

Soln:

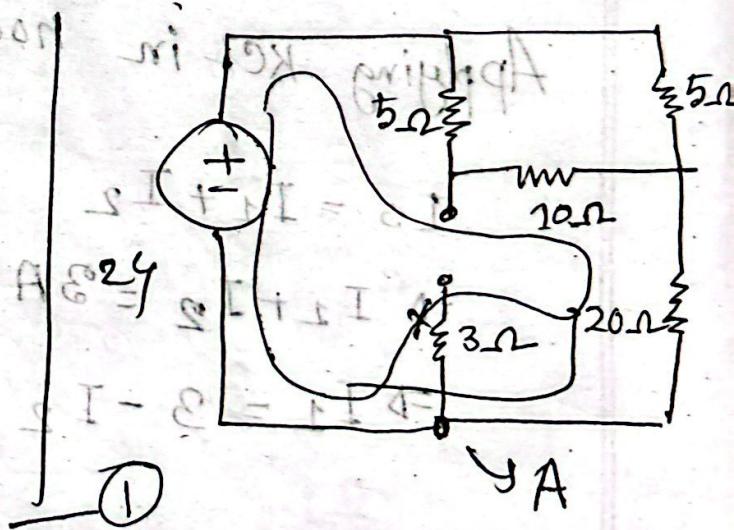

KVL, In mesh ③,

$$+5(I_3 - I_1) + 5I_3 + 10(I_3 - I_2) = 0$$

$$\Rightarrow 5I_3 - 5I_1 + 5I_3 + 10I_3 - 10I_2 = 0 \quad \text{---} \quad ⑪$$

$$\Rightarrow 20I_3 - 5I_1 - 10I_2 = 0 \quad \underline{\text{---}} \quad ⑪$$

Applying KCL in node A;

$$\cancel{4 + i_2 + i_1} \quad 4 + i_2 = i_1$$


$$20I_3 - 5(4 + I_2) - 10I_2 = 0$$

$$\Rightarrow 20I_3 - 20 - 5I_2 - 10I_2 = 0 \quad \text{---}$$

$$\Rightarrow 20I_3 - 15I_2 = 20 \quad \text{---}$$


$$\Rightarrow 4I_3 - 3I_2 = 4$$

$$\therefore I_2 = \frac{4 - 4I_3}{-3}$$

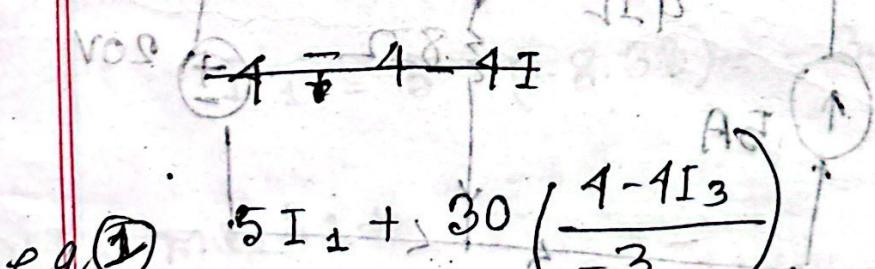

$$\text{eq } ⑪ \quad 5I_1 + 30 \left(\frac{1 - 4I_3}{-3} \right)$$

wrong

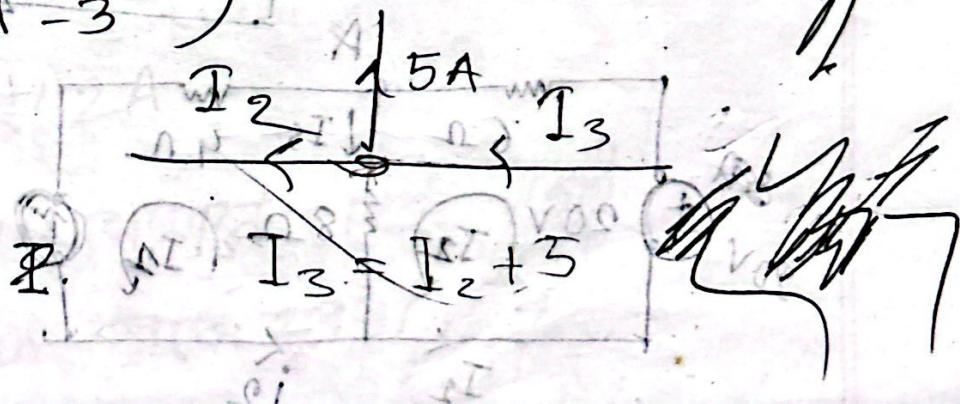

15/07/24 - Quiz - Mesh Analysis পদ্ধতি

$$-15i_2 + 20i_3 = 20 \quad (B)$$

$$35i_2 - 15i_3 = 4$$

$$\Rightarrow \cancel{35} \quad i_2 = \frac{4 + 15i_3}{35}$$

$$-15\left(\frac{4 + 15i_3}{35}\right) + 20i_3 = 20$$



$$\Rightarrow -60 - 225i_3 + 20i_3 = 700 \quad \text{Wrong}$$

$$\Rightarrow -205i_3 = 760$$

$$\therefore i_3 = -3.7$$

$$i_2 =$$

Find mesh current

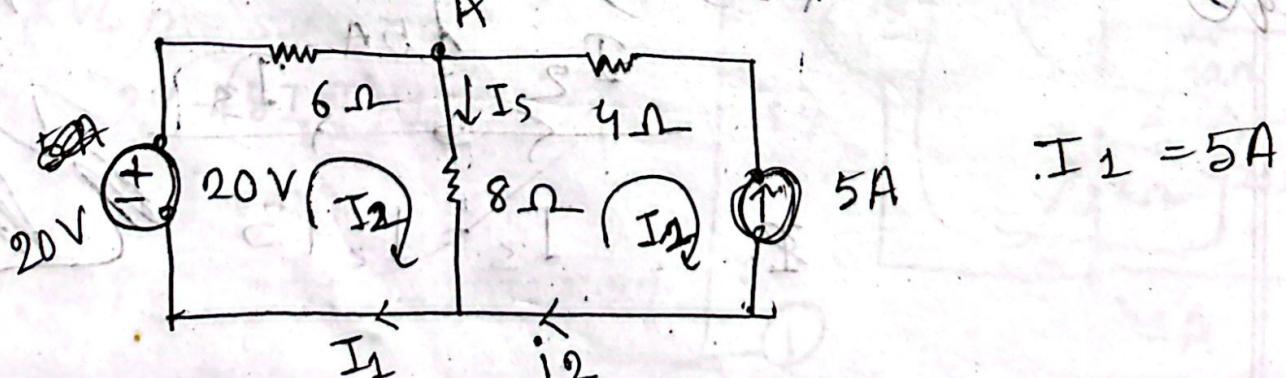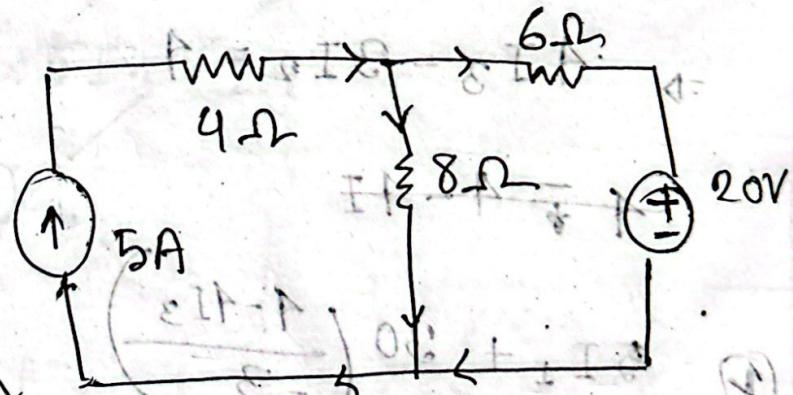

$$I_1 = 5A$$

KVL in mesh 1,

$$-20 + 6I_1 + 8(I_1 - I_2) = 0$$

$$\Rightarrow -20 + 6I_1 + 8I_1 - 8I_2 = 0$$

$$\Rightarrow -14I_1 - 8I_2 = 20 \text{ volt}$$

KCL in node A,

$$I_1 = 5 + I_2$$

$$-14(5 + I_2) - 8I_2 = 20$$

$$\Rightarrow 70 + 14I_2 - 8I_2 = 20$$

$$\Rightarrow 6I_2 = -50$$

$$\therefore I_2 = -8.33 \text{ A}$$

$$I_1 = 5 + (-8.33) = -3.33 \text{ A}$$

KVL in mesh 2,

~~$$\text{Solt}: I_2 = 14.2 \text{ A}$$~~

I_5 mesh এর সামুহিক নেট ত্বরণ ক্ষেত্রে circuit
open কর্তৃতে দ্রবণ

~~10V~~


KVL in mesh 1,

$$-10 + 20I_1 + 10(I_1 - I_2) = 0$$

$$\Rightarrow -20I_1 + 10I_1 - 10I_2 = 10$$

$$\Rightarrow 30I_1 - 10I_2 = 10$$

$$\therefore 3I_1 - I_2 = 1 \quad (1)$$

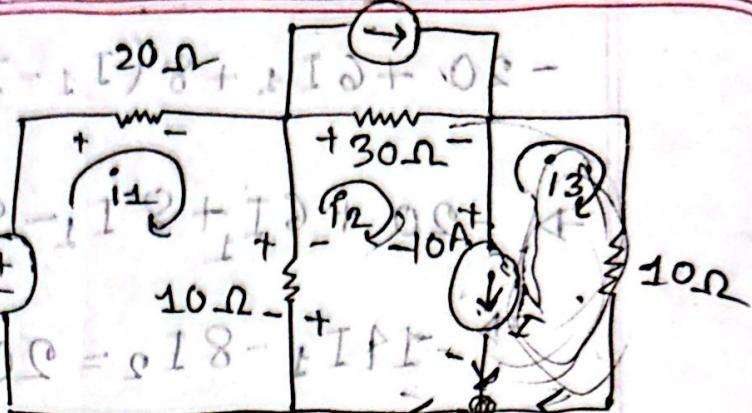

KVL in mesh 2 and 3

Supermesh,

$$10(I_2 - I_1) + 30(I_2 - 3) + 10(I_3) = 0$$

$$\Rightarrow 10I_2 - 10I_1 + 30I_2 - 90 + 10I_3 = 0$$

$$\Rightarrow 40I_2 - 10I_1 + 10I_3 = 90$$

$$\Rightarrow -I_1 + 4I_2 + I_3 = 9$$

KCL in node A, $I_3 + I = I_2$

$$\Rightarrow I_3 + (-10) = I_2$$

$$\Rightarrow I_3 = I_2 + 10$$

$$-I_1 + 4I_2 + (I_2 + 10) = 0$$

$$\Rightarrow -I_1 + 4I_2 + I_2 + 10 = 0$$

$$\Rightarrow 5I_2 + 10 = I_1$$

putting this value in eqn ①

$$3(5I_2 + 10) - I_2 = 1$$

$$\Rightarrow 15I_2 + 30 - I_2 = 1$$

$$\Rightarrow 14I_2 = 29$$

$$\therefore I_2 = \frac{29}{14} A$$

$$3I_1 + 2.07 = 1$$

$$\therefore I_1 = 1.023 A$$

$$\text{eqn ②, } -1.023 + (4 \times 2.07) + I_3 = 9$$

$$\Rightarrow I_3 = 7.783 A$$

$$+1 \quad -1 \quad 1 \\ (1) \quad (2) \quad (3)$$

$$\left[\begin{array}{ccc|c} + & - & + & 0 \\ 3 & -1 & 0 & 1 \\ -1 & 4 & 1 & -1 \\ 0 & 0 & 0 & 0 \end{array} \right]$$

$$3(-4 + 1) - (-1)(1 + 0) \\ = 12 + 3 + 1 \\ = 14$$

$$\Delta = 14$$


$$\Delta_1 = -4$$

$$\Delta_2 = 58$$

$$\Delta_3 = -39$$

$$I_1 = \frac{-4}{14} = -\frac{2}{7}$$

Lab 04

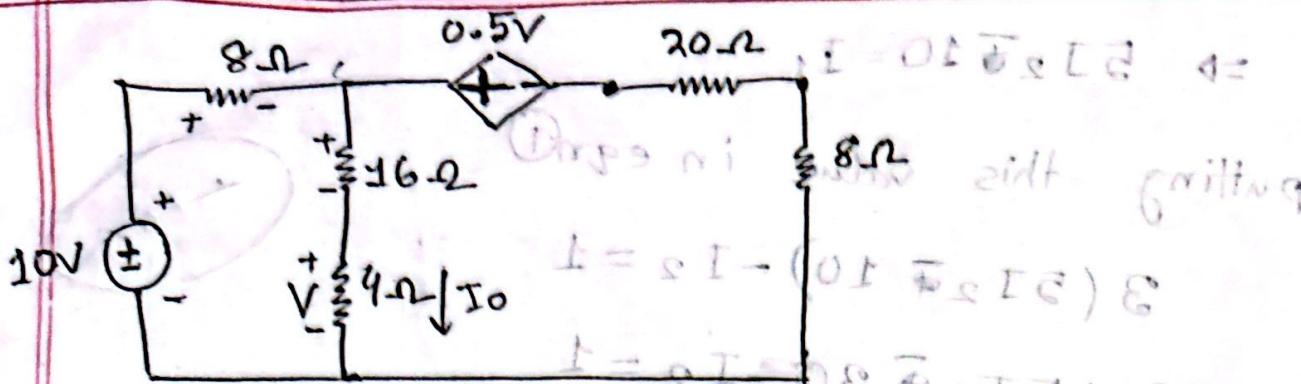

KVL in mesh 1,

$$-10 + 8I_1 + 16(I_1 - I_2) + 4(I_1 - I_2) = 0 \quad \therefore$$

$$\Rightarrow 8I_1 + 20I_1 - 20I_2 = 10$$

$$\Rightarrow 28I_1 - 20I_2 = 10 \quad \therefore \quad 14I_1 - 10I_2 = 5 \quad \text{---} \quad (1)$$

KVL in mesh 2,


$$4(I_2 - I_1) + 16(I_2 - I_1) + 0.5 + 20I_2 + 8I_2 = 0$$

$$\Rightarrow 4I_2 - 4I_1 + 16I_2 + 16I_1 + 28I_2 = -0.5 \quad \text{---} \quad (2)$$

$$\Rightarrow -20I_1 + 48I_2 = -0.5 \quad \text{---} \quad (2)$$

$$\Rightarrow 10I_1 + 24I_2 = \frac{0.5}{2} \quad \text{---} \quad (1)$$
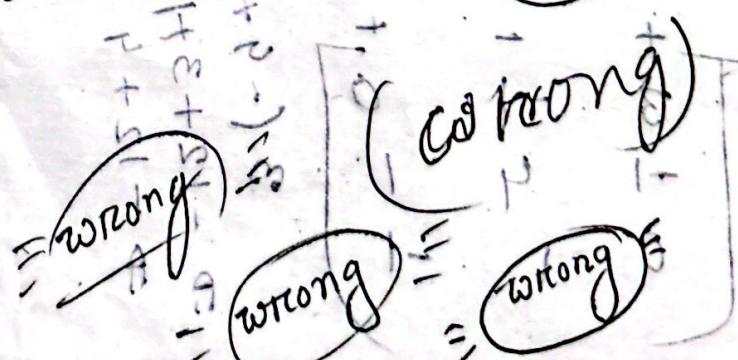
$$\Rightarrow 5I_1 + 12I_2 = 0.5 \quad \text{---} \quad (1)$$



$$8 + 20 = 28 \Omega$$

$$16 + 4 \Omega = 20 \Omega$$

$$20 \parallel 28 = 14.67 \Omega = R'$$

~~$$V_{ab} = E = 11.67 + 8$$~~

$$\therefore R_{eq} \Rightarrow 19.67 \Omega$$

$$I = \frac{V_s}{R_{eq}} = \frac{10}{19.67} = 0.5 A$$

~~$$V_{ab} = IR' = 11.67 \times 0.5 = 5.835 V$$~~

~~KVL Applying KVL in mesh 1,~~

~~$$4I_1 - 10I_2 = 5$$~~

Applying ~~KVL~~ in mesh 2, $0.5A(I_1 - I_2)$

~~$$4I_2 - 4I_1 + 16I_2 - 16I_1 + V_{ab} + 20I_2 + 8I_2 = 6$$~~

~~$$\Rightarrow -20I_1 + 48I_2 + (0.5 \times 5.835) = 0$$~~


~~$$\Rightarrow 20I_1 + 48I_2 = 2.9175$$~~

~~$$\Rightarrow 5I_1 + 12I_2 = 0.73$$~~

~~$$\Rightarrow -9I_1 + 23I_2 = 0$$~~

$$\begin{bmatrix} 14 & -10 \\ -5 & 23 \end{bmatrix} = 115 + 108 = 223$$

$$= -232$$

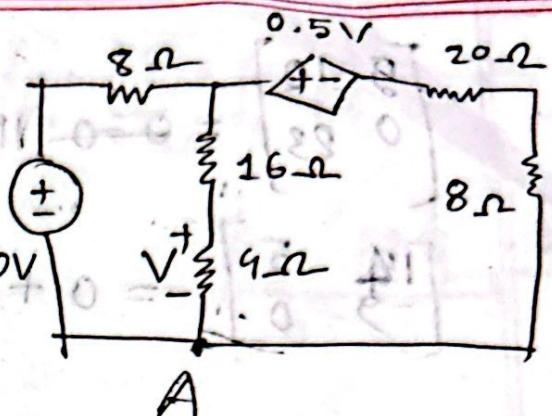

$$V_{ab} = 4I_0$$

$$= 4(I_1 - I_2)$$

KCL at node

$$I_1 = I_0 + I_2$$

$$\therefore I_0 = I_1 - I_2$$

EF

$$\begin{bmatrix} 5 & 10 \\ 0 & 23 \end{bmatrix} = 0 - 0 \quad 115$$

$$\rightarrow (-6V)$$

$$\begin{bmatrix} 14 & 5 \\ -5 & 0 \end{bmatrix} = 0 + 45 = 45$$

$$\therefore I_1 = \frac{\Delta_1}{\Delta} = \frac{0.5A}{0.49A} = 1.02 \quad I_2 = \frac{\Delta_2}{\Delta} = \frac{0.2A}{0.49A} = 0.41A$$

Phase

$$I_1 = \frac{10}{3} = 3.33 \text{ A}$$

$$I_2 = \frac{10 \times 6}{3+6} = 6.67 \text{ A}$$

$$I_3 = 1 \cdot 11 \cdot \frac{1}{(1+3)} = 11 \cdot \frac{1}{4} = 2.75$$

$\text{I}^8 + \text{S} \text{I}^8 \text{O}_2 + \text{H}_2\text{O}_2 + \text{H}_2\text{O} \rightarrow \text{I}^8 \text{I}^8 + \text{H}_2\text{O} + \text{H}_2\text{O}$

$$R_1 = \frac{R_b R_C}{R_A + R_b + R_C} + 1.8\Omega + 10\Omega = 4\Omega$$

34. 68. ~~FILE 8 = 181 + 100 4~~

~~ST 102 + 1781 - 10 - C.F.O = ST 102 + 1781 - 10~~

ST 62 + TP - 4

$$882 = 80F + 8H =$$

835 - 2 - 55

c.w
1510720°
(Quiz Ans)

MID
29/7/29


Quiz Ans

$$R_2 \parallel R_3 = 2 \Omega$$


$$R_5 || R_6 = 4\ \Omega$$

$$\textcircled{1+2+3+6=20}$$

۷۹

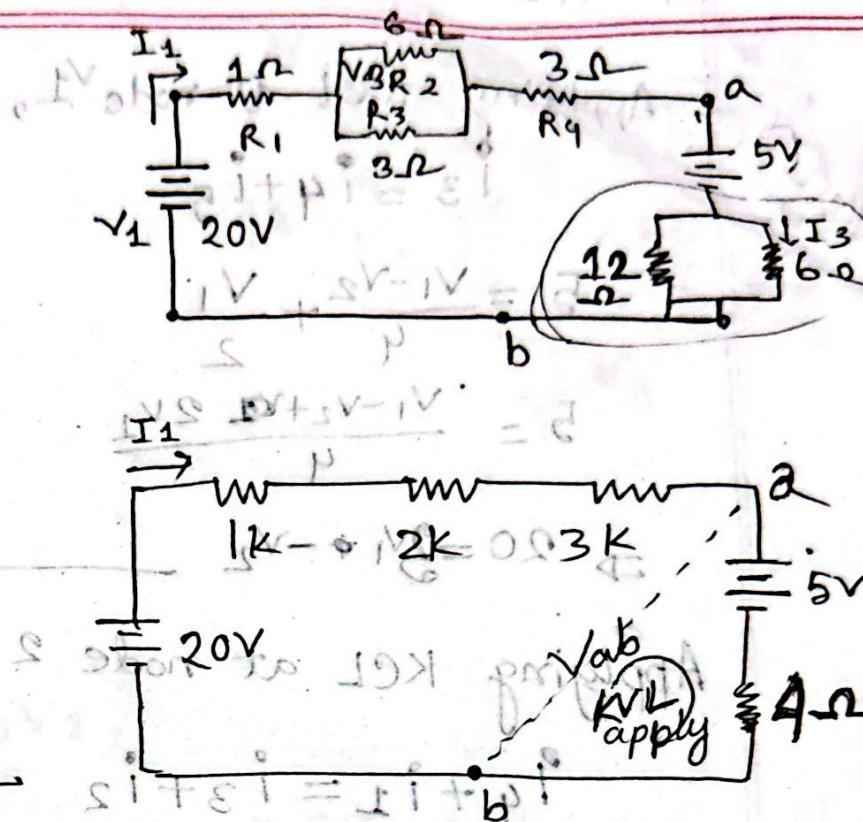

Nodal Analysis:

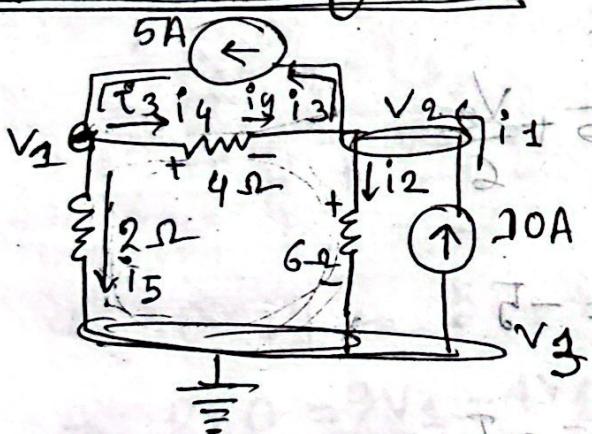

Applying Ohm's law,

$$i_1 = 10A$$

$$i_2 = \frac{V_2 - 0}{6} = \frac{V_2}{6}$$

$$i_3 = 5A$$

$$i_4 = \frac{V_1 - V_2}{R} = \frac{0.8}{1} = 0.8 \text{ A}$$

$$Q = V \cdot I = V \cdot \frac{q}{t} = \frac{Vq}{t} = \frac{V}{t} \cdot q = \frac{V}{t} \cdot C = \frac{V}{R} \cdot C$$

- i) node identification
 - ii) reference/ground node
 - iii) Flows of current

$$\begin{array}{l} \text{G.M.} \\ \frac{14,6}{2,3} \\ 4 \times 3 = 12 \end{array}$$

Applying KCL at node V_1 ,

$$\begin{aligned} i_3 &= i_4 + i_5 \\ 5 &= \frac{V_1 - V_2}{4} + \frac{V_1}{2} \\ 5 &= \frac{V_1 - V_2 + 2V_1}{4} \\ \Rightarrow 20 &= 3V_1 - V_2 \quad \text{--- (1)} \end{aligned}$$

Applying KCL at node V_2 ,

$$i_4 + i_1 = i_3 + i_2$$

$$\Rightarrow \frac{V_1 - V_2}{4} + i_{10} = 5 + \frac{V_2}{6}$$

$$\Rightarrow \frac{V_1 - V_2}{4} - \frac{V_2}{6} = -5$$

$$\Rightarrow \frac{3V_1 - 3V_2 - 2V_2}{12} = -5$$

$$\Rightarrow 3V_1 - 5V_2 = -60$$

$$(1) + (2) \Rightarrow 20 + 60 = 3V_1 - V_2 \Rightarrow 3V_1 + 5V_2$$

$$\Rightarrow 80 = 4V_2$$

$$\Rightarrow V_2 = \frac{80}{4} = 20V \quad (\text{Ans})$$

$$3V_1 = 20 + 20 = 40 \quad \therefore V_1 = 13.33V \quad (\text{Ans})$$

Determine node voltage :-

Applying KCL


$$i_1 = 14A$$

$$i_2 = \frac{V_1}{4}$$

$$i_3 = \frac{V_1 - V_2}{5}$$

$$i_4 = \frac{V_2}{5}$$

$$i_5 = 7$$

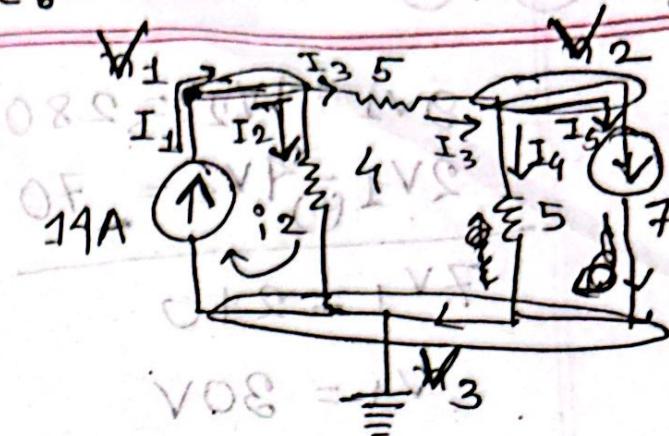

$$20 = 5V_2 - 1V$$

$$7 = 5V_2 - 4V_1$$

$$5V_2 - 4V_1 = 20$$

Applying KCL at V_1 ,

$$i_1 = i_2 + i_3$$

$$14 = \frac{V_1}{4} + \frac{V_1 - V_2}{5}$$

$$\Rightarrow 20 \times 14 = 5V_1 + 4V_1 - 4V_2$$

$$280 = 9V_1 - 4V_2$$

Applying KCL at V_2 ,

$$i_3 = i_4 + i_5$$

$$\Rightarrow \frac{V_1 - V_2}{5} = \frac{V_2}{5} + 7$$

$$V_1 - V_2 - V_2 = 35$$

$$\Rightarrow V_1 - 2V_2 = 35$$

$$2V_1 - 4V_2 = 70$$

$$AD = \epsilon i$$

$$\frac{\epsilon V - 1V}{P} = \epsilon i$$

$$(I)$$

$$\frac{0 - \epsilon V}{P} = \epsilon i$$

$$\frac{\epsilon V - \epsilon V}{P} = \epsilon i$$

$$(II)$$

i - ii

$$9V_1 - 4V_2 = 280$$

$$-2V_1 + 4V_2 = 70$$

$$7V_1 = 210$$

$$V_1 = 30V$$

$$V_1 - 2V_2 = 35$$

$$\Rightarrow -2V_2 = 5$$

$$\therefore V_2 = -2.5V$$


D Determine node voltages and i_x .

$$i_1 = 3A$$

$$i_2 = \frac{V_1 - V_3}{4}$$

$$i_3 = \frac{V_2 - V_3}{4}$$

$$i_4 = \frac{V_2 - V_1}{8}$$

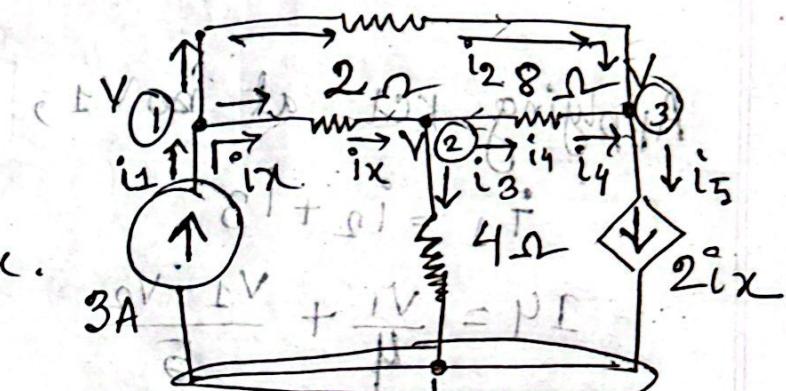

$$i_5 = 2ix = 2 \frac{V_1 - V_2}{2} = V_1 - V_2$$

$$i_x = \frac{V_1 - V_2}{2}$$

Apply KCL in node 1,

$$i_1 = i_2 + i_x \quad \text{or } 3 = 2V_1 - 2V_2 + \frac{V_1 - V_2}{2}$$

$$3 = \frac{V_1 - V_3}{4} + \frac{V_1 - V_2}{2} \quad \text{or } 12 = 2V_1 - 2V_2 + \frac{5V_1 - 4V_2 - V_3}{4} \quad \text{or } 12 = 2V_1 - 2V_2 + 2V_1 - 2V_2 - V_3 \quad \text{or } 12 = 4V_1 - 4V_2 - V_3 \quad \text{or } 12 = 4(V_1 - V_2) - V_3 \quad \text{or } 12 = 4(30 - (-2.5)) - V_3 \quad \text{or } 12 = 130 - V_3 \quad \text{or } V_3 = 118V$$

$$12 = 2V_1 - 2V_2 + 2V_1 - 2V_2 - V_3$$

Applying KCL in V_2 ,

$$i_x = i_3 + i_4$$

$$\Rightarrow \frac{V_1 - V_2}{2} = \frac{V_2}{4} - \frac{V_2 - V_3}{8}$$

$$\Rightarrow 8V_1 - 8V_2 = 2V_2 - V_2 + V_3$$

$$\Rightarrow -8V_1 - 9V_2 - V_3 = 0$$

$$-8V_1 - 7V_2 + V_3 = 0 \quad \text{--- (II)}$$

Applying KCL at node 3,

$$i_2 + i_4 = i_5$$

$$\Rightarrow \frac{V_1 - V_3}{4} + \frac{V_2 - V_3}{8} = V_1 - V_2$$

$$2V_1 - 3V_2 + V_3 = 0 \quad \text{--- (III)}$$

$$\Delta = \begin{bmatrix} 0 & -2 & 1 \\ 3 & -7 & 1 \\ 4 & -3 & 1 \end{bmatrix} = 3(-7+3) + 2(4-2) - 1(-12+14) = -10$$

$$\Delta_1 = \begin{bmatrix} 12 & -2 & -1 \\ 0 & -7 & 1 \\ 0 & -3 & 1 \end{bmatrix} = 12(-7+3) = -48$$

$$\Delta_2 = \begin{bmatrix} 3 & 12 & -1 \\ 9 & 0 & 1 \\ 2 & 0 & 1 \end{bmatrix} = 3(0-0) + 12(4-2) - 1(0-0) = -24$$

$$\Delta_3 = \begin{bmatrix} 3 & -2 & 12 \\ 4 & -7 & 0 \\ 2 & -3 & 0 \end{bmatrix} = 12(-12+14) = 24$$

$V_S \rightarrow$ short circuit
 $I_S \rightarrow$ open "



$$V_1 = \frac{-48}{-10} = 4.8 V$$

$$V_2 = \frac{-24}{-10} = 2.4 V$$

$$V_3 = \frac{24}{-10} = -2.4 V$$


$$i_x = \frac{V_1 - V_2}{2} = 1.2 A$$

Q

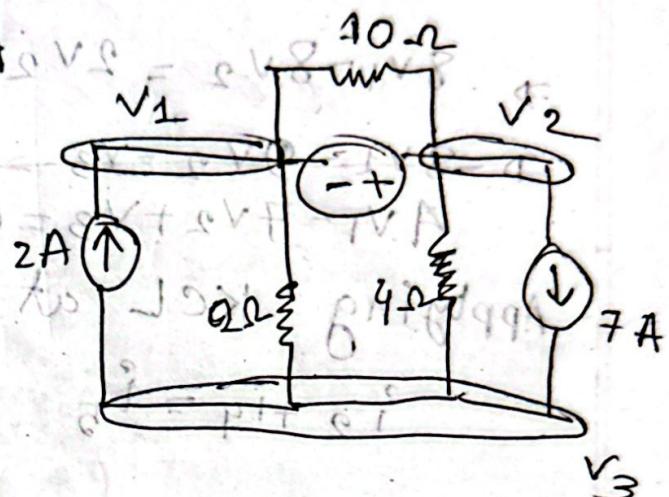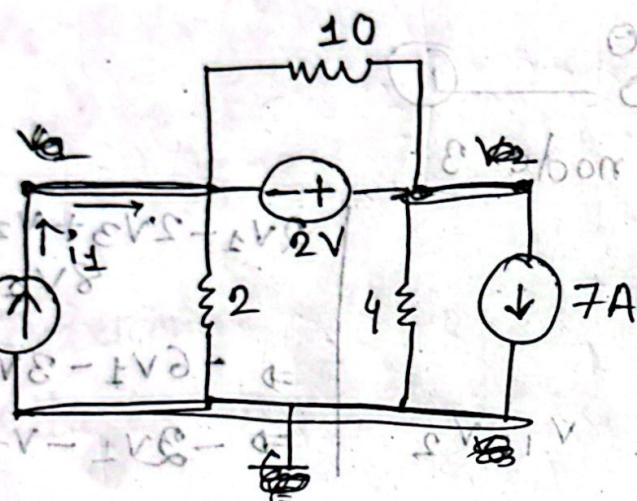

Step Solution

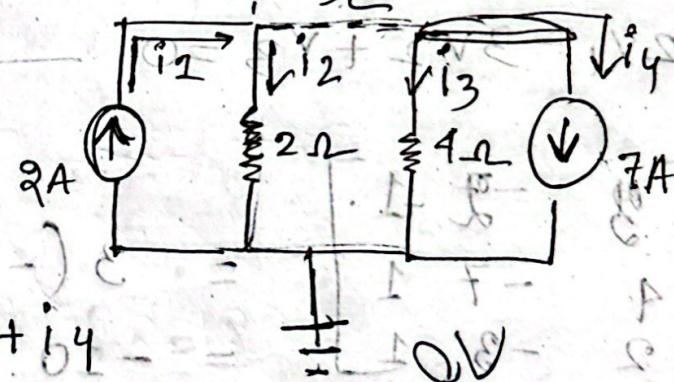Applying KCL in Super node $\Rightarrow i_1 = i_2 + i_3 + i_4$



$$2 = i_2 + i_3 + 7$$

$$\Rightarrow \frac{i_1}{2} + \frac{V_2}{4} = -5$$

$$\begin{bmatrix} 1 & S & S \\ 1 & F & 0 \\ 1 & S & 0 \end{bmatrix} = 1 A$$

$$(0-0) \leftarrow (2V_1 + V_2) = -20 \quad (1) \quad [1 \quad 0 \quad 0] = 1 A$$

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} = 1 A$$

$$PS = (S^E + S^F -) S^F = \begin{bmatrix} S^E & S^F & S^F \\ 0 & S^F & S^F \\ 0 & 0 & S^F \end{bmatrix} = S^A$$

Applying KVL in loop 1,

$$-V_1 - 2 + V_2 = 0$$

$$\Rightarrow -V_1 + V_2 - 2 = 0 \quad (1)$$

$\text{eq } ① - \text{eq } ②$,

$$2V_1 + V_2 = -20$$

$$(-) -V_1 + V_2 = -2$$

$$\cancel{V_1 + 2V_2 = -20}$$

$$3V_1 = -22$$

$$\therefore V_1 = -\frac{22}{3} = -7.33V$$

Putting $V_1 = -7.33V$ in eq (1)

$$-(-7.33) + V_2 = 2$$

$$\Rightarrow V_2 = 2 - 7.33 = -5.33V \quad (\text{Ans})$$

* * *

২টি Node এর মাঝের V_s হিসেবে Super node

* * *



২টি mesh এর মাঝের I_s হিসেবে Super mesh

$$\frac{e \times 2 - s}{e + s} = I$$

19/08/29
Revision

Determine $I_1, I_2, I_3,$

I_4 & V_1, V_2

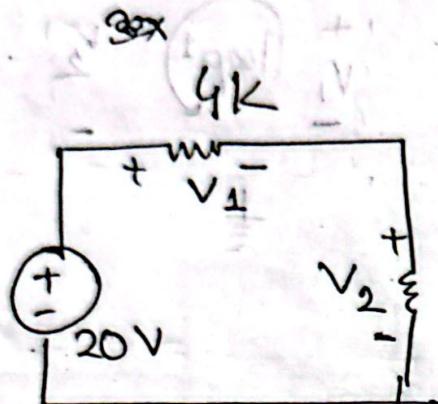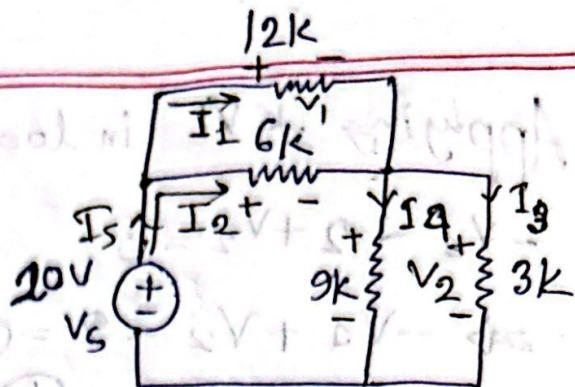

$$V_1 = \frac{20 \times 4}{4 + 2.25} = 12.8V$$

$$V_2 = \frac{20 \times 2.25}{4 + 2.25} = 7.2V$$

$$R_{eq} = 6.25k\Omega = \frac{20}{6.25} = 3.2A$$

$$I = \frac{20}{6.25} = 3.2A$$

$$(mA) V_{EE} : \frac{3.2 \times 6}{12+6} = 6.67mA$$



$$\checkmark I_1 = \frac{3.2 \times 6}{12+6} = 1.067A$$

$$\checkmark I_2 = \frac{3.2 \times 12}{12+6} = 2.13A$$

$$I_3 = \frac{3.2 \times 3}{3+9} = 0.8A$$

$$I_4 = \frac{3.2 \times 9}{3+9} = 2.4A$$

Determine, V_1, V_2, V_3 & I_1, I_2, I_3

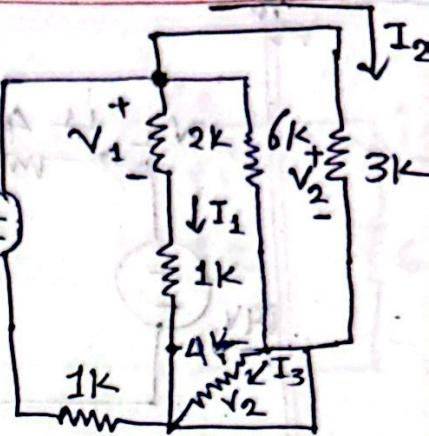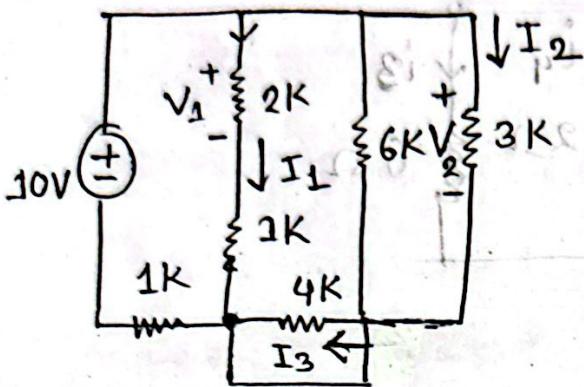


$$R_{eq} = 1 + ((2+1) \parallel (3 \parallel 2))$$

$$= 1 + (3 \parallel 2)$$


$$= 1 + 1 \cdot 2$$

$$= 2 \cdot 2 - 2$$
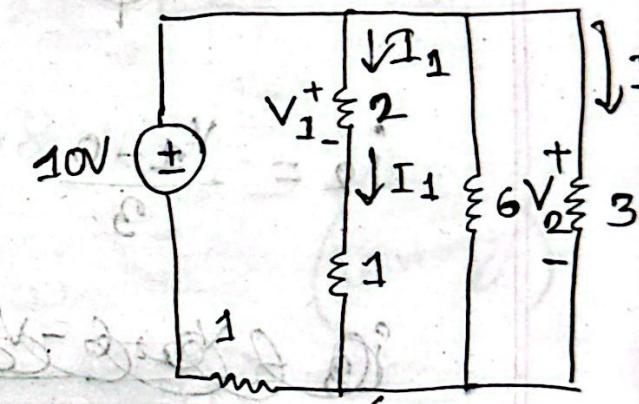
$$I_S = \frac{V_S}{R_{eq}} = \frac{10}{2 \cdot 2} = 4.54 \text{ A}$$



$$V_1 = I_1 \times 2 = 3.6 \text{ V}$$

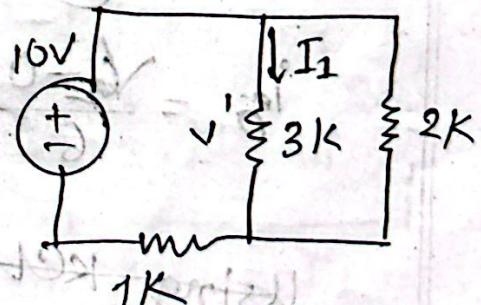


$$I_1 = \frac{4.54 \times 2}{3+2} = 1.816 \text{ A}$$

$$I_2 = 2.724 \text{ A} = \frac{4.54 \times 3}{6+}$$

$$V' = I_1 \times 3 = 5.4$$

10K hour

Determine V_1, V_2, V_3 & I_1, I_2, I_3

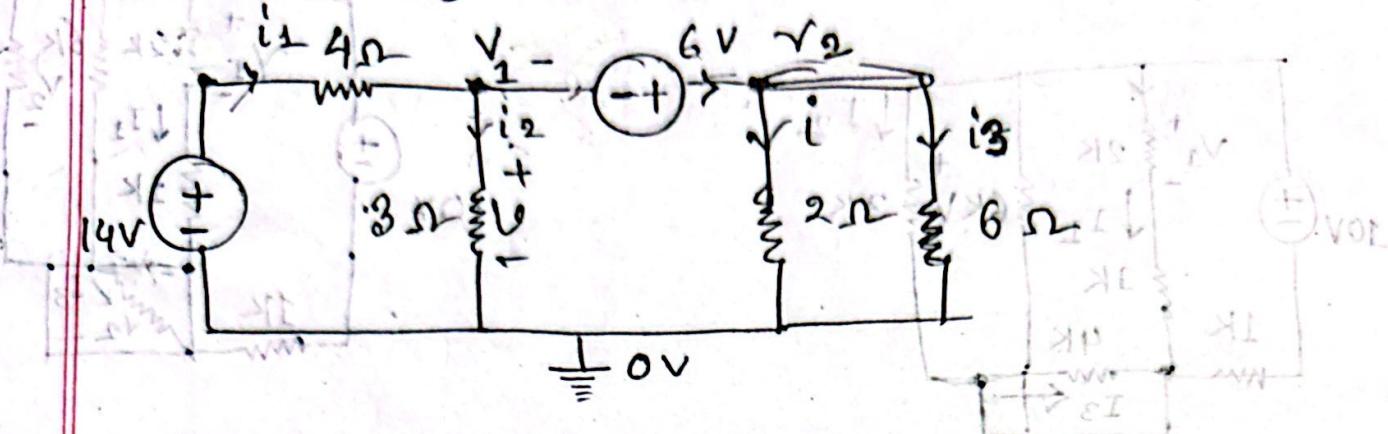

$$i_1 = \frac{V_1 - 0}{4\Omega} = \frac{14 - V_1}{4\Omega}$$

$$i_2 = \frac{V_1 - 0}{3\Omega} = \frac{V_1}{3\Omega}$$

~~$i_3 = \frac{V_2 - V_3}{2\Omega}$~~

$$i = i_3 = \frac{V_2 - V_3}{2\Omega}$$

$$i_3 = \frac{V_2 - 0}{6\Omega} = \frac{V_2}{6\Omega}$$

Using KCL at node V_3

$$V_3 = C \times I = V$$


$$\frac{V_2 - V_3}{2\Omega} = C \times I = V$$

3.13, 6, 2
1, 2, 2

KCL at supernode,

$$i_1 = i_2 + i_3 + i$$
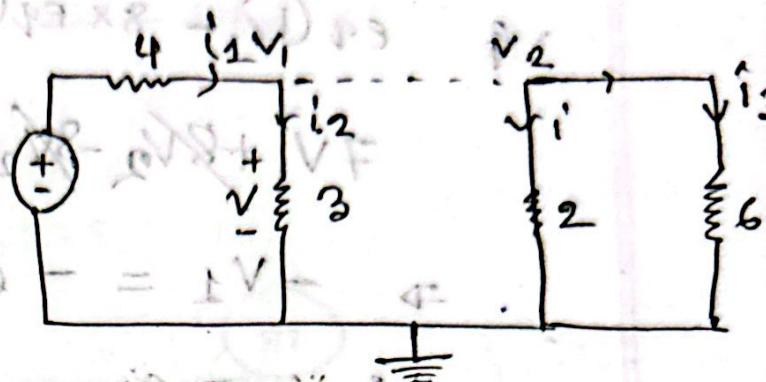
$$\Rightarrow \frac{14 - V_1}{4} = \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2}{2}$$



$$\Rightarrow \frac{14 - V_1}{4} = \frac{4V_1 + 2V_2 + 6V_2}{6}$$

$$\Rightarrow 168 - 12V_1 = 16V_1 + 8V_2 + 24V_2$$

$$\Rightarrow -28V_1 - 32V_2 = -168$$

$$\Rightarrow 14V_1 + 16V_2 = 84$$

(wrong)

$$\Rightarrow 7V_1 + 8V_2 = 42 \quad (1)$$


KVL in loop 1,

$$= V_1 - 6 + V_2 = 0$$

$$\Rightarrow -3I = 0$$

$$-V_1 - 6 + V_2 = 0$$

$$\Rightarrow V_2 - V_1 = 6$$

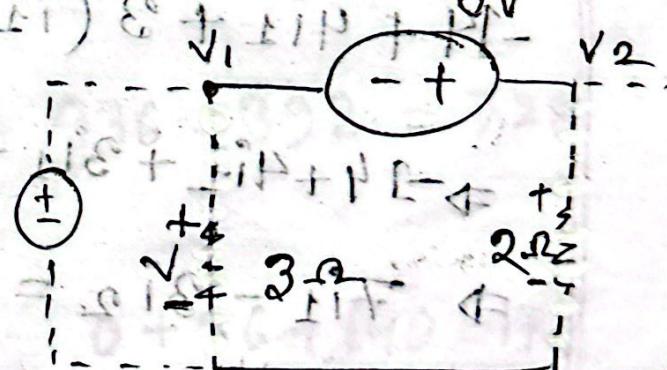


(R) \rightarrow (KVL)
current in +
out - } mesh analysis

$\Rightarrow \text{eq } ① - 8 \times \text{eq } ⑪$, add both eq to 3.94

$$7V_1 + 8V_2 - 8V_2 - 8V_1 = 42 - 48 \quad \text{or}$$

$$\Rightarrow -V_1 = -6 \quad \frac{V}{4} + \frac{V}{3} + \frac{1V}{8} = \frac{V - 12}{4}$$
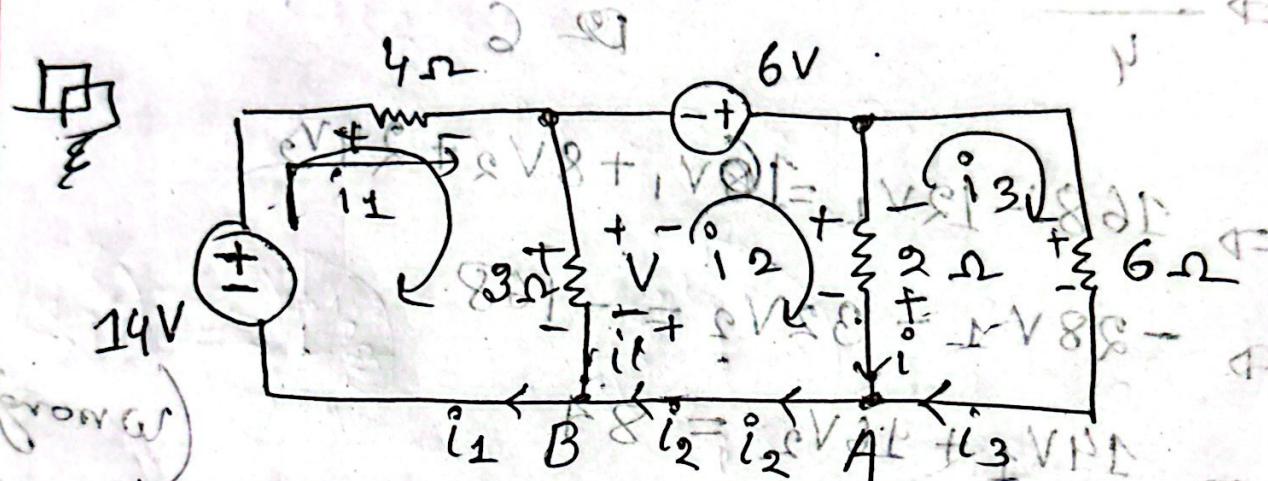
$$\therefore V_1 = 6 \quad \text{or} \quad V_1 = \frac{V - 12}{4}$$



KVL in mesh 1,

$$-14 + 4i_1 + 3(i_1 - i_2) = 0$$

$$\Rightarrow -14 + 4i_1 + 3i_1 - 3i_2 = 0$$

$$\Rightarrow 7i_1 - 3i_2 = 14$$

KVL in mesh 2,

$$+ 3(i_2 - i_1) - 6 - 2(i_2 - i_3) = 0$$

$$\Rightarrow 3i_2 - 3i_1 + 2i_2 - 2i_3 = 6$$

$$\Rightarrow -3i_1 + 5i_2 + 2i_3 = 6 \quad \text{--- (1)}$$

KVL in mesh 3,

$$2i_3 - 2i_1 + 6i_3 - \cancel{2i_2} = 0$$

$$\Rightarrow 8i_3 - 2i_1 = 0 \quad \text{--- (2)}$$

$$\begin{bmatrix} 7 & -3 & 0 \\ -3 & 5 & -2 \\ -2 & 0 & 8 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 14 \\ 6 \\ 0 \end{bmatrix}$$

$$\Delta = 280 - 84 = 196$$

$$\Delta_1 = \begin{bmatrix} 14 & -3 & 0 \\ 6 & 5 & -2 \\ 0 & 0 & 8 \end{bmatrix} = 560 + 144 = 704$$

$$\Delta_2 = \begin{bmatrix} 7 & 14 & 0 \\ -3 & 6 & -2 \\ -2 & 0 & 8 \end{bmatrix} = 336 + 392 = 728$$

$$\Delta_3 = \begin{bmatrix} 7 & -3 & 14 \\ -3 & 5 & -6 \\ -2 & 0 & 80 \end{bmatrix} = 0 + 36 + 140 = 176$$

$I_1 = 3.6 A$	$I_2 = 3.7 A$	$I_3 = 0.89 A$
---------------	---------------	----------------

KCL in node A,

$$i_2 = i + i_3$$

$$i = i_2 - i_3 = 2.8A + 1.5 - 1.5$$

③ Apply KCL at node B,

$$i' + i_2 = i_1$$
$$\Rightarrow i' = i_1 - i_2 = -3.6 - 3.7 = -0.13A$$



8:00



Clock

Wall mounted Watch

Clock Wall Clock

$$OF = PHI + ODE$$

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} = 1A$$

$$SCE = SCE + OEE = \begin{bmatrix} 0 & PHI & F \\ S & 0 & E \\ 0 & 0 & S \end{bmatrix} = 2A$$

$$OFL = OPI + OEE + 0 = \begin{bmatrix} PHI & E & F \\ 0 & E & E \\ 0 & 0 & S \end{bmatrix} = 2A$$



$$AE8.0 = CT \quad | AF.E = CT \quad | AD.E = CT |$$

Final

25/08/2021

Superposition (Theorem)

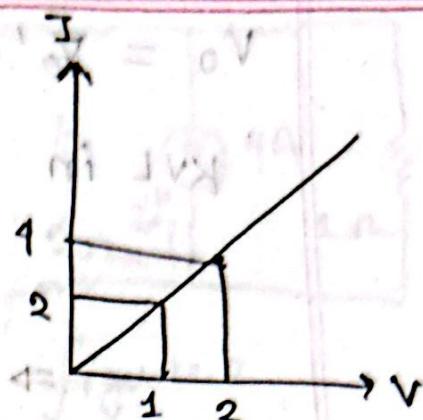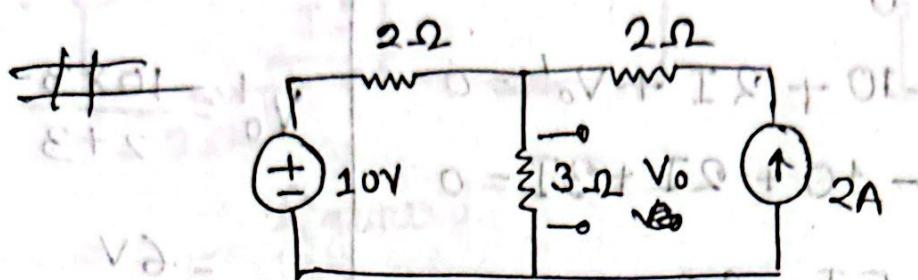(Only Applicable for) ~~Non~~ Linear circuit



Determine V_o voltage: (using superposition)

প্রতিবায়ুর একটি source নিয়ে কাজ করবে,

$$V_s \rightarrow \left\{ \begin{array}{l} \text{scircuit} \\ \text{source} \end{array} \right.$$

$$I_s \rightarrow \left\{ \begin{array}{l} \text{scircuit} \\ \text{source} \end{array} \right.$$

Step 1 :
(ক্ষেত্র)

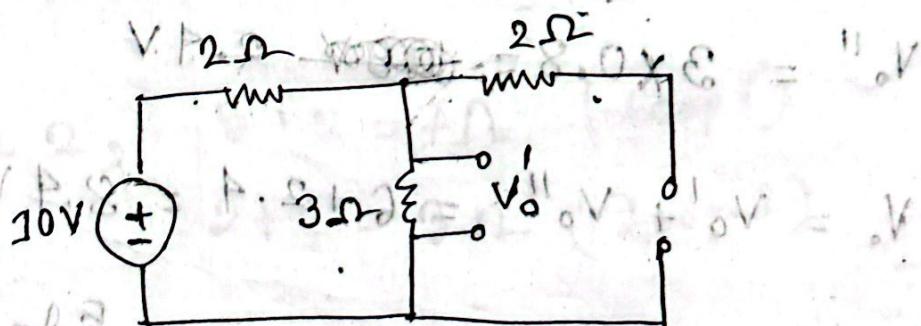


Figure 11. ~~arbitrary~~ #

Step 2 :

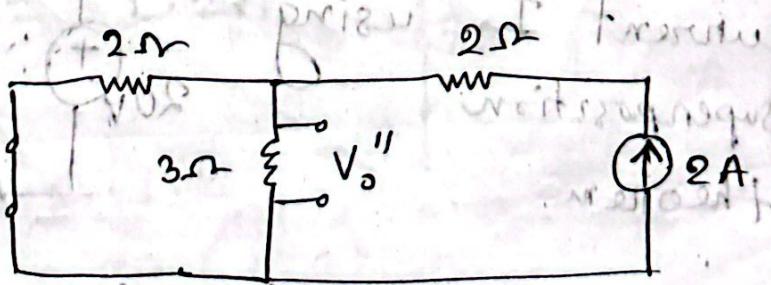


Figure 9

Page 180/85

(initial) voltage source

$$V_o = V_o' + V_o''$$

KVL in figure 1,

$$-10 + 2I + V_o' = 0$$

$$\Rightarrow -10 + 2I + 3I = 0$$

$$\Rightarrow 5I = 10$$

$$\therefore I = 2A$$

$$V_o' = 3 \times 2 = 6V$$


CDR in figure 2,

$$I_{o''} = \frac{2 \times 2}{2+3} = 0.8A$$

$$V_o'' = 3 \times 0.8 = 2.4V$$

$$\therefore V_o = V_o' + V_o'' = 6 + 2.4 = 8.4V \quad (\text{Ans})$$

Determine the current I_o using superposition theorem

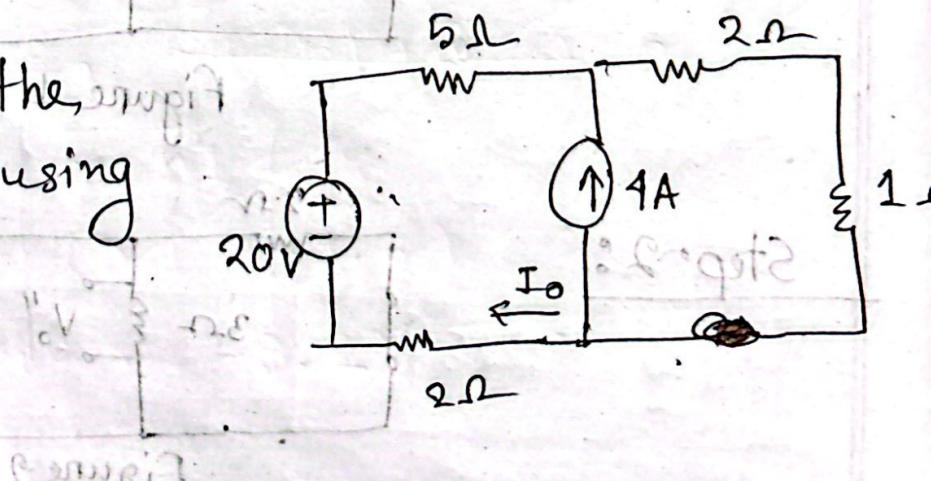

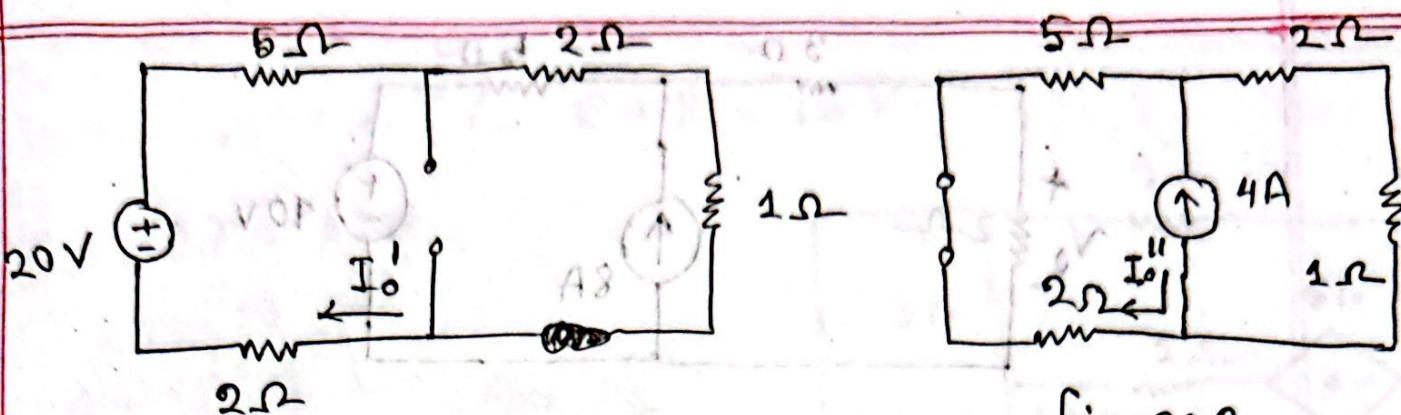


figure 1

figure 2

$$\text{At } A_1, I_o = \frac{V_o}{R} = \frac{20}{10} = 2 \text{ A}$$

$$\text{At } A_2, V' = \frac{20 \times 2}{10} = 4 \text{ V}$$

$$I_o' = \frac{V'}{R} = \frac{4}{2} = 2 \text{ A}$$

in figure 2,


$$5 + 2 = 7 \Omega \text{ (loop 1)}$$

$$2 + 1 = 3 \Omega \text{ (loop 2)}$$

$$I_o'' = \frac{-4 \times 3}{7+3} = -1.2 \text{ A}$$

$$I_o = I_o' + I_o'' = 2 - 1.2$$

$$I_o = 0.8 \text{ A (Ans)}$$

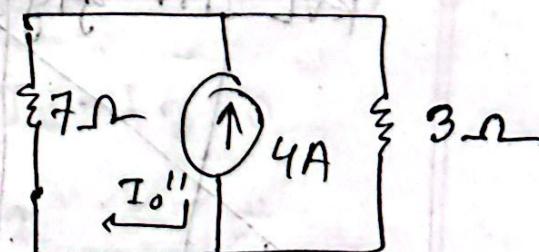

using superposition theorem, find V_o

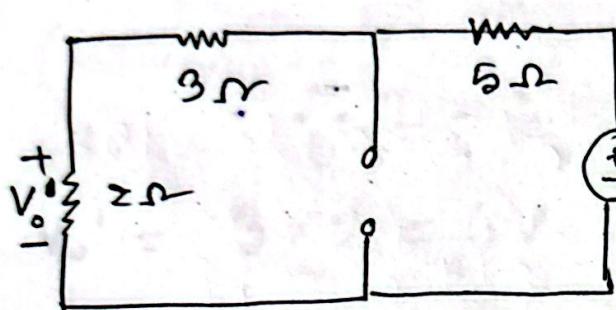
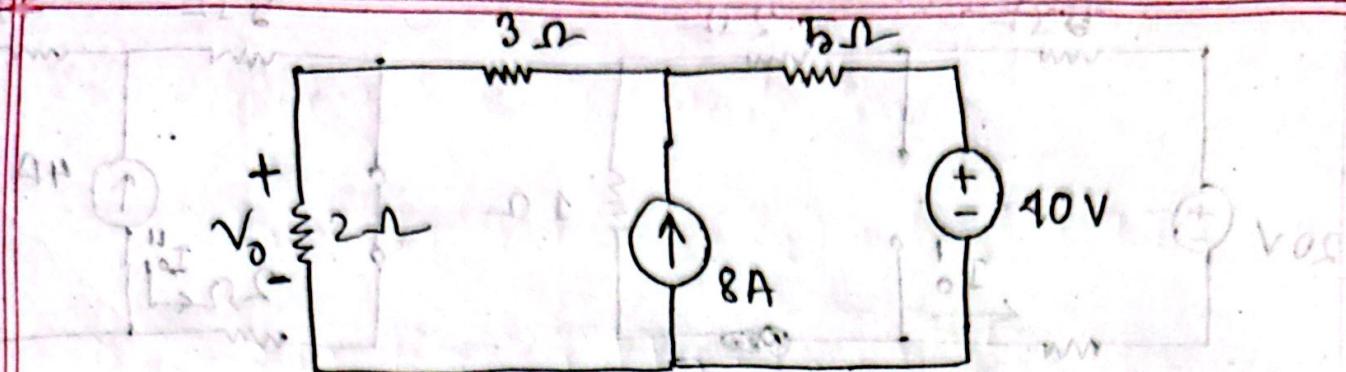


figure 1

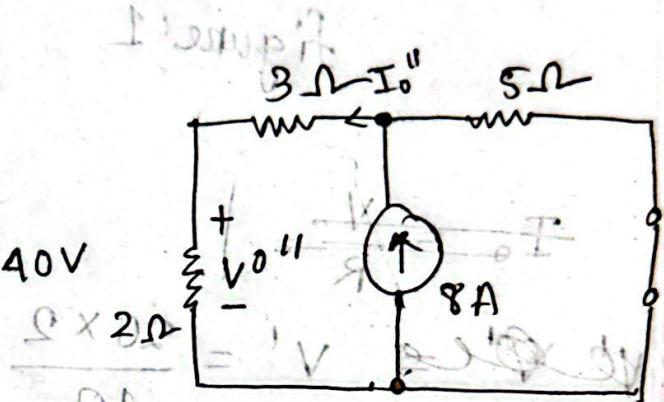


fig 2

@ VDR in fig 1,

$$V_o' = \frac{40 \times 2}{(2 + 5 + 3 + 2)}$$

$$(8V) - 2I = 2 + 3 + I$$

$$A_S = \frac{V}{I} = \frac{8}{2+5} \\ I_0' = \frac{8}{5+5} \\ = 9A$$

$$V_o'' = 2I = 4 \times 2 = 8V$$

KVL in fig 2,

$$2I + 3I + 8 = 0$$

$$\Rightarrow 5I = -8 \\ I = -1.6A$$

$$V_o'' = 2 \times -1.6 = -3.2V$$

$$V_o = V_o' + V_o'' \quad \varepsilon = 8 + 8 = 16V$$

$$\delta = \varepsilon I + \frac{3}{2} \cdot 2 = 8I + 8$$

Find I_o using

① Superposition theorem.

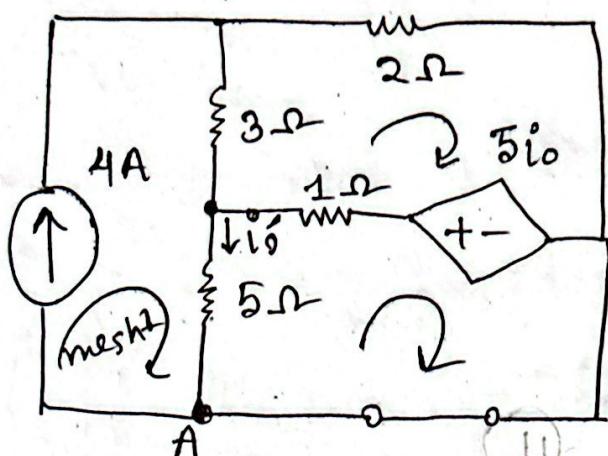
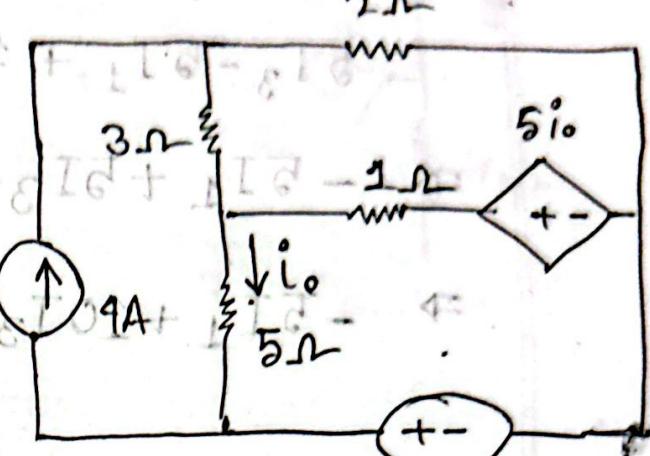


figure 1

KVL in mesh 1,

$$I_1 = 4A$$

KVL in mesh 2,

$$3(I_2 - I_1) + 2(I_2) - 5i_o + 1(I_2 - I_3) = 0$$

$$\Rightarrow 3I_2 - 12 + 2I_2 - 5i_o + I_2 - I_3 = 0$$

$$\Rightarrow 6I_2 - I_3 - 5(4 - I_3) = 12$$

$$\Rightarrow 6I_2 + 4I_3 = 32$$

111

Applying KVL in mesh 3, $V_1 + V_2 = 0V$

$$5I_3 - 5I_1 + 1(I_3 - I_2) + 5i_0' + 4I_3 = 0$$

~~$$\Rightarrow -5I_1 + 5I_3 + 1I_3 - I_2 + 5i_0' + 4I_3 = 0.$$~~


~~$$\Rightarrow -5I_1 + 10I_3 - I_2 + 5i_0' = 0 \quad \text{eqn 1}$$~~

Applying KCL at node A,

$$i_1 = i_0' + i_3$$

~~$$\Rightarrow 4 = i_0' + i_3$$~~
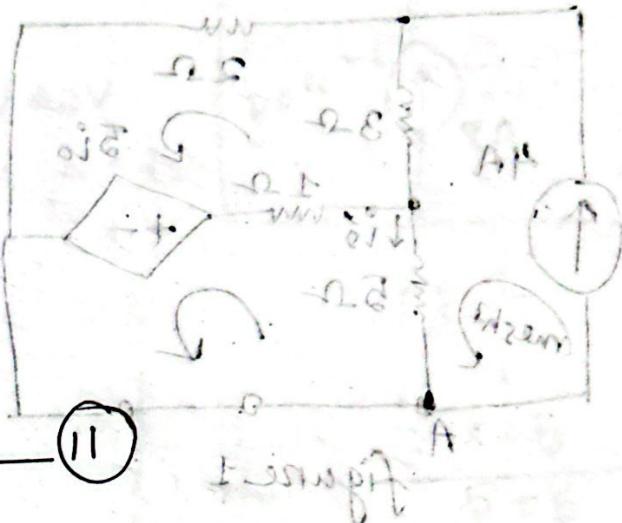
$$\therefore i_0' = 4 - i_3 \quad \text{--- eqn 11}$$



~~$$-5(4) - (5 \times 4) + 10I_3 - I_2 + 5(4 - I_3) = 0$$~~

~~$$\Rightarrow -20 + 10I_3 - I_2 + 20 - 5I_3 = 0 \quad \text{KVL}$$~~

~~$$\Rightarrow 5I_3 - I_2 = 0 \quad \text{--- eqn 12}$$~~

~~$$0 = 4I - 2I + 10I_3 - 5I_3 \quad \text{--- eqn 12}$$~~

$$I_3 = 0.95 \quad \text{--- eqn 12}$$

i_3 value in eqn 11, $i_0' = 4 - 0.95 = 3.05A$


$$i_1 = 3.05 + 0.95 = 4A$$

KVL in mesh 1,

$$3(i_a) + 2(i_a) - 5i_o'' \\ + 1(i_a - i_b) = 0$$

$$\Rightarrow 3i_a + 2i_a - 5i_o'' \\ + i_a - i_b = 0$$
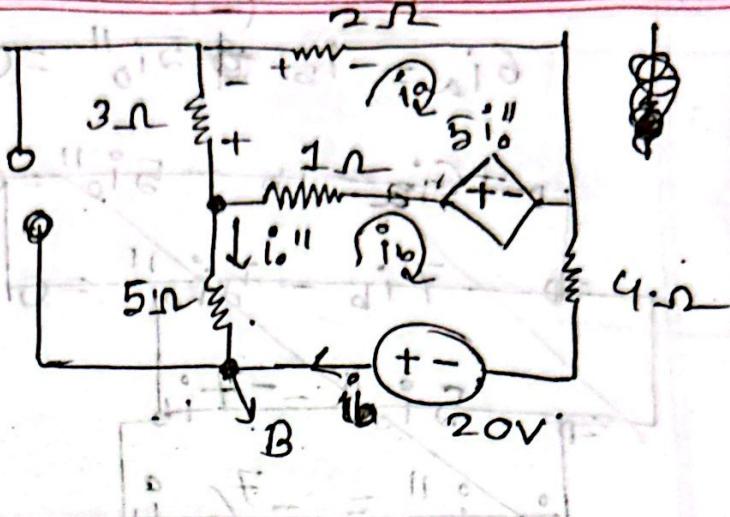
$$\Rightarrow 6i_a - i_b - 5i_o'' = 0 \quad \text{--- (1)}$$



KVL in mesh 2,

$$-20 + 5i_b + 1(i_b - i_a) + 5i_o'' + 4i_b = 0$$

$$\Rightarrow 5i_b + i_b - i_a + 5i_o'' + 4i_b = 20 \quad \text{--- (2)}$$

$$\Rightarrow (20 - i_a + 5i_o'') = 20 \quad \text{--- (2)}$$

$$\begin{aligned} & \text{--- (1) + (2)} \Rightarrow 6i_a - i_b - 5i_o'' + 10i_b - i_a + 5i_o'' = 20 \\ & \Rightarrow 5i_a + 9i_b = 20 \\ & \Rightarrow 5i_a = 20 - 9i_b \end{aligned}$$

Applying KCL at
node B,
 $i_o'' + i_b = 0$,
 $\Rightarrow i_o'' = -i_b$

$$6i_a - i_b - 5i_o'' = 0 \rightarrow$$

$$6i_a - i_b - 5(-i_b) = 0$$

$$\Rightarrow 6i_a - i_b + 5i_b = 0$$

$$\Rightarrow 6i_a + 4i_b = 0$$

$$10i_b - i_a + 5i_o'' = 20$$

$$\Rightarrow 10i_b - i_a + 5(-i_b) = 20$$


$$\Rightarrow 5i_b - i_a = 20$$

$$i_o'' = i_o' + i_o'' = 3.05 + (-3.53)$$


$$= -0.48 \text{ (Ans)}$$

Source Transformation


Use source transformation to find V_o .

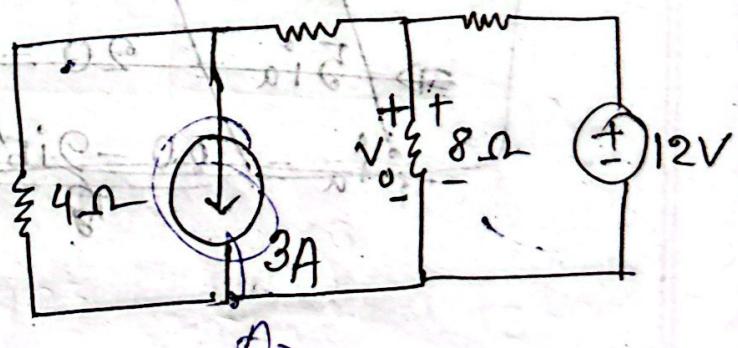


Theory:

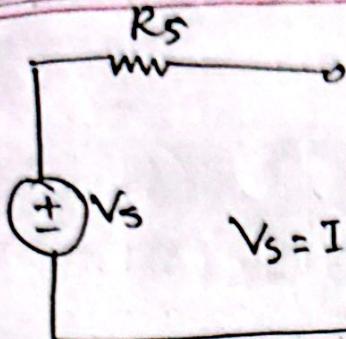
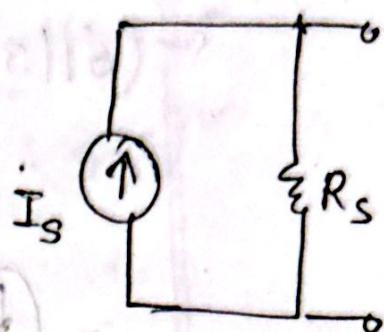
$$V_s = I_s R_s \Rightarrow I_s = \frac{V_s}{R_s} \Rightarrow$$





Ans:

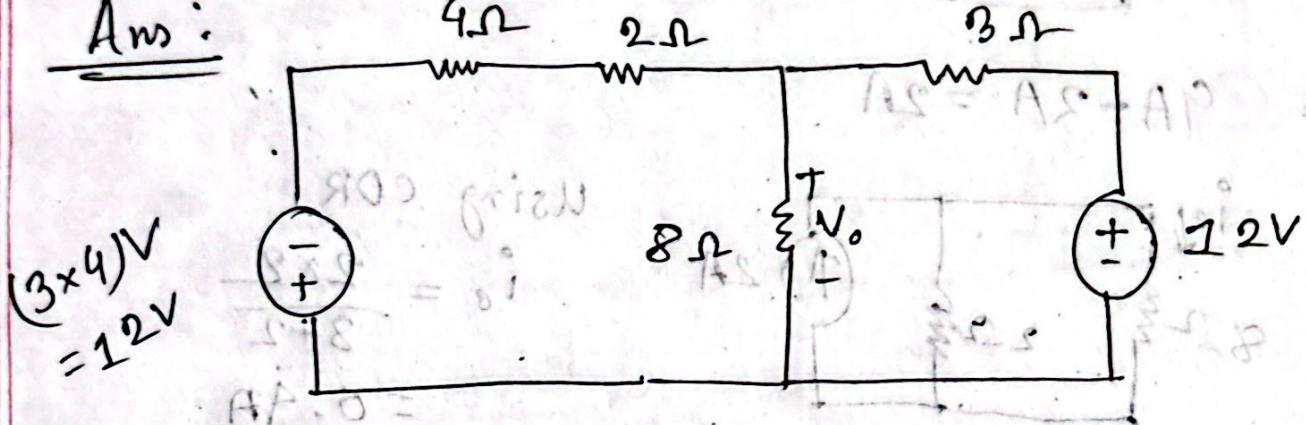


$$(3 \times 4)V = 12V$$

$$(1+2) = 6\Omega$$

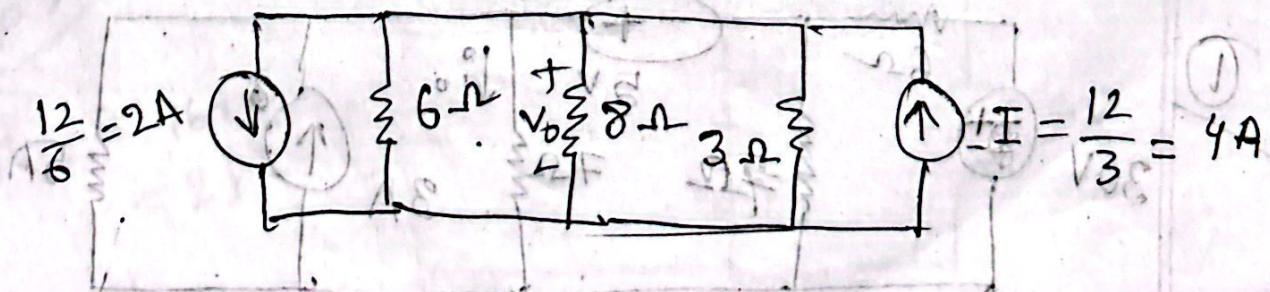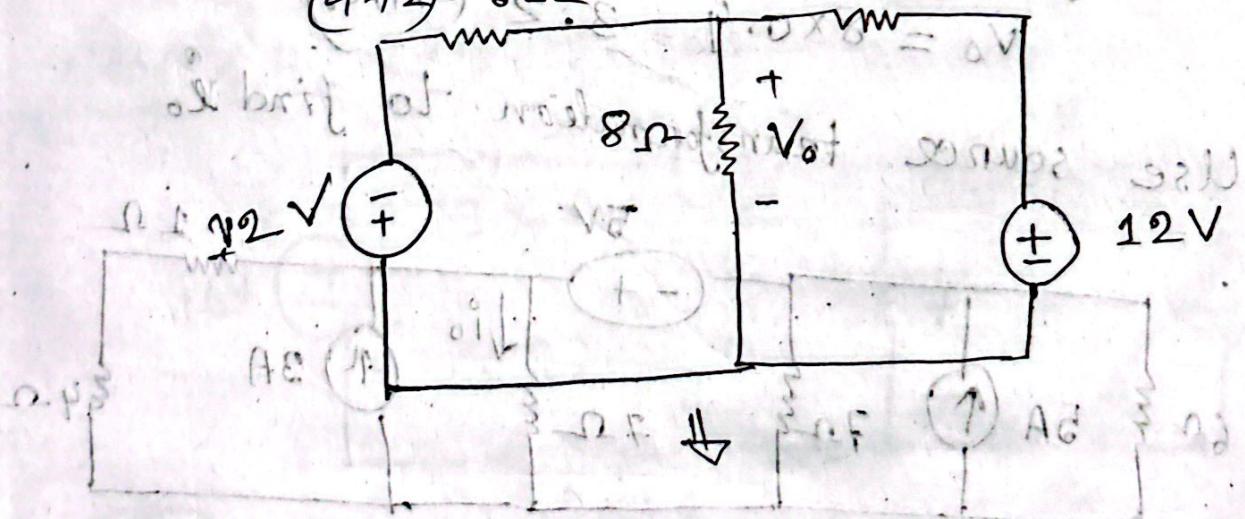


$$\frac{12}{16} = 2A$$

$$\frac{6+3}{6+3} = 2\Omega$$

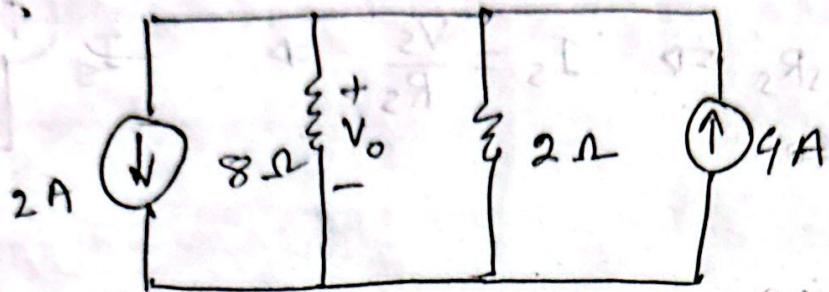

$$9A - 2A = 2A$$

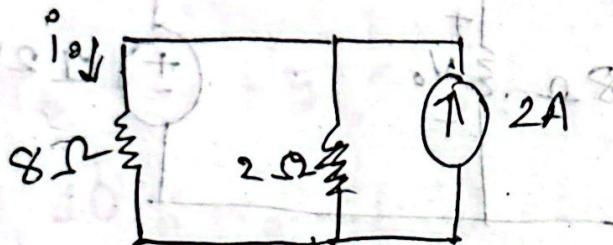


using CDR,

$$i_o = \frac{2 \times 2}{8+2} = 0.4A$$


using Ohm's Law,

$$V_o = 8 \times 0.4 = 3.2 \text{ (Ans)}$$

Use source transformation to find i_o

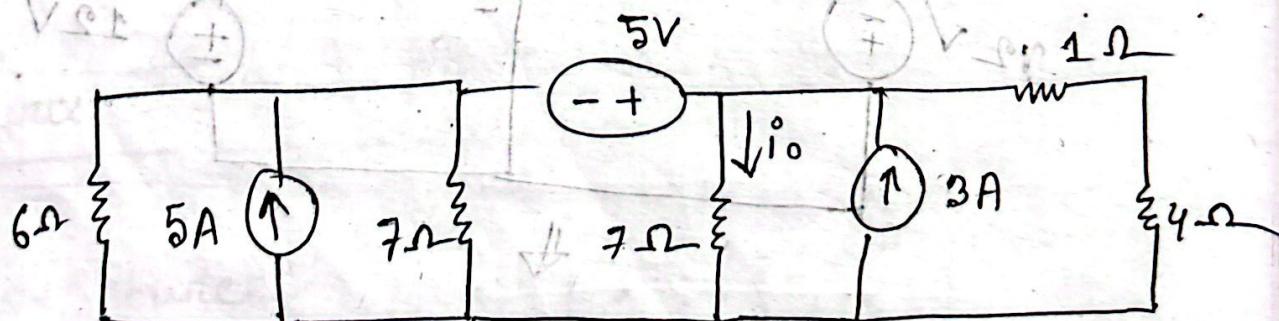


Step ①

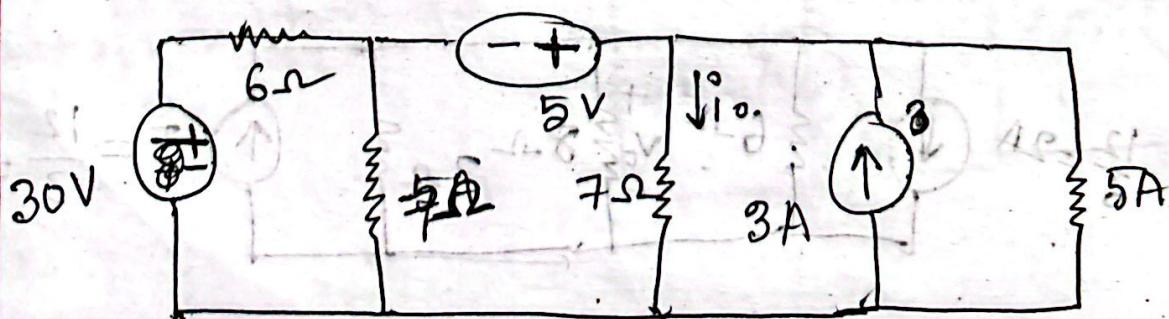


V_S = Series
 I_S = Parallel

Step 2

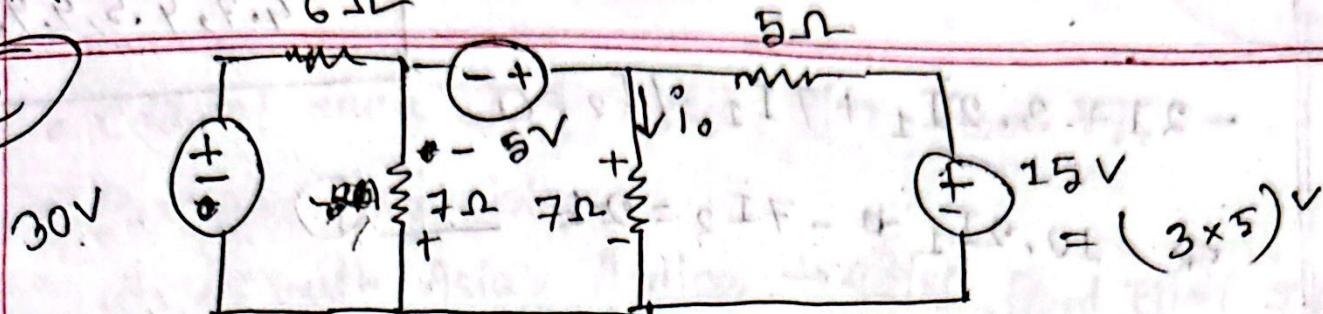


Step-3

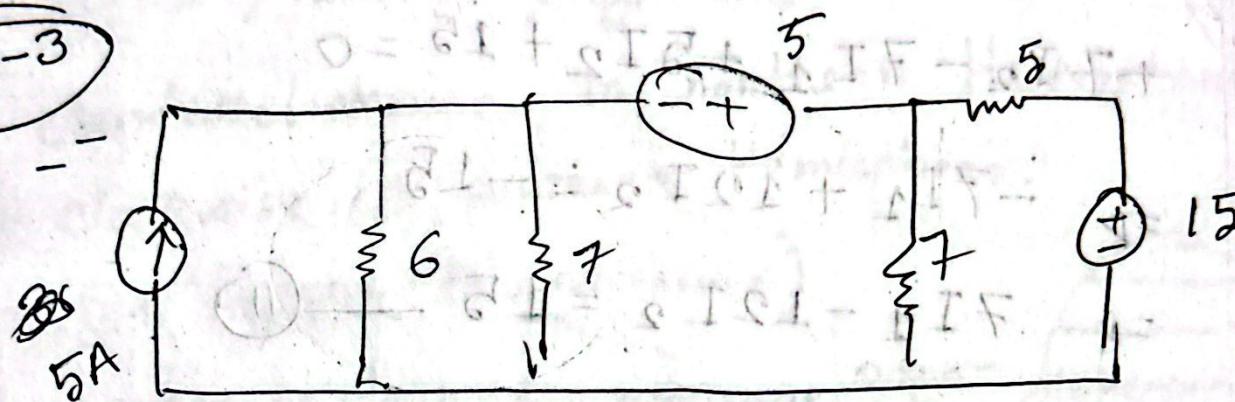

$$6 \parallel 7 = \frac{6 \times 7}{6 + 7} = 3.2 \Omega$$


Step 4

$$5 \times 3.2 = 16 \text{ V}$$

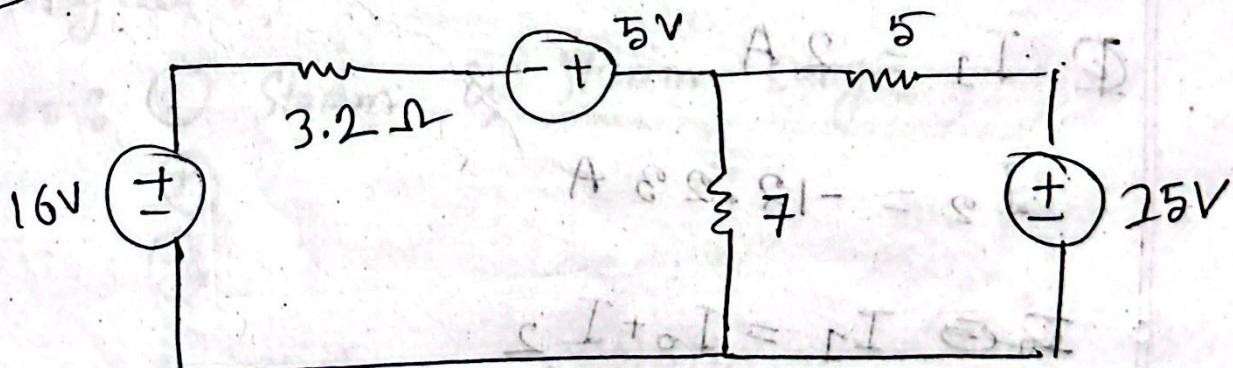

Step 5
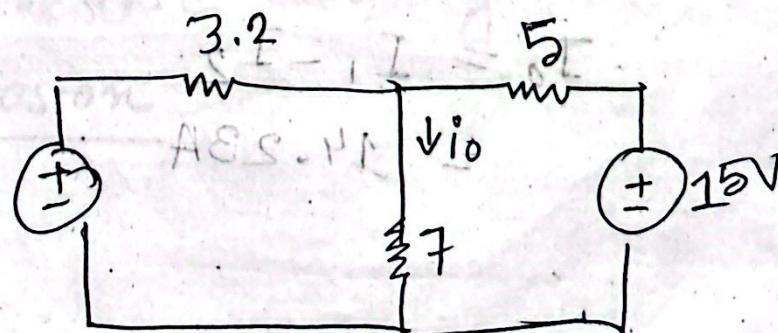
$$\frac{1}{R_{\text{eq}}} = \frac{1}{16} + \frac{1}{5} = \frac{21}{80}$$



LX- 4.7, 4.9, 8.5

Prac prob -
4.7, 4.5, 9.4.

mesh 1

$$-21 + 3 \cdot 2I_1 + 7I_1 - 7I_2 = 0$$

$$\Rightarrow 10.2I_1 - 7I_2 = 21 \quad \text{--- (1)}$$

mesh 2

$$+7I_2 - 7I_1 + 5I_2 + 15 = 0$$

$$\Rightarrow -7I_1 + 12I_2 = -15$$

$$\Rightarrow 7I_1 - 12I_2 = 15 \quad \text{--- (11)}$$

$$\begin{bmatrix} 10.2 & -7 \\ 7 & -12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 21 \\ 15 \end{bmatrix}$$

$$\Delta = -73.4$$
$$\Delta_1 = -147$$

$$\Delta_2 = 6$$

$$\textcircled{1} \quad I_1 = 2A$$

$$I_2 = -12.23A$$

$$\textcircled{2} \quad I_1 = I_o + I_2$$

$$I_o = I_1 - I_2$$

$$= 14.23A$$

MID

Assignment — 15

Class Test. — 15

→ (mesh, Node Analysis)




(Next Monday)

02/09/2024

28/08/2024

Thevenin's Theorem -

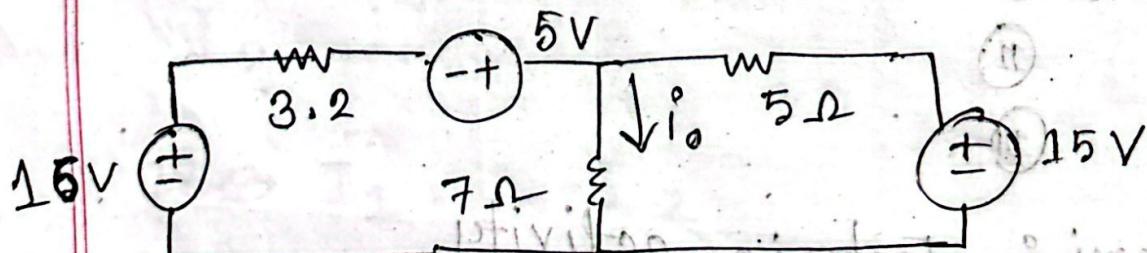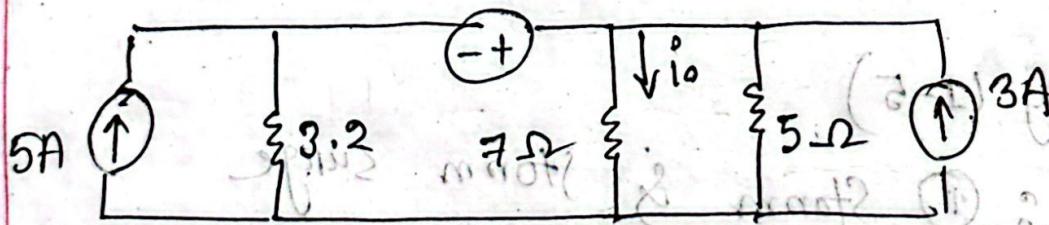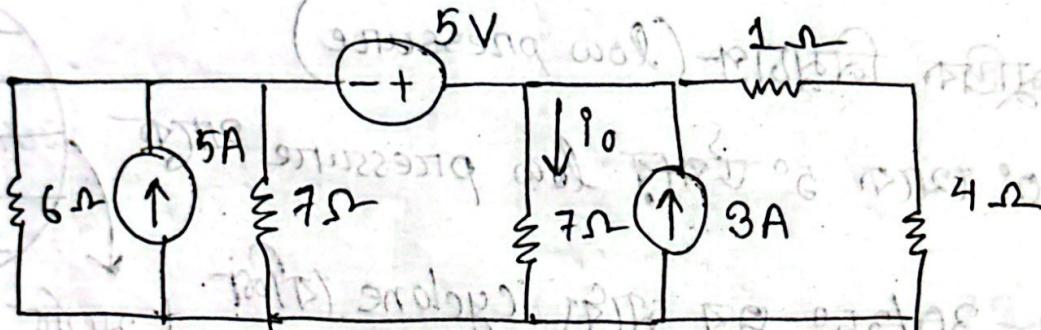Find i_o
using
super-source
transformation



$$\text{KCL at node A}, \quad i_0 + i_2 = i_1$$
$$\therefore i_0 = i_1 - i_2$$

Applying KVL in mesh 1,

$$-21 + 3 \cdot 2i_1 + 7(i_1 - i_2) = 0$$

$$\Rightarrow 10.2i_1 - 7i_2 = 21$$

Applying KVL in mesh 2,

$$-7i_1 + 12i_2 = -15 \quad \text{--- (1)}$$

$$i_1 = 2A$$

$$i_2 = -0.081A$$

$$i_o = i_1 - i_2$$


$$= 2 - (-0.081)$$

$$= 2.081A \text{ (Ans)}$$

Thevenin's Theorem

Find the Thevenin equivalent

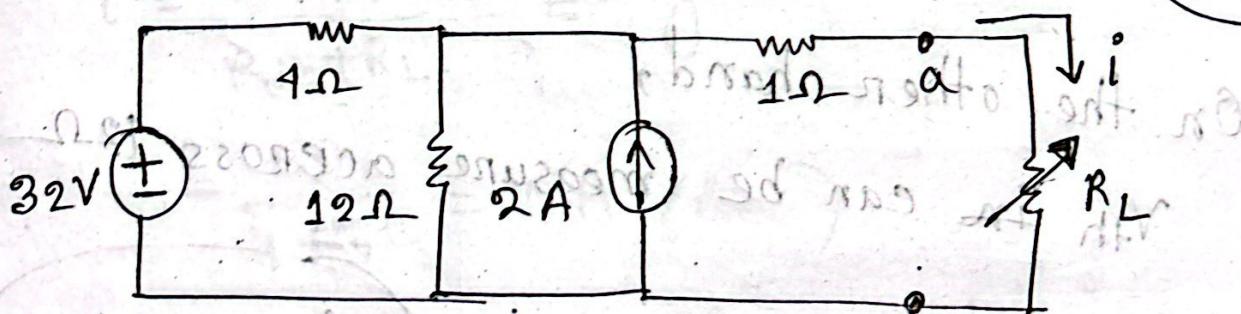
circuit the following figure to the left of the terminal a-b then find i , ($R_L = 6\Omega, 76-$)




R_{th} = Thevenin Equivalent Resistance

V_{th} = 11 Voltage

Step 1: Open R_L ,

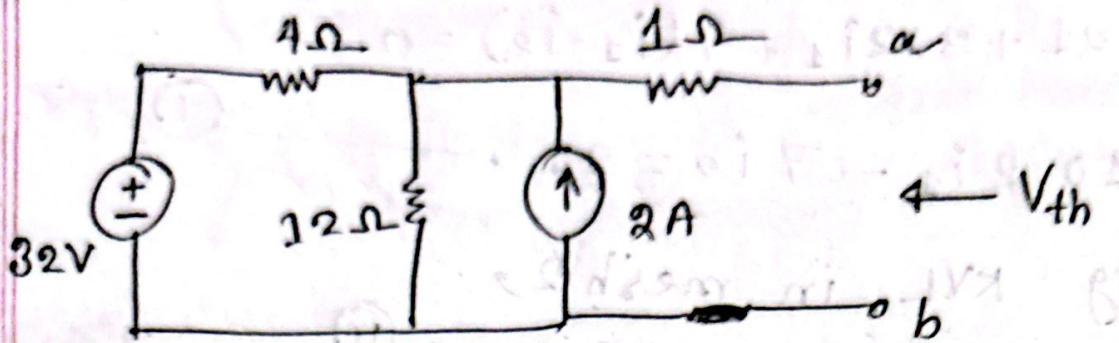

Step 2: Superposition formula,

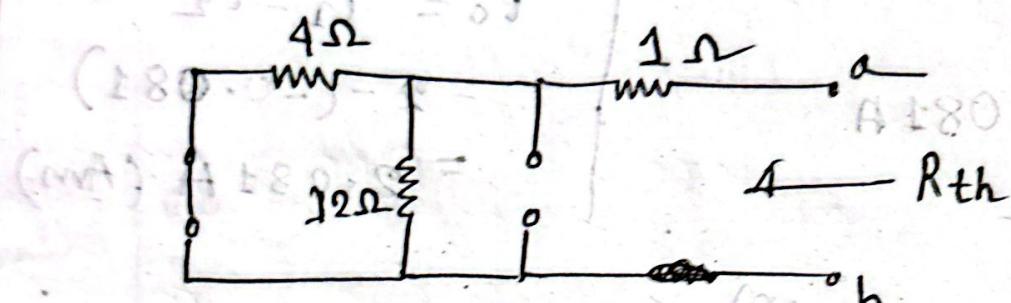


$$\therefore R_{th} = [(4 \parallel 12) + 1] \Omega$$

$$= (3 + 1) \Omega = 4 \Omega$$

On the other hand,

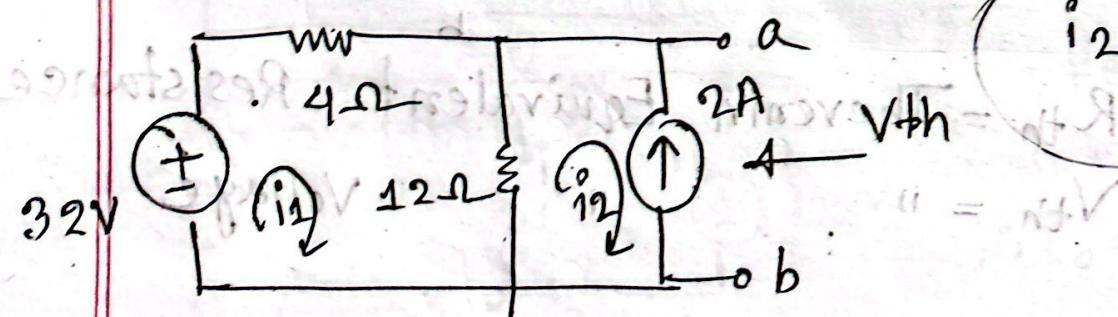V_{th} can be measured across $\underline{12\Omega}$



$$i_2 = -2A$$


KVL in mesh 1,

$$-32 + 4I_1 + 12I_1 - 12 \times (-2) = 0$$

$$\Rightarrow I_1 = 0.5 \text{ A}$$

$$\therefore V_{th} = 12(I_1 - I_2) = 12(0.5 - (-2)) = 30 \text{ V}$$

\therefore Thernin Equivalent circuit,

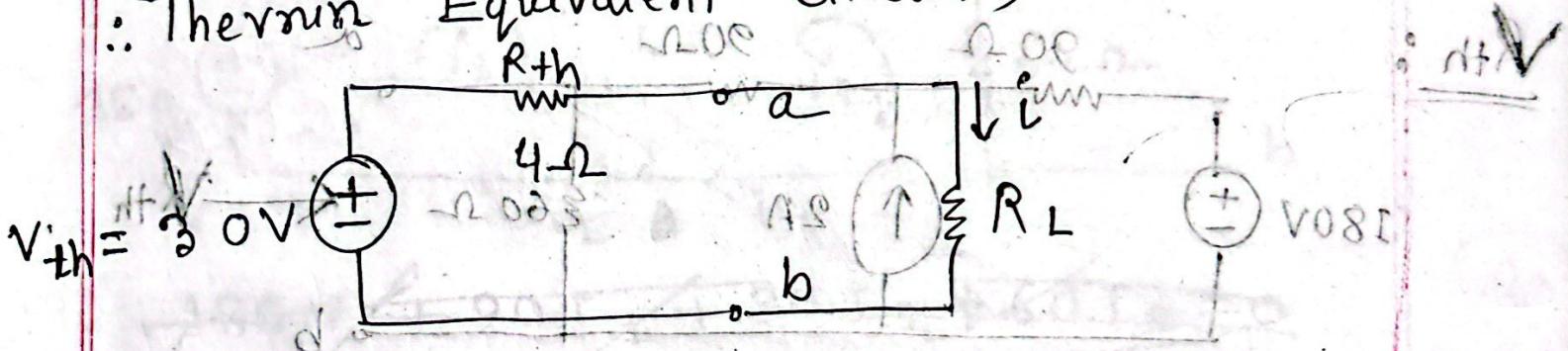

$$i = \frac{V_{th}}{R_{th} + R_L} \quad [\text{Using Ohm's Law}]$$


$$\Rightarrow \frac{30}{4+6} = 3 \text{ A (Ans)}$$

$$\text{On } i = \frac{30}{4+16} = 1.5 \text{ A. (Ans)}$$

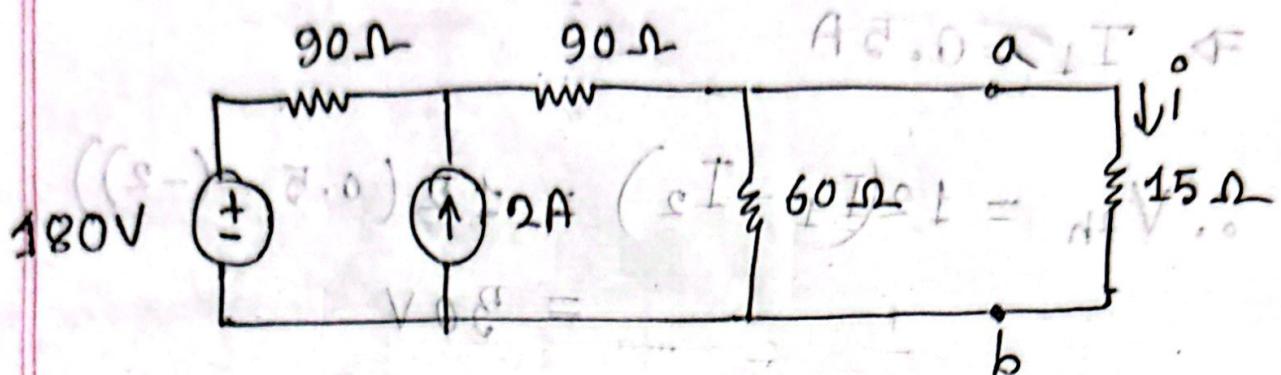
-2.6A =

Q


Find the Thvenin equivalent circuit for the following figure to the left of terminals a-b.



V_{th} :

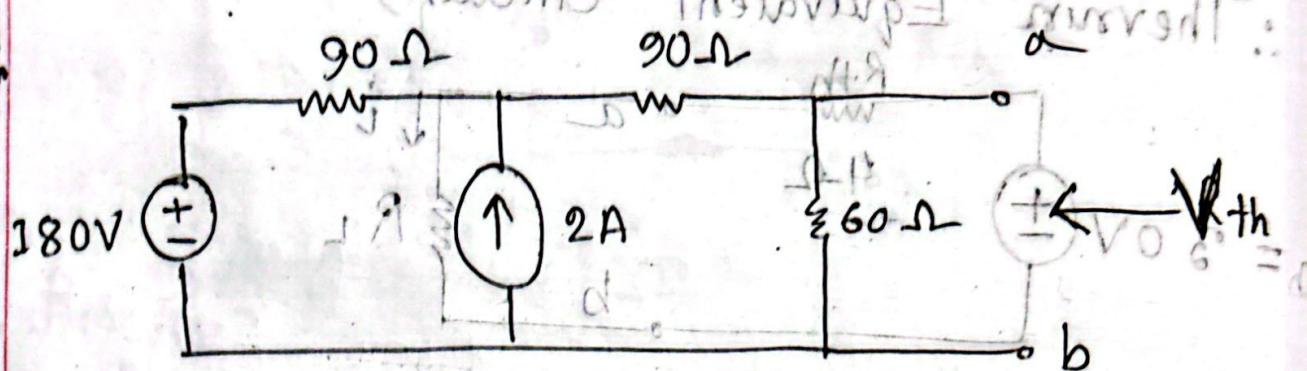


R_{th} :

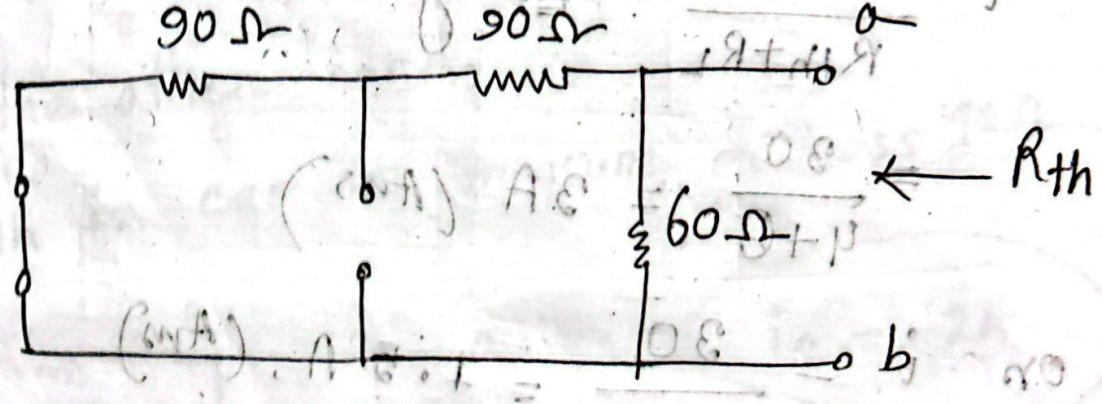

$$R_{th} = (90 + 90) \parallel 60$$

$$= 45\Omega$$

V_{th} can be measured across 60Ω .

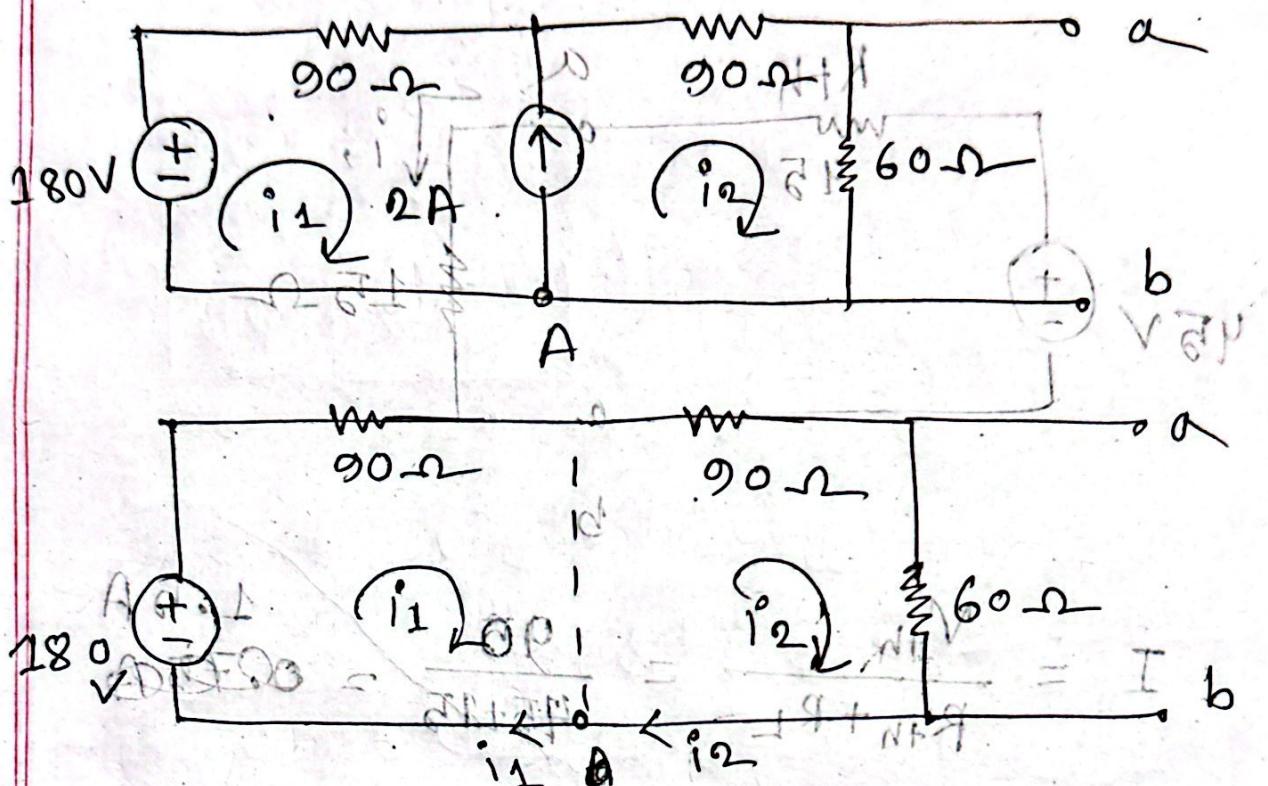

~~$$180V + 90I_1 + 90I_2 + 60I_2 = 0$$~~

VDR,

$$\therefore V_3 = \frac{180 \times 60}{90 + 90 + 60}$$


$$V_{th} = 45V$$

$$i_2 = i_1 + i_s$$

~~$$V_{th} = 45V$$~~

~~$$0.08L = 1.108L + 1.108$$~~

Thevenin Equivalent Circuit

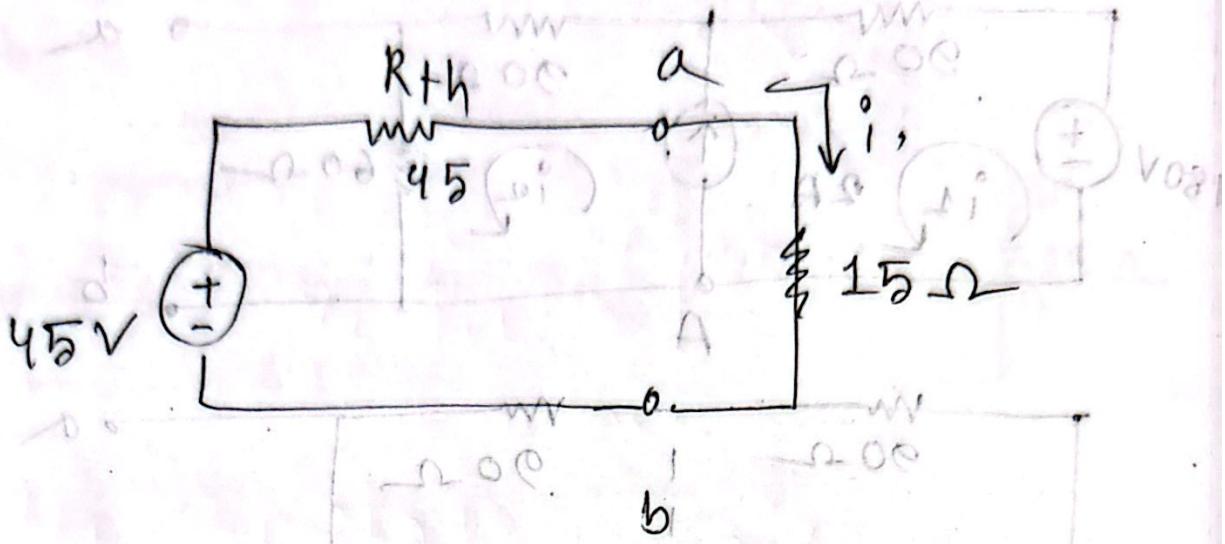

$$I = \frac{V_{th}}{R_{th} + R_L} = \frac{90}{90 + 15} = 0.75 \text{ A}$$

with superposition

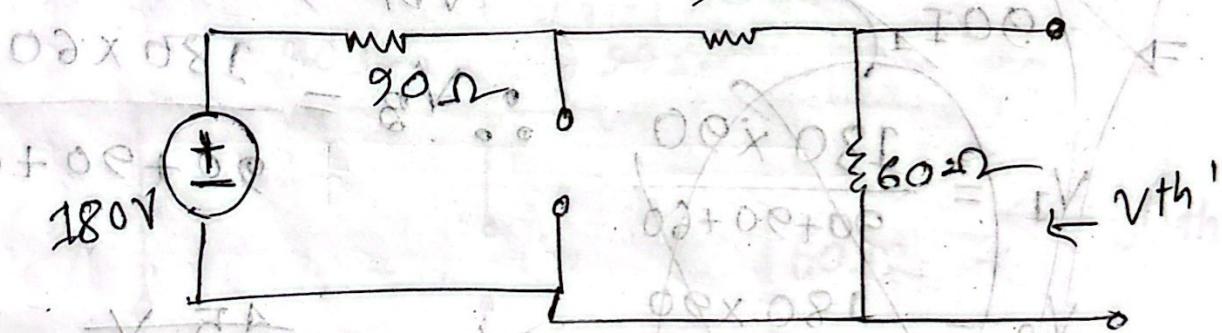


Fig 1


$$-180 + 90I_1 + 90I_2 + 60I_2 = 0$$

$$V_{th}' = 45$$

$$\therefore 90I_1 + 150I_2 = 180$$

CDR,

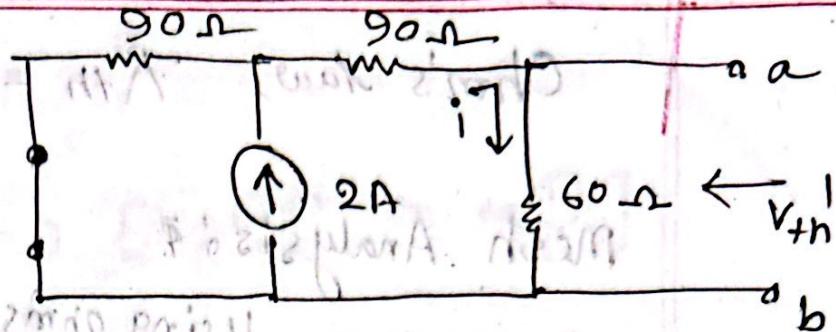
$$i = \frac{2 \times 90}{90 + (90 + 60)} = 0.75 \text{ A}$$



Using Ohm's law,

$$V_{th}'' = 60 i = 60 \times 0.75 = 45 \text{ V}$$
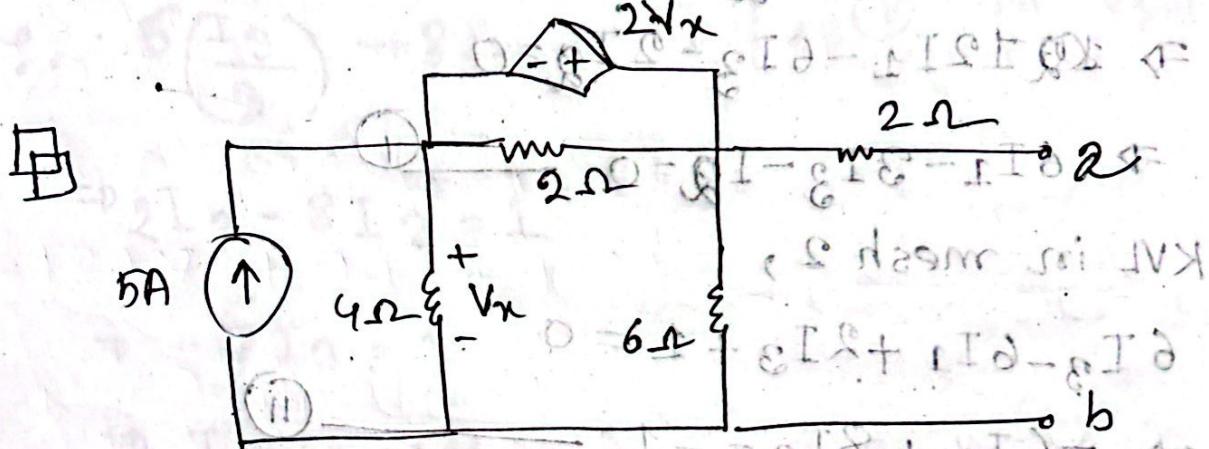
$$V_{th} = V_{th}' + V_{th}'' = 45 + 45 = 90 \text{ V}$$




Find the Thvenin equivalent circuit at terminal a-b:-

~~aff dependent source after OT&CT~~

aff terminal ২৮৮ ১A রমাত্র

R parallel ২৮৮ ১A রমাত্র

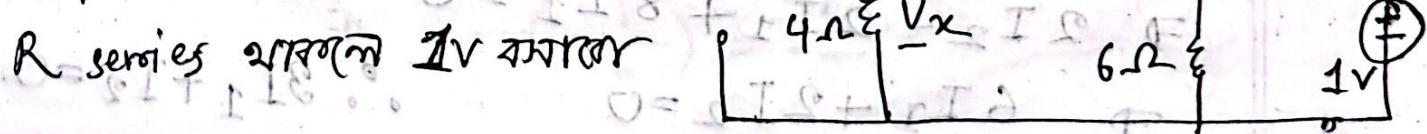


$$\text{Ohm's law, } R_{th} = \frac{V}{I} = \frac{1}{I}$$

Mesh Analysis;

~~KVL~~ ~~Branch~~ \rightarrow Using Ohm's law,

$$-V_x \rightarrow V_x = 4I_1$$

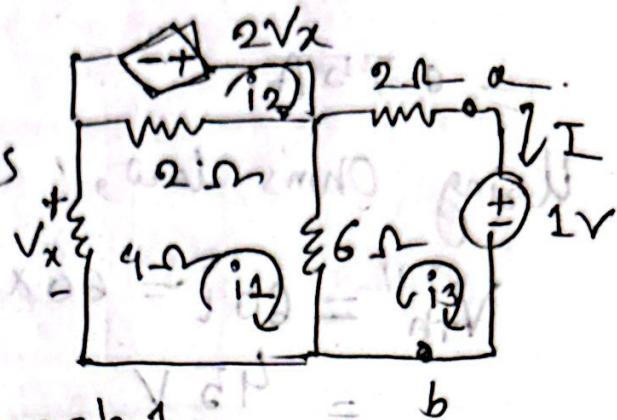

~~+8I_1 - 6I_2~~: KVL in mesh 1,

$$4I_1 + 2I_1 - 2I_2 + 6I_1 - 6I_3 = 0$$

$$\Rightarrow 12I_1 - 2I_2 - 6I_3 = 0$$

$$\Rightarrow 6I_1 - 3I_3 - I_2 = 0 \quad \textcircled{I}$$

KVL in mesh 2,

$$6I_3 - 6I_1 + 2I_3 + 1 = 0$$

$$\Rightarrow -6I_1 + 8I_3 = -1 \quad \textcircled{II}$$

$$\Rightarrow -3I_1 + 4I_3 = 1 \quad \textcircled{II}$$

KVL in mesh 2,

$$2I_2 - 2I_1 - 2V_x = 0$$

$$\Rightarrow 2I_2 - 2I_1 - 2(4I_1) = 0$$

$$\Rightarrow 2I_2 - 2I_1 + 8I_1 = 0$$

$$\Rightarrow 6I_1 + 2I_2 = 0$$

$$\therefore 3I_1 + I_2 = 0 \quad \textcircled{III}$$

$$\Rightarrow I_2 = -\frac{1}{3}I_1 \quad \text{--- (IV)}$$

$$\therefore 6I_1 - 3I_3 + 3I_1 = 0 \quad [\text{eq (IV) in eq (I)}]$$

$$\Rightarrow 9I_1 - 3I_3 = 0$$

$$\Rightarrow 3I_1 - I_3 = 0$$

$$\Rightarrow I_1 = \frac{I_3}{3} \quad \text{--- (V)}$$

$$\therefore 6\left(\frac{I_3}{3}\right) - 8I_3 = 1 \quad [\text{eq (V) in eq (II)}]$$

$$\Rightarrow 2I_3 - 8I_3 = 1$$

$$\Rightarrow -6I_3 = 1$$

$$\Rightarrow I_3 = -\frac{1}{6}$$


Applying KCL at node 'a',

$$i_3 + I = 0 \quad \text{--- (VI)}$$

$$\Rightarrow I = i_3$$

$$\Rightarrow = -\left(-\frac{1}{6}\right) = \frac{1}{6}$$
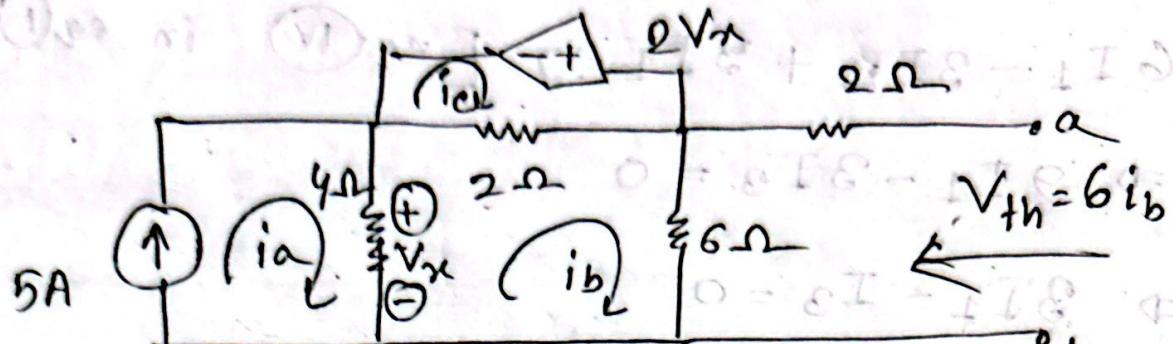
$$R_{th} = \frac{V}{I} = \frac{1}{\frac{1}{6}} = \frac{1}{\frac{1}{6}} = 6\Omega$$



$$i_a = 5A$$

KVL in mesh b,

$$4I_b - 4I_a + 2I_b - 2I_c + 6I_b = 0$$

$$\Rightarrow \frac{19}{10}I_b - 20 - 2I_c = 0$$

$$\Rightarrow 6I_b - I_c = 10 \quad \text{--- (1)}$$

KVL in mesh c,

$$2I_c - 2I_b - 2V_x = 0$$

$$\therefore V_x = I_c - I_b$$

~~$$= 0I_c - 0I_b - V_x = 4(5 - I_b)$$~~

~~$$\therefore V_x = 20 - 4I_b$$~~

$$\cancel{I_c - I_b = 4I_b - 20 \quad \text{---} \quad 4I_b^2 - 20I_b - 4I_b = 25 - I_b}$$

$$\Rightarrow I_c - I_b = 5 \quad \text{(1)}$$

$$[5 \quad -1] [I_b] = [10] \quad \text{from this trimming solution}$$

$$[-5 \quad 1] [I_c] = [20]$$

$$I_b = 1A$$

$$I_c = 5A$$

$$25 - I = 5I_b - 5 = 10$$

$$\Rightarrow I_b = 1$$

$$I_c - I_b = V_x = 20 - 4I_b$$

$$\Rightarrow I_c = 20 \quad \text{Def.} \quad -3I_b - I_c = -20$$

$$I_b = -3.333$$

$$\therefore I_b - I_c = 20$$

$$6I_b - I_c = 10$$

$$3I_b + I_c = 20$$


$$9I_b = 30$$

$$\therefore I_b = 3.333$$

$$V_{th} = 6I_b$$

$$= 6 \times 3.333$$

$$\approx 20V$$

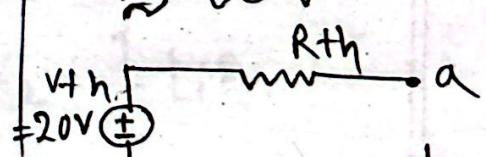


Norton Theorem

$$I_N = \text{Norton Current} = \frac{V_{th}}{R_{th}}$$

$$R_N = \text{Norton Resistance} = R_{th}$$

Norton equivalent circuit,

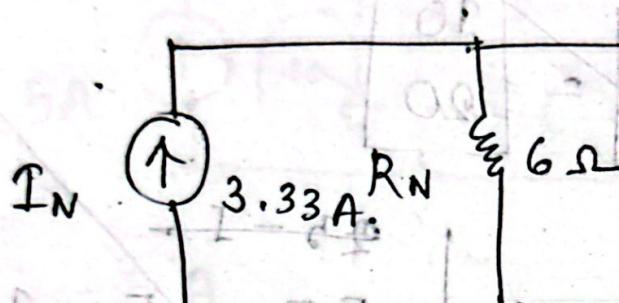

$$\dot{I} = dI / \partial \alpha$$

$$A_D = \partial I / \partial \alpha$$

$$\partial I / \partial \alpha = xV = dI - \beta I$$

$$0\alpha = \beta I - dI + \text{if } \alpha = 0\alpha = \beta I - dI$$

$$0\alpha = \beta I - dI \therefore$$

$$0\alpha = \beta I - dI$$

$$0\alpha = 14V$$

$$0\alpha = \beta I - dI$$


$$0\alpha = \beta I + dI$$


$$0\alpha = dI$$

$$0\alpha \times \beta =$$


$$V_{AB} \approx$$

$$0\alpha = dI$$

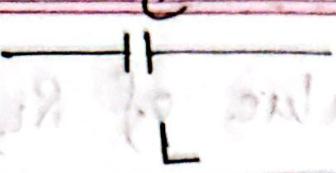Capacitor 


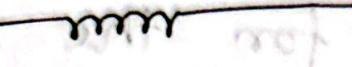
Inductor 

(S)

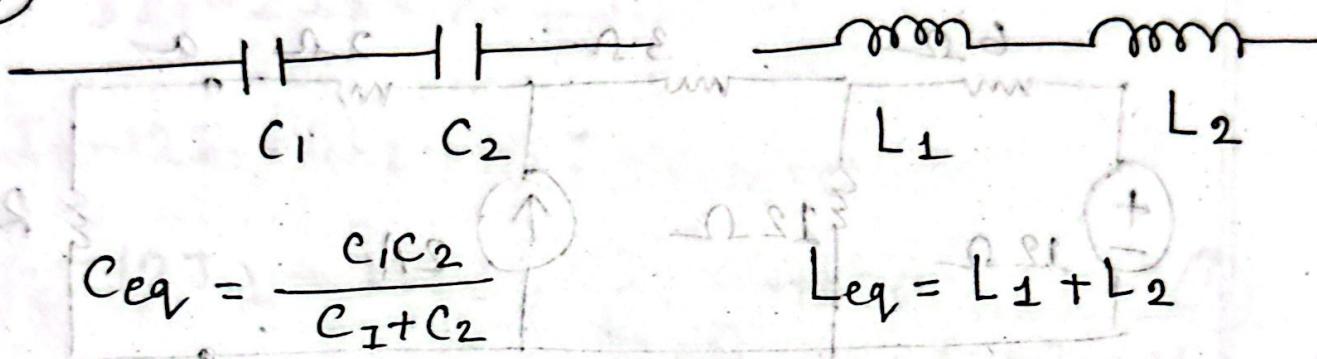

Energy: $W_C = \frac{1}{2} C V_C^2$

(P)

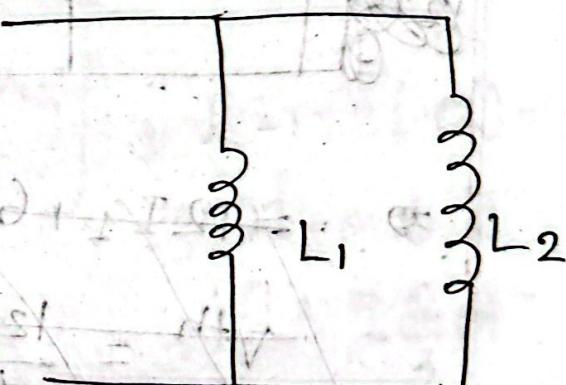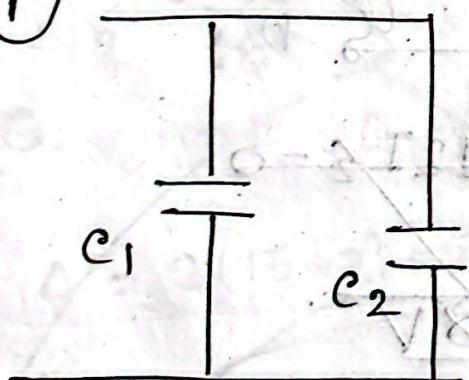



$$C_{eq} = C_1 + C_2$$

$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

Energy: $W_L = \frac{1}{2} L i^2$

Maximum Power Transfer Theorem

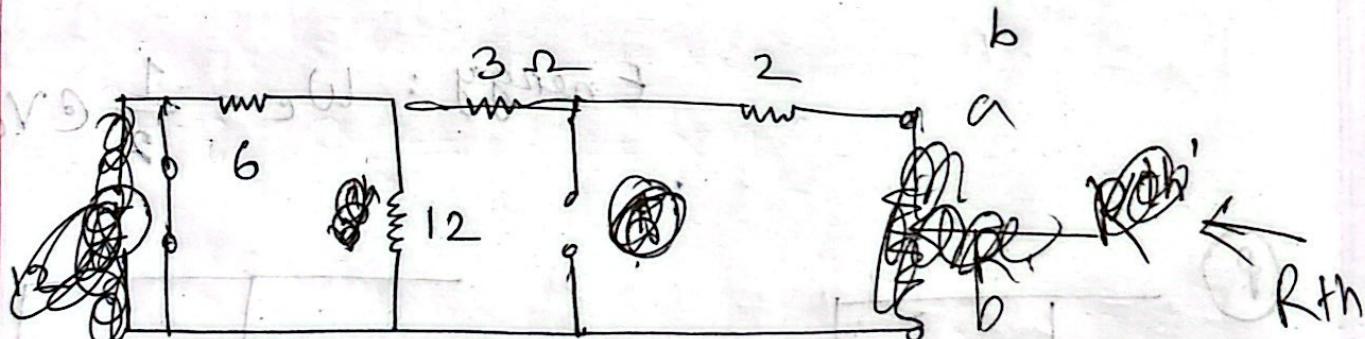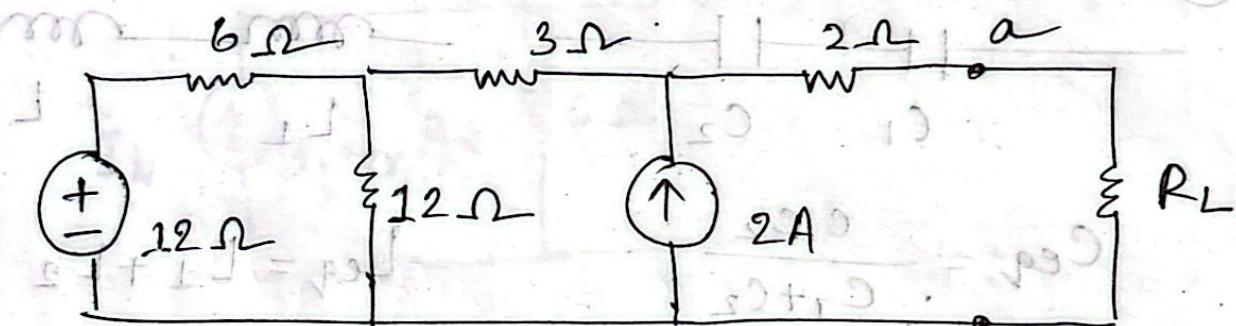Find the value of R_L for maximum power transfer for the following circuit, find the maximum power.



$$12I_1 + 6I_1 + 12I_2 - 12I_2 = 0$$

$$V_{th} = \frac{12 \times 12}{6+12} = 8V$$

$$R_{th} = 3+2+12+6 = 23\Omega$$

$$R_{th} = (6||12) + 3+2$$


$$= 4+3+2 = 9\Omega$$

$$-12 + 6I_1 + 12I_1 - 12I_2 = 0$$

$$\Rightarrow 18I_1 - 12I_2 = 12$$

$$\Rightarrow 9I_1 - 6I_2 = 6 \quad \text{--- (i)}$$
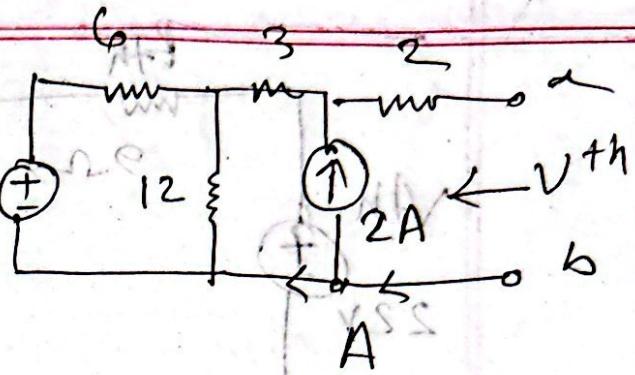
$$\Rightarrow 3I_1 - 2I_2 = 2 \quad \text{--- (ii)}$$



$$12I_2 - 12I_1 + 3I_2 + 2I_3 + V_{th} = 0$$

$$\Rightarrow -12I_1 + 15I_2 + 2I_3 = -V_{th} = 0 \quad \text{--- (iii)}$$

KCL at node A, $I_3 = 2 + I_2$

$$I_3 - I_2 = 2 \quad \text{--- (iv)}$$

$$\Rightarrow I_2 = -2$$


$$\begin{bmatrix} 3 & -2 & 0 \\ -12 & 15 & 2 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 2 \\ -V_{th} \\ 2 \end{bmatrix}$$

$$3I_1 - 2(-2) = 2$$

$$\therefore I_1 = \frac{2}{3} A$$

$$\left(-12 \times \frac{2}{3} \right) + (15 \times -2) + V_{th} = 0$$

$$\therefore V_{th} = 22 V$$

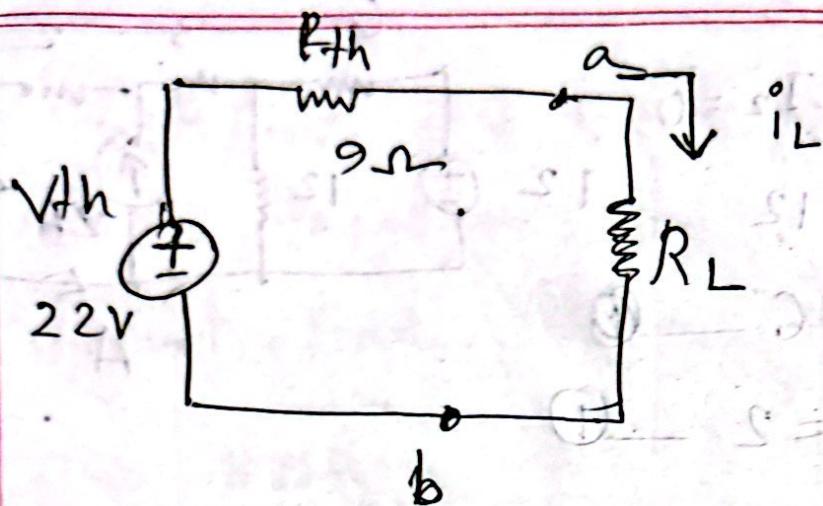

For maximum power transfer

$$R_L = R_{th} = 9 \Omega$$

$$P = i_L^2 R_L = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 \times R_L$$

$$= \left(\frac{V_{th}}{R_{th} + R_{th}} \right)^2 \times R_{th}$$

$$[R_L = R_{th}]$$

$$= \frac{V_{th}^2}{4R_{th}} = \frac{(22)^2}{4 \times 9} = 13.4 W$$


(AM)

DC


\square (Farad) Capacitor \rightarrow Resistor \rightarrow open
 (Henry) Inductor \rightarrow Resistor \rightarrow short circuit
 low to high

Under (dc) conditions, find (a) i , v_c , i_L .

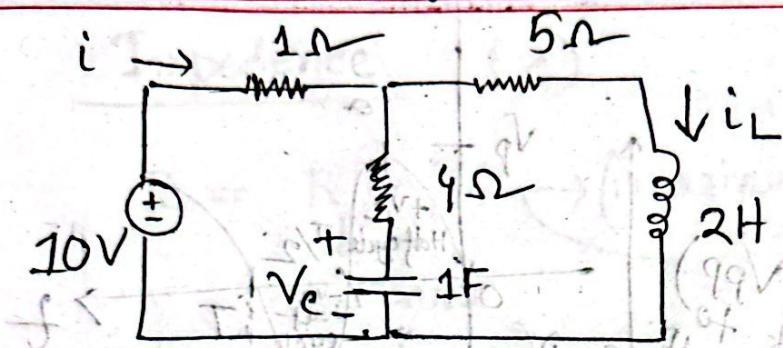(b) The energy stored in capacitor and Inductor.



Soln : @

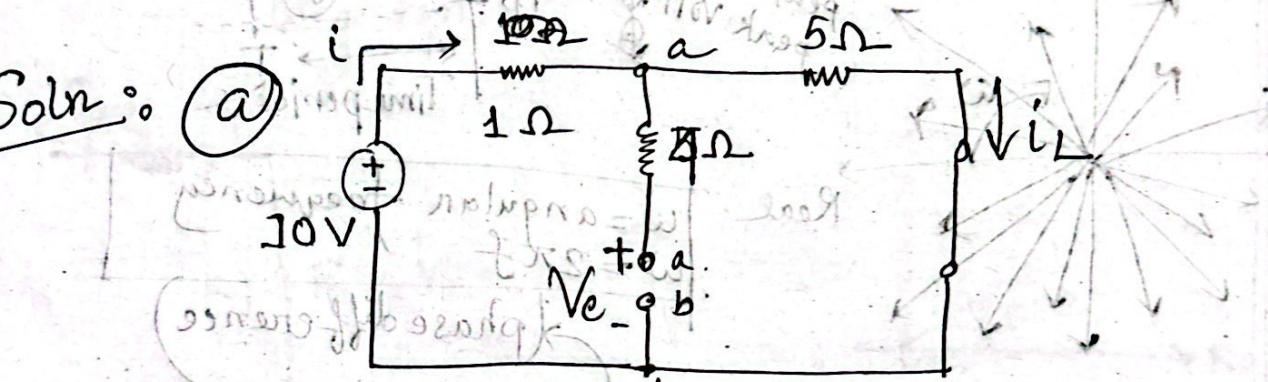

$$i = i_L = \frac{12}{(1+5)} = 2A$$

$$v_c = 5i_L = 5 \times 2 = 10V$$

$$(b) w_c = \frac{1}{2} C v_c^2 = \frac{1}{2} \times 1 \times 10^2 = 50 J$$



$$(b) w_L = \frac{1}{2} L i_L^2 = \frac{1}{2} \times 2 \times 2^2 = 4 J$$

Amplitude

AC

V_p = Peak Voltage

T = Period

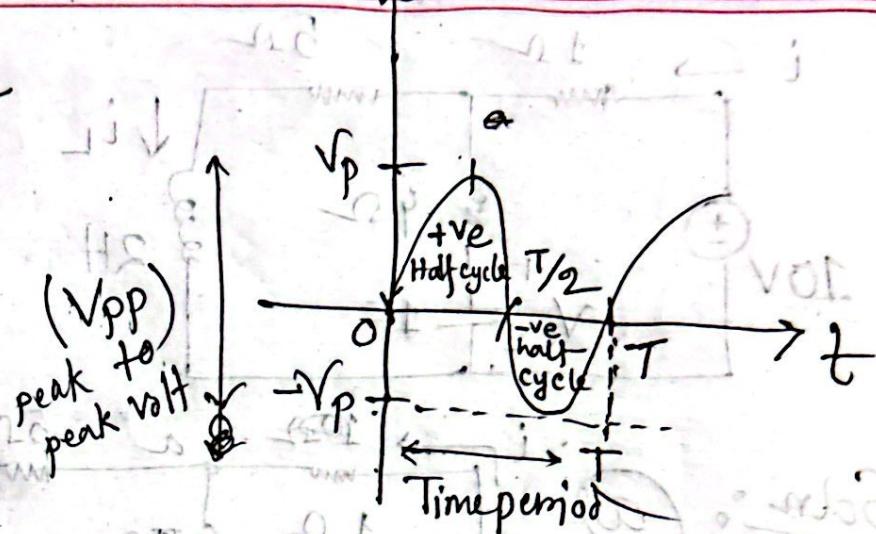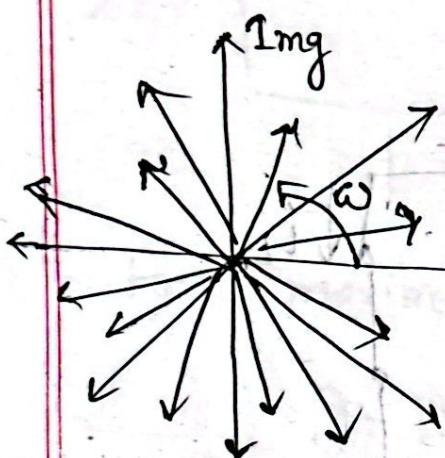

ω = angular frequency

$$\omega = 2\pi f$$


(phase difference)

$$V(t) = \text{Amp} \sin(\omega t \pm \theta)$$

$$= V_p \sin(\omega t \pm \theta)$$



$$20 \sin 4t$$



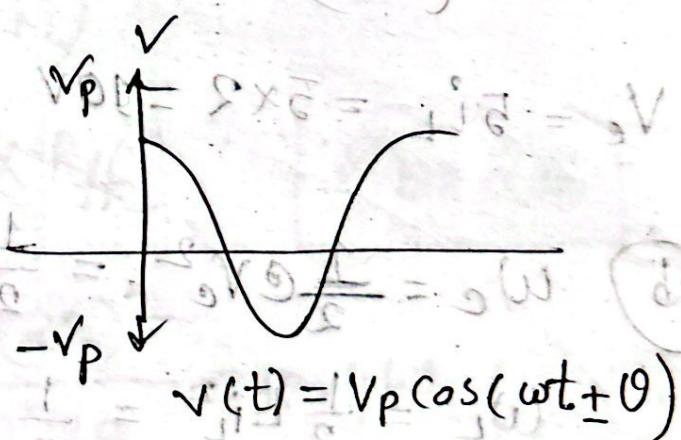


$$V(t) = V_p \cos(\omega t \pm \theta)$$

01/09/2024



Impedance (Z)

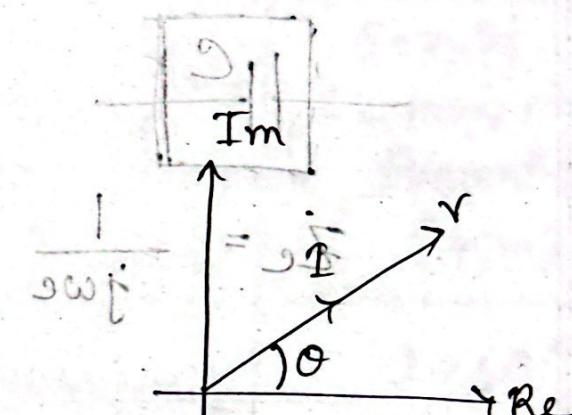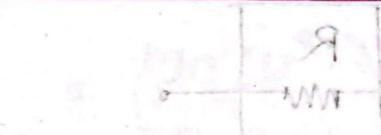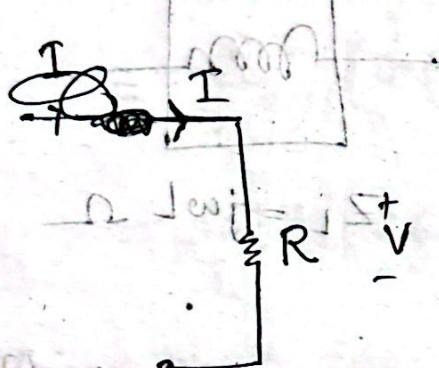
$$Z = R + jX \rightarrow \begin{matrix} \text{(imaginary part / reactance part)} \\ \downarrow \\ \text{Real part (Resistance)} \end{matrix} \rightarrow \text{depends on } L, C$$



(f) I bres (f) V brefit #

Here, Resistance is
a linear property

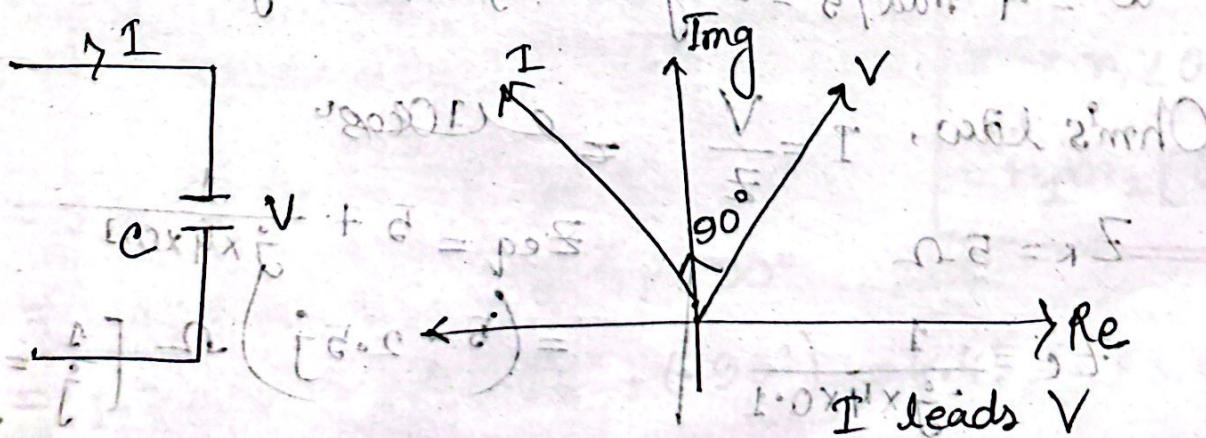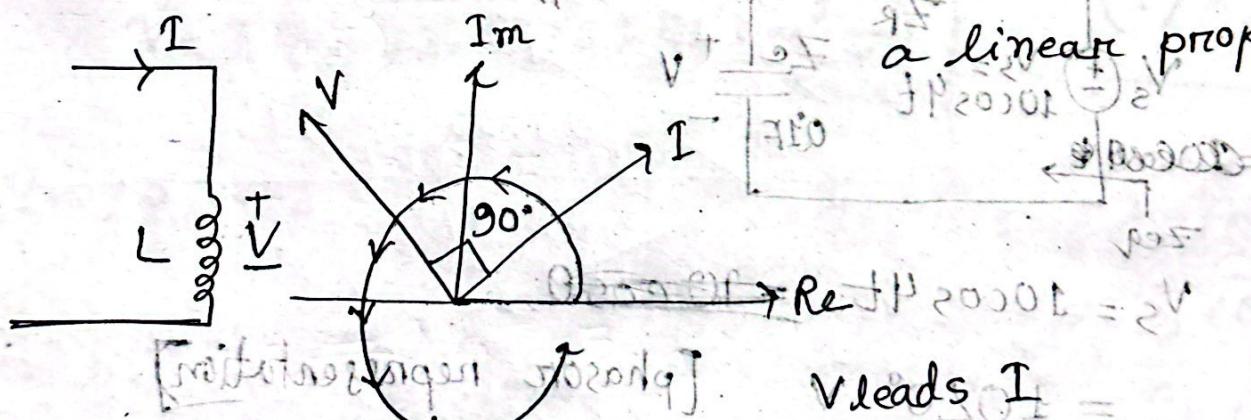


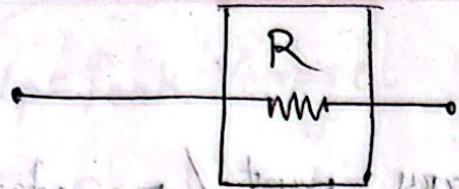


(14)

Temporary


$$Z_R = R + 0 = R$$

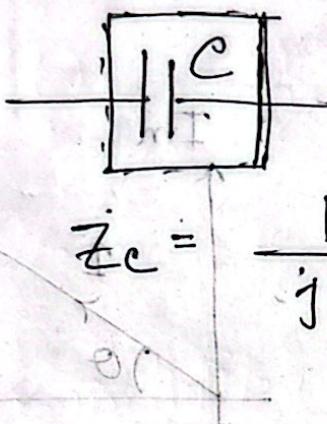
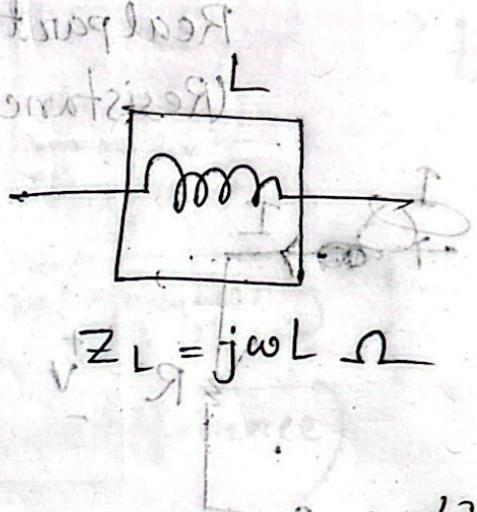
$$\bar{Z}_c = \frac{1}{j\omega c} \Omega$$



$$Z_L = j\omega L \quad \Omega$$

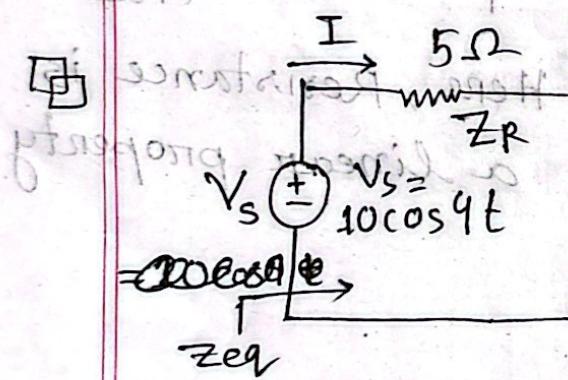

$$V_s = 10 \cos 4t$$

$$= 1020^\circ \text{V} \quad [\text{phasor representation}]$$

$\omega = 4 \text{ rad/s}$ = angular frequency

$$\text{Ohm's law, } I = \frac{V}{R} = e^{i10\pi s^6}$$

$$Z_R = 5 \Omega$$

$$Z_C = \frac{1}{\pi \times 4 \times 0.1}$$

$$Z_{eq} = 5 + \frac{1}{j \times 4 \times 0.1} \\ = (5 - 2.5j) \Omega \quad \left[\frac{1}{j} = -j \right]$$

~~Per-pole shift (+)~~

angle - polar form
 j - rectang form

$$I = \frac{V_s}{Z_{eq}} = \left(\frac{10 \cos 4t}{5 - 2.5j} \right) A = \left(\frac{10 \angle 0^\circ}{5 - 2.5j} \right) A = 2V$$

$$= \frac{10 \angle 0^\circ}{5.59 \angle -26.56^\circ}$$

$$= \frac{10}{5.59} \angle (0^\circ - (-26.56^\circ))$$

$$= 1.78 \angle 26.56^\circ A$$

Using Ohm's law,

$$V = I Z_C = 1.78 \angle 26.56^\circ \times \left(\frac{1}{j\omega C} \right)$$

$$V = I Z_C = I \times \left(\frac{1}{j\omega C} \right)$$

$$= 1.78 \angle 26.56^\circ \times \frac{1}{j \times 4 \times 10^{-9}}$$

$$= \frac{1.78 \angle 26.56^\circ}{0.4f}$$

$$= 1.78 \angle 26.56^\circ \times (-j2.5)$$

$$= 1.78 \angle 26.56^\circ \times 2.5 \angle -90^\circ$$

$$= (1.78 \times 2.5) \angle (26.56^\circ + (-90^\circ)) = 4.45 \angle -63.44^\circ V$$

$5 - 2.5j$

(Rectangular formation)

$(+/-)$

$10 \angle 0^\circ$

(polar formation)

(\div/x)

$$\div \rightarrow \frac{r_1 \angle \theta_1}{r_2 \angle \theta_2}$$

I choose V

$$= \frac{r_1}{r_2} (\theta_1 - \theta_2)$$

$$X \rightarrow r_1 \angle \theta_1 \times r_2 \angle \theta_2$$

$$= r_1 r_2 (\theta_1 + \theta_2)$$

$$V_s = 10 \cos(4t) \text{ V} = A \left(\frac{\sin(4t + 90^\circ)}{\sin 90^\circ} \right) = \frac{eV}{j\omega L} = I$$

$$v(t) = 4.45 \cos(4t - 63.44^\circ) \text{ V}$$

$$I(t) = (1.78 \cos(4t + 26.56)) \text{ A}$$

$$(-V) =$$

Phasor
(with respect to voltage)


$$(x \div)$$

$$\frac{35 \text{ rad}}{50 \text{ rad}}$$

Diagram,

Img

$$1.78$$

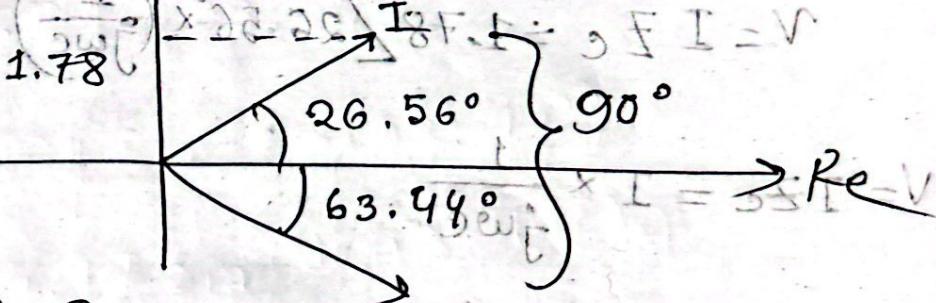

V leads I

This circuit behaves like an inductor.

$$(3 + 0) \angle 0^\circ =$$

$$(3.2t) \times 22.38 \angle 87.1^\circ =$$

$$0.08 \angle 87.1^\circ \times 22.38 \angle 87.1^\circ =$$

$$V = 1.78 \angle 63.44^\circ = (0.08 + 0.22 \angle 87.1^\circ) \times (3.2 \times 87.1) =$$

$$V(t) \text{ & } I(t)$$

Soln:

$$V_s = 20 \sin(10t + 30^\circ)$$

$$= 20 \angle 30^\circ V$$

$$I = \frac{V}{Z}$$

$$Z_R = 4 \Omega$$


$$Z_L = j\omega L = 0.2 \times 10 j = 2 j$$

$$Z_{eq} = (4 + 2j) \Omega$$

$$I = \frac{V_s}{Z_{eq}} = \frac{(20 \sin(10t + 30^\circ))}{4 + 2j} A$$

$$= \frac{20 \angle 30^\circ}{4 + 2j} = \frac{20 \angle 30^\circ}{4.47 \angle 26.56^\circ}$$
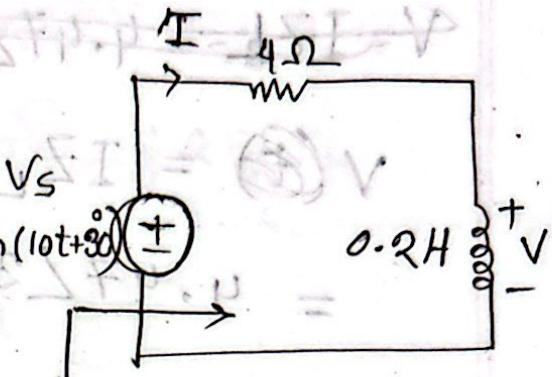
$$= 4.47 \angle (30^\circ - 26.56^\circ) = 4.47 \angle 3.44^\circ$$



$$\omega = 10 \text{ rad/s}$$

Using Ohm's law,

$$(f) \mathbf{E} = \mathbf{V}$$

~~$$\mathbf{V} - \mathbf{I}Z_L = 4.47 \angle 56.56^\circ \times 2 \angle (102^\circ)$$~~

$$\mathbf{V} = \mathbf{I}Z_L \quad (\text{open for } 0\Omega = 2V)$$

$$= 4.47 \angle 3.44^\circ \times -j\omega L$$


$$= 4.47 \angle 3.44^\circ \times j \times 10 \times 0.2$$

$$= 4.47 \angle 3.44^\circ \times 2j$$

$$= 4.47 \angle 3.44^\circ \times 2 \angle 90^\circ$$


$$= 4.47 \times 2 \angle 3.44^\circ + 90^\circ$$

$$= 8.94 \angle 93.44^\circ$$

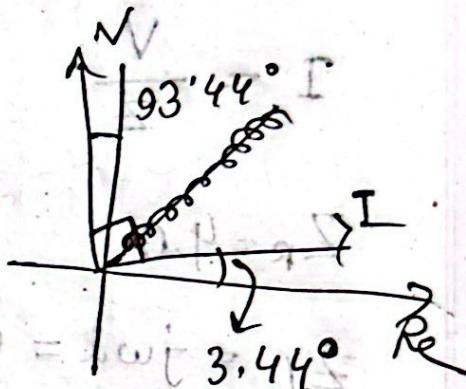

$$V(t) = 8.94 \sin(10 + 93.44^\circ) V$$

$$I(t) = 4.47 \sin(10 + 3.44^\circ) A$$

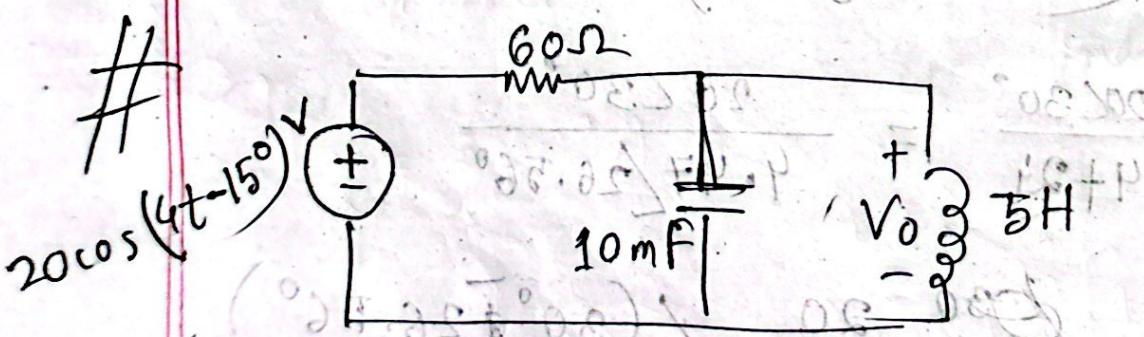

$$V_s = 20 \cos(4t - 15^\circ) V \quad | \quad \omega = 4 \text{ rad/s}$$

$$= 20 \angle -15^\circ V$$

$$Z_R = 60 \Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{4j \times 10 \times 10^{-3}} = -j 25 \Omega$$

$$Z_L = j\omega L = j 4 \times 5 = 20j \Omega$$

$$Z_C \parallel Z_L = (-j 25 \parallel j 20)$$

$$V = \frac{-j 25 \times j 20}{-j 25 + j 20}$$

$$= \frac{25 \angle -90^\circ \times 20 \angle 90^\circ}{-j 5}$$

$$= \frac{25 \times 20 (\angle -90^\circ + 90^\circ)}{5 \angle -90^\circ}$$


$$= \frac{25 \times 20}{5} \angle 0^\circ - 90^\circ$$

$$= 100 \angle 90^\circ \Omega$$

$$Z_{eq} = Z_R + Z_C \parallel Z_L$$

$$= 60 + j 100 \Omega$$


$$= 116.61 \angle 59.03^\circ$$

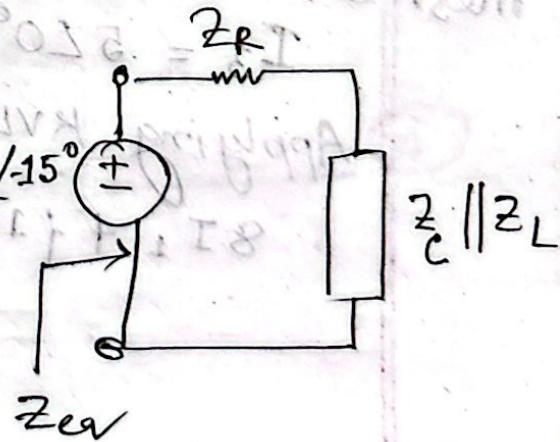

Applying VDR,

$$V_o = \frac{20 \angle -15^\circ \times 100 \angle 90^\circ}{60 + j100}$$
$$= \frac{20 \times 100 \angle -15^\circ + 90^\circ}{60 + j100} \approx 116.61 \angle 59.03^\circ$$
$$= 17.15 \angle 15.96^\circ \text{ V}$$
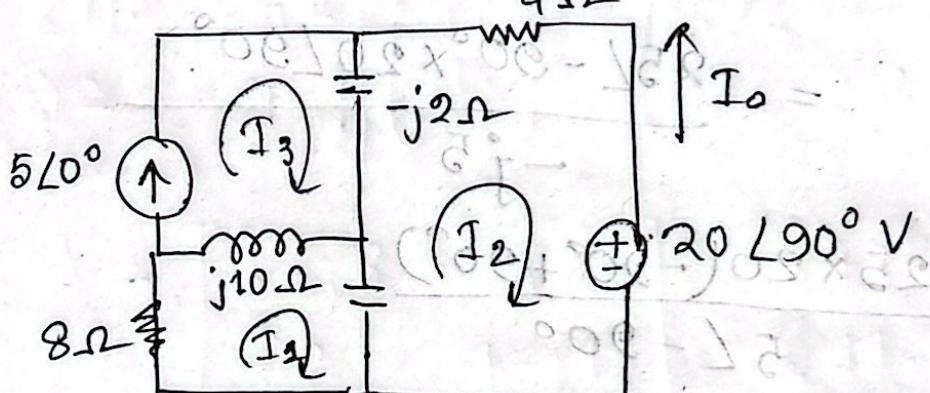
$$v_o(t) = 17.15 \cos(4t + 15.96^\circ) \text{ V}$$



Determine current I_o using mesh analysis.

From mesh 3,

$$I_3 = 5 \angle 0^\circ \text{ A}$$

Applying KVL in mesh 1,

$$8I_1 + j10(I_1 - I_3) + (-j2)(I_1 - I_2) = 0$$

$$\Rightarrow 8I_1 + j10I_1 + j10I_3 - j2I_1 + j2I_2 = 0$$

$$\Rightarrow (8+j8)I_1 + 12I_2 - j10I_3 = 0 \quad (11)$$

Applying KVL in mesh 2,

$$+ (j2)(I_2 - I_1) + (-j2)(I_2 - I_3 + 4I_2 + 20\angle 90^\circ = 0$$

$$\Rightarrow -j2I_1 + j2I_1 - j2I_2 + j2I_3 + 4I_2 + 20\angle 90^\circ = 0$$

$$\Rightarrow j2I_1 + 4I_2 - j4I_2 + j2I_3 + j20 = 0$$

$$\Rightarrow j2I_1 + (4-j4)I_2 + j2I_3 = -j20$$

$$\Rightarrow j2I_1 + (4-j4)I_2 + j2I_3 + j2I_3 = 20\angle -90^\circ \quad (11)$$

In equation (ii) & (iii) substituting $I_3 = 5\angle 0^\circ A$

$$I_1(8+j8) + j2I_2 - j10 \times 5\angle 0^\circ = 0$$

$$\Rightarrow I_1(8+j8) + 12I_2 - 10\angle 90^\circ \times 5\angle 0^\circ = 0$$

$$\Rightarrow I_1(8+j8) + j2I_2 - 50\angle 90^\circ = 0$$

$$\therefore I_1(8+j8) + j2I_2 = 50\angle 90^\circ \quad (A)$$

$$A^2 8F \xrightarrow{\text{PHE}} S.C.D. = \frac{S.A.}{A} = S.F. = I$$

$$j2I_1 + (4 - j4)I_2 + j2 \times 5 \angle 0^\circ = 20 \angle -90^\circ$$

$$\Rightarrow j2I_1 + (4 - j4)I_2 + 2 \angle 90^\circ \times 5 \angle 0^\circ = 20 \angle -90^\circ$$

$$\Rightarrow j2I_1 + (4 - j4)I_2 + \underbrace{10 \angle 90^\circ}_{j10} = 20 \angle -90^\circ$$

$$\Rightarrow j2I_1 + (4 - j4)I_2 = j20 - j10$$

$$\Rightarrow j2I_1 + (4 - j4)I_2 = -j30 = 30 \angle -90^\circ \quad \text{(B)}$$

$$\begin{bmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 50 \angle 90^\circ \\ 30 \angle -90^\circ \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{bmatrix} = (8 + j8)(4 - j4) - j2 \cdot j2 = 11.31 \angle 45^\circ \times 5.65 \angle -45^\circ - 2 \angle 90^\circ \times 2 \angle 90^\circ$$

$$\Delta_1 = \begin{bmatrix} 50 \angle 90^\circ & j2 \\ 30 \angle -90^\circ & 4 - j4 \end{bmatrix} = 6.3 \cdot 90^\circ - (-4) = 67.90^\circ = \Delta$$

$$\Delta_2 = \begin{bmatrix} 8 + j8 & 50 \angle 90^\circ \\ j2 & 30 \angle -90^\circ \end{bmatrix}$$

$$I_0 = -I_2 = \frac{-\Delta_2}{\Delta} = 6.12 \angle 144^\circ \quad 78^\circ A$$