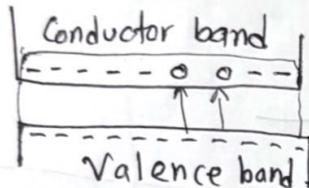
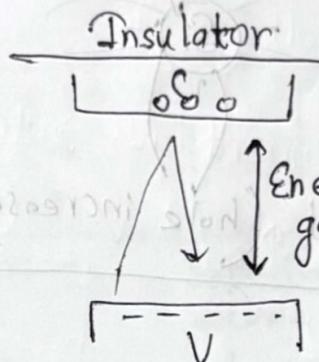
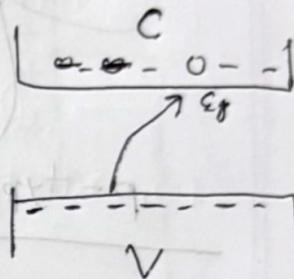


Diode

Conduction band  
Valence band

Conductor


Electrons can create bond on its own

Semiconductor

Electrons cannot create bond on its own. So no H has to be applied.

$$\text{Ge} \rightarrow 0.67 \text{ eV}$$



$$\text{Si} \rightarrow 1.1 \text{ eV}$$

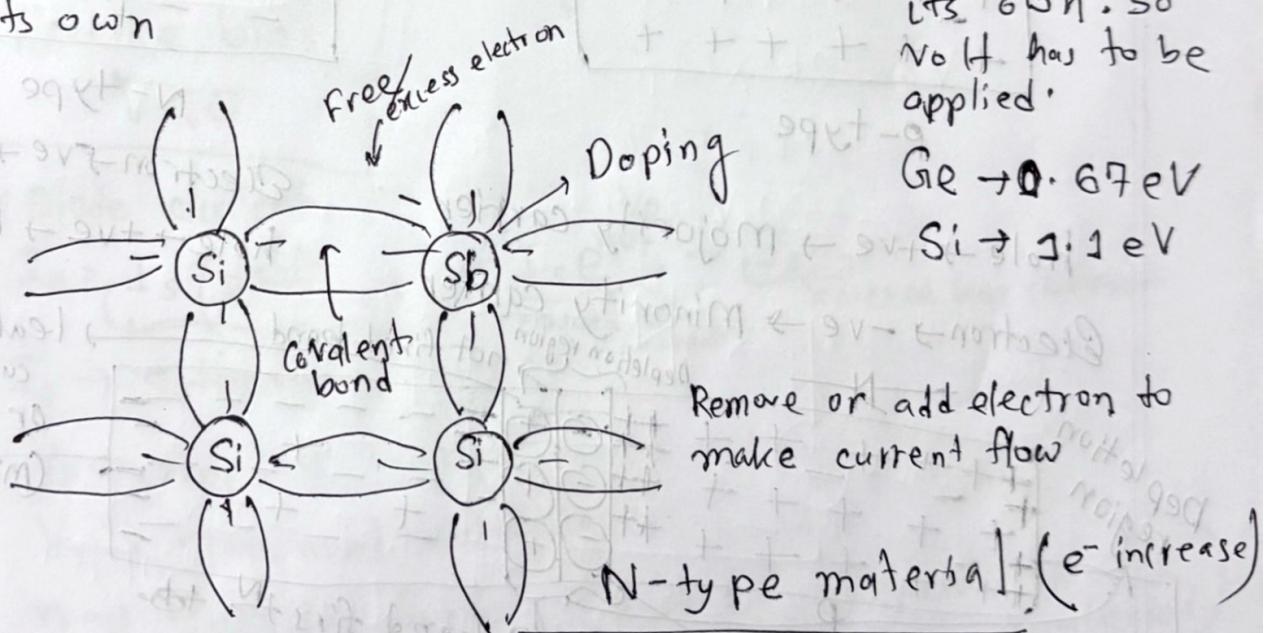


Remove or add electron to make current flow

\* Intrinsic material  $\rightarrow$  no impurity

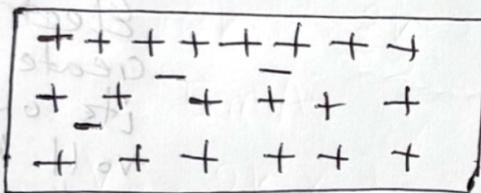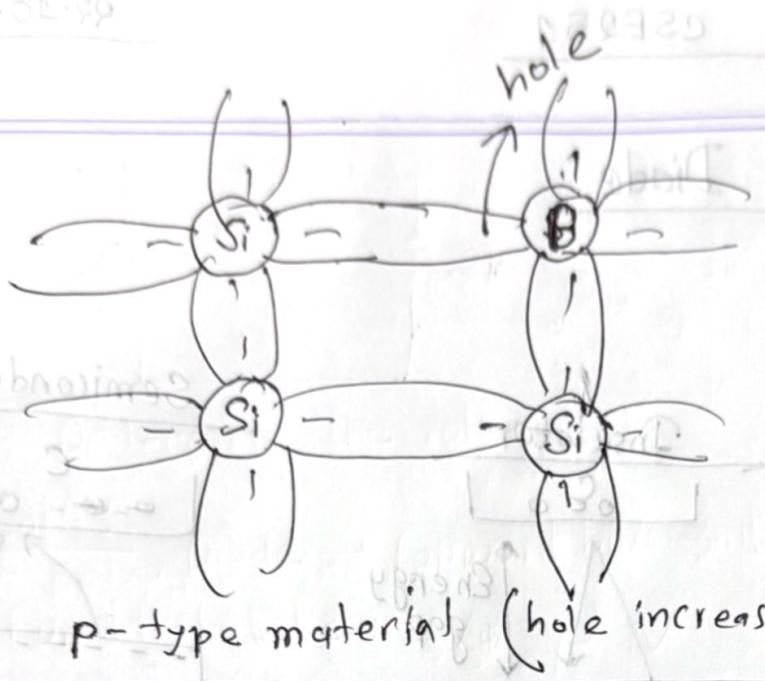\* Extrinsic material  $\rightarrow$  impure  $\rightarrow$  Dope





p-type

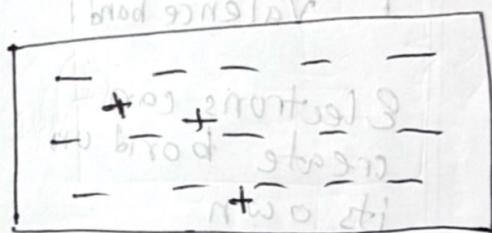

N-type

Electron → -ve → Majority  
hole → +ve → Minority

Electron → -ve → Minority carrier

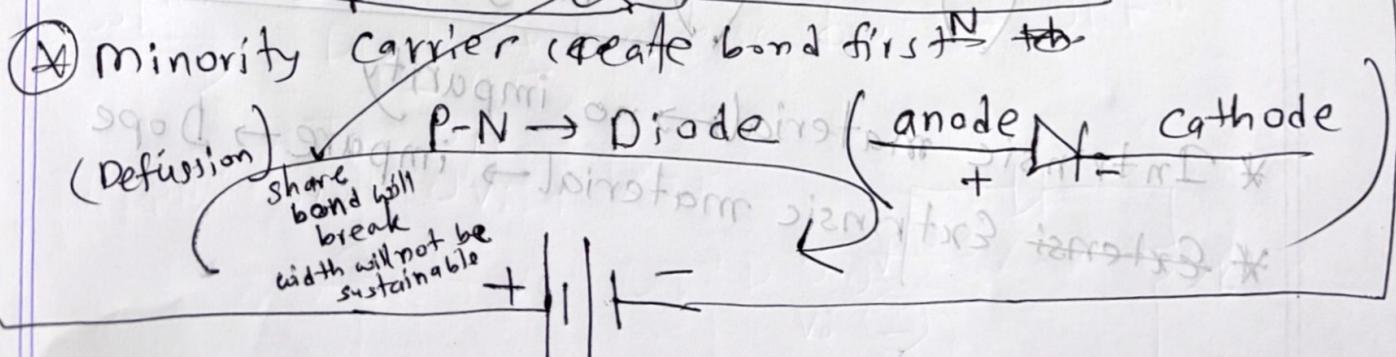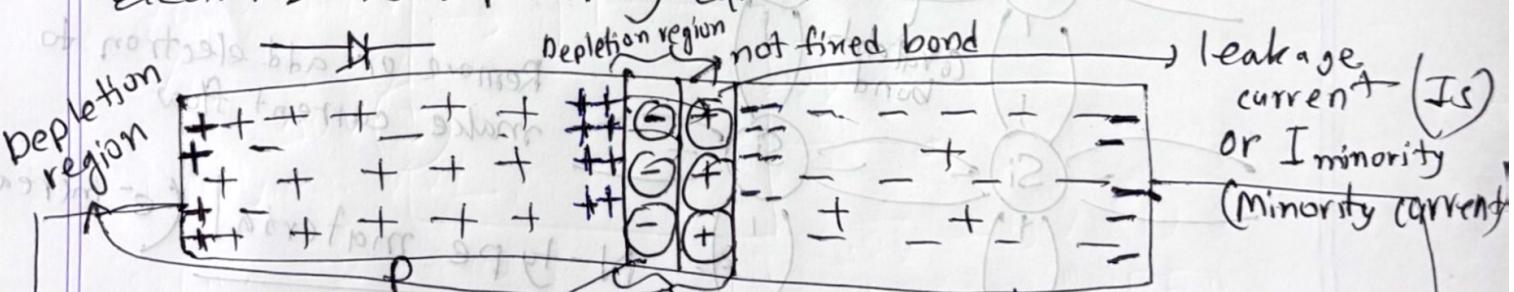

After defusion current will increase at an exponential rate

Cut-in Voltage - The voltage at which a diode's forward current increases rapidly


Cut-off voltage - The voltage at which a battery is considered fully discharged and further discharge could cause harm

$$I_D = I_{\text{majority}} - I_{\text{minority}}$$

Forward bias

$$V > 0$$

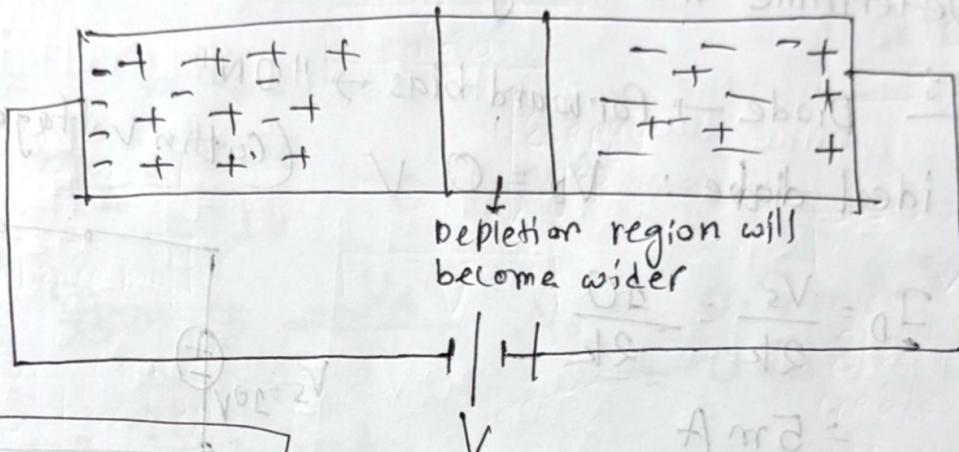If we remove the battery it will be back to its previous state. Then  $V = 0 \rightarrow \text{cutoff}$



Reverse bias

$$V < 0$$

\* Diode current:

$$I_D = I_s (e^{\frac{V_D}{nV_T}} - 1) = I_s e^{\frac{V_D}{nV_T}} - I_s$$

Forward bias current      Reverse bias current


$I_s \rightarrow$  Saturation current


$V_D \rightarrow$  Applied voltage

$V_T \rightarrow$  Thermal voltage

$n \rightarrow$  Ideality factor (1 or 2) (Depends on the material)

I-V characteristic curve

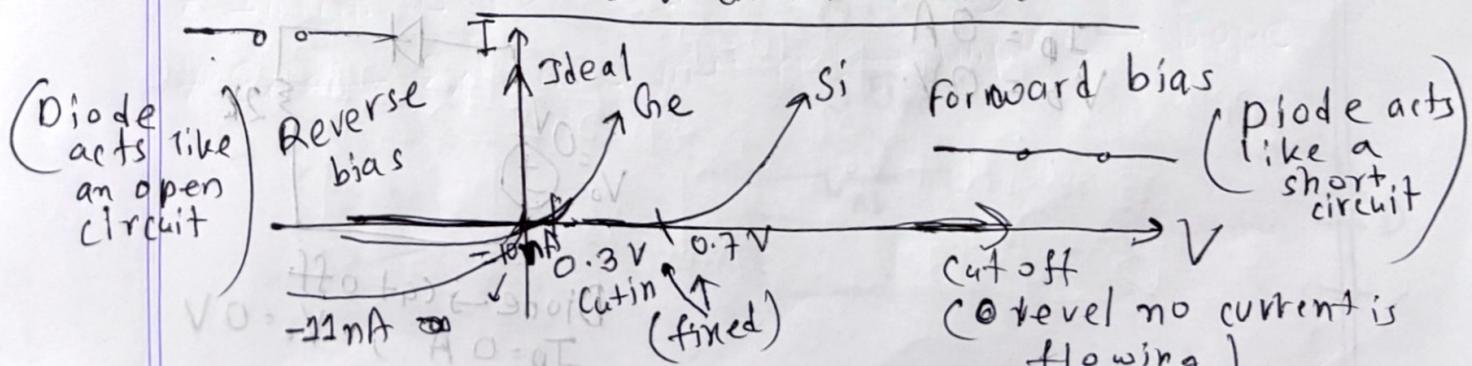

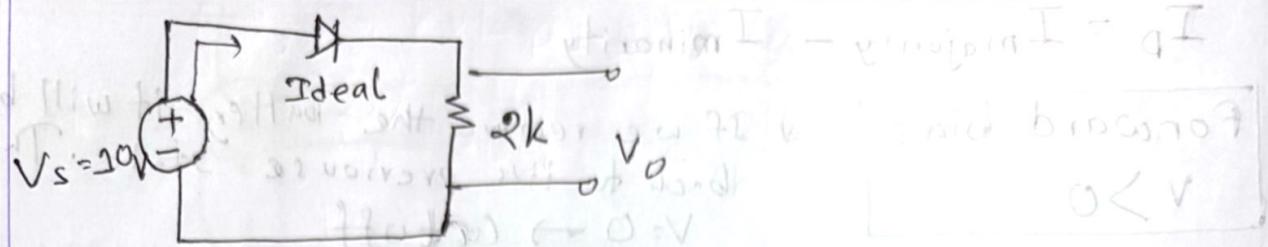

# Determine the voltage  $V_o$

Sol<sup>n</sup>: Diode  $\rightarrow$  forward bias  $\rightarrow$  "ON"

For ideal diode:  $V_D = 0 \text{ V}$  (cutting voltage  $= V_o$ )



$$I_D = \frac{V_s}{2k} = \frac{10}{2k} \text{ A}$$

$$\approx 5 \text{ mA}$$

$$V_o = 2k \times I_D$$

$$= 2k \times 5 \text{ mA}$$


$$= 10 \text{ V}$$

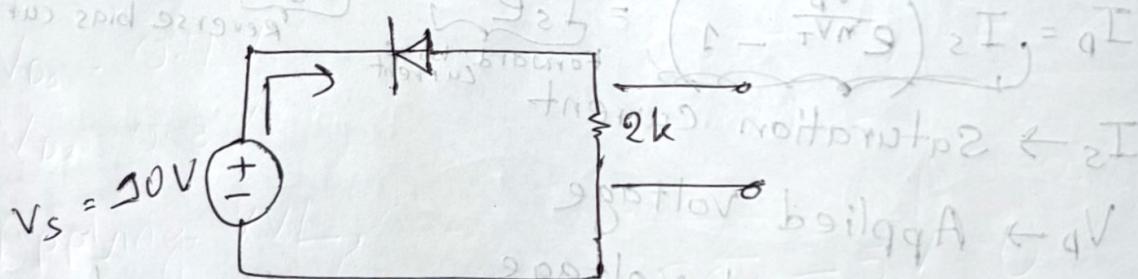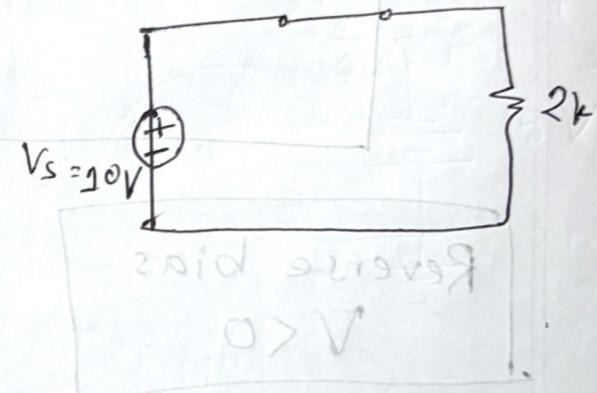


Sol<sup>n</sup>: Diode  $\rightarrow$  Reverse bias  $\rightarrow$  "OFF"

$$I_D = 0 \text{ A}$$

$$V_D = 0 \text{ V}$$

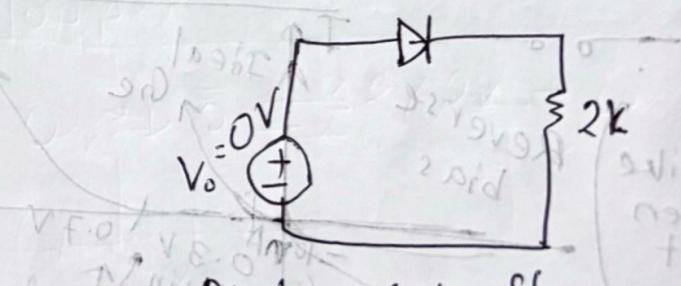

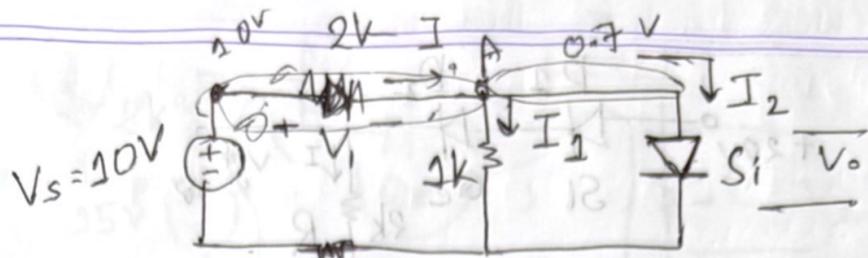Diode  $\rightarrow$  (at off)  
 $I_D = 0 \text{ A}$ ,  $V_o = 0 \text{ V}$



(Diode "ON")  
Forward bias

# Determine  $I$ ,  $I_1$ ,  $I_2$  and  $V_1$

Soln:

$$V_o = 0.7 \text{ V}$$

$$I_2 = \frac{0.7}{1k} = 0.7 \text{ mA}$$

$$\text{Diode } \text{D} \rightarrow V_s \quad V_o = 0.7 \text{ mA} \times 1 = 0.7 \text{ V}$$

$$I = \frac{10}{2k} = 5 \text{ mA}$$

$$\therefore I_1 = I - I_2 = 4.3 \text{ mA}$$

$$V_1 = 10 - 0.7 = 9.3 \text{ V}$$

Applying KVL,

$$-10 + V_1 + 0.7 = 0$$



$$V_1 = 9.3 \text{ V}$$


$$I = \frac{V_1}{2k} = \frac{9.3}{2k} = 4.65 \text{ mA}$$

Applying KCL at node A,

$$I = I_1 + I_2 \Rightarrow 4.65 = 0.7 + I_2$$

$$\therefore I_2 = 3.95 \text{ mA}$$

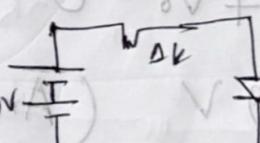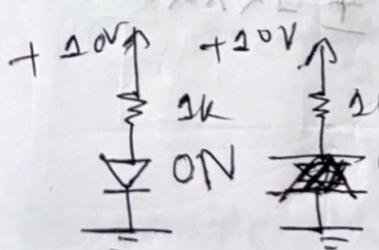


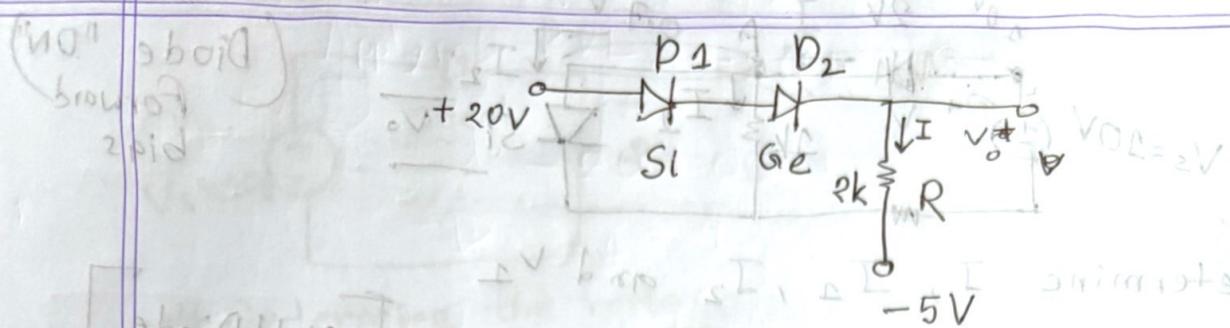

# Determine the current  $I$  and the voltage  $V_0$ .

$$I = \frac{-5}{2k} = -2.5 \text{ mA}$$

Applying KVL,

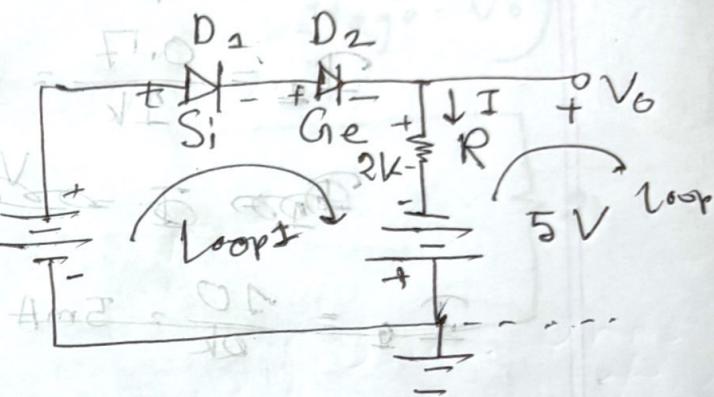

$D_1$  and  $D_2 \rightarrow$  forward bias  $\rightarrow$  "ON"

$$V_{D_1} = 0.7 \text{ V}$$

$$V_{D_2} = 0.3 \text{ V}$$

Applying KVL,


$$-20 + 0.7 + 0.3 + I \cdot 2k - 5V = 0$$

$$\Rightarrow I = 12 \text{ mA} \quad (\text{Ans})$$

Applying KVL, (loop 2)

$$5 - IR + V_0 = 0 \Rightarrow 5 - 12 \times 2k + V_0 = 0$$
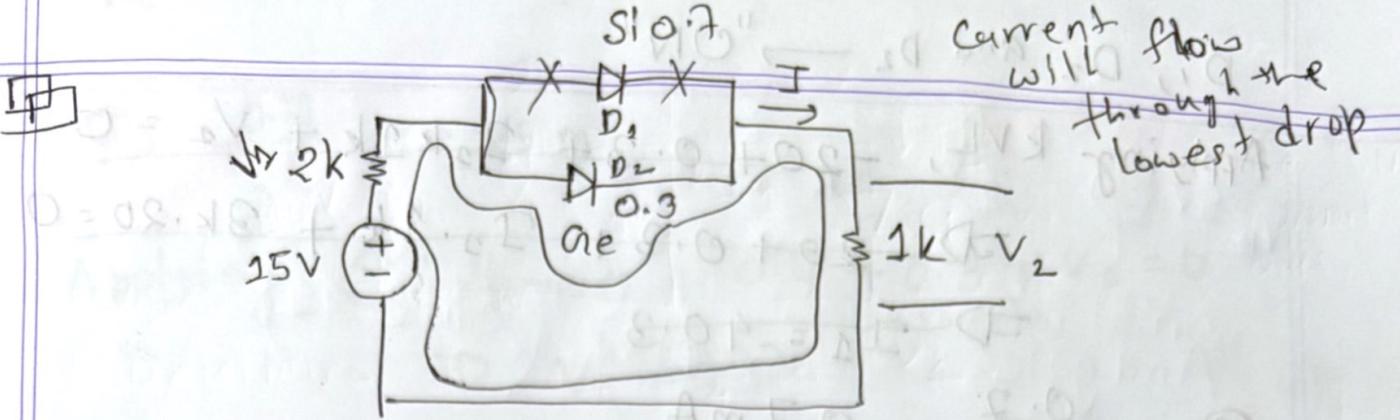
$$\Rightarrow V_0 = 19 \text{ V} \quad (\text{Ans})$$



# Determine  $I$  and the voltage  $V_1$  and  $V_2$

$D_1 \rightarrow \text{OFF}$

$D_2 \rightarrow \text{ON}$

Applying KVL,

$$-15 + 2k + 0.3 + I \cdot 1k = 0$$


$$\Rightarrow I \cdot 1k = -19.3$$

$$\therefore I = 4.9 \text{ mA} \\ \approx 5 \text{ mA}$$

Using Ohm's law,

$$V_1 = I \cdot 2k = 5 \text{ mA} \times 2k = 10 \text{ V} \quad (\text{Ans})$$
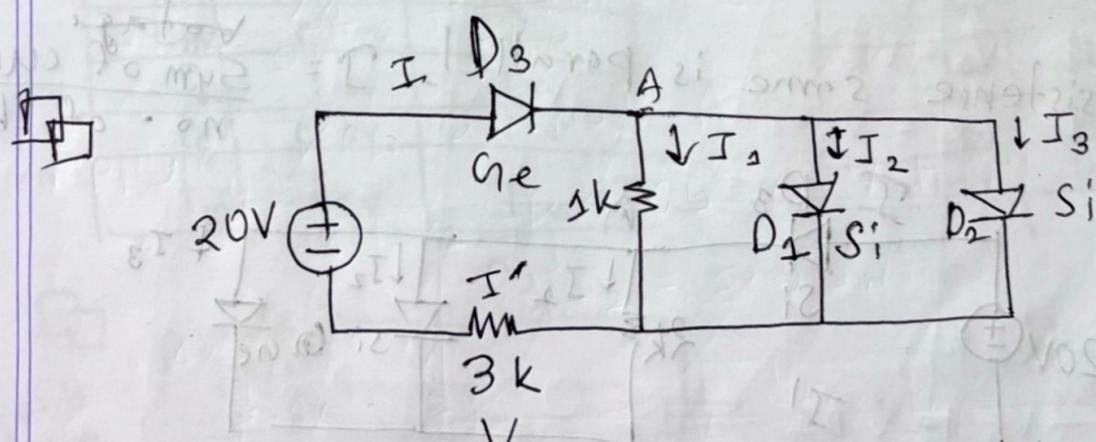
$$V_2 = I \cdot 1k = 5 \text{ mA} \times 1k = 5 \text{ V}$$



# Determine the voltage  $V_1$  and the currents  $I_1, I_2, I_3$

$D_1, D_2$  and  $D_3 \rightarrow \text{"ON"}$

Applying KVL,  $-20 + 0.3 + I_1 \cdot 1k + V_2 = 0$

$$\Rightarrow -20 + 0.3 + I_1 \cdot 1k + 3k \cdot 20 = 0$$

$$\Rightarrow I_1 = -40.3$$

$$I_1 = \frac{0.7}{1k} = 0.7 \text{ mA}$$

Now Applying KVL,

$$-20 + 0.3 + 0.7 + V_2 = 0$$

$$\Rightarrow V_2 = 19 \text{ V}$$

$$\therefore I' = \frac{V_2}{3k} = 6.33 \text{ mA} = I$$

Applying KCL,  $I = I_1 + I_2 + I_3$

$$\Rightarrow I_2 + I_3 = I - I_1$$


$$= (6.33 - 0.7) \text{ mA}$$

$$= 5.6 \text{ mA}$$

$$I_2 = I_3 = \frac{5.6}{2} \text{ mA} = 2.8 \text{ mA}$$

If resistance same is parallel,  $I = \frac{\text{Voltage}}{\text{no. of branches}}$

Symbol of current

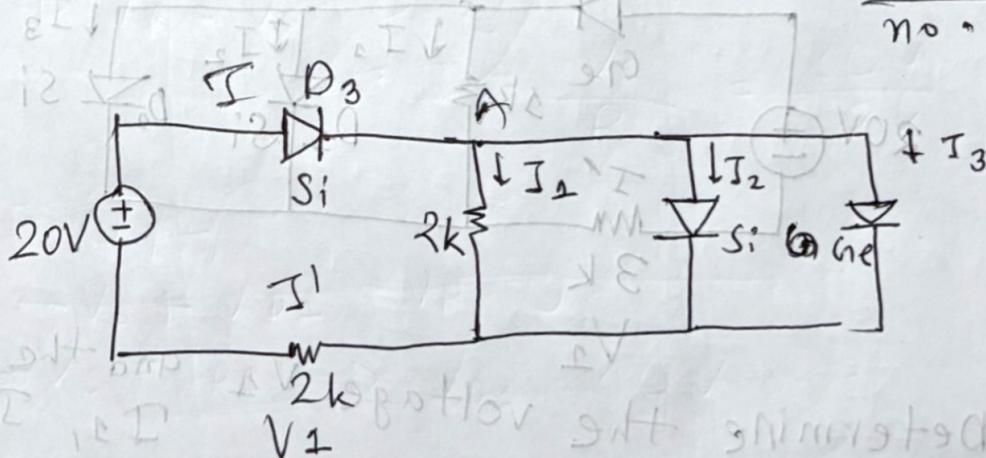

Forward bias  $\rightarrow$  short circuit  
 Reversed bias  $\rightarrow$  open circuit

$$I_1 = \frac{0.3}{2k} = 0.15 \text{ mA}$$

Applying KVL,  $-20 + 0.7 + 0.3 + V_s = 0$   
 $\Rightarrow V_s = 19 \text{ V}$

$$I' = 9.5 \text{ mA} = I$$

Here,  $I_2 = 0 \text{ mA}$

Applying KCL at A,  $I = I_1 + I_2 + I_3$

$$\Rightarrow I_3 = I - I_1 - I_2$$

$$= 9.35 \text{ mA}$$



Logic "0"  $\rightarrow$  0V


Logic "1"  $\rightarrow$  5V

OR gate

| A   | B   | Output |
|-----|-----|--------|
| 0ov | 0ov | 0ov    |
| 0ov | 1sv | 1sv    |
| 1sv | 0ov | 1sv    |
| 1sv | 1sv | 1sv    |

AND gate

| A   | B   | Output |
|-----|-----|--------|
| 0ov | 0ov | 0ov    |
| 0ov | 1sv | 0ov    |
| 1sv | 0ov | 0ov    |
| 1sv | 1sv | 1sv    |

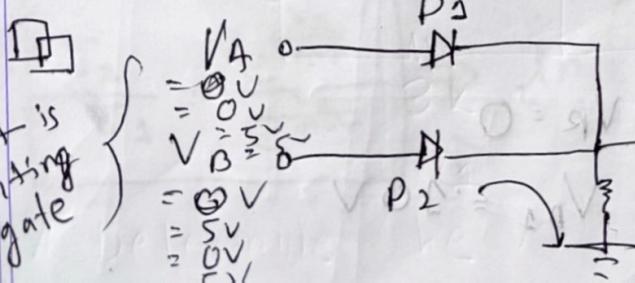


$$\begin{aligned}
 V_o &= 0 \text{ V} \\
 &= 5 \text{ V} \\
 &= 5 \text{ V} \\
 &= 5 \text{ V}
 \end{aligned}$$


$D_1$  and  $D_2$   
 ideal diode

$$V_{D1} \text{ and } V_{D2} = 0 \text{ V}$$

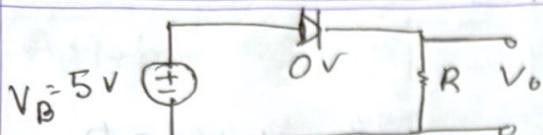① Maximum current will flow through diode if its short time ratings & rated voltage



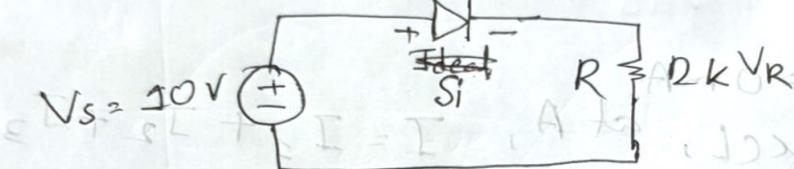② Circuit representing And gate  $\rightarrow$  HW (Slide 12)



# Draw the load line for the following circuit and determine the Q point.

Sol<sup>n</sup>:

Applying KVL,

$$-V_s + V_{D1} + V_R = 0$$

*(Chord of Diode Let)*


$$V_{D1} = 0V$$

$$-V_s + R V_R = 0$$

$$\Rightarrow V_s = V_R$$

$$\Rightarrow V_R = V_s \Rightarrow I \times R = V_s$$
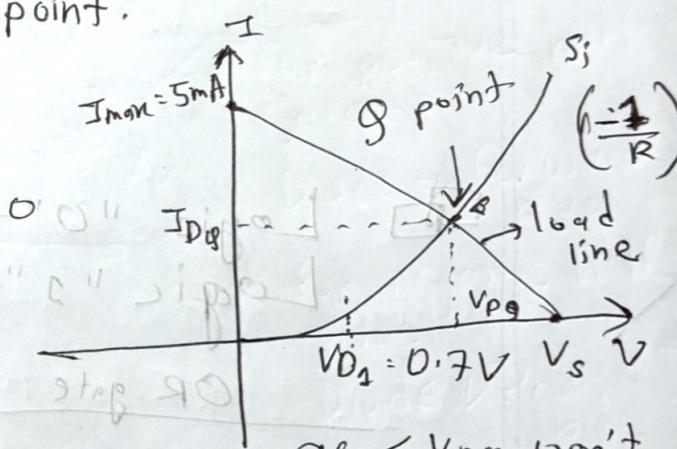
$$\therefore I = \frac{V_s}{R} = \frac{10V}{2k} = 5mA$$




(Open diode)

Let,  $I = 0A$ ,

$$-V_s + V_{D2} + V_R = 0$$

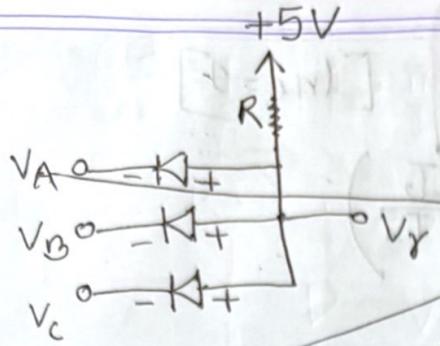
$$\Rightarrow V_s = V_{D2} \Rightarrow V_{D2} = 10V$$



Current will flow through the diode with the lowest voltage.  
So if any of these is zero then the output will be zero, which represents an AND gate.

CSE251

29.10.24

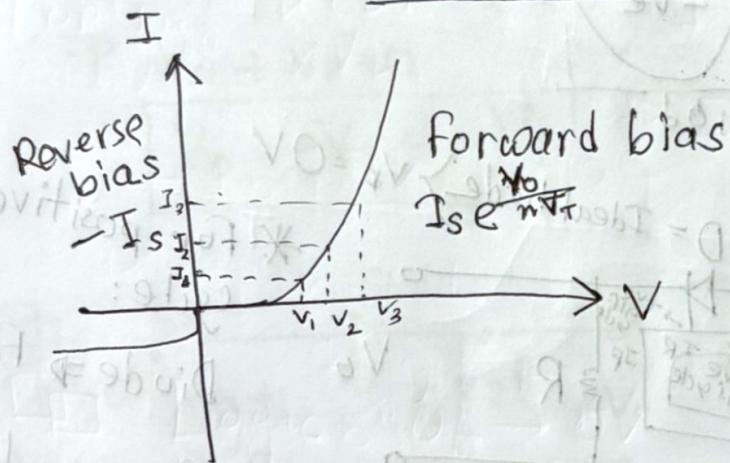

$$I \rightarrow \text{Saturated current}$$

$$V_T \rightarrow \text{Thermal voltage}$$

$$I = I_s \left( e^{\frac{V_o}{nV_T}} - 1 \right)$$

$$= I_s e^{\frac{V_o}{nV_T}} (-I_s)$$

Forward bias      Reverse bias

$$V_T = \text{Thermal voltage}$$

$$= \frac{kT}{q}$$

(25.3 ~ 26 mV) difference  
(use 26 for easy calculation)

$$\text{Let, } n=1, \quad I_1 = I_s e^{\frac{V_1}{nV_T}}$$

$$I_2 = I_s e^{\frac{V_2}{nV_T}}$$



$$\frac{I_2}{I_1} = \frac{e^{\frac{V_2}{nV_T}}}{e^{\frac{V_1}{nV_T}}}$$

$$\Rightarrow \ln \left( \frac{I_2}{I_1} \right) = \ln e^{\frac{(V_2 - V_1)}{V_T}}$$

$$\Rightarrow \ln \left( \frac{I_2}{I_1} \right) = \frac{(V_2 - V_1)}{V_T} \ln e$$

$$\Rightarrow V_2 - V_1 = V_T \ln \left( \frac{I_2}{I_1} \right) \quad [lne = 1]$$
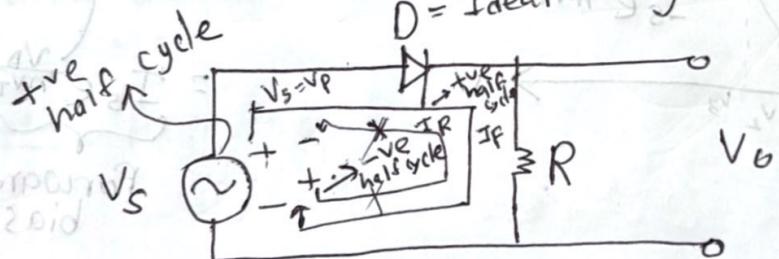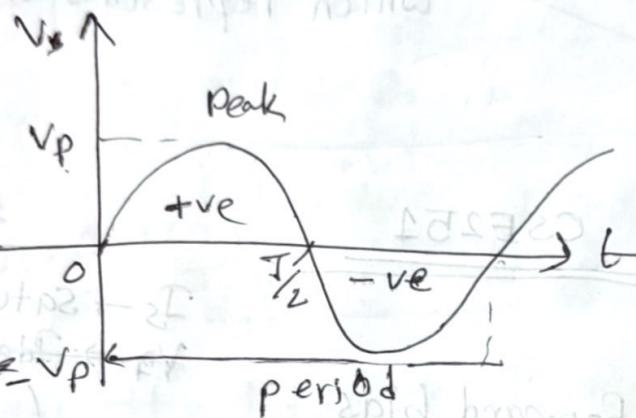
$$V_2 - V_1 = 2.3 V_T \log \left( \frac{I_2}{I_1} \right)$$




\* for positive half cycle:

Diode  $\Rightarrow$  Forward bias

\* for negative half cycle:

Diode  $\Rightarrow$  Reverse bias

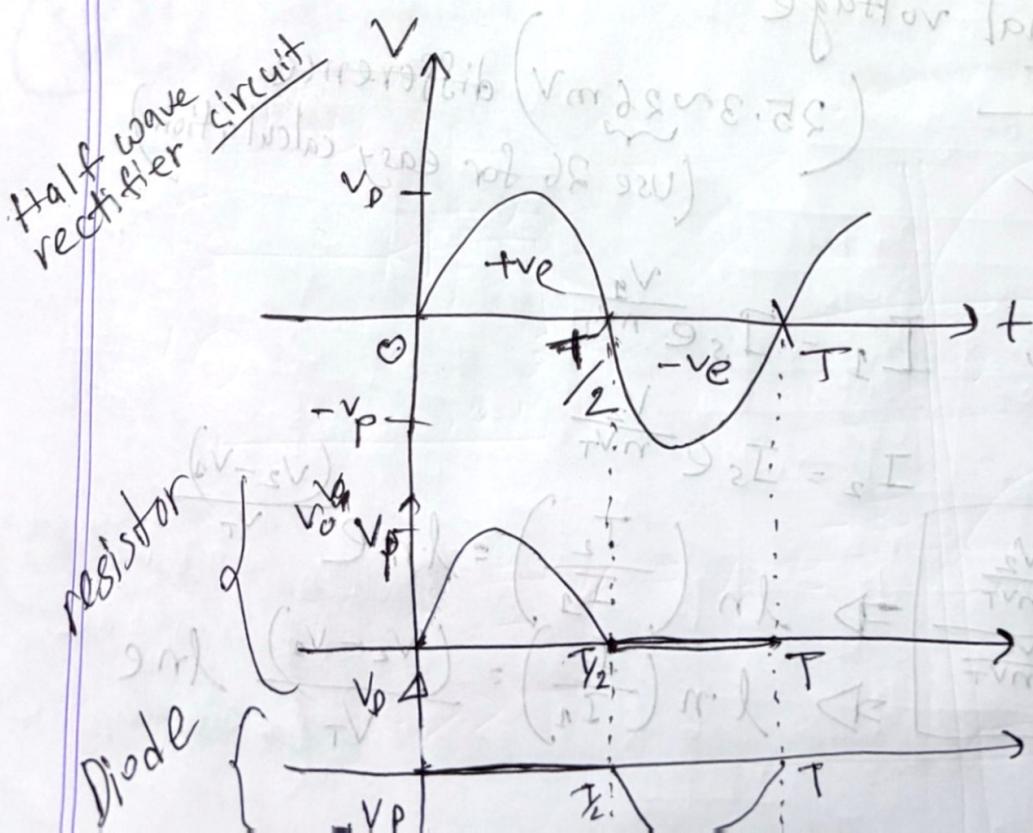

For +ve half cycle:

Applying KVL,

$$-V_p + V_D + V_o = 0$$

$$\Rightarrow V_o = V_p - V_D \quad [V_D = 0 \text{ for ideal diode}]$$

$$\therefore \boxed{V_o = V_p}$$

(sketch wave form)


For -ve half cycle:

$$V_s + V_D + V_o = 0$$

$$\Rightarrow V_s + V_D + I_R R = 0 \quad [I_R = 0 \text{ for reverse bias}]$$

$$\Rightarrow V_s + V_D = 0$$

$$\therefore \boxed{V_D = -V_s = -V_p}$$

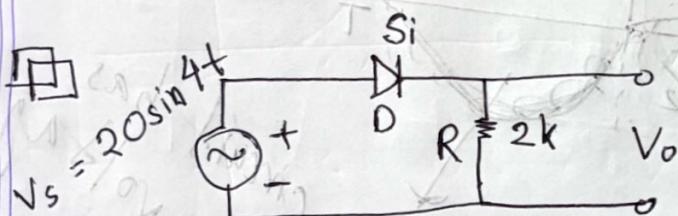

\* Determine the output voltage  $V_o$  and sketch the wave form across the output resistance and diode.

$$V_s = 20\sin 4t = \underline{20\angle 0^\circ}$$




Only amplitude in electronics

$$\Rightarrow -V_s + V_D + V_o = 0$$



$$\Rightarrow -V_s + \cancel{V_D} + 0.7 + V_o = 0$$

$$\Rightarrow -20\sin 4t + 0.7 + V_o = 0$$

$$\therefore V_o = 19.3 \text{ V}$$

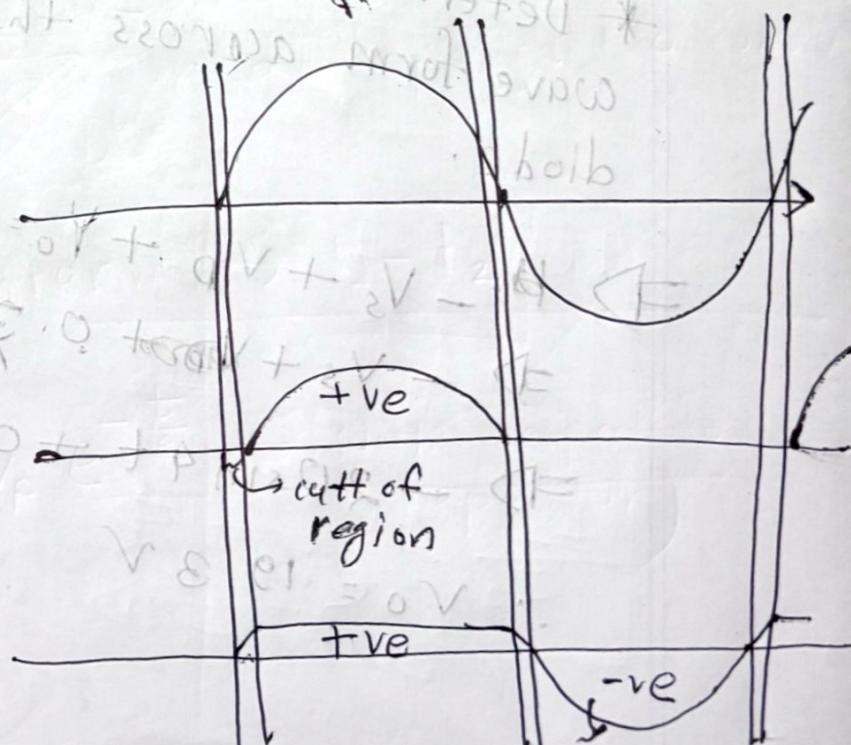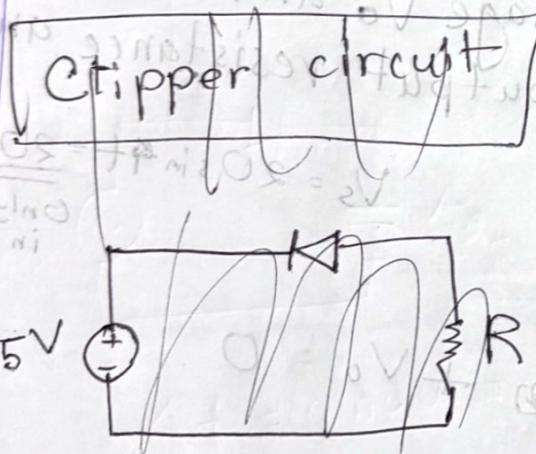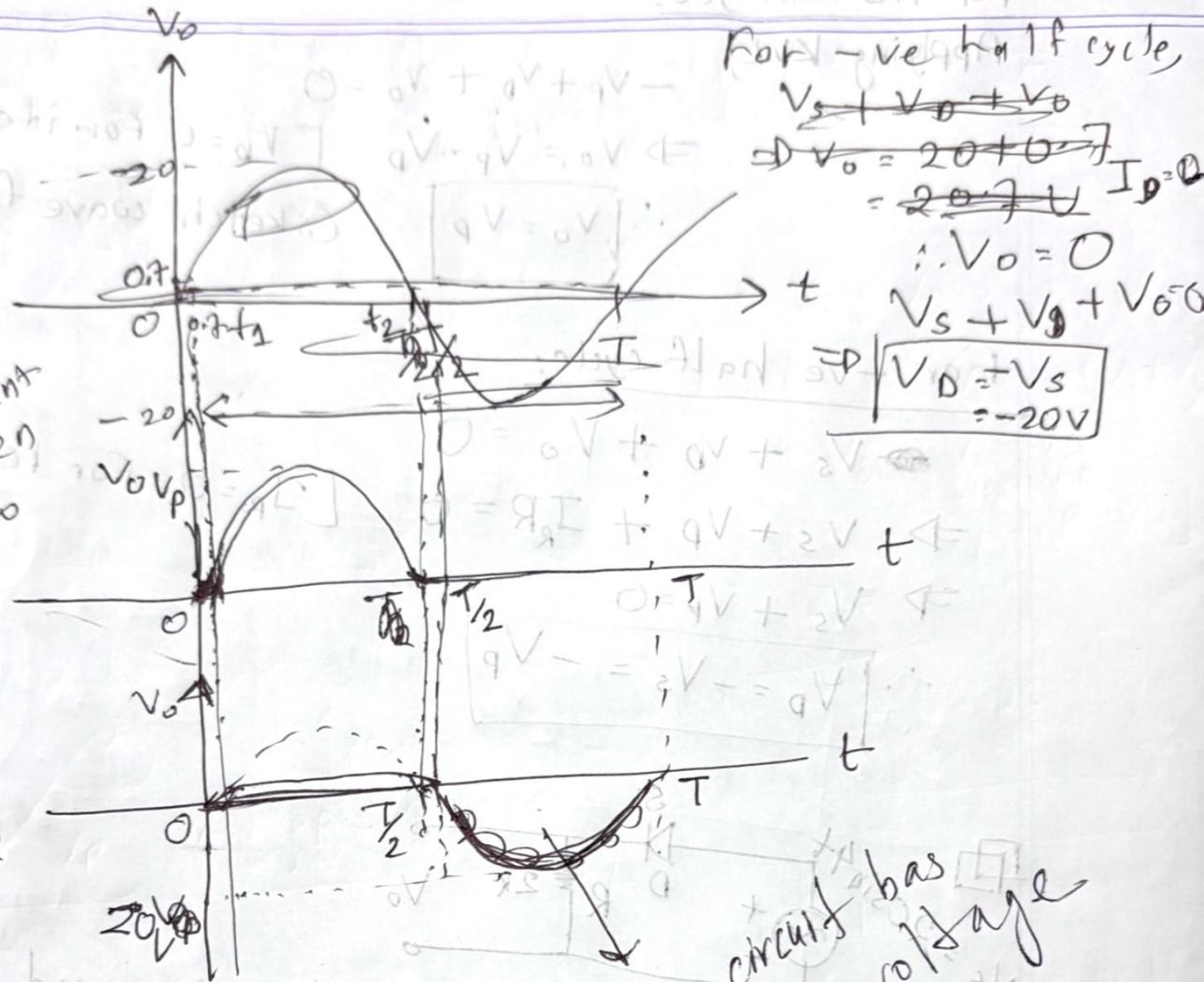

## Half wave rectifier circuit

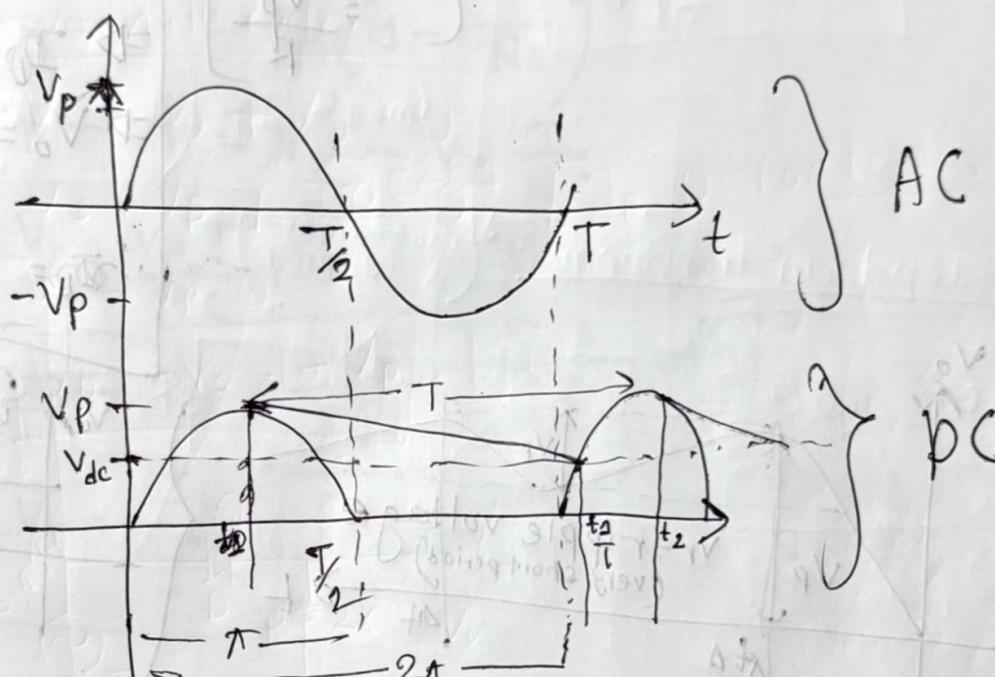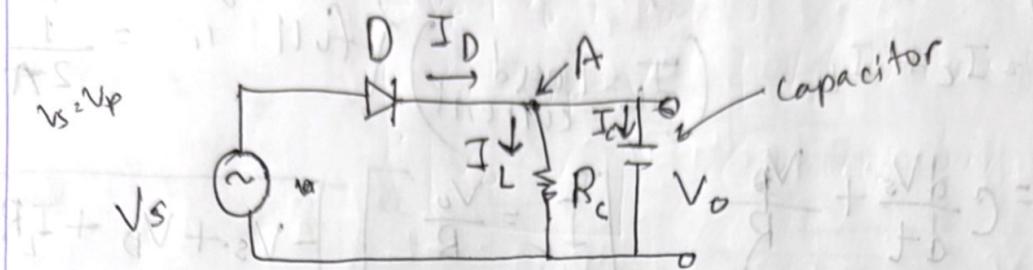


$$V_{dc} = 0.318 (V_p - V_D)$$

$RC = \tau$  = time constant

capacitor individually

$$V_C = e^{-\frac{t}{RC}} + V_0$$

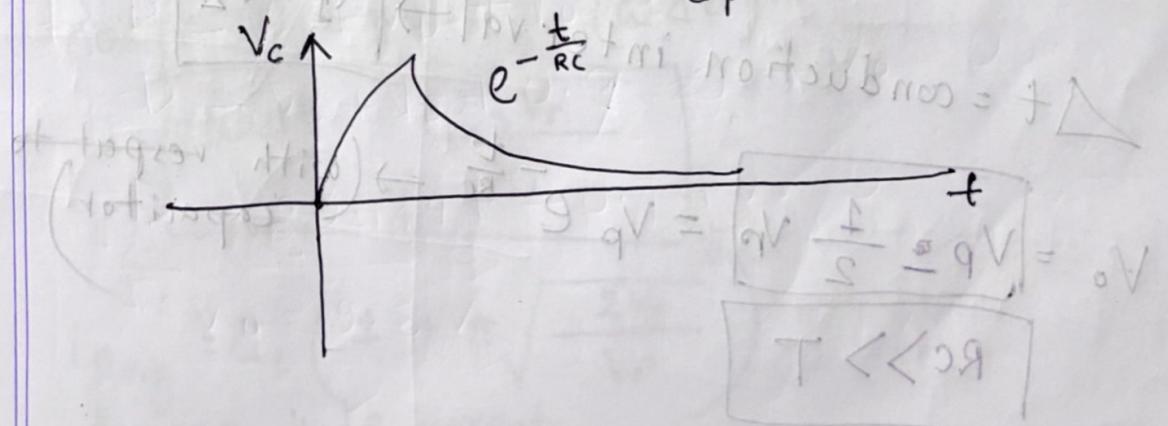

Applying KCL at node A,

$$I_D = I_C + I_L \quad (I_L = \text{Load current})$$

$$= C \frac{dV_S}{dt} + \frac{V_P}{R}$$

half cycle  $\Rightarrow \frac{1}{\pi}$

full "  $= \frac{1}{2\pi}$


$$\left[ I_L = \frac{V_o}{R} = \frac{V_P}{R} \right]$$

$$-V_S + V_D + I_L R = 0$$


$$\Rightarrow I_D \cdot V_D = -(V_S + V_D)$$

$$\therefore V_o = V_S - V_D = V_P - V_D \quad [I_L R = V_o]$$

$$\therefore I_D =$$

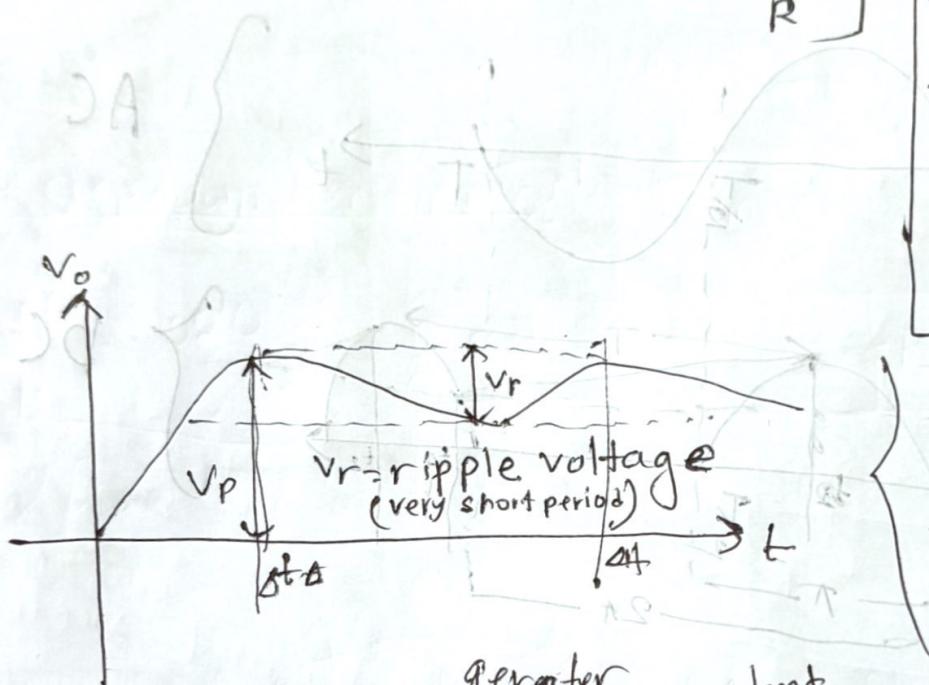

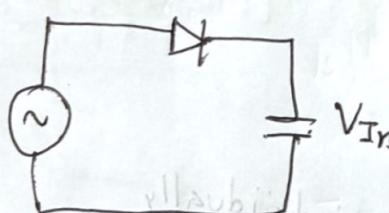The DC current was supposed to be like this



- ① ~~less time~~ constant more straightened line
- ② Capacitor is applied to convert in DC

$\Delta t$  = conduction interval  $\rightarrow [t_1 - t_2]$

$$V_o = \boxed{V_p \pm \frac{1}{2} V_r} = V_p e^{-\frac{t}{RC}} \rightarrow (\text{with respect to capacitor})$$

$$\boxed{RC \gg T}$$

$$\therefore V_o = V_p \cdot e^{-\frac{T}{RC}} \quad (\text{since } RC \gg T \text{ we can replace } t \text{ by } T)$$

$$\Rightarrow V_o = V_p - V_r \quad \left[ e^{-\frac{T}{RC}} \approx 1 - \frac{T}{RC} \right]$$

$$\Rightarrow V_p - V_r = V_p \left( 1 - \frac{T}{RC} \right)$$

$$\Rightarrow V_p - V_r = V_p - V_p \frac{T}{RC}$$

$$\Rightarrow V_r = \frac{V_p T}{RC}$$

$$\Rightarrow V_r = \frac{V_p}{f \cdot RC} \quad \left[ f = \frac{1}{T} \right]$$

$$\Rightarrow V_r = \frac{I_L}{f C} \quad \left[ I_L = \frac{V_p}{R} \right]$$

Ripple depends on  $RC$

$$V_s = V_p \cos(\omega \Delta t)$$

$$\omega = \text{Angular frequency} = 2\pi f = 2\pi \frac{1}{T}$$

$\Delta t$  = conduction Interval

$$\cos(\omega \Delta t) = 1 - \frac{1}{2} (\omega \Delta t)^2$$

$$\omega \Delta t = \sqrt{\frac{2V_r}{V_p}}$$

$$i_{D\text{avg}} = I_L \left( 1 + \pi \sqrt{\frac{2V_p}{V_r}} \right)$$

Average diode current

$$i_{D\max} = I_L \left( 1 + 2\pi \sqrt{\frac{V_p}{V_r}} \right)$$

maximum diode current


For full wave rectifier,

$$V_r = \frac{V_p}{2fRC}$$


$$i_{D\text{avg}} = I_L \left( 1 + \pi \sqrt{\frac{V_p}{2V_r}} \right)$$

$$i_{\max} = I_L \left( 1 + 2\pi \sqrt{\frac{V_p}{2V_r}} \right)$$

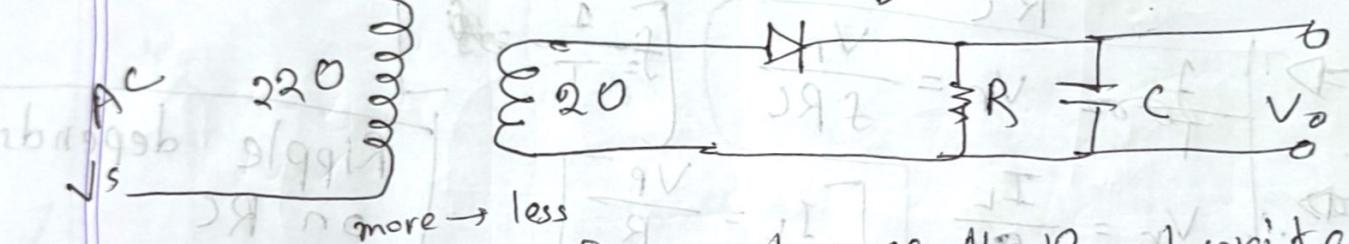Step down transformer (also known as X former)




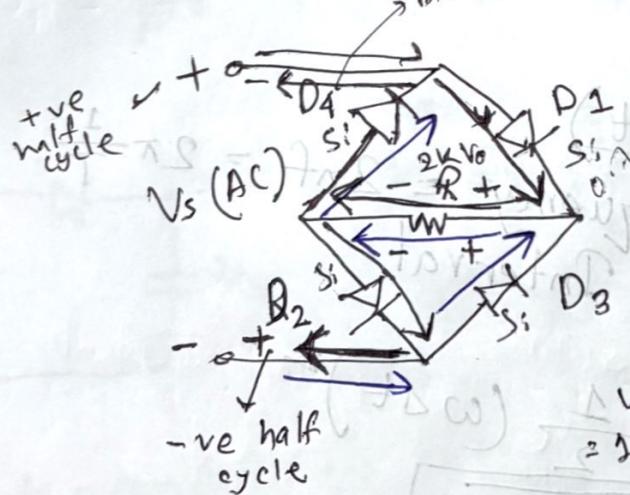Draw the wave form across the R and write the wave equation



Blue → for negative half cycle

Black → for positive half cycle

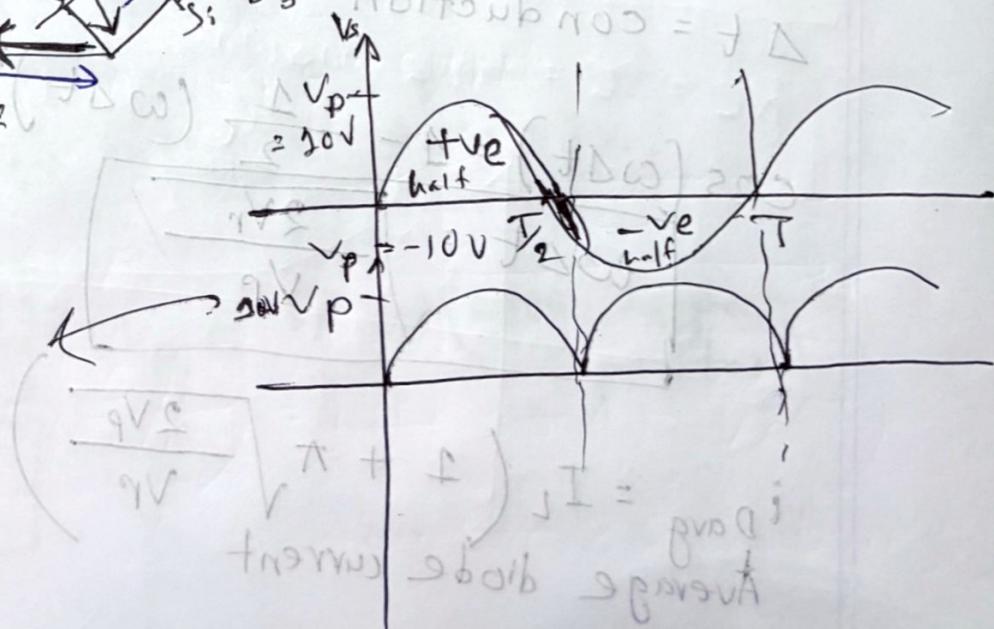

full wave  
Rectifier  
circuit

$$V_{dc} = 0.318 (V_p - V_D) \rightarrow \text{half}$$

$$V_{dc} = 2 \times 0.318 (V_p + 2V_D) \rightarrow \text{Full} \quad \text{(Current flows through 2 diodes)}$$

For +ve half cycle,

$D_1$  and  $D_2 \rightarrow \text{ON}$  and  $D_3$  and  $D_4 \rightarrow \text{OFF}$

For -ve half cycle,

$D_3$  and  $D_4 \rightarrow \text{ON}$  and  $D_1$  and  $D_2 \rightarrow \text{OFF}$

# Determine  $V_o$

Applying KVL, (for +ve half cycle)


$$-V_s + V_{D2} + V_{D1} + V_o = 0$$

$$\Rightarrow -10 + 0.7 + V_o + 0.7 = 0$$

$$\Rightarrow V_o = 8.6 \text{ V}$$


Similarly

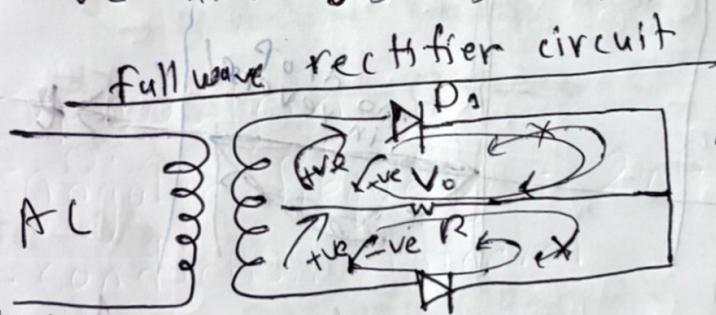
For -ve half cycle,  $V_o = 8.6 \text{ V}$




For this,
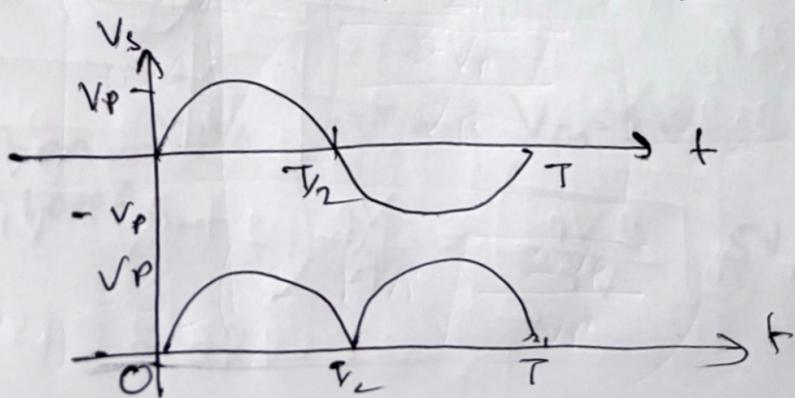
$$V_{dc} = (2 \times 0.318) (V_p - V_D) \quad [1 \text{ diode used}]$$



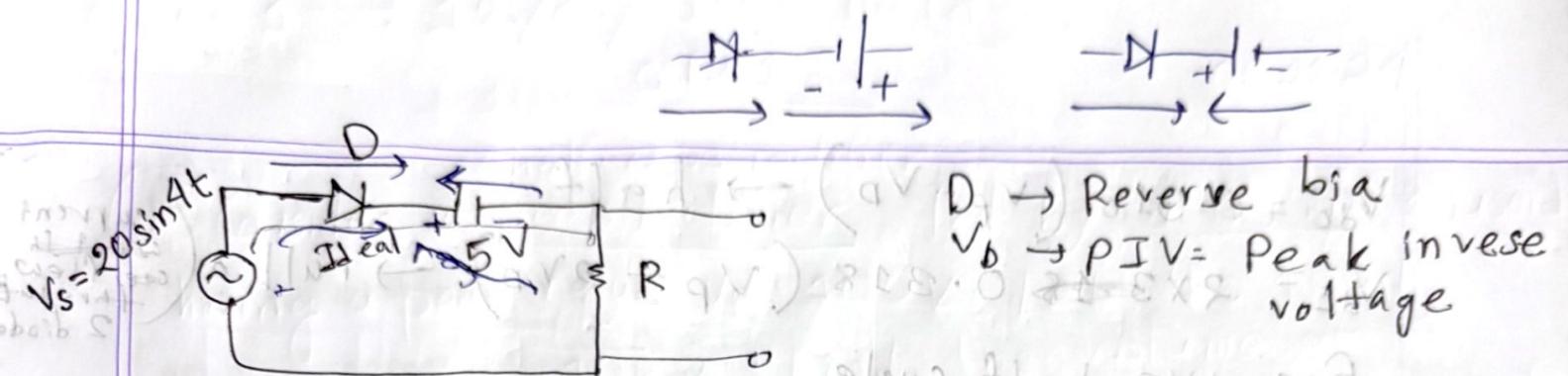


Draw the output waveform:

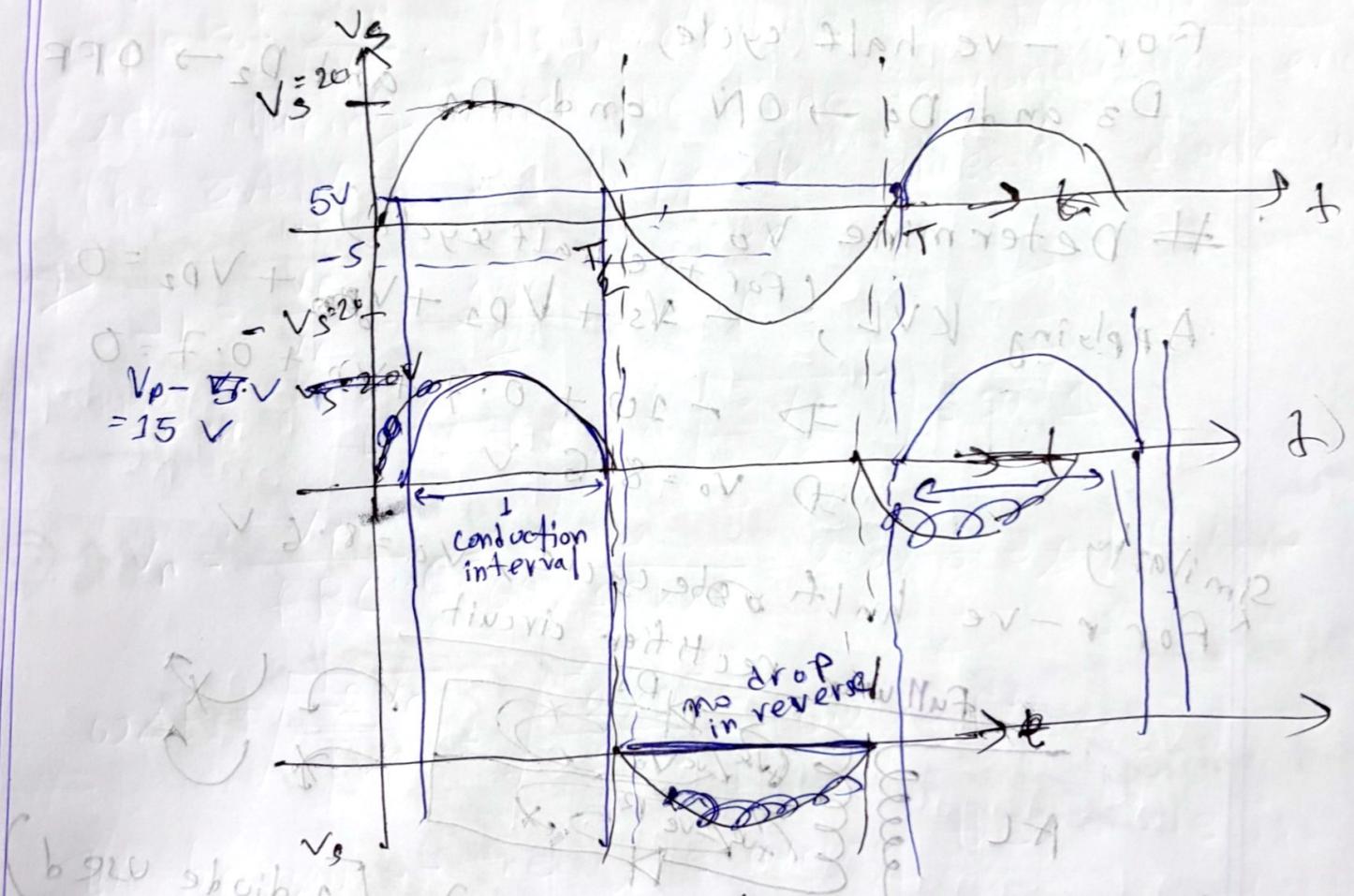

Only consider the direction of current

Ques

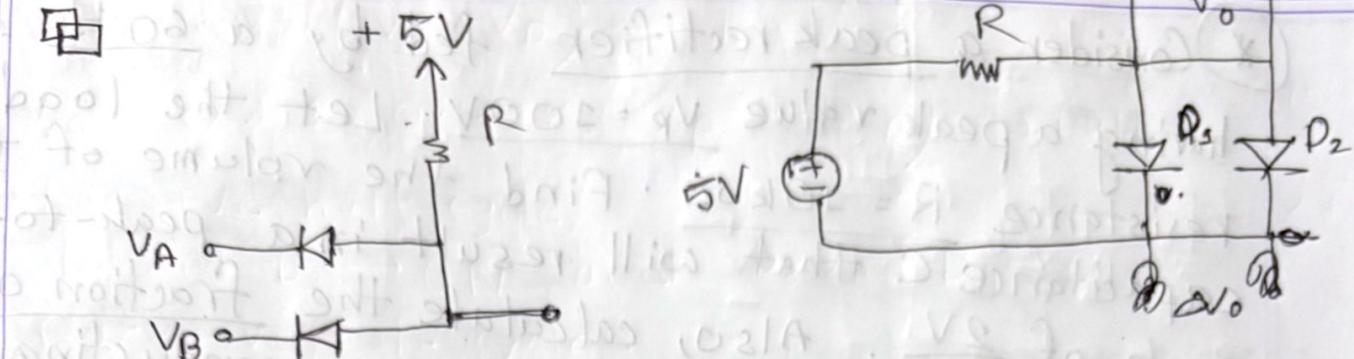


\* When,  $V_{D1} = 0V$  and  $V_{D2} = 0V$

Applying KVL in Loop 1,

$$-V_{D2} + V_{D2} + V_o = 0$$

$$\Rightarrow -0 + 0 + V_o = 0$$

$$\therefore V_o = 0$$

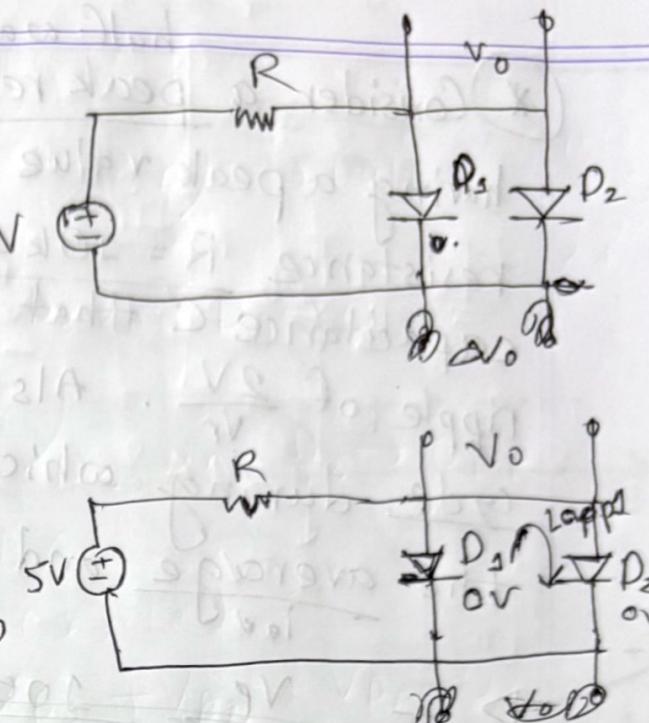

\* When  $V_{D1} = 1V$  and  $V_{D2} = 0V$


Applying KVL,

$$-5 + V + \cancel{V_{D2}} = 0$$

$$\Rightarrow -5 + V + 0 = 0$$


$$\therefore V = 5V$$

Here  $V_o = V_{D2} = 0V$

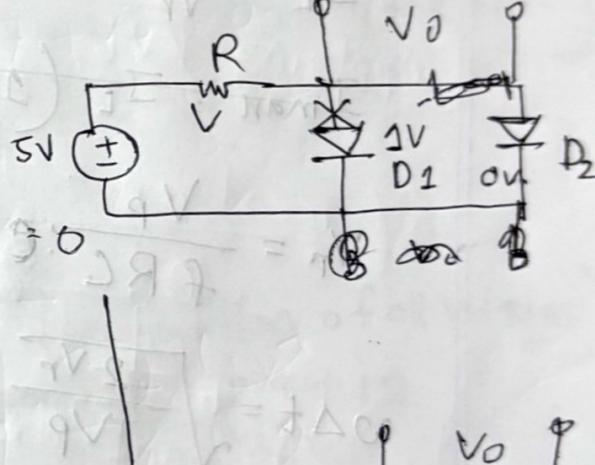


\* When  $V_{D1} = 0V$  and  $V_{D2} = 1V$

so Here  $V_o = V_{D1} = 0V$

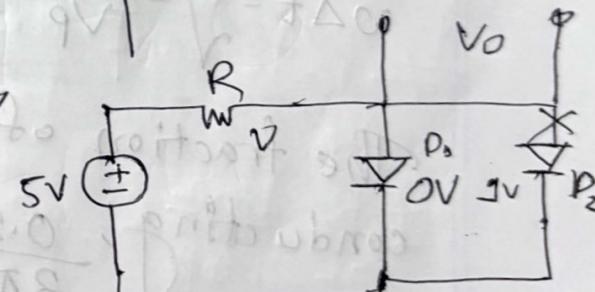

\* When  $V_{D1} = 1V$  and  $V_{D2} = 1V$

for Loop 1,

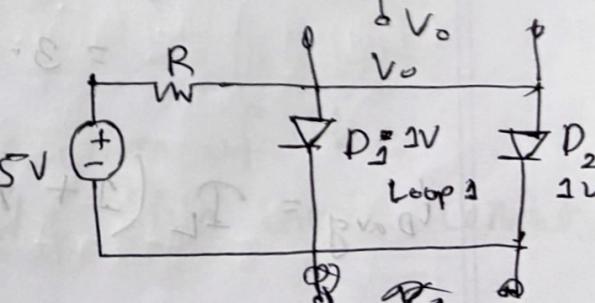

## half wave rectifier

f

- \* Consider a peak rectifier fed by a 60 Hz sinusoid having a peak value  $V_p = 100V$ . Let the load resistance  $R = 10k\Omega$ . Find the volume of ~~to~~ capacitance  $C$  that will result in a peak-to-peak ripple of  $\frac{2V}{V_r}$ . Also, calculate the fraction of the cycle during which the diode is conducting and the average and the peak values of diode current.

$$\Rightarrow I_L = \frac{V_p}{V_r} = \frac{100}{2} = 50A$$

$$I_{max} = I_L \left( 1 + 2 \pi \sqrt{\frac{V_p}{V_r}} \right) = 50 \left( 1 + 2 \pi \sqrt{\frac{100}{2}} \right) = 50 \left( 1 + 2 \pi \sqrt{50} \right)$$


$$V_r = \frac{V_p}{f R C} \therefore C = \frac{100}{60 \times 10k \times 2} = 8.3333 \mu F$$

$$\omega \Delta t = \sqrt{\frac{2 V_r}{V_p}} = \sqrt{\frac{2 \times 2}{100}} = 0.2 \text{ rad}$$

The fraction of the cycle during the diode is conducting

$$\frac{0.2}{2\pi} \times 100\% =$$

$$= 3.18\%$$

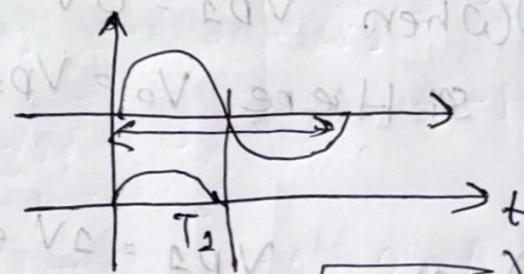


$$i_D^{avg} = I_L \left( 1 + \pi \sqrt{\frac{2 V_p}{V_r}} \right) = \frac{V_p}{R} \left( 1 + \pi \sqrt{\frac{2 V_p}{V_r}} \right) = 85.42832415 \text{ mA}$$

Reverse bias voltage = summation of all voltages

$$i_{D\max} = I_L \left( 1 + 2\pi \sqrt{\frac{V_p}{V_r}} \right) = 454.288 \text{ mA}$$


$$= 638.318 \text{ mA}$$

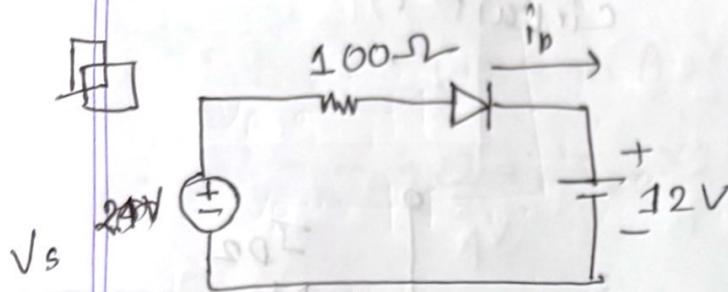

$$2\theta = ?$$

$i_D = ?$  (forward)

$V_p = ?$  (reverse)

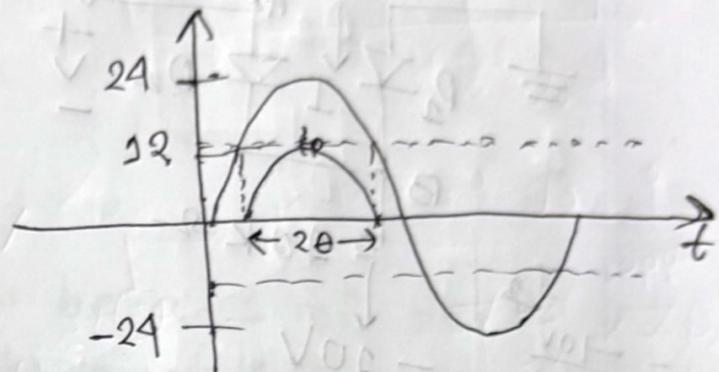

Considering ideal diode

$$\text{Applying KVL, } -V_s + 100i_p + V_p + 12 = 0$$

$$\Rightarrow -24 + 100i_p + 0 + 12 = 0$$

$$\Rightarrow i_p = 0.12 = I_L$$

reverse bias  $\rightarrow$  max current

(summation of all voltages)

$$\text{Reverse bias voltage, } V_D = \cancel{V_s} + \cancel{V_p} = 24 + 12$$

$$\cancel{-V_s} - 12 - V_D + 100i_p = 0$$

= PIV

$$@ 24 \cos \theta = 12$$


$$\Rightarrow \theta = \cos^{-1} \left( \frac{12}{24} \right) = 60^\circ$$

$\therefore 2\theta = 2 \times 60^\circ = 120^\circ \rightarrow$  fraction of the cycle the diode conducts


To understand what is a Zener diode circuit

Question 11:

+10V

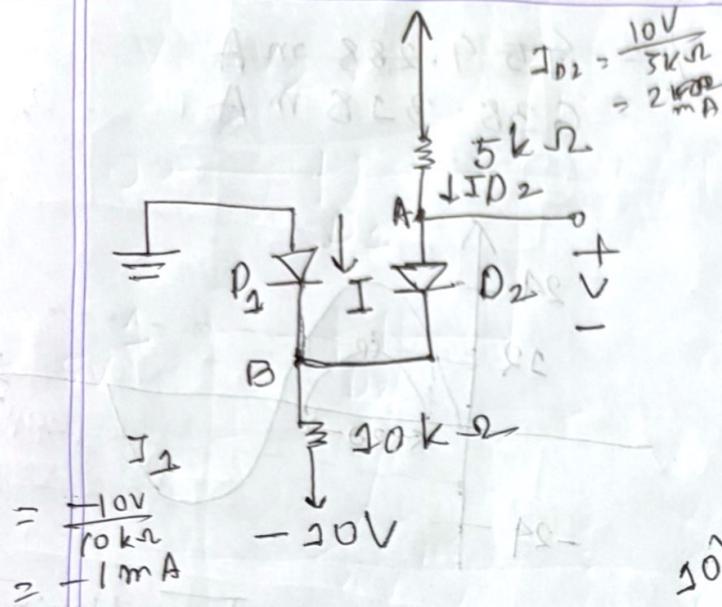


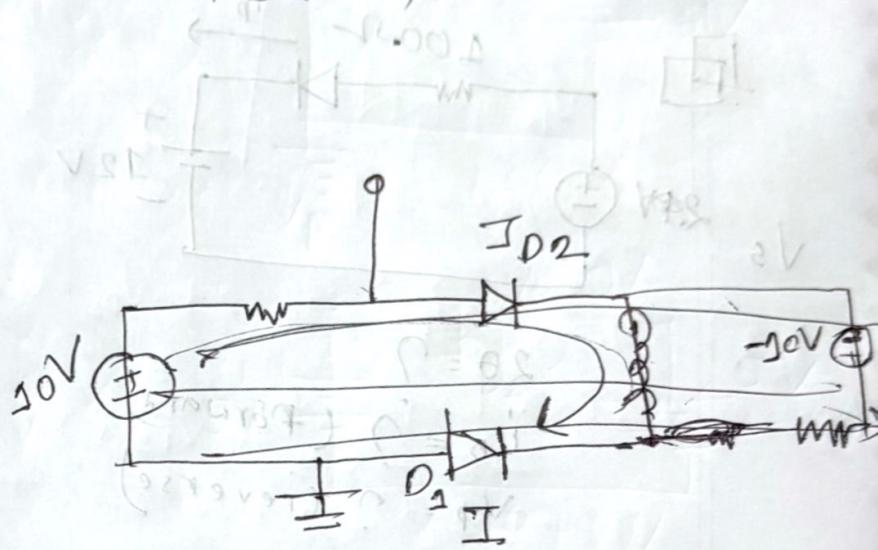What difficulties are associated with multi-diode circuit?



Applying KVL,  $-10 + V_D = 10$

⊗ Current can't flow from the ground

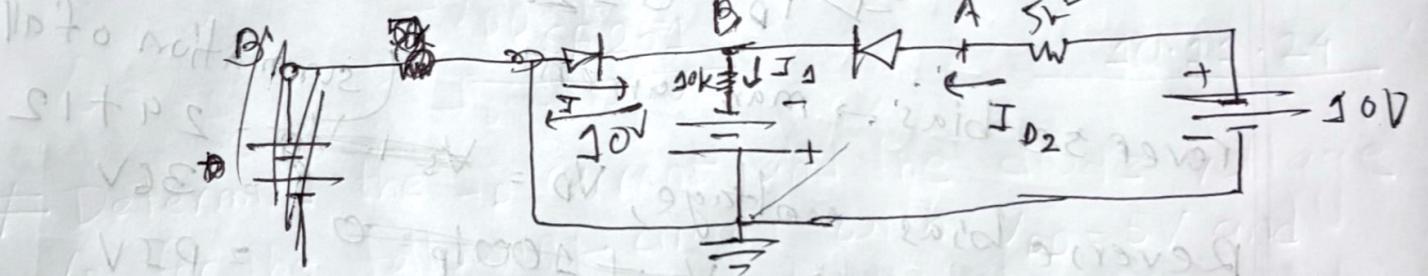

$$I_{D2} = \frac{10 - 0}{5k} = 2mA$$

Applying KCL at B,  $I + I_{D2} = I_1$

$$\Rightarrow I = I_1 - I_{D2}$$

$$= 0 - 2mA \cdot (-1) = 2mA$$

$$I_1 = \frac{0 - (-10)}{10} = 1mA$$

For  $I = -1mA$  Diode  $\Rightarrow$  "OFF"

Applying KVL,

$$-10 + 10i_{D2} + 0.7 + \frac{V}{5i_{D2}} - 10 = 0$$

$$\Rightarrow i_{D2} = 1.33 \text{ mA}$$

$$\therefore V = -10 + I_{D2} \times 10k = -10 + 1.33 \times 10k \\ = 3.3 \text{ V}$$

# A silicon diode said to be a 1 mA device displays a forward voltage of 0.7 V at a current of 1 mA. Evaluate the junction constant  $I_s$ . What scaling constants would apply for a 1A diode of the same manufacture that conducts 1 A at 0.7 V?

$$I = I_s \left( e^{\frac{V_D}{nV_T}} - 1 \right)$$

$$= I_s e^{\frac{V_D}{nV_T}}$$




$$V_T = 25.3 \text{ mV} - 26 \text{ mV} \\ = 25 \text{ mV}$$

$$= \frac{1 \times 10^{-13}}{e^{\frac{0.7}{2 \times 25 \times 10^{-3}}}} \quad [n=1]$$

$$= 8.9 \times 10^{-16} \text{ A}$$

$$I_s = \frac{6.9 \times 10^{-13} \text{ A}}{5000 \text{ times}} \quad [\text{when } I = 1 \text{ A}]$$


(Scaling factor)

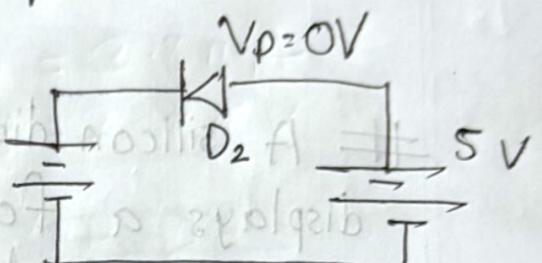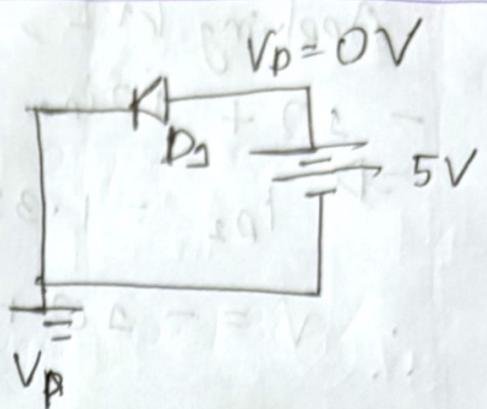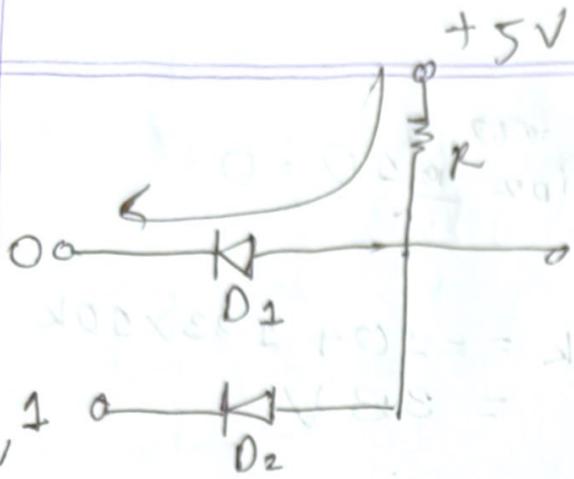

CSE251

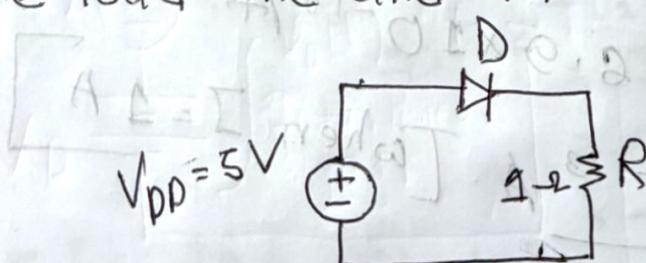10.11.24

// Determine the  $I_D$  current and the diode voltage  $V_D$  for the following circuit with  $V_{DD} = 5V$  and  $R = 1k\Omega$ . Assume that the diode has a current of 1mA and at a voltage of 0.7V. Draw the load line and find  $V_{Dg}$  and  $I_{Dg}$ .




Using KVL,  $-5 + 0.7 + I_D \cdot 1k\Omega = 0$

$$\Rightarrow I_D = 4.3 \text{ mA} = I_2$$

Now, Let  $I_D = 0$ , (open circuit)

$$-5 + V_{D1} + I_D \cdot 1k\Omega = 0$$

$$\Rightarrow V_{D1} = 5V$$

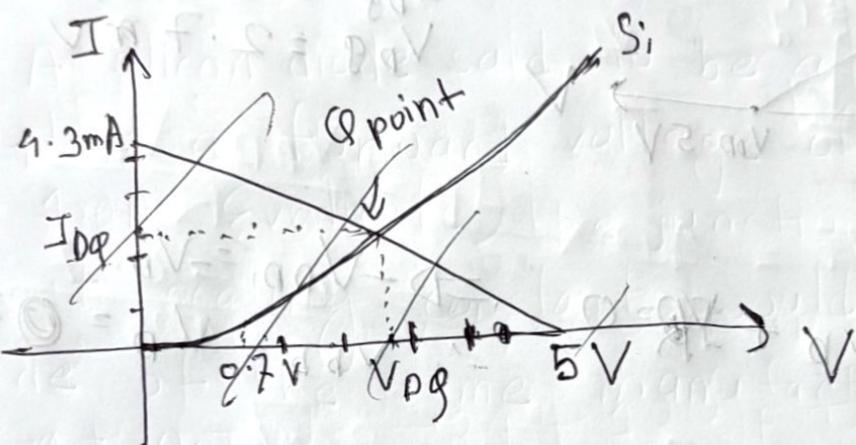

$$V_{DQ} = 2.7 \text{ V}$$

$$I_{DQ} = 2.3 \text{ mA}$$

$$V_2 - V_1 = 2.3 V_T \log \left( \frac{I_2}{I_1} \right)$$

$$\Rightarrow V_2 = 2V_1 + 2.3 V_T \log \left( \frac{I_2}{I_1} \right)$$

$$\begin{cases} 2.3 V_T = 60 \text{ mA} \\ \text{if } I_2 = 10I_1 \end{cases}$$

$$= 0.7 + 2.3 \times 25 \log \left( \frac{4.3 \text{ mA}}{0.3 \text{ mA}} \right)$$

$$= 0.7 + 0.06 \log \left( \frac{4.3 \text{ mA}}{0.3 \text{ mA}} \right)$$


$$= 0.738 \text{ V}$$

For,  $I_D = 4.3 \text{ mA}$   
 $V_2 = 0.738 \text{ V}$

$$I_D = \frac{V_{DD} - V_D}{R} = \frac{5 - 0.738}{1k} = 4.262 \text{ mA} = I_3$$

$$V_3 = V_2 + 2 \cdot 3 V_T \left( \frac{I_3}{I_2} \right)$$
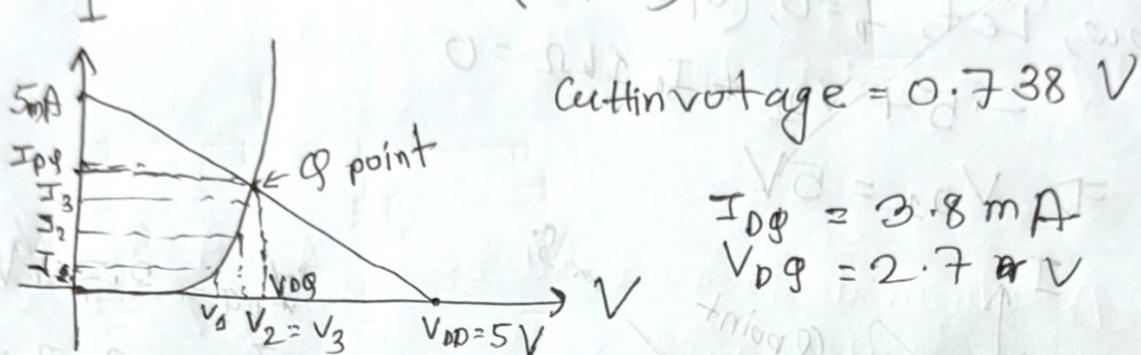
$$= 0.738 + 0.06 \log \left( \frac{4.262}{4.3} \right) = 0.738 \text{ V}$$



Let,  $I_0 = 0$

$$-V_{SD} + V_D + \frac{V_D}{R} = 0 \Rightarrow -V_{DD} = -V_D$$


$$\therefore V_{DD} = V_D = 5 \text{ V}$$

Let,  $V_D = 0$

$$-V_{DD} + 0 + I_D R = 0$$

$$\Rightarrow I_D = \frac{V_{DD}}{R} = \frac{5}{1k} = 5 \text{ mA}$$

### Small Signal Model

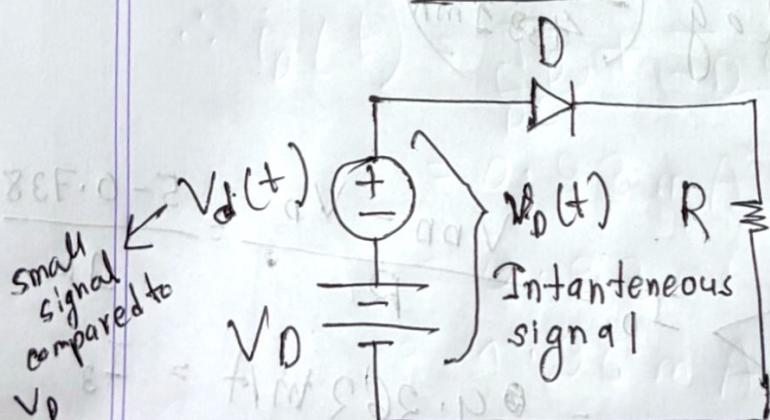

$$V_D(t) = i_D(t) + V_D$$

For forward bias

$$I_D = I_s e^{\frac{V_D}{nV_T}}$$

$V_d \rightarrow AC$

$V_d \rightarrow DC$

$\therefore V_d \rightarrow AC + DC$

$$i_D = I_s e^{\frac{V_d}{nV_T}} = I_s \left[ e^{\frac{V_d}{V_T}}, e^{\frac{V_p}{V_T}} \right] = I_D e^{\frac{V_d}{V_T}}$$

$$= I_s e^{\frac{V_d + V_p}{V_T}} = I_s e^{\frac{V_d}{V_T} + \frac{V_p}{V_T}}$$

$$= I_s e^{\frac{V_d}{V_T}} \cdot e^{\frac{V_p}{V_T}} = I_s e^{\frac{V_d}{V_T}} \cdot DC \cdot e^{\frac{V_d}{V_T}}$$

$$I_D = I_s e^{\frac{V_d}{V_T}}$$

$$\therefore i_D = I_D e^{\frac{V_d}{V_T}}$$

$$\Rightarrow i_D(t) = I_D \left[ 1 + \frac{V_d}{V_T} \right] \quad \frac{V_d}{V_T} \ll 1$$

Instantaneous diode current

$$e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots$$

$$\text{Let } x = \frac{V_d}{V_T}$$

$$i_D(t) = I_D \left[ 1 + \frac{V_d}{V_T} \right] = I_D + \frac{I_D V_d}{V_T}$$


$$= I_D + V_d \left[ \frac{I_D}{V_T} \right] \quad \begin{array}{l} \text{DC} \\ \text{AC} \end{array}$$

$$\begin{aligned} \frac{V}{I} &= R \\ \frac{V}{R} &= I \\ V \cdot G &= I \end{aligned}$$

$$G_d = \frac{I_D}{V_T}$$

$$\text{Diode internal resistance } r_d = \frac{V_T}{I_D} = \frac{26 \text{ mV}}{I_D}$$

while using AC and DC together

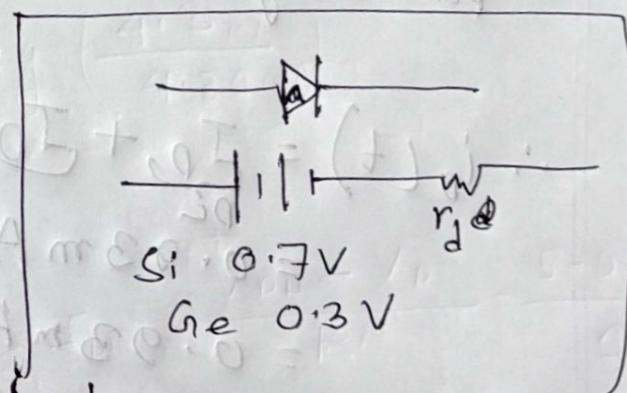

$$i_D(t) = I_D + I_D e^{\frac{V_d}{V_T}}$$

$R = 10k\Omega$



$V^+ = 10V$  dc

$f = 60Hz$

$V_{ac} = 1 - V_{peak} = V_{dp}$

$V^+$

10V

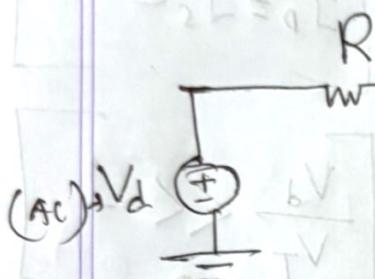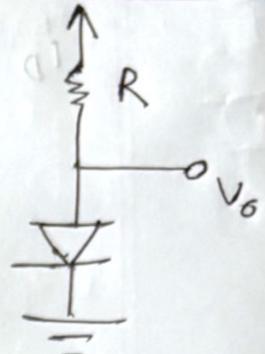

$$I_D = I_S e^{\frac{V_p}{V_T}} = 200mA$$

$$I_D = \frac{V_{pp} - V_D}{R}$$

$$= \frac{10 - 0.7}{10k} = 0.93mA$$

$$r_d = \frac{V_T}{I_D} = 27.9 \Omega$$

$$[V_T = 26mV]$$

Using VDR,

$$V_d = \frac{V_{ac}}{R + r_d} = 1 \times \frac{27.9 \Omega}{10k + 27.9}$$

peak voltage

$$= 2.78 mV = 2.78 \times 10^{-3} V$$


$$\therefore i_D(t) = I_D + I_D e^{\frac{V_d}{V_T}}$$

$$= 0.93mA + 0.93mA \times e^{-\frac{2.78 \times 10^{-3}}{26}}$$

$$= 0.93mA + 1.03mA$$


$$= 1.96mA$$

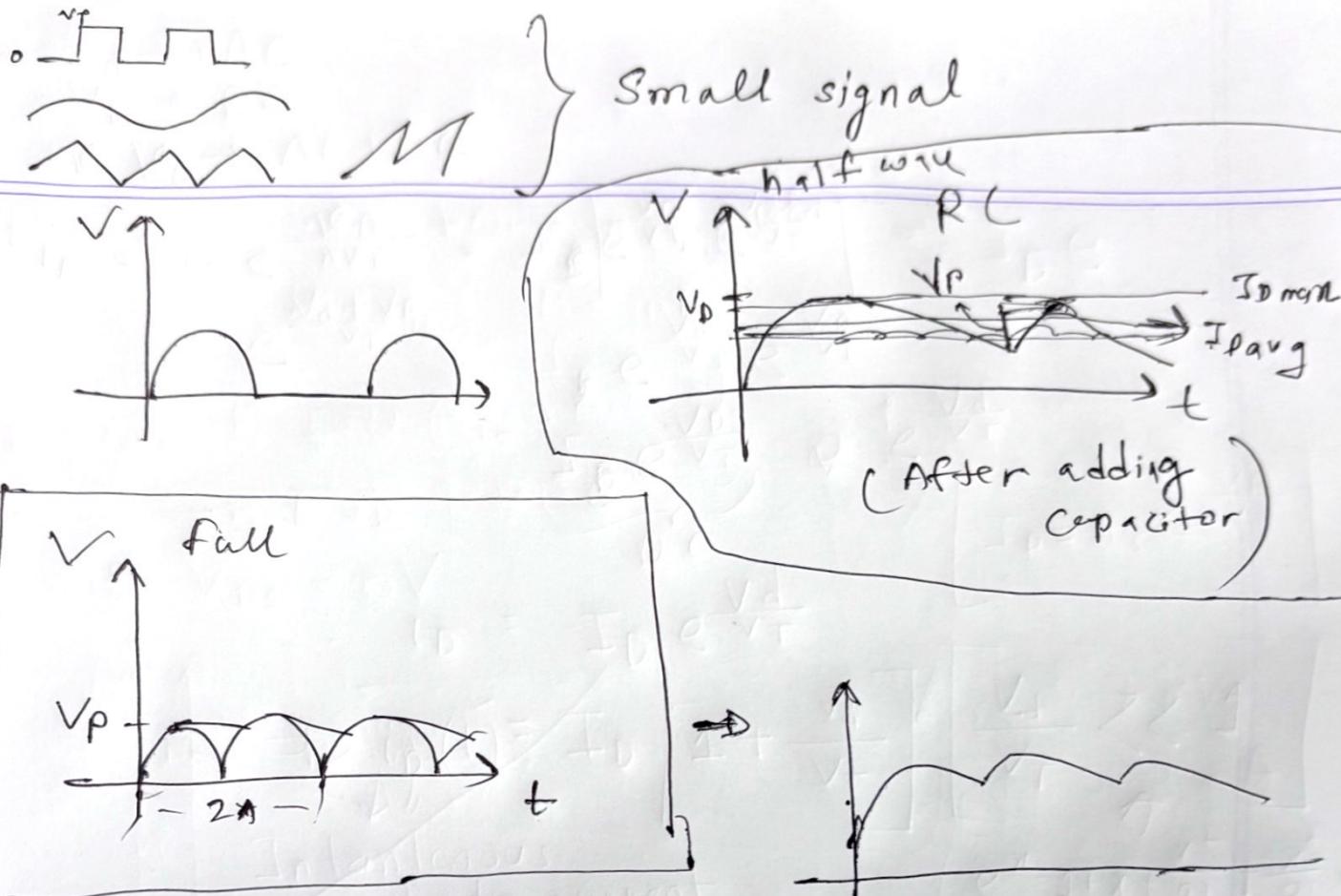Internal resistance is created with respect to DC



$V_{dc}$  = before ripple

$$V_{dc} = 0.318 (V_p - V_0)$$

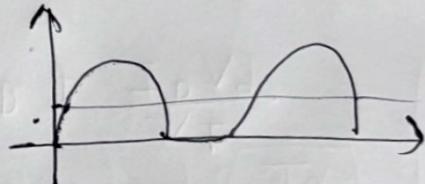

$$G_d = \frac{I_D}{V_T}$$

$$R_d = \frac{V_T}{I_D} = \frac{26mV}{10mA} = 2.6\Omega$$

Diode using AC and DC  
together