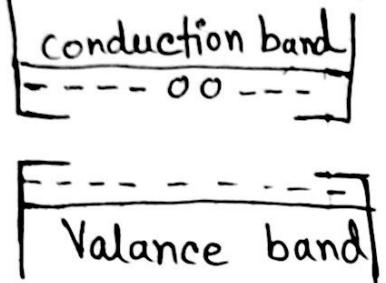


C.W
22/10/2024


CSE251

Diode


Conductor




Semi-Conductor

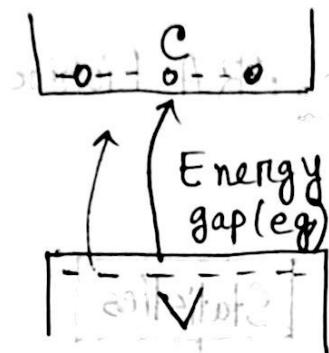


Insulator

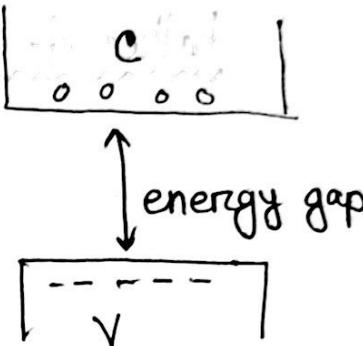

Si : crystal

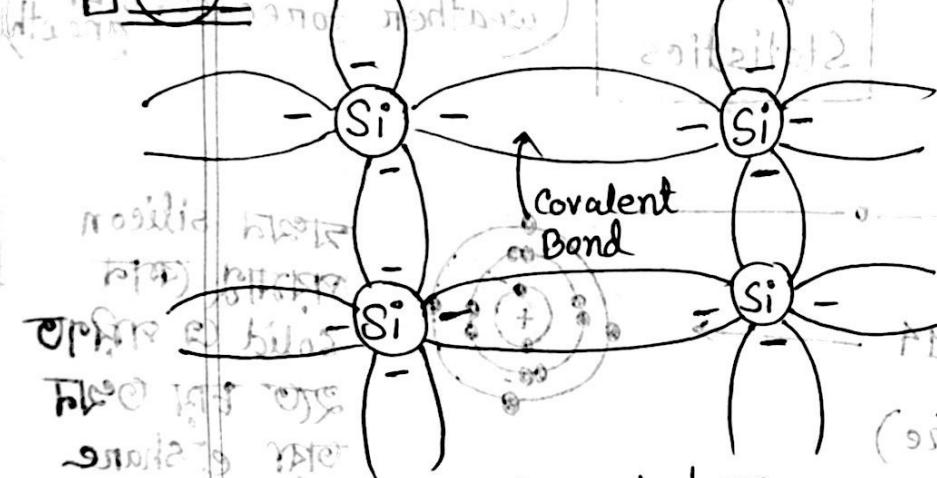

Dope :

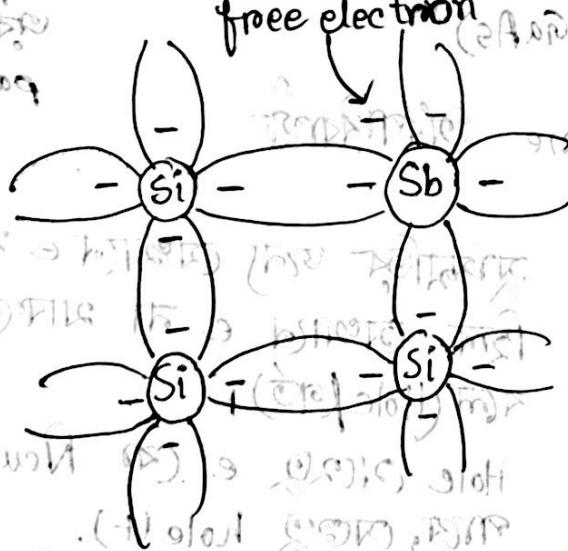

Intrinsic material: No impurity or pure
(all silicon)

or pure

is



is

is


is

is

is

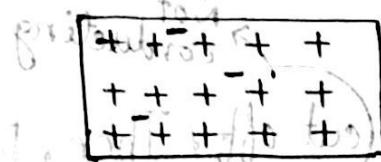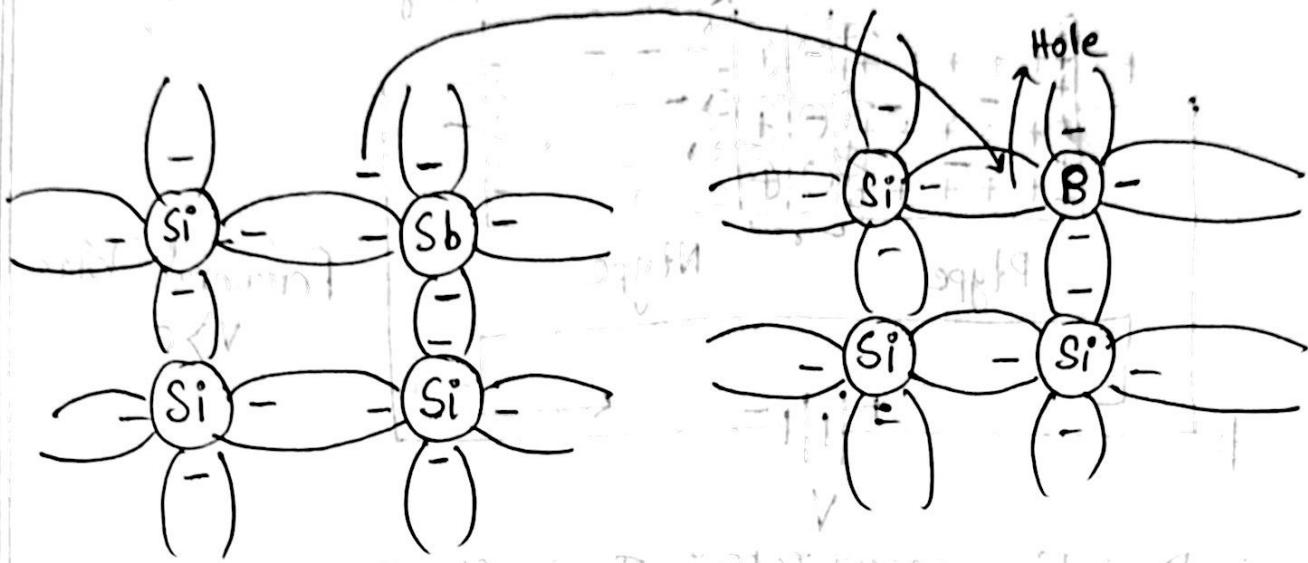

P type
↓

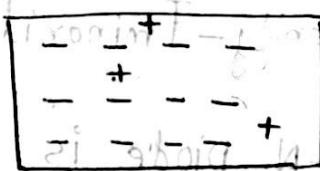

N-type
↓

Hole \rightarrow +ve \rightarrow Majority carrier
Electron \rightarrow -ve \rightarrow Minority carrier

Electron \rightarrow -ve \rightarrow Minority carrier
Hole \rightarrow +ve \rightarrow Majority carrier

P-N Diode :

+ + + + +	- →	(-)	(+)	-- --
+ + + + +	- →	(-)	(+)	- + - -
+ + + + +	- →	(-)	(+)	- + - -


Ptype (Junction) Ntype

Depletion region

P-N \rightarrow Diode

Anode \rightarrow Cathode

Applying V on P-N Diode :

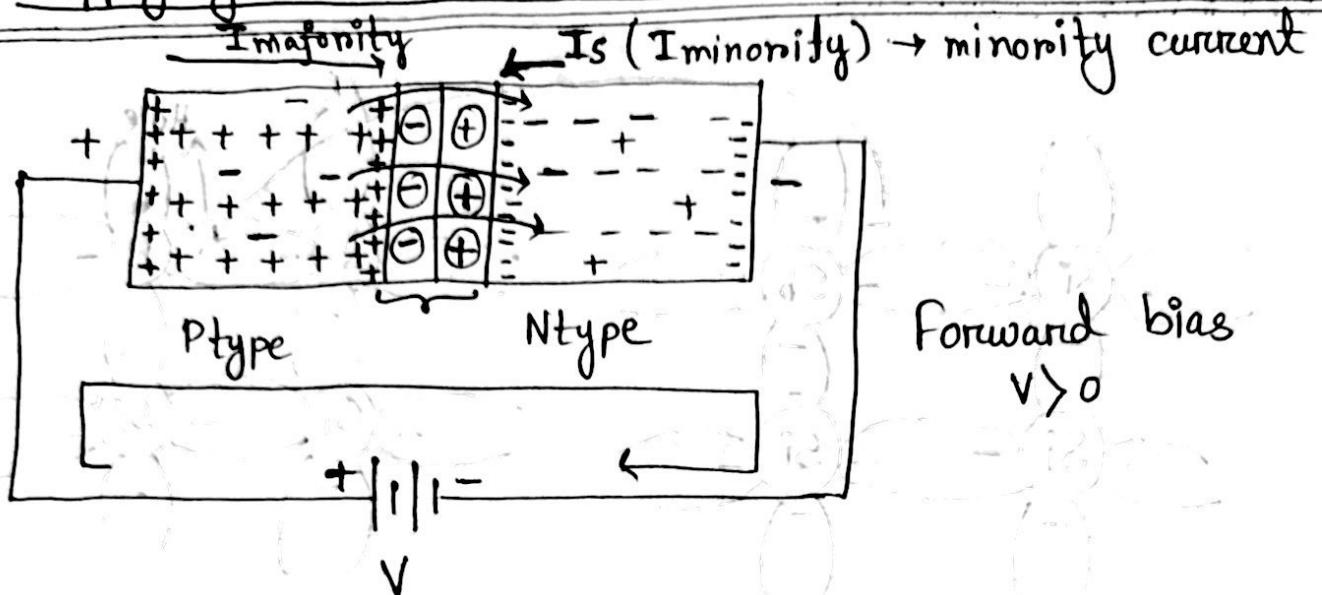


Depletion ক্ষেত্রটির I minority হলু।

$$I_D = I_{\text{majority}} - I_{\text{minority}}$$

* If $V=0$, P-N Diode is called **cut off**. Then, Depletion region will be reformed.

□ Reverse bias condition when $V < 0$.
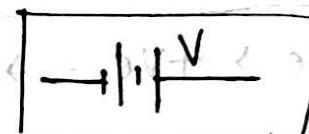
$$\text{Diode current, } I_D = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$



$$\text{Forward Bias} = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right) \quad \text{Reverse Bias}$$

$I_S \rightarrow$ Saturation current

$V_D \rightarrow$ Applied Voltage (F-Bias)


$$V_T \rightarrow \text{Thermal Voltage} = \frac{KT}{q} \quad [K = \text{Boltzmann constant}]$$

$\eta \rightarrow$ Identity factor (1 or 2) } $\eta \rightarrow 1 : \text{Ge}$
 depends on construction } $\eta \rightarrow 2 : \text{Si}$

$$1.38 \times 10^{-23} \text{ J/K}$$

Determine the voltage V_o

I-V characteristic curve

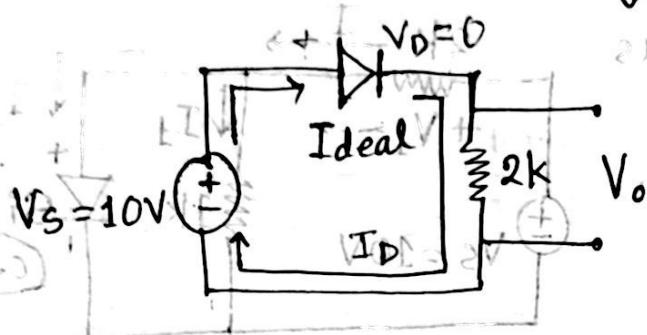

Soln:

Diode \rightarrow forward bias \rightarrow "ON"

Ideal Diode, $V_D = 0V$



$$I_D = \frac{V_s}{2k} = \frac{10}{2k} \quad [Ohm's Law]$$

$$= 5mA$$

$$V_o = 2k \times I_D$$

$$= 2k \times 5mA$$

$$= 10V$$

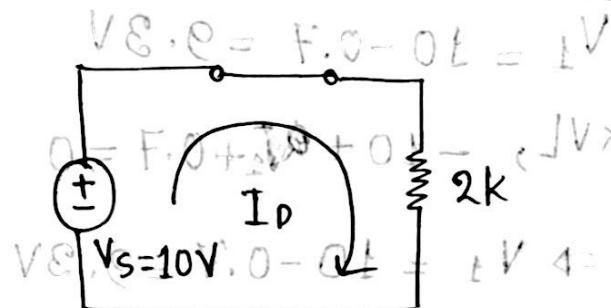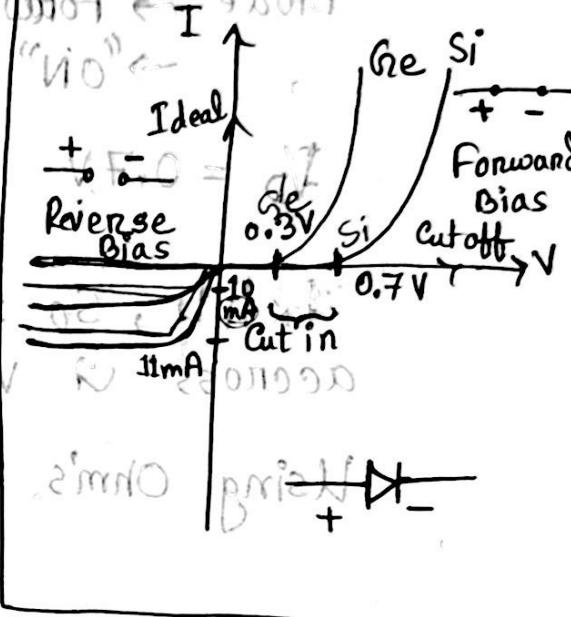

$$Amperes = \frac{V \cdot e}{2} = \frac{V}{2k} = I$$

Reverse Diode এর ক্ষেত্রে,



Diode \rightarrow Reverse bias \rightarrow "OFF"

$$I_D = 0A$$

$$V_o = 0V$$

Diode \rightarrow cut off

$$I_D = 0A$$

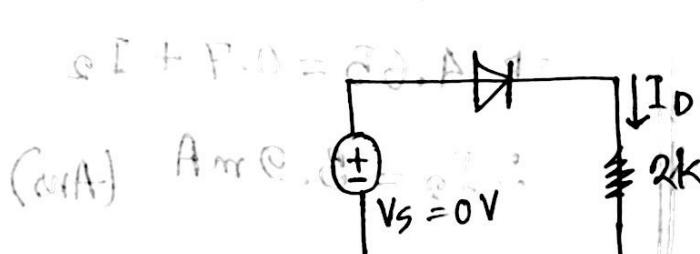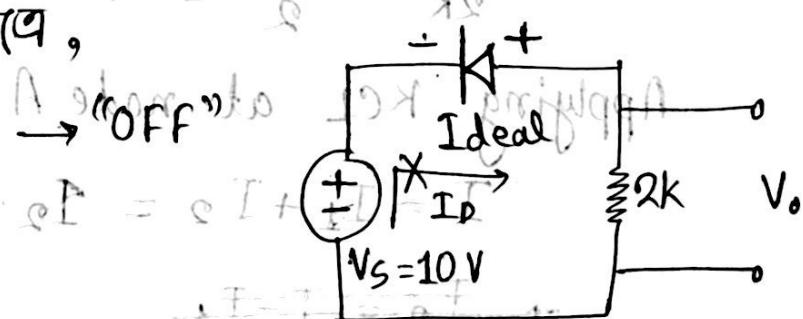

Determine I , I_1 , I_2 & V_1

Diode \rightarrow forward bias
 \rightarrow "ON"

$$V_D = 0.7V$$

$1k \parallel D$, so $1k$ এর
 across $V = 0.7V$

Using Ohm's law, $I_1 = \frac{0.7}{1k} = 0.7mA$

$$V_1 = 10 - 0.7 = 9.3V$$

OR, KVL, $-10 + V_1 + 0.7 = 0$

$$\Rightarrow V_1 = 10 - 0.7 = 9.3V$$

$$I = \frac{V_1}{2k} = \frac{9.3}{2} = 4.65mA$$



Applying KCL at node A,




$$I = I_1 + I_2$$

$$\Rightarrow I_2 = I - I_1$$

$$\Rightarrow 4.65 = 0.7 + I_2$$
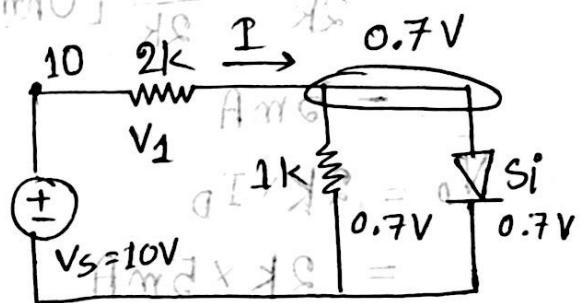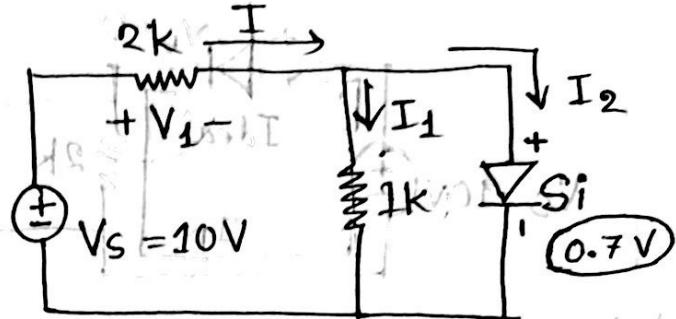
$$\therefore I_2 = 3.9mA \quad (\text{Ans})$$



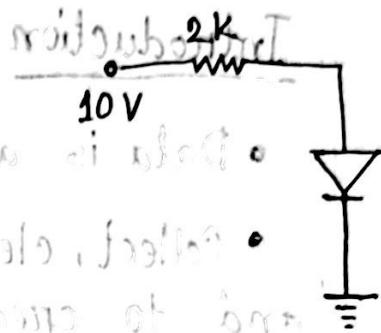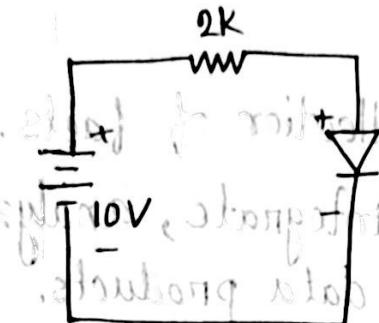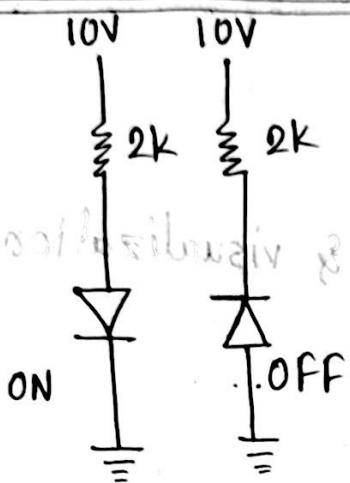

Forward Bias \rightarrow Short circuit

Reverse Bias \rightarrow Open circuit

~~+~~ - K+

vs $\textcircled{-}$


missing task

+ K-

-

C.W
27/10/2024

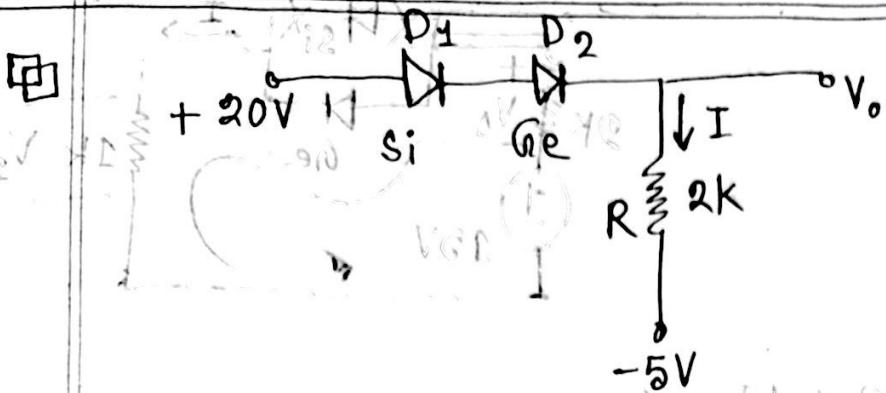
Determine the current I & the voltage V_o



$$Si = 0.7 \text{ V}$$

~~$Ge = 0.3 \text{ V}$~~

$$Ge = 0.3 \text{ V}$$

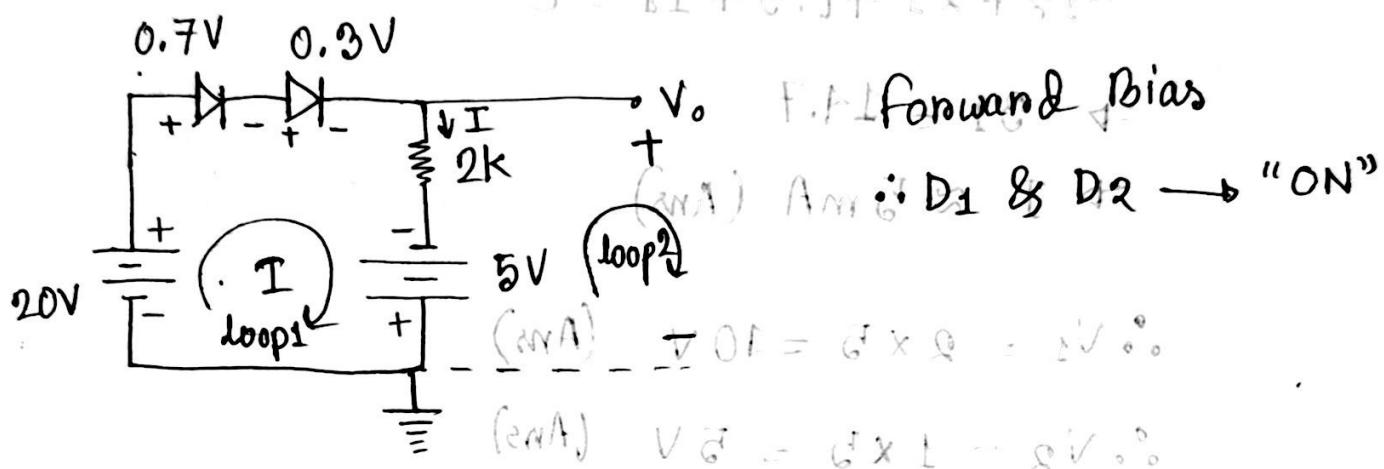

KVL,

$$-20 + 0.7 + 0.3 + 2I - 5 = 0$$

$$\Rightarrow 2I = 24$$

$$\Rightarrow I = 12 \text{ mA} \quad (\text{Ans})$$

$$\text{KVL in loop 2, } +5 - 2I + V_o = 0$$

$$\Rightarrow 5 - 24 + V_o = 0$$

$$\Rightarrow V_o = 19 \text{ V} \quad (\text{Ans})$$


$$0 = I_1 + I_2 + I_3 + I_4 + I_5$$

F.C.L - E.O.F.E.P.A.

Determine the current I & the voltage V_1 & V_2

D₁ → "OFF"

D₂ → "ON"

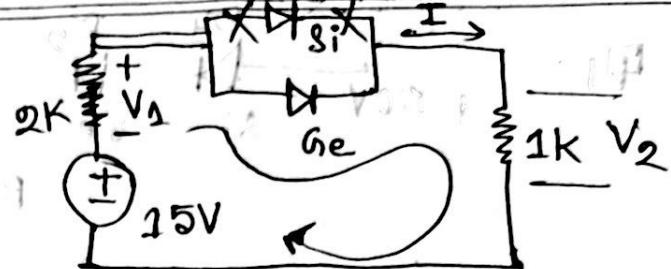

Applying KVL,

$$-15 + 2I + 0.3 + 1I = 0$$

$$\Rightarrow 3I = 14.7$$


$$\Rightarrow I \approx 5 \text{ mA} \quad (\text{Ans})$$

$$\therefore V_1 = 2 \times 5 = 10 \text{ V} \quad (\text{Ans})$$

$$\therefore V_2 = 1 \times 5 = 5 \text{ V} \quad (\text{Ans})$$

Determine the voltage V_1 & the currents I_1, I_2, I_3

(b)

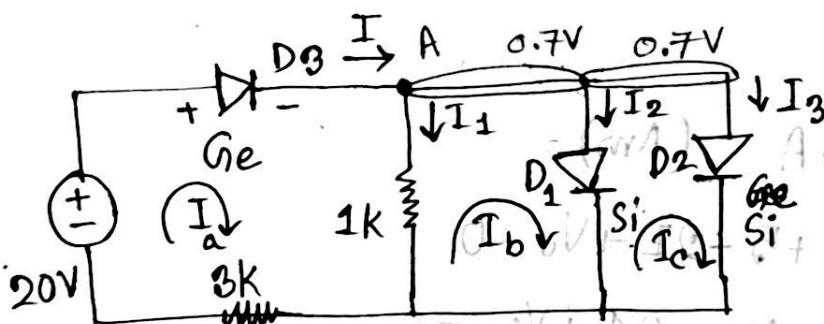

Applying mesh analysis in loop 1,

$$-20 + 0.3 + I_a - I_b + 3I_a = 0$$

$$\Rightarrow 4I_a - I_b = 19.7$$

Applying mesh analysis in loop 2,

$$I_b - I_a + 0.7 = 0$$

$$\Rightarrow I_a - I_b = 0.7$$

Applying mesh analysis in loop 3,

$$4I_a - I_b - I_a + I_b = 19.7 - 0.7$$

$$\Rightarrow 3I_a = 19$$

$$\therefore I_a = 6.33 \text{ mA}$$

Wrong Answer

Soln:

D_1, D_2 & D_3 are "ON"

$$V_{D_3} = 0.3V$$

$$V_{D_1} = V_{D_2} = 0.7V$$

Since, $R \parallel D_1 \parallel P_2$


$$V_R = V_{D_3} = V_{D_2} = 0.7V$$

Applying KVL, $-20 + V_{D_3} + V_R + V_1 = 0$

$$\Rightarrow -20 + 0.3 + 0.7 + I' 3k = 0$$

$$\therefore I' = 6.33 \text{ mA} = I$$

Answer is 6.33 mA (Ans)

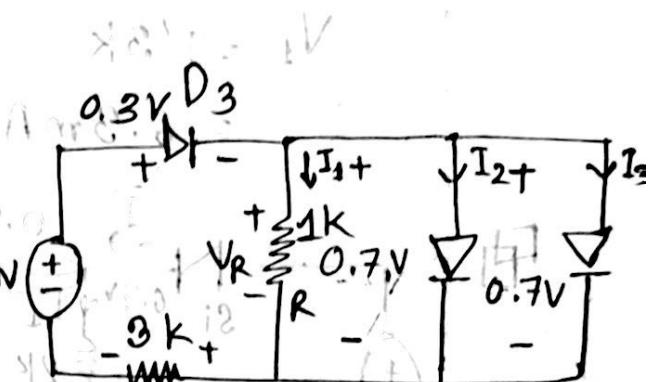

Applying KCL, at node A

$$I = I_1 + I_2 + I_3$$

Using Ohm's law,

$$I_1 = \frac{0.7}{1k} = 0.7 \text{ mA}$$

$$\Rightarrow I_2 + I_3 = I - I_1$$

$$V_o = dI - dT$$


$$= 6.3 \text{ mA} - 0.7 \text{ mA}$$

$$= 5.6 \text{ mA}$$

$$I_2 = I_3 = \frac{5.6}{2} \text{ mA} = 2.8 \text{ mA} \quad (\text{Ans})$$

$$V_1 = I' 3k$$
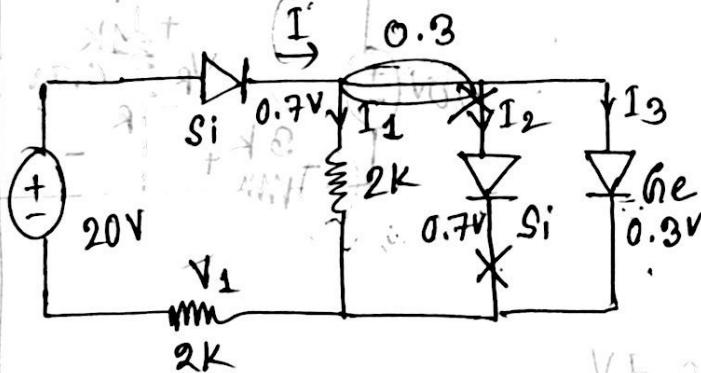
$$= 6.3 \text{ mA} \times 3 = 18.9 \text{ V} \quad (\text{Ans})$$



KVL,

$$-20 + 0.7 + 0.3 + 2I = 0$$

$$\Rightarrow 2I = 19$$

$$\therefore I = 9.5 \text{ mA}$$

As D_2 = "OFF", $I_2 = 0 \text{ mA}$

~~$V_1 = I_1, I_2 \text{ & } I_3$~~

$$V_F = 0.7 \text{ V} = 1 \text{ V}$$

~~Since $R_{F1} = R_{F2}$~~

$$V_F = 0.7 \text{ V} = 1 \text{ V}$$

~~I_S~~

~~$R_{F1} = R_{F2}$~~

Ohm's law:

$$\text{KVL in loop, } \text{EDR}, I_1 = \frac{20V - 0.3}{2} = 0.15 \text{ mA}$$

$$\text{Applying KCL, } I = I_1 + I_3$$

$$\Rightarrow I_3 = I - I_1$$

$$\therefore I_3 = 0.5 - 0.15 = 0.35 \text{ mA}$$

$$\therefore V_1 = 2 \times I = 2 \times 0.5 = 10 \text{ V}$$

Slide-11

AND Gate

A	B	Output
0V	0V	0V
0V	5V	5V
5V	0V	5V
5V	5V	5V



{ logic "0" \rightarrow 0V }
 { logic "1" \rightarrow 5V }

A	B	Output
0V	0V	0V
0V	5V	5V
5V	0V	0V
5V	5V	5V

OR Gate


D_1 & $D_2 \rightarrow$ Ideal diode.
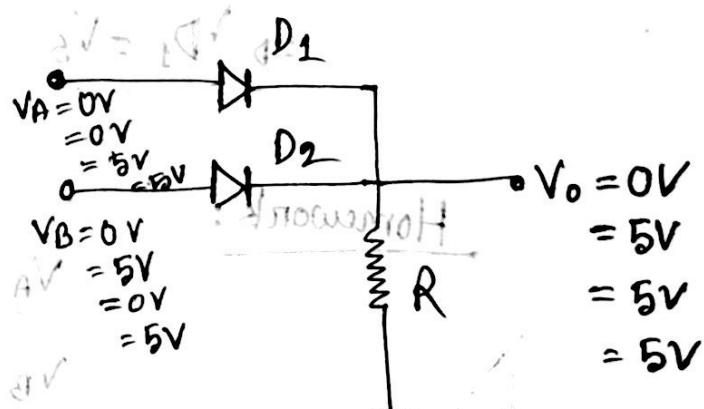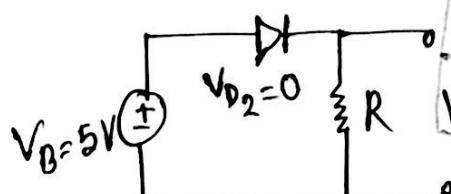
$$V_{D1} \text{ & } V_{D2} \rightarrow 0V$$



This circuit is representing OR gate

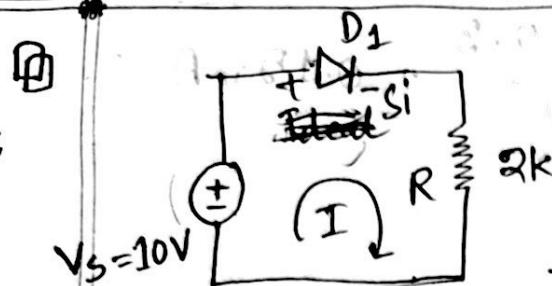Determine the load line for the following circuit and determine the Q point.



Soln: Applying KVL, $-V_s + V_D + V_o = 0$
 $\Rightarrow I = \frac{V_s - V_o}{R} = \frac{10 - V_o}{2k}$


Let $V_{D_1} = 0V$

$$\begin{aligned} -V_s + V_R &= 0 \\ \Rightarrow V_R &= V_s \\ \Rightarrow IR &= V_s \end{aligned}$$

$$\Rightarrow I = \frac{V_s}{R}$$

$$= \frac{10}{2} = 5mA$$

$$V_{oQ} = 0.7V$$


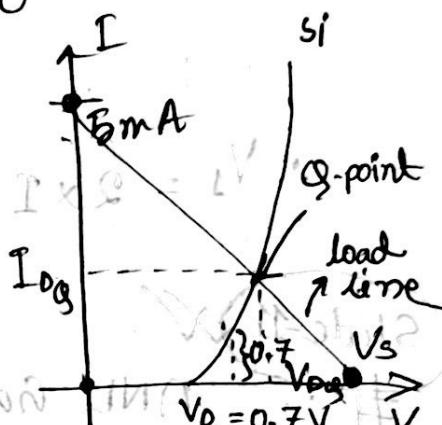


Let, $I = 0A$, From eqn ①


$$\begin{aligned} -V_s + V_{D_1} + IR &= 0 \\ \Rightarrow -V_s + V_{D_1} &= 0 \quad [IR = 0] \end{aligned}$$

$$\Rightarrow V_{D_1} = V_s$$

$$[IR = 0]$$

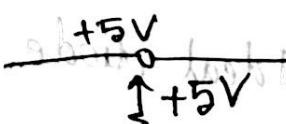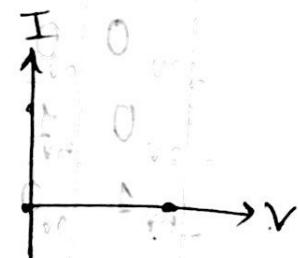

Homework:

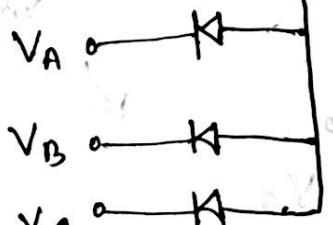


29/10/29

$$I = I_s \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$

$$= I_s e^{\frac{V_D}{nV_T}} - I_s$$

Forward Bias Reverse Bias

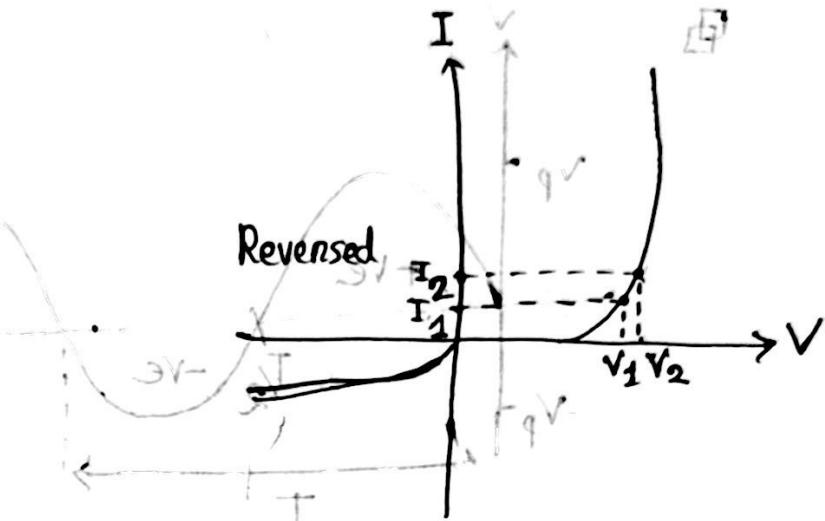

V_T = Thermal Voltage

$$V_T = \frac{kT}{q} = 25.5 \approx 26 \text{ mV}$$

~~Let, $n = 1$~~

$$\therefore I_1 = I_s e^{\frac{V_1}{V_T}}$$

$$\therefore \frac{I_2}{I_1} = \frac{I_s e^{\frac{V_2}{V_T}}}{I_s e^{\frac{V_1}{V_T}}} = \frac{e^{\frac{V_2}{V_T}}}{e^{\frac{V_1}{V_T}}}$$

$$\Rightarrow \frac{I_2}{I_1} = \frac{e^{\frac{V_2}{V_T}}}{e^{\frac{V_1}{V_T}}}$$

$$\Rightarrow \frac{I_2}{I_1} = e^{(V_2 - V_1)/V_T}$$


$$\Rightarrow V_2 - V_1 = V_T \ln \left(\frac{I_2}{I_1} \right)$$


$$\Rightarrow V_2 - V_1 = 2.3 V_T \log \left(\frac{I_2}{I_1} \right)$$

60 mV

$$\frac{V_2}{V_T} = \frac{I_2}{I_1} = e^{\frac{V_2}{V_T}}$$

Result:

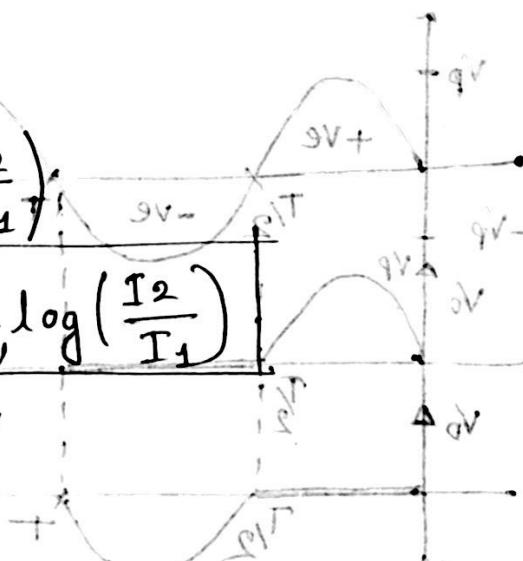

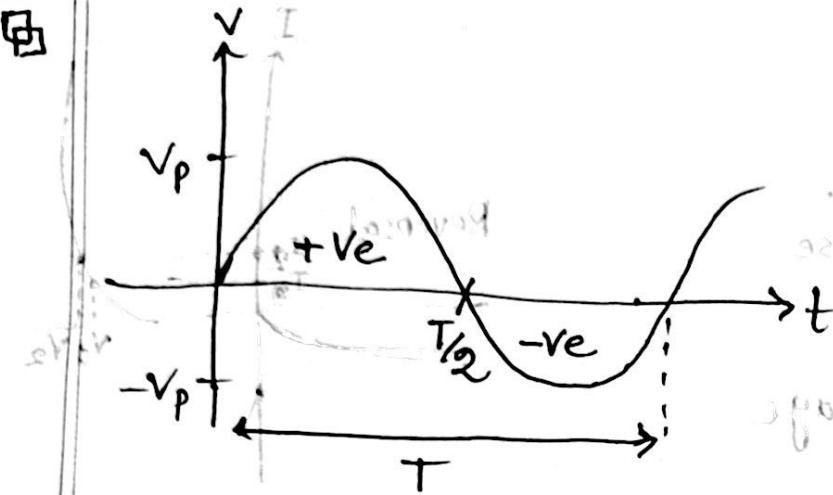

(1) ω = angular frequency


9V
1.5V

202

Blue *Cyanomyia*

~~Agalloch~~ ~~Wormwood~~ = V

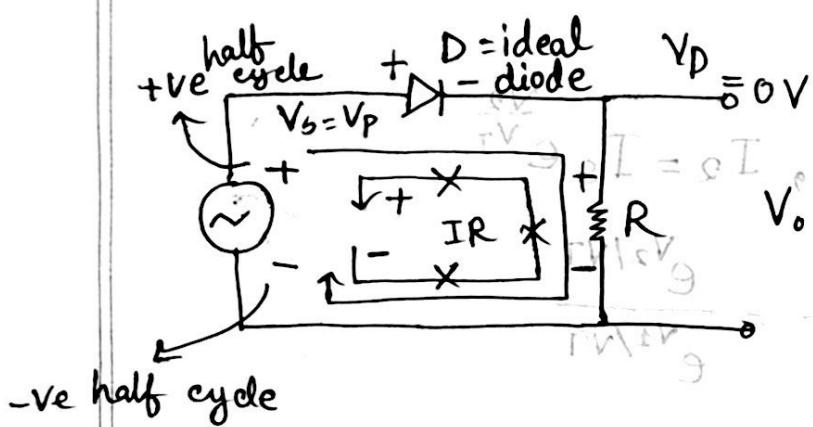
* For +ve half cycle
 $D \Rightarrow$ forward bias



* For -ve half cycle
 $D \Rightarrow$ Reverse bias

D \Rightarrow Reverse bias

Halfwave Rectifier:

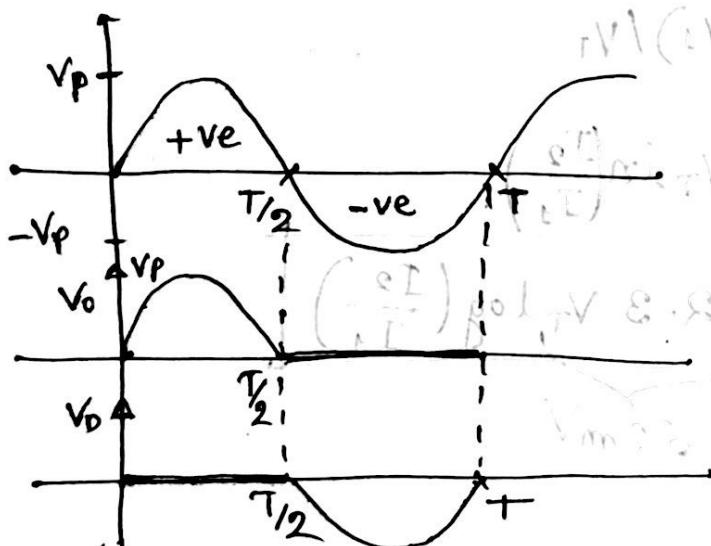

halfwave
Rectifier
Circuit

For, +ve half cycle, Applying KVL, fixed bias case

$$-V_p + V_D + V_o = 0$$

and Diode $\Delta = 0$

$$\Rightarrow V_o = V_p - \frac{V_p}{R}^0$$

$$V_F = 0.7V$$

$$\therefore V_o = V_p$$


For, negative (-ve) half cycle, Applying KVL,

$$\left\{ \begin{array}{l} V_S + V_D + V_o = 0 \\ \Rightarrow V_o = -V_S = -V_p \end{array} \right.$$


Hence, $IR = 0, V_o = IR$

(T-~~X~~) shows that $V_o = 0$

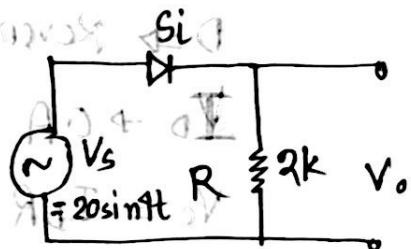- # Determine the output voltage V_o and sketch the wave forms across the output resistance and diode




Soln:

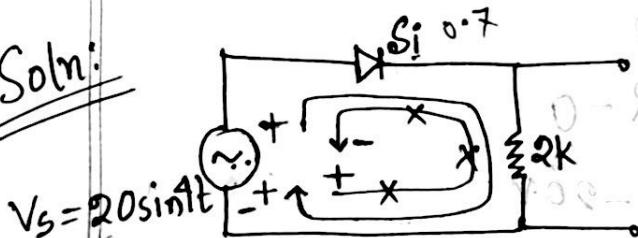

$$V_s = 20 \sin \omega t$$

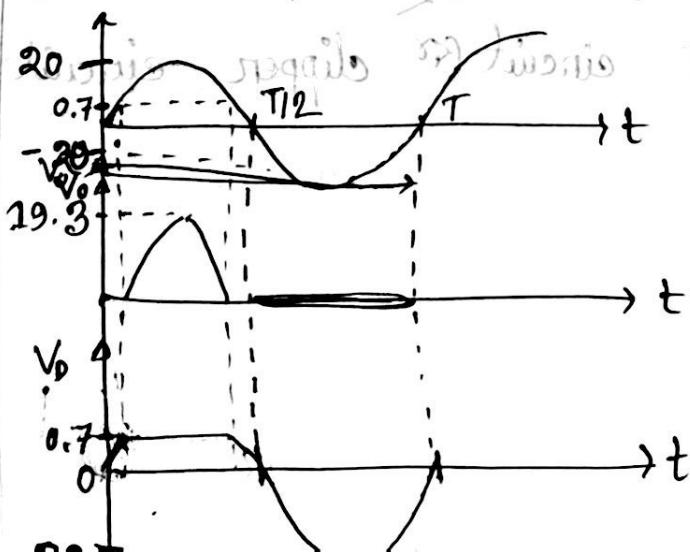Reverse bias fixed voltage drop মাত্রে না, ঠিক maximum voltage অবসর এবং Reverse bias এ open circuit



for +ve half cycle ($0 - T/2$)

D \Rightarrow Forward bias

$$V_D = 0.7V$$

\therefore Applying KVL, $-V_s + V_D + V_o = 0$

$$\Rightarrow -20 + 0.7 + V_o = 0$$

$$\therefore V_o = 19.3V$$

for (-ve) half cycle ($T/2 - T$)

D \Rightarrow Reverse bias

$$I_D \Rightarrow 0A$$

$$V_o = I_D R = 0 \times 2K = 0V$$

\therefore Applying KVL, $V_s + V_D + V_o = 0$

$$\Rightarrow V_s + V_D + I_D R = 0$$

$$\Rightarrow V_D = -V_s = -20V$$

* Diode প্রেগটি অংশ কেটে যাচ্ছে আর একটা অংশ



যেখন যাচ্ছে এই ধৰনের circuit বা clipper circuit বলে।

C.W
03/11/29

Capacitor \rightarrow Open circuit
Inductor \rightarrow Short circuit

$$V_o = V_p \sin(\omega t + \phi) \quad \text{Eqn of V_o}$$

Half wave Rectifier circuit

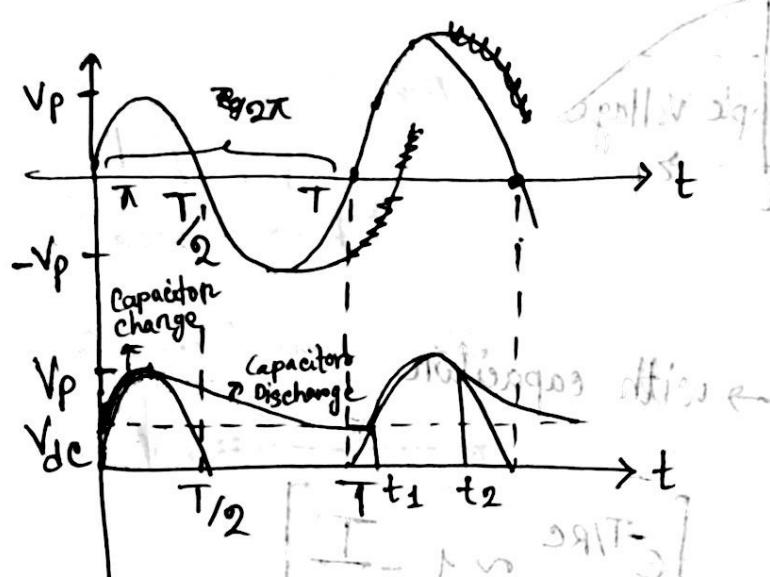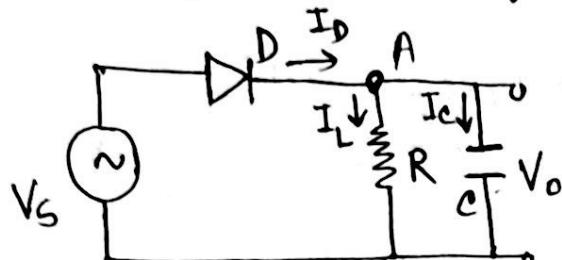


$$V_{dc} = 0.318(V_p - V_D)$$

V_p = Peak Voltage

V_D = Diode Voltage

Δt = Conduction Interval
 $= t_1 \rightarrow t_2$

I_L = Load current

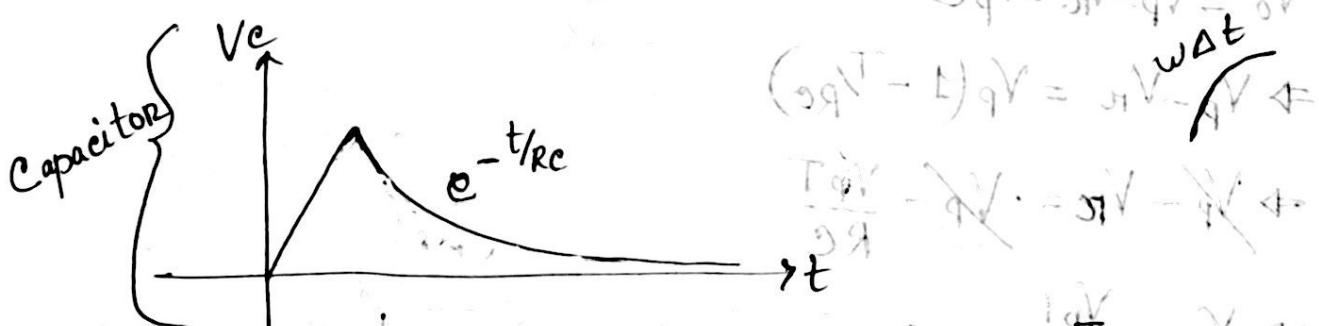

Applying KVL at node A, $I_D = I_C + I_L$

$$\begin{aligned} I_D &= C \frac{dV_s}{dt} + I_L \\ &= C \frac{ds}{dt} + \frac{V_o}{R} \\ &= C \frac{ds}{dt} + \frac{V_D}{R} \end{aligned}$$


* RC এর Value বাড়ালে Ripple কমবে

Ripple যত কম হবে তত ভালো

$$\text{KVL in loop 1, } -V_s + V_D + V_o = 0$$

$$-V_s + V_D + I_L R = 0$$
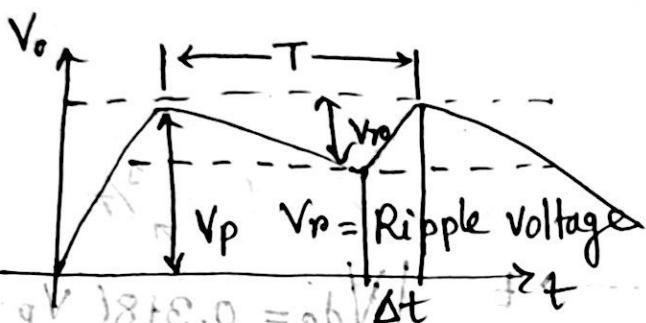
$$\Rightarrow V_o = V_s - V_D = V_p - V_D$$



$$V_o = V_p - \frac{1}{2} V_r$$

$$V_o = V_p e^{-t/RC}$$

→ with capacitor

$$RC \gg T$$

$$V_o = V_p e^{-T/RC}$$

$$V_o = V_p - V_R = V_p e^{-T/RC}$$

$$\Rightarrow V_p - V_R = V_p (1 - e^{-T/RC})$$

$$\Rightarrow V_p - V_R = V_p - \frac{V_p T}{RC}$$

$$\Rightarrow V_R = \frac{V_p T}{RC}$$

$$\Rightarrow f = \frac{1}{T}$$

$$\therefore V_R = \frac{V_p}{fRC}$$

$$\Rightarrow V_R = \frac{V_p / R}{f_c}$$

$$\Rightarrow \frac{I_L}{f_c} \quad [I_L = \frac{V_p}{R}]$$

$$V_S = V_p \cos(\omega \Delta t) + \dots$$

$\omega = \text{Angular frequency}$

$$\cos(\omega \Delta t) \approx 1 - \frac{1}{2}(\omega \Delta t)^2$$

* $\boxed{\omega \Delta t = \sqrt{\frac{2V_n}{V_p}}}$

* $i_{D \text{ avg}} = I_L \left(1 + \pi \sqrt{\frac{2V_p}{V_n}} \right)$ \Rightarrow Average diode current


Half wave rectifier $i_{D \text{ max}} = I_L \left(1 + 2\pi \sqrt{\frac{2V_p}{V_n}} \right)$ \Rightarrow Maximum diode current

For, full wave Rectifier,

$$V_n = \frac{V_p}{2fRC}$$



$$i_{D \text{ avg}} = I_L \left(1 + \pi \sqrt{\frac{V_p}{2V_n}} \right)$$
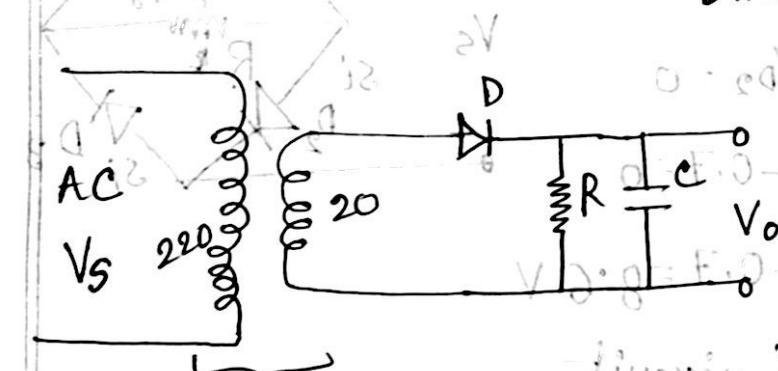
$$i_{D \text{ max}} = I_L \left(1 + 2\pi \sqrt{\frac{V_p}{2V_n}} \right)$$



X Transformer / Stepdown transformer

Full wave Rectifier

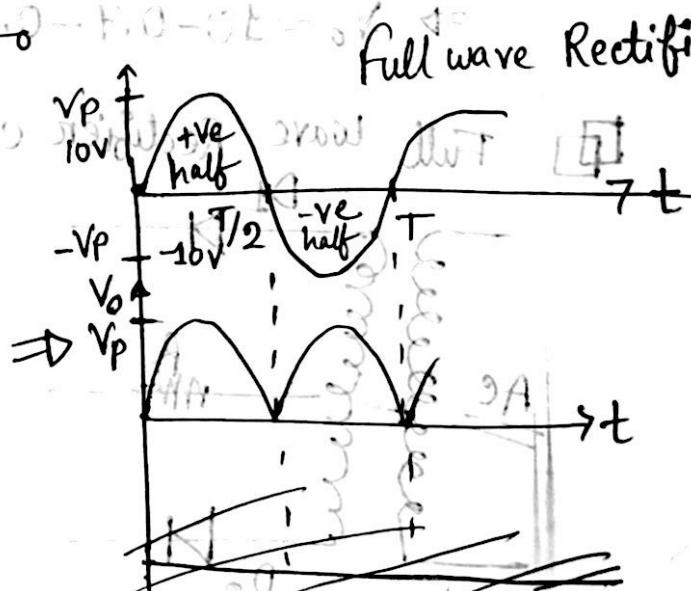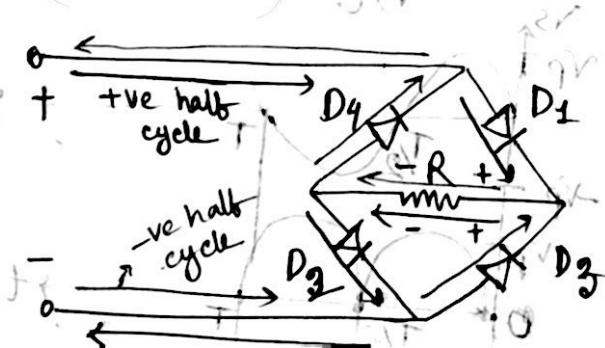

$$V_{dc} = 0.318 (V_p - V_D) - \text{Half (AC) } 200\sqrt{2} \text{ V}$$

$$= (2 \times 0.318) (V_p - 2V_D) + \text{full (AC) } 200$$

for +ve half cycle

D_1 & D_2 — ON

D_3 & D_4 — OFF

for -ve half cycle

D_3 & D_4 — ON

D_1 & D_2 — OFF

Determine V_o

Apply KVL,




$$-V_s + V_{D1} + V_o + V_{D2} = 0$$

$$\Rightarrow V_o = V_s - 0.7 - 0.7 = 0$$

$$\Rightarrow V_o = 10 - 0.7 - 0.7 = 8.6 \text{ V}$$




Full wave Rectifier circuit

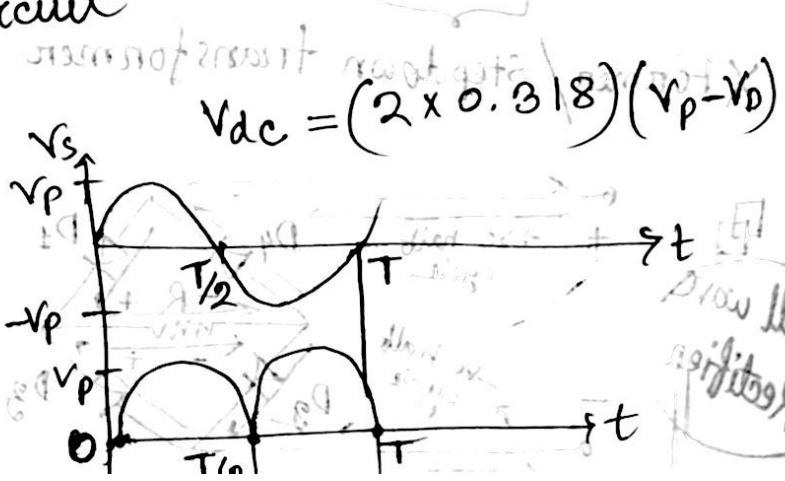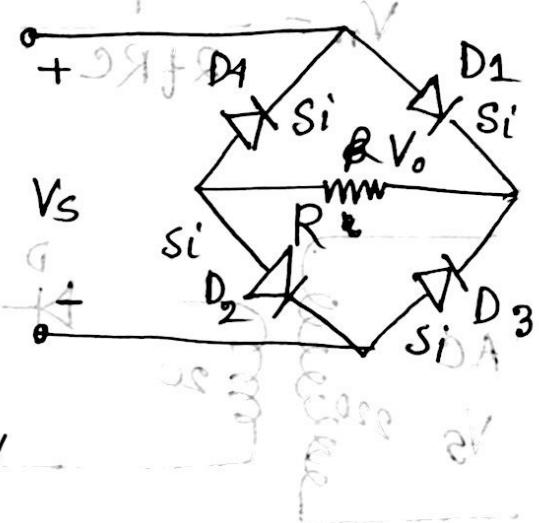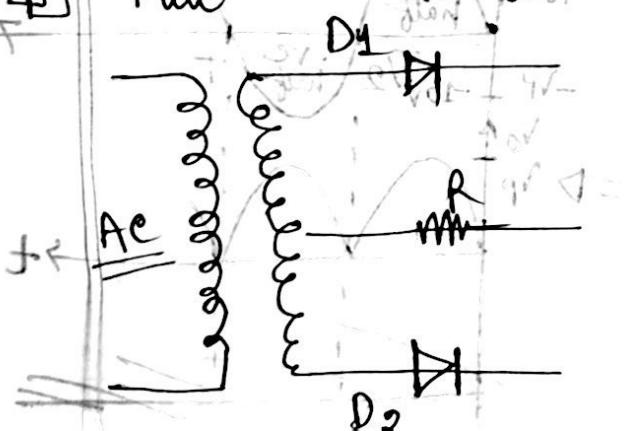

$$V_{dc} = (2 \times 0.318)(V_p - V_D)$$


Draw the output wave form.

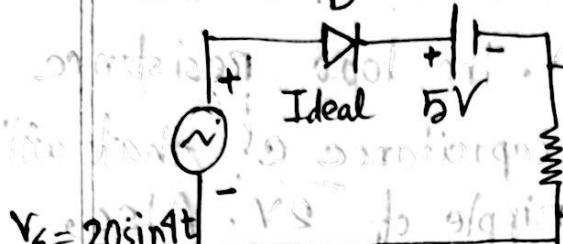

$$V_p = 20V$$

D → Reverse Bias

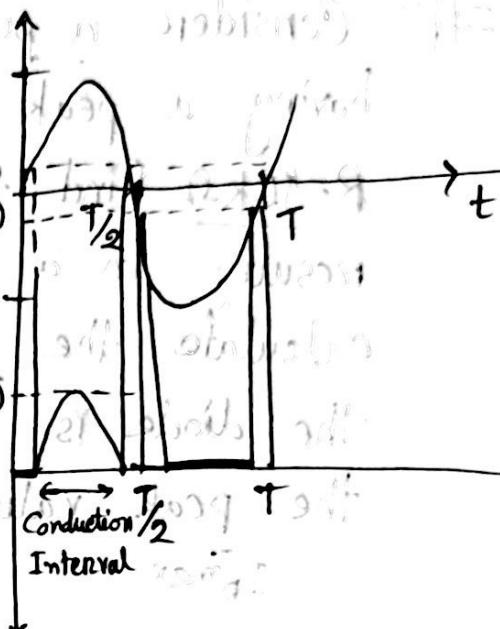$V_D \rightarrow PIV \rightarrow$ Peak inverse Voltage



$$V_o = \frac{V_p}{2} = 10V$$

$$(10V)^2 / 2R = I^2 R \Rightarrow I = 10A$$

$$I = 10A \Rightarrow 10A = \frac{10V}{R}$$

$$10A = \frac{10V}{R}$$

$$10A = \frac{10V}{R} \Rightarrow R = 1\Omega$$

$$P = I^2 R = 10A \times 1\Omega = 100W$$

$$A_m = 10A$$

$$20A$$

$$\frac{10}{20} = 50\%$$

$$(20A) \times 50\% = 10A$$

C.W
05/11/2021


Half wave rectifier

Consider a peak rectifier fed by a 60Hz sinusoid having a peak value $V_p = 100V$. The load resistance $R = 10k\Omega$ Find the value of capacitance C ? that will result in a peak-to-peak ripple of 2V. Also, calculate the fraction of the cycle during which the diode is conducting and the average and the peak values of diode current. $I_{D \text{ avg}}$

$I_{D \text{ max}}$

$$V_p = 100V, I_L = \frac{V_o}{R} = \frac{V_p}{10} = 10$$
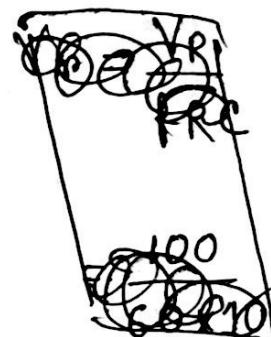
$$\begin{aligned} i_{D \text{ avg}} &= I_L \left(1 + \pi \sqrt{\frac{2V_p}{V_{D \text{ drop}}}} \right) \\ &= 10 \left(1 + \pi \sqrt{\frac{2 \times 100}{2}} \right) \\ &= 324.16 \text{ mA} \end{aligned}$$



$$\begin{aligned} i_{D \text{ max}} &= I_L \left(1 + 2\pi \sqrt{\frac{2V_p}{V_{D \text{ drop}}}} \right) \\ &= 10 \left(1 + 2\pi \sqrt{\frac{200}{2}} \right) = 454.288 \\ &\quad 638 \text{ mA} \end{aligned}$$

$$V_p = \frac{V_p}{fRC} \quad (\text{Ans})$$

$$\begin{aligned} C = \frac{V_p}{fRV_p} &= \frac{100}{60 \times 10k \times 2} = 0.833 \text{ F} \\ &= 83.3 \mu\text{F} \quad (\text{Ans}) \end{aligned}$$

$$\omega \Delta t = \sqrt{\frac{2V_r}{V_{P.M.}}}$$

$$= \sqrt{\frac{2 \times 2}{100}}$$

$$= 0.2 \text{ rad}$$

The fraction of the cycle during the diode is conducting,

$$= \frac{0.2}{2\pi} \times 100\%.$$

= 3.18% (Ans)

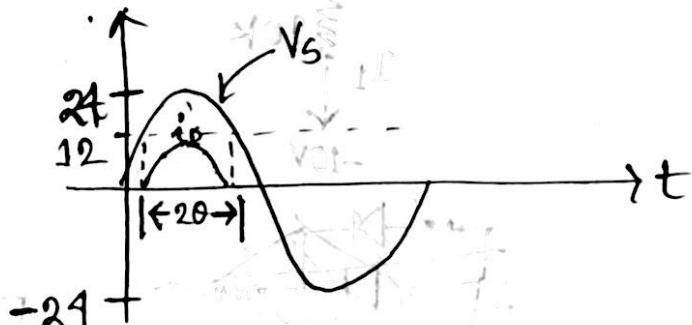
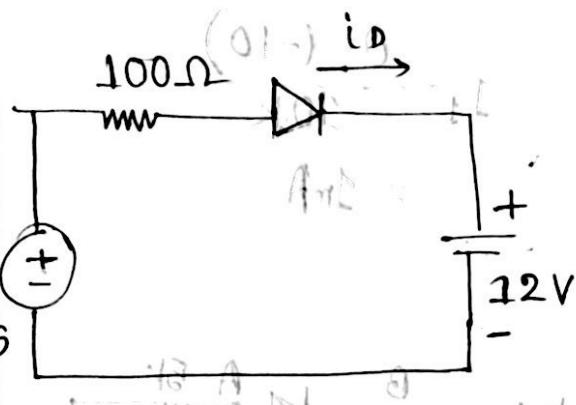


figure 4.4

Q: $i_D = ?$ in forward bias.

$$2\theta = ?$$

Applying KVL,

$$-V_s + 100i_D + V_D + 12 = 0$$

$$\Rightarrow 124 - 24 + 100i_D + 0 + 12 = 0$$

$[V_D = 0]$

ideal diode

$$\Rightarrow 100i_D = 12 \quad \text{Ans} = i_D = 0.12 \text{ A}$$

$$\therefore i_D = 0.12 \text{ A}$$

Again, $24 \cos \theta = 12$

$$\Rightarrow \cos \theta = 1/2$$

$$\therefore \theta = 60^\circ$$

function of the cycle
the diode conducts

conduction interval


Q: Reverse bias voltage = ?

Soln:

$$24 + 12 = 36 \text{ V} = \text{PIV}$$


মন্তব্য AC, DC কেওমা
থাবে গুহলে সমান
ধরণে, নাহলে 0
Previous

#

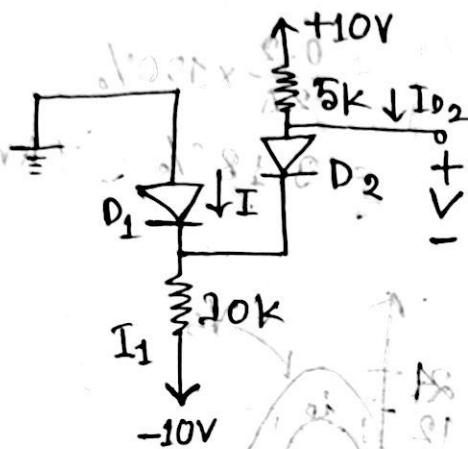

$$ID_2 = \frac{10 - 0}{5k} = 2 \text{ mA}$$
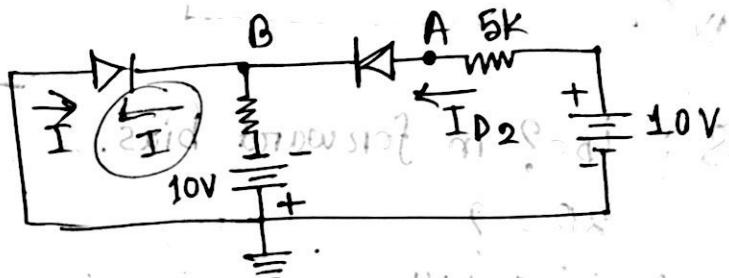
$$I_1 = \frac{0 - (-10)}{10k} = 1 \text{ mA}$$



$$\text{KCL at point } B, I + ID_2 = I_1$$

[0 or 1
কোথা কোথি]

$$\Rightarrow I + 2 \text{ mA} = 1 \text{ mA}$$

$$\Rightarrow I = -1 \text{ mA} \quad [D = OFF]$$

This means the diode is in reverse bias condition. To conduct current, the diode must be forward biased and flow in the opposite direction.


+10 +10

$$-10 + 5I_{D_2} + V_D + 10I_{D_2} - 10 = 0$$

$$\Rightarrow 15I_{D_2} - 20 = 0$$

$$\Rightarrow 15I_{D_2} = 20$$

$$\therefore I_{D_2} = 1.33 \text{ mA}$$

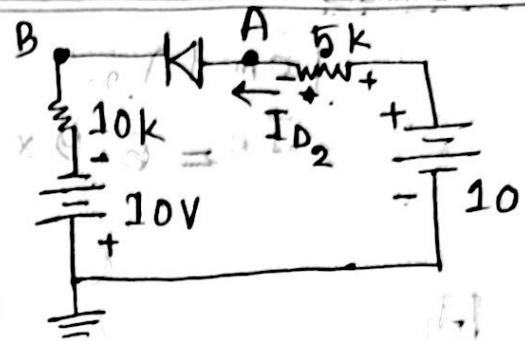

So, A to Ground Voltage, $V = -10 + I_{D_2} 10k =$
 $= (-10 + 1.33 \text{ mA} \times 10k)$
 $= 3.33 \text{ V}$

A silicone diode said to be a 1-mA device displays a forward voltage of 0.7V at a current of 1mA. Evaluate the junction constant I_s . What scaling constants would apply for a 1A diode of the same manufacture that conducts 1A at 0.7V?

$$i = I_s \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$

$$i = I_s \left(e^{\frac{1}{1 \times 25}} - 1 \right)$$

$$I_s = i e^{-\frac{V_D}{nV_T}} = 1 \times 10^{-3} e^{-\frac{1}{25}} = 6.9 \times 10^{-6} \text{ A}$$



$$V_T = 25.3 \text{ mV} - 26 \text{ mV}$$

$$= 25 \text{ mV}$$

$$i = 1 \text{ mA} = 1 \times 10^{-3} \text{ A}$$

For 1A,


$$I_s = 6.9 \times 10^{-13} A$$

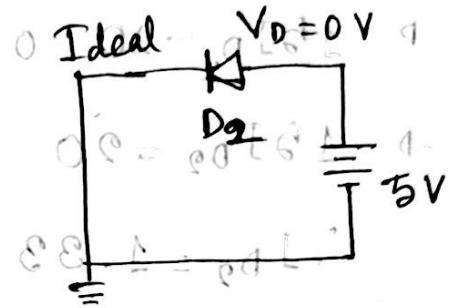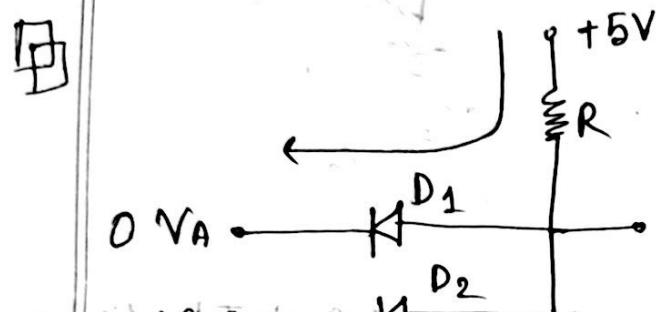



$V_o = 5V$, option b based at A, 02.
 $(+0V - A n E - L + 0E -)$

$$V_{CE(S)} = x$$

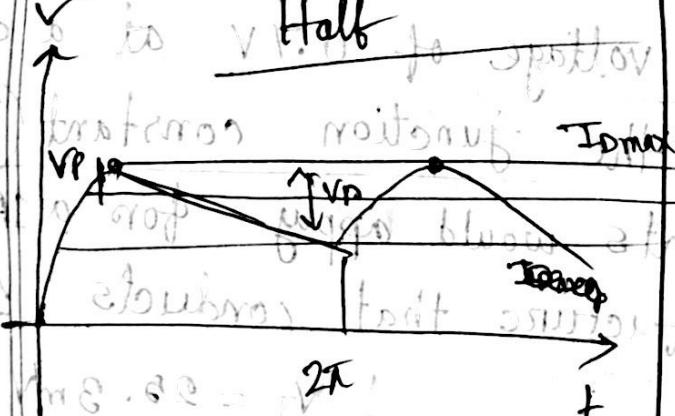point A n L o ad at bise shift profile A is
 from us to V_{Half} to option



Full
 from us to option

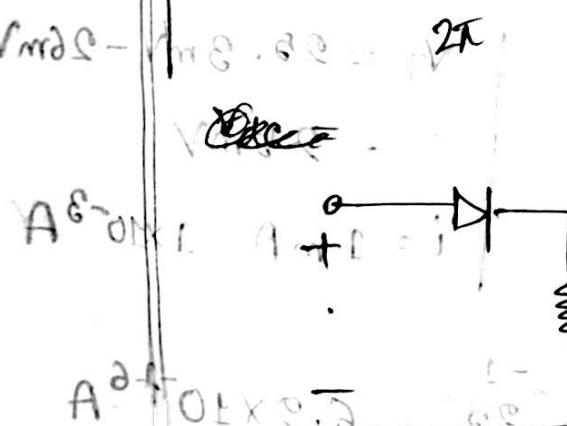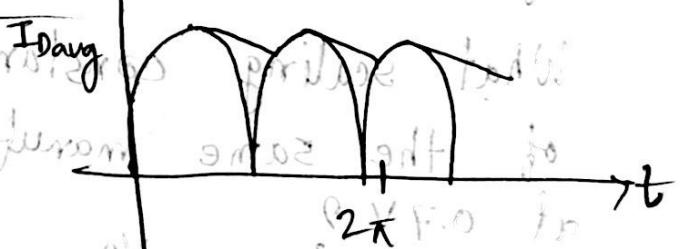

$$(1 - \frac{1}{\pi}) e^{-\frac{t}{\tau}} + \frac{1}{\pi}$$


$$(1 - \frac{1}{\pi}) e^{-\frac{t}{\tau}} + \frac{1}{\pi}$$

$$= \frac{1}{\pi} e^{-\frac{t}{\tau}}$$

C.W
01/11/24

Determine the current I_D and the diode voltage V_D for the following circuit with $V_{DD} = 5V$ and $R = 1k\Omega$. Assume that, the diode has a current of $\frac{1}{2} \text{ mA}$ at a voltage of $\frac{0.7V}{V_2}$. Draw the load line and find V_{DQ} & I_{DQ} .

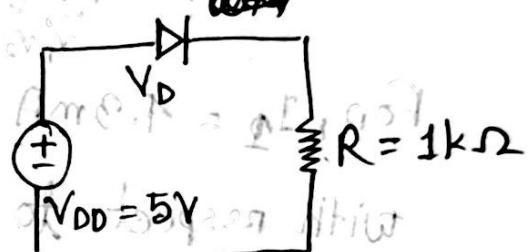Soln: $I_D = \frac{V_{DD} - V_D}{R} = \frac{5 - 0.7}{1k\Omega} \text{ mA} = 4.3 \text{ mA}$



$$I_D = \frac{5}{1} = 5 \text{ mA}$$

Applying KVL, $-V_{DD} + V_D + IR = 0$

$$\Rightarrow -5 + V_D + (5 \times 1) = 0$$

$$\Rightarrow V_D = 0V$$

\therefore Ideal diode

KVL, $-V_{DD} + V_D + I_D R = 0$

$$\therefore I = \frac{V_{DD} - V_D}{R}$$

Again: Let, current 1 mA , $V_D = 0.7V$

when,

$$I_1 = 1 \text{ mA}$$

Then

$$V_1 = 0.7V$$

$$V_2 - V_1 = 2.3V_T \log\left(\frac{I_2}{I_1}\right)$$

$$\Rightarrow V_2 = V_1 + 2.3V_T \log\left(\frac{I_2}{I_1}\right)$$


$$= 0.7 + 0.06 \log \frac{4.3}{1}$$

$$= 0.738V$$

Assumption
 $V_1 = 0.7V$

$$2.3V_T = 60 \text{ mV}$$

$$I_2 = 10I_1$$

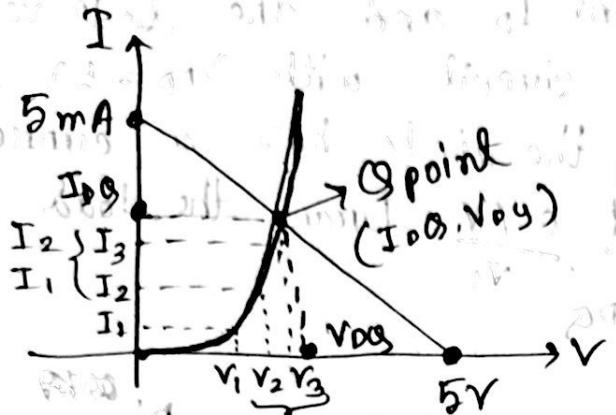

For, $I_{DQ} = 4.3 \text{ mA}$, Then $V_1 = 0.738 \text{ V}$

with respect to I_1, V_1 ,

$$I_{DQ} = \frac{V_{DD} - V_D}{R_L} = \frac{5 - 0.738}{1k} = 4.262 \rightarrow V_2$$

$$V_2 = V_1 + 2.3 V_T \left(\frac{I_2}{I_1} \right)$$

$$= 0.738 + 0.06 \left(\frac{4.262}{1.3} \right)$$

$$V_2 = 0.737 \text{ V}$$

Cutting voltage $0.738 \text{ V} = V_D$. So, Current rate is changing but the voltage is same.

$$\text{let, } I_D = 0 \\ V_D = V_{DD} = 5 \text{ V}$$

$$\left| \begin{array}{l} V_D = 0 \\ I = \frac{V_{DD} - V_D}{R} = \frac{5}{1} = 5 \text{ mA} \end{array} \right.$$

$$V_d = AC$$

$$V_D = DC$$

Small Signal Model (AC+DC)

$$V_D(t) = V_d(t) + V_D$$

For forward bias,

$$I_D = I_s e^{\frac{V_D}{nV_T}}$$

$$I_D = I_s e^{\frac{V_D}{nV_T}}$$

$$= I_s e^{\frac{(V_d + V_D)}{nV_T}}$$

~~$$= I_s e^{\frac{V_d + V_D}{nV_T}}$$~~


$$= I_s e^{\frac{(V_d + V_D)}{nV_T}}$$

$$= I_s \left[e^{\frac{V_d}{nV_T}} \cdot e^{\frac{V_D}{nV_T}} \right]$$

$$= I_s e^{\frac{V_D}{nV_T}} \cdot e^{\frac{V_d}{nV_T}}$$

$$I_D = I_s e^{\frac{V_d}{nV_T}}$$
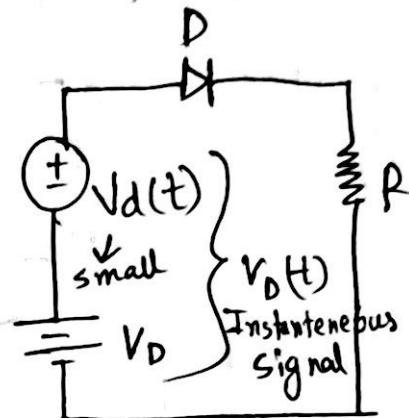
$$\boxed{*** \quad i_D(t) = I_D \left[1 + \frac{V_d}{nV_T} \right]}$$



$$e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots$$

$$\frac{V_d}{nV_T} \ll 1$$

$$\therefore \text{Let, } x = \frac{V_d}{nV_T}$$

যখন DC
ব্যাকে
পর্যাপ্ত
জাহ

Si 0.7V
Ge 0.3V
Ideal 0V

Ac (Gnd)
কো বাইলি
হবে

$$i_D(t) = I_D \left[1 + \frac{V_d}{V_T} \right]$$

$$= I_D + \frac{I_D V_d}{V_T}$$

$$= I_D + V_d \frac{I_D}{V_T}$$

DC

small signal
AC

$$\frac{V}{I} = R$$

$$\sqrt{\frac{1}{R}} = I$$

$$\Rightarrow V_R = I$$


$R = 10K \Omega$

$V^+ = 10V$

$f = 60Hz$

$V_{ac} = 1 - V_{peak} = V_d(t)$

①

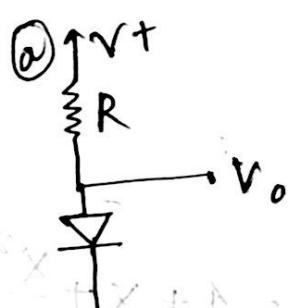

We know,

$$i_D(t) = I_D + I_D \frac{V_d}{V_T}$$

$$G_d = \frac{I_D}{V_T}$$

$$r_d = \frac{V_T}{I_D}$$


$$r_d = \frac{26mV}{I_D}$$

Diode Internal
resistance

$I_D = \frac{V_o}{R}$

$$= \frac{V_o - V_D}{R}$$

$$= \frac{10 - 0.7}{10} = 0.93mA$$

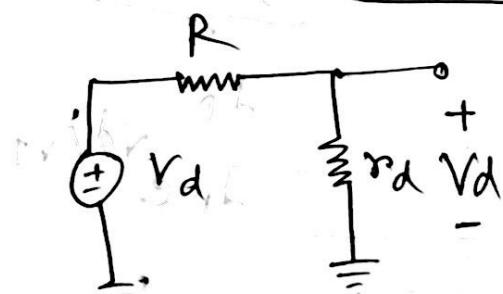

$$V_f \approx (25 \text{~} 26) \text{ mV}$$

AC } $r_d = \frac{26 \text{ mV}}{I_D} = \frac{26 \text{ mV}}{0.93 \text{ mA}} = 27.9 \Omega$

Using VDR,

$$V_d = 1 \times \frac{r_d}{R + r_d} = 1 \times \frac{27.9 \Omega}{10k + 27.9 \Omega} = 0.73 \text{ mV}$$

$$= 2.78 \text{ mV}$$

$$I_D = \frac{V_d}{V_T}$$

AC + DC

$$\therefore i_b(t) = 0.93 \text{ mA} + I_D \frac{V_d}{V_T}$$

instantaneous current

$$= 0.93 + \left(0.93 \frac{2.78}{26} \right)$$

$$= 1.029 \text{ mA}$$



For the case @ $R = 10k\Omega$. The power supply V_+ has a dc value of 10V on which is superimposed a 1860Hz sinusoid of 1-V peak amplitude. calculate both the dc voltage of the diode and the amplitude of the sine-wave signal appearing across it. Assume, the diode to have a 0.7V drop at 1-ma current.

12/11/24
Zener diode

Reverse bias & current pass




V_Z = Zener Voltage

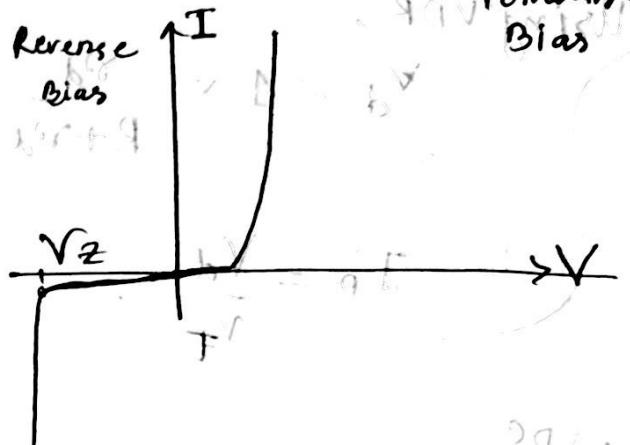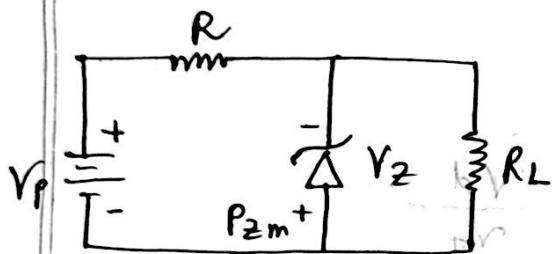

P_{Zm} = maximum Zener power = $\frac{1}{2} I_{Zm} V_Z$

① যখন Zener কে open করবে,

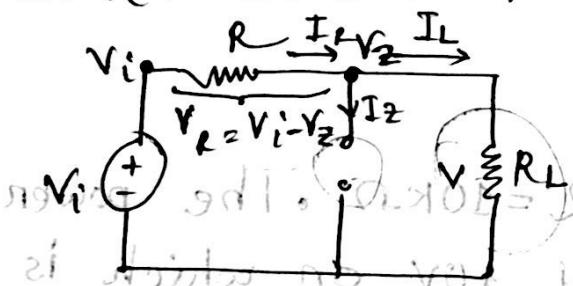

Using VDR,

$$\therefore I_{Zm} = \frac{P_{Zm}}{V_Z}$$

$$V = \frac{Vi R_L}{R + R_L}$$

$V > V_Z \rightarrow$ Zener ON (Reverse Bias & current pass)

$V < V_Z \rightarrow$ Zener OFF

Using Ohm's law, $I_R = \frac{V_i - V_Z}{R}$

$$I_L = \frac{V_Z}{R_L}$$


Applying KCL at node Z, $I_R = I_Z + I_L$

$$\Rightarrow I_L = I_R - I_Z$$

For the Zener diode of the following circuit, find V_L , V_R , I_z , P_z

Repeat for $R_L = 3k\Omega$
 $V < V_z$, Zener 'OFF'

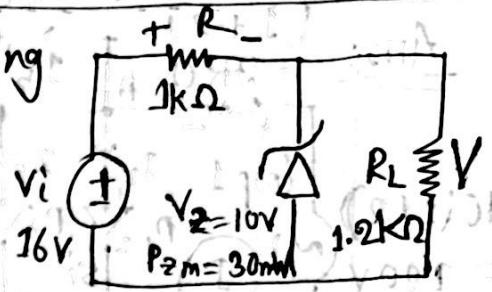Using VDR, $V = \frac{V_i R_L}{R + R_L} = \frac{16 \times 1.2}{1 + 1.2} = 8.7V$



$$I_R = I_L = \frac{V_i}{R + R_L} = \frac{16}{1 + 1.2} = 7.27 \text{ mA}$$

$$V_R = I_R R = 7.27 \text{ mA} \times 1k = 7.27V$$

$$V_L = I_L R_L = 7.27 \times 1.2k = 8.724V$$

$$I_z = 0 \therefore P_z = 0W$$



for $3k\Omega$,

$V > V_z$, Zener 'ON'

$$\therefore V = \frac{V_i R_L}{R + R_L} = \frac{16 \times 3}{1 + 3} = 12V$$

$$I_R = \frac{V_R}{R} = \frac{6}{1k} = 6 \text{ mA}$$
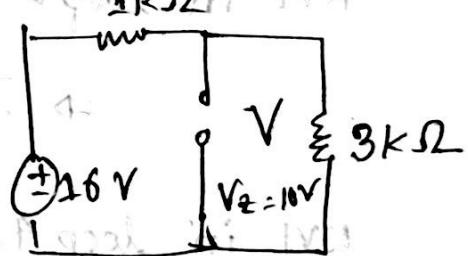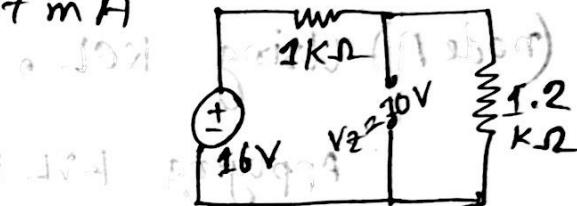
$$I_L = \frac{V_z}{R_L} = \frac{10}{3k} = 3.33 \text{ mA}$$





$$V_R = V_i - V_z = 16 - 10 = 6V$$

$$\left. \begin{aligned} I_z &= I_R - I_L = 6 - 3.33 \\ &= 2.67 \text{ mA} \end{aligned} \right\} \text{KCL}$$

$$P_z = V_z I_z = 10 \times 2.67$$

Quiz-1

Wrong Answer

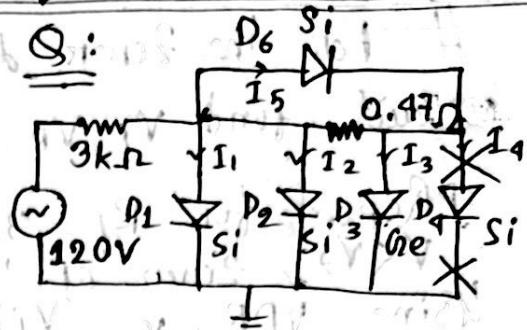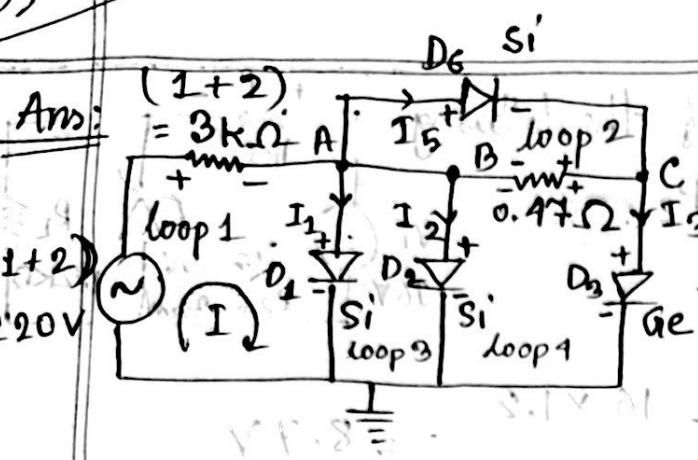

$$I_4 = 0A$$

(node A) Using KCL, $I = I_1 + I_2 + I_5 = 0.3976$

Applying KVL in loop 1, $-120 + 3kI + 0.7 = 0$

$$\Rightarrow 3kI = 119.3$$

$$\therefore I = \frac{119.3}{3000} = 0.3976 A$$

KVL in loop 2, $+0.7 + 0.47I_3 = 0$

$$\Rightarrow I_3 = \frac{-0.7}{0.47} = -1.489 A.$$

KVL in loop 4, $-0.7 - 0.47I_3 + 0.3 = 0$


$$\Rightarrow -0.47I_3 = 0.4$$

$$\Rightarrow I_3 = -0.85 A$$

Solution

$$V_R = (40 - 0.7) V = 39.3 \text{ V}$$
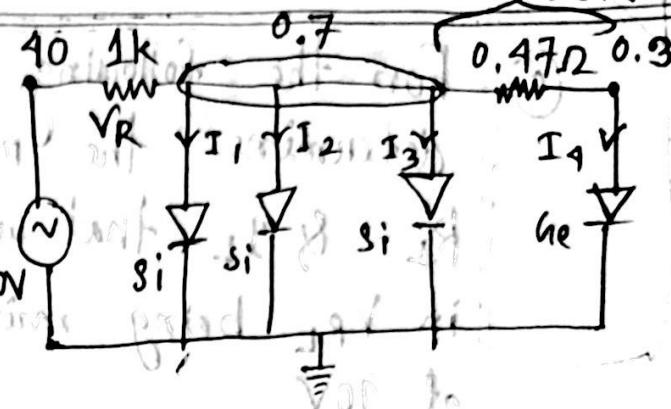
$$I_R = \frac{39.3}{1k} = 39.3 \text{ mA}$$




$$I_{1B} = \frac{0.4V}{0.47\Omega} = 0.85A$$

$$39.3 - 0.85A = -38.4 \text{ mA}$$

$$I_1 = I_2 = I_3 = \frac{-38.4}{3} = -12.8 \text{ mA}$$

$$AB = AC = BC$$

VCA

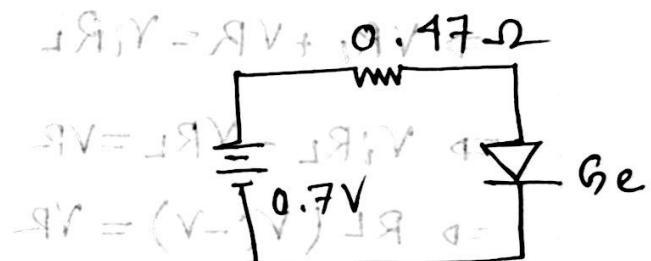

load current = ?


VL <= V : "No load voltage < V"

$$\sin \theta = \frac{VR}{VL} = \sin \theta = \frac{0.47}{0.7} = 0.67$$



Classwork

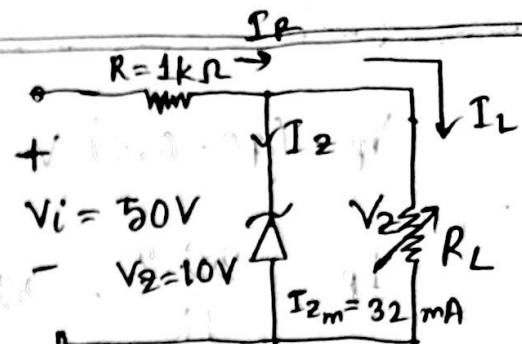- (a) For the following circuit, determine the range of R_L & I_L that will result in V_{RL} being maintained at 10V



- (b) Determine the maximum voltage rating of the diode.


$$V = \frac{Vi R_L}{R_L + R} = \frac{50 \times 1000}{1000 + R}$$

$$\Rightarrow V_{RL} + V_R = V_i R_L$$

$$\Rightarrow V_i R_L - V_{RL} = V_R$$

$$\Rightarrow R_L (V_i - V) = V_R$$
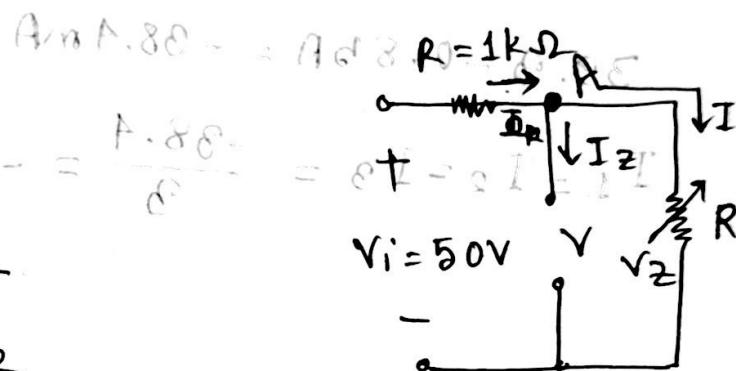
$$\Rightarrow R_{L \min} = \frac{V_R}{V_i - V}$$



$$V_R = 50 - 10 \\ = 40V$$

$V \geq V_z$, for Zener "ON" ; $V = V_z = 10V$

$$R_{L \min} = \frac{10 \times 1k}{50 - 10} = 250\Omega$$

$$I_L = \frac{V_i}{R + R}$$

KVL in loop 1, $-50 + 1I_R + V_z = 0$

$$\Rightarrow I_R = 50 - 10$$

$$\therefore I_R = 40 \text{ mA}$$

$$I_{L \max} = \frac{V}{R_{L \min}} = \frac{V_2}{R_{L \min}} = \frac{10}{250} = 0.04 A = 40 \text{ mA}$$

$$R_{L \max} = \frac{V_2}{I_L}$$



KCL at node A,

$$I_R = I_{Z_m} + I_L$$

$$\Rightarrow 40 = 32 + I_L$$

$$\Rightarrow I_L = 8 \text{ mA}$$
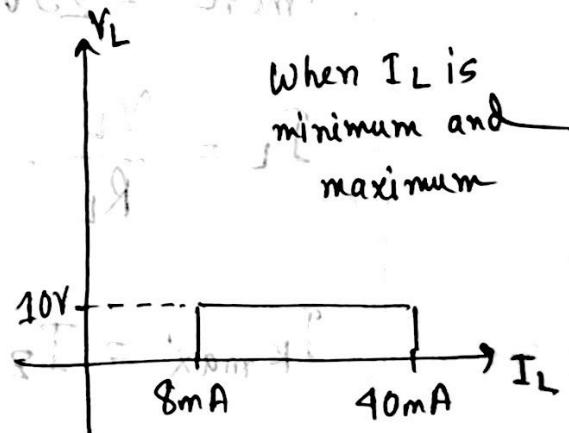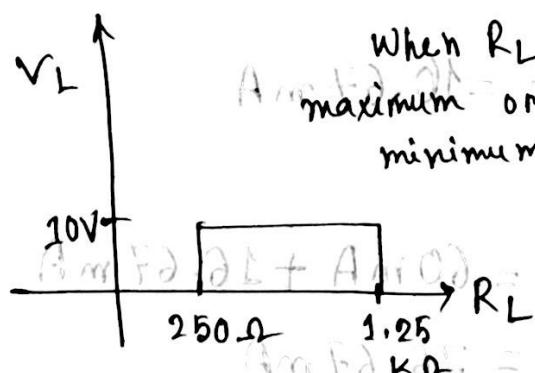
$$R_{\max} = \frac{10}{8} = 1.25 \text{ k}\Omega$$



$$P_Z = V_2 I_{Z_m} = 10 \times 32 \text{ mA} = 0.32 \text{ W}$$

$$= 0.32 \text{ W}$$

$$= 0.32 \text{ W}$$



Determine the range of V_i .

Ans P Ans Q

$$V = \frac{V_i R_L}{R_L + R}$$

$$\Rightarrow V_{RL} + V_R = V_i R_L$$

$$\Rightarrow V_i = \frac{R_L + R}{R_L} V_{RL}$$

$$= \frac{20 (1.2k + 220)}{1.2k}$$

$$\therefore V_{min} = 23.67 \text{ V}$$



$$I_L = \frac{V_L}{R_L} = \frac{20}{1200} = 16.67 \text{ mA}$$

$$I_{R_{max}} = I_{2m} + I_L = 60 \text{ mA} + 16.67 \text{ mA} \\ = 76.67 \text{ mA}$$

$$V_{imax} = (I_{R_{max}} \times R) + V_2$$

$$= (76.67 \text{ mA} \times 220) + 20$$


$$= 36.87 \text{ V}$$

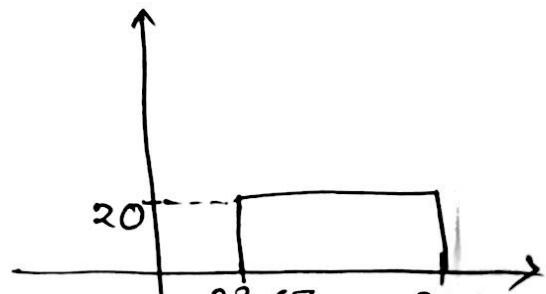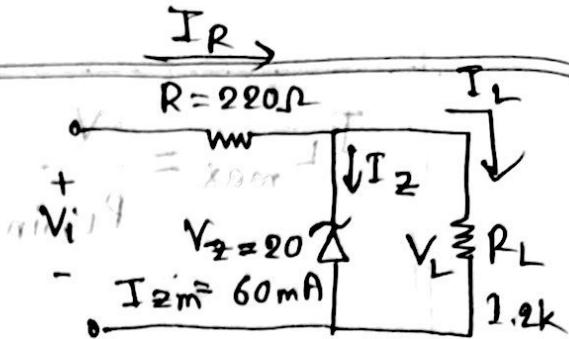

Example - 4.7 → Sedra (Page - 205)

The 6.8 V Zener diode in the following circuit is specified to have $V_Z = 6.8V$ at $I_{ZK} = 5mA$, $R_Z = 20\Omega$ and $I_{ZK} = 0.2mA$. The supply voltage V^+ is nominally 10V but can vary by $\pm 1V$.

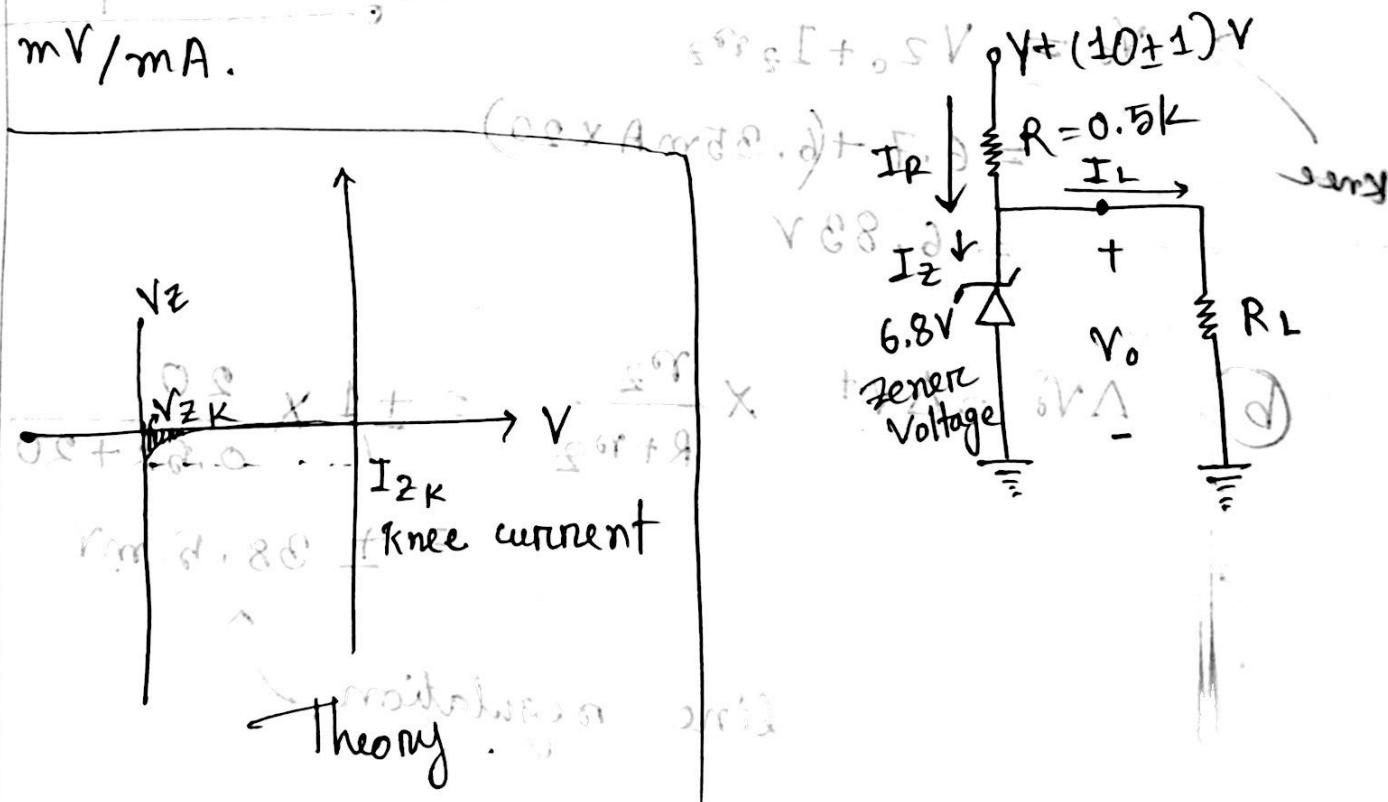- (a) Find the V_o with no load and with V^+ at its nominal value.
- (b) Find the change in voltage V_o resulting from the change $\pm 1V$ change in V^+ .
- (c) Find the change in V_o resulting from connecting a load R_L that draws a current $I_L = 1mA$ and hence find the load regulation in mV/mA .




(due to open mouth & F.P. distance)

$$V_0 = V_2 + I_2 r_2$$

$$I_R = I_2 + I_L \quad \text{but } I_L = 0 \quad \Rightarrow \quad I_R = I_2$$


$$0.5k\Omega = I_2 + 0$$

$$\therefore I_2 = 5 \text{ mA}$$

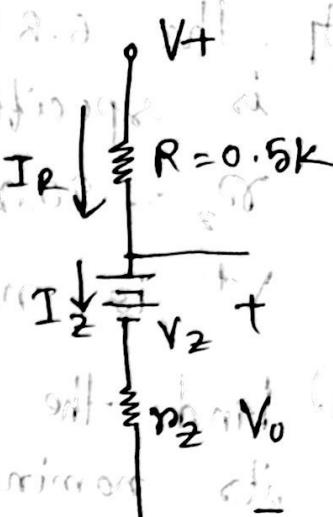

$$\text{Ohm's law} \rightarrow I = I_2 = \frac{V^+ - V_{20}}{R + r_2}$$
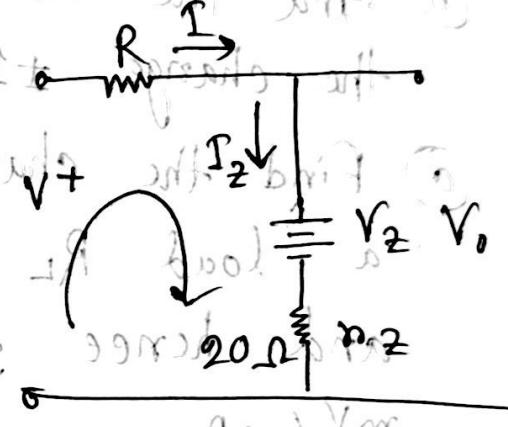
$$A_m = I_{\text{max}} = \frac{10 - 6.7}{0.5k + 20}$$



$$V_0 = V_{20} + I_2 r_2$$

$$= 6.7 + (6.35 \text{ mA} \times 20) \\ = 6.83 \text{ V}$$

$$(b) \Delta V_0 = \Delta V^+ \times \frac{r_2}{R + r_2} = \pm 1 \times \frac{20}{0.5k + 20}$$

$$\therefore \Delta V_0 = \pm 38.5 \text{ mV}$$

line regulation




C.29

2029

11/11/21

SPY Exam 1


Clamper circuit with

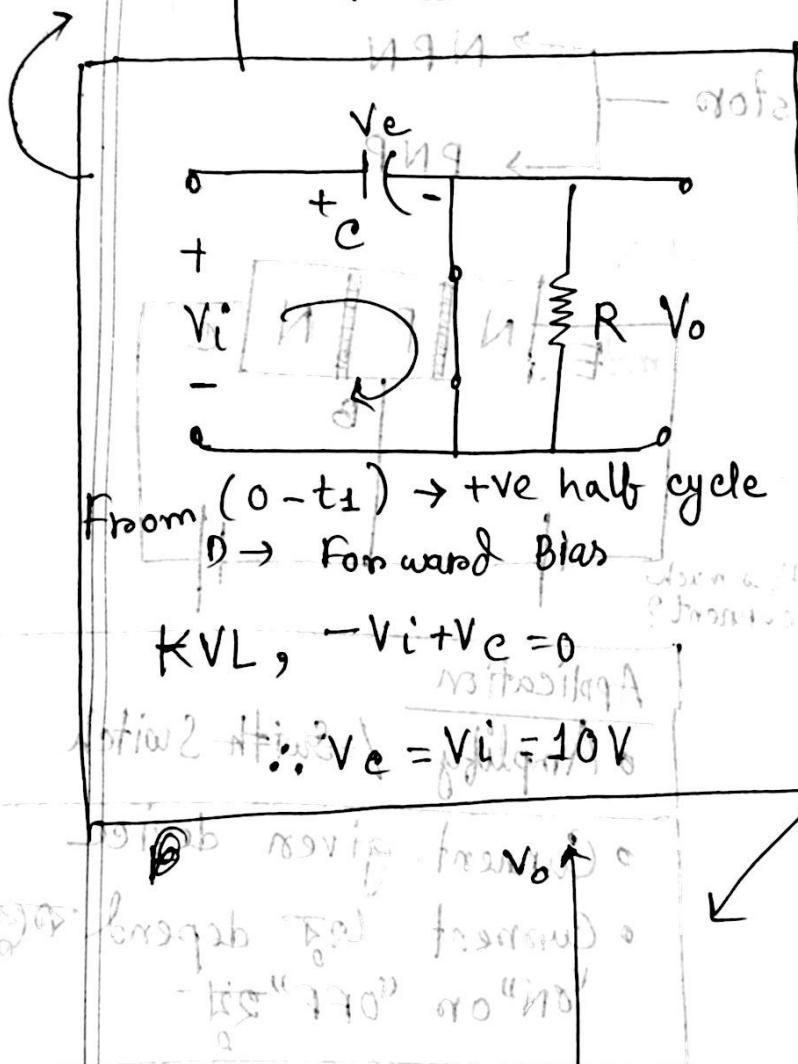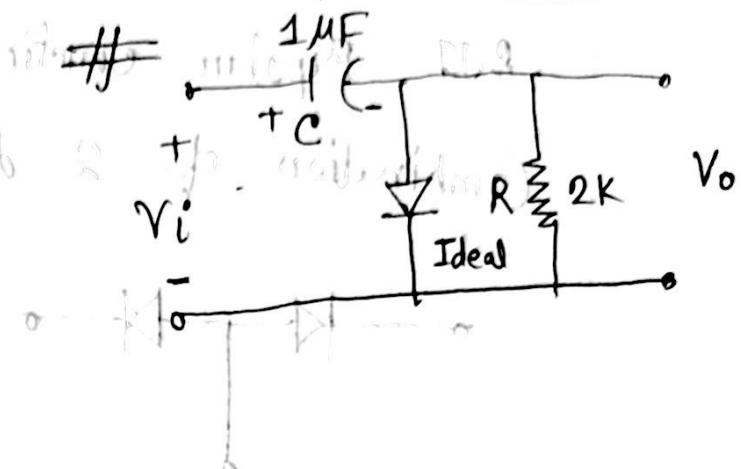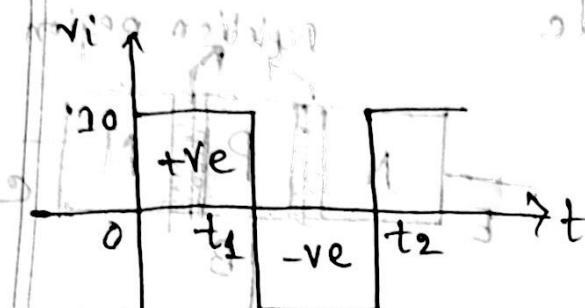

$$\text{KVL}, -V_i + V_c = 0$$

$$\therefore V_c = V_i = 10V$$

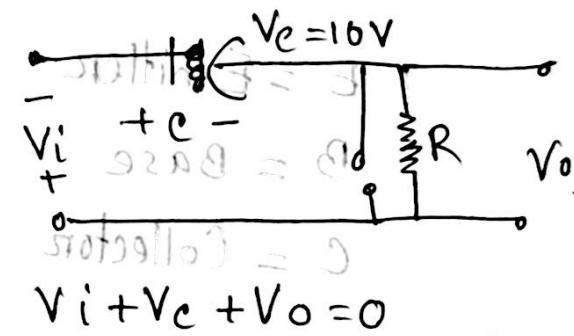From $(t_1 - t_2) \rightarrow$
-ve half cycle




$$10 + 10 + V_o = 0$$

$$\therefore V_o = -20V$$

∴ Discharge time
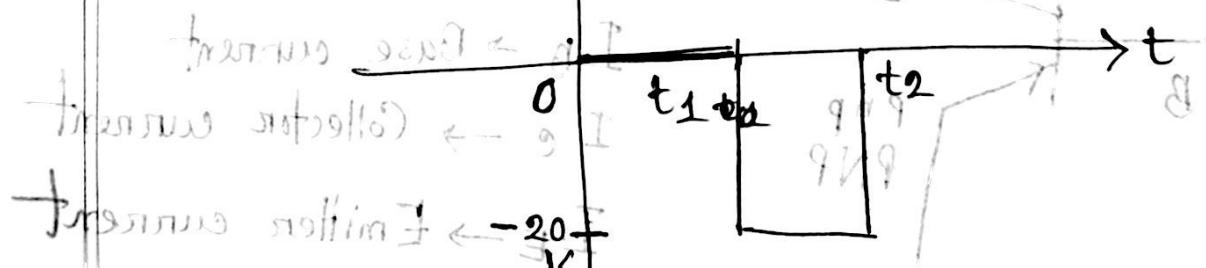
$$RC = \tau = 1\text{ mF} \times 2K = s$$




Transistors

BJT

BJT = Bipolar Junction Transistor

Combination of 2 diode

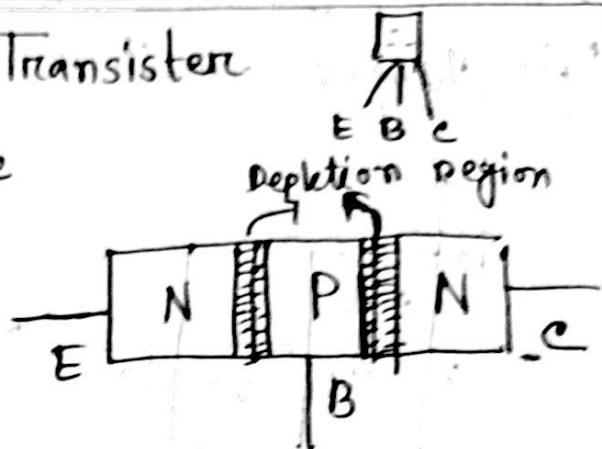

2 types of transistors

→ NPN



→ PNP

E = Emitter

B = Base


C = Collector

Transistor
on or off

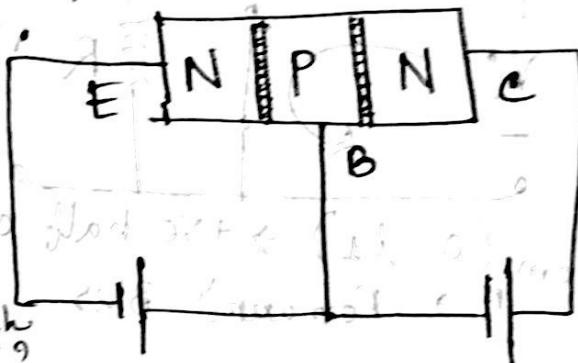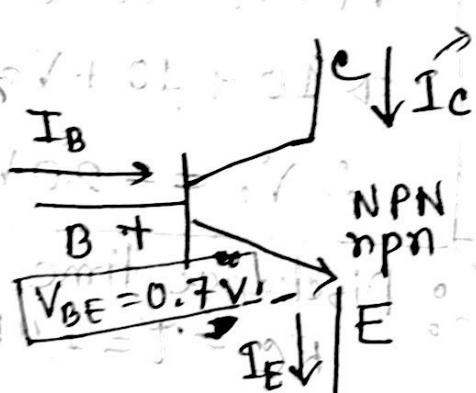

Application

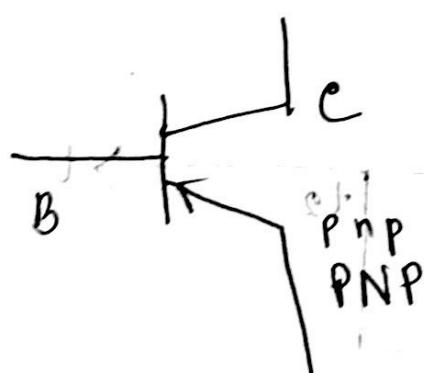- Amplify / ~~switch~~ Switch
- Current given device
- Current এর depend করে "ON" or "OFF" হয়



$I_B \rightarrow$ Base current

$I_C \rightarrow$ Collector current

$I_E \rightarrow$ Emitter current



$$I_B \rightarrow I_C$$

$$I_E$$

KCL, $I_E = I_B + I_C$

α } current gain
 β

$$\alpha = \frac{I_C}{I_E} \approx 1$$

$$I_C = \alpha I_E$$


I_B is much less than I_C, I_E

Common Base = Base to ground ম্যান

Common Collector = Collector " " "

Common Emitter = Emitter " " "


$$I_C = \beta I_B$$

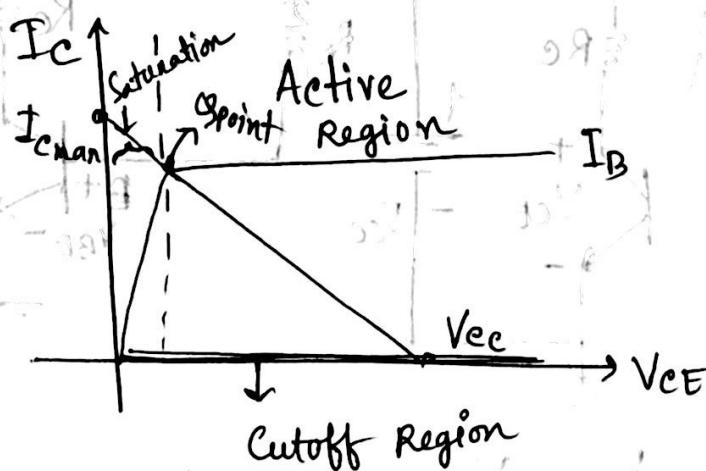

Cutoff Region

Fixed Bias

Boil State


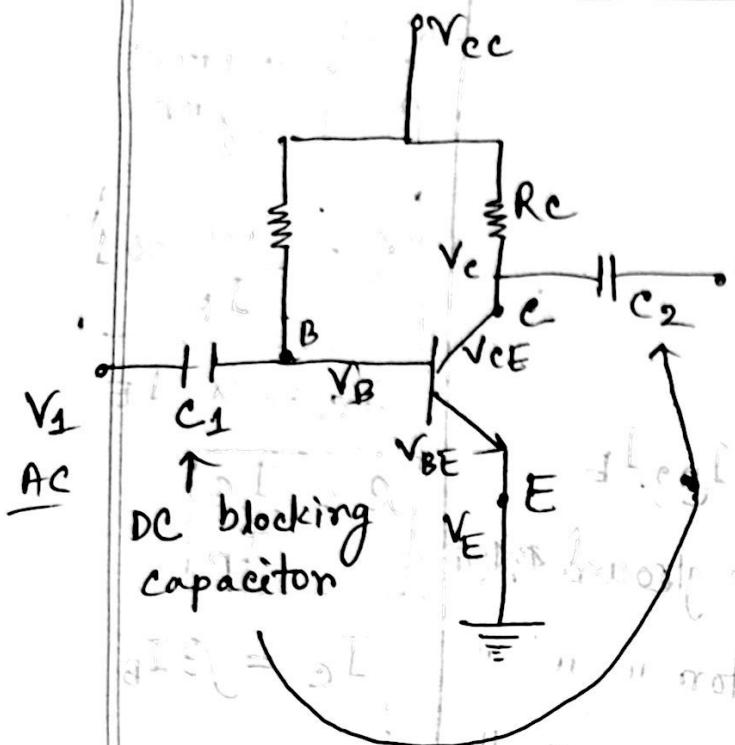


$A_{c,dc}$

$$V_{BE} = 0.7$$

$$V_c = V_{ce}$$

$$V_{ce} = I_c R_c$$

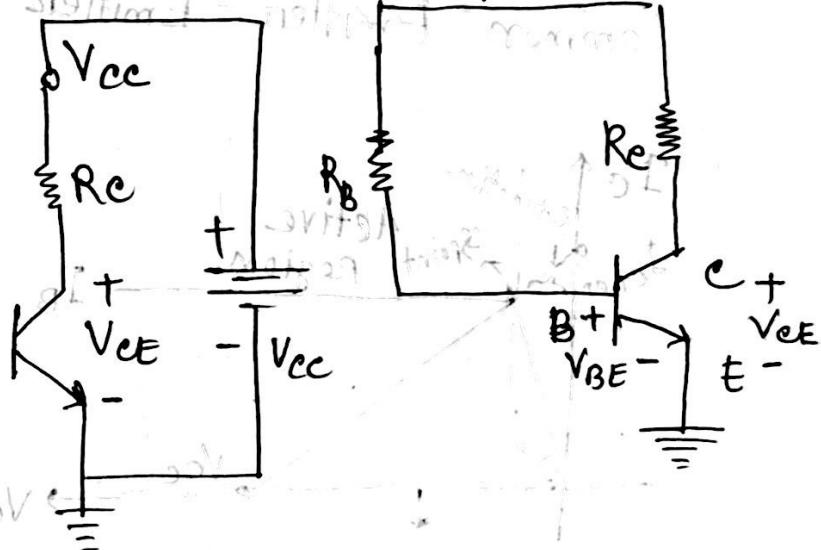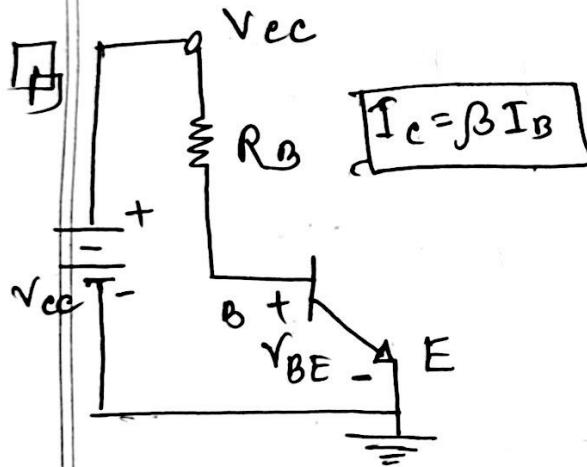

BE loop,

$$-V_{cc} + I_B R_B + V_{BE} = 0$$

$$\Rightarrow I_B = \frac{V_{cc} - V_{BE}}{R_B}$$

$$I_c = \beta I_B$$

$$T_F = T_n + T_e$$

$$-V_{cc} + I_c R_c + V_{ce} = 0$$

$$\Rightarrow V_{ce} = V_{cc} - I_c R_c$$

$V_{BE} = 0.7V$


$V_{CC} = 20V$

Determine

$I_B, I_C, I_E \& V_{CE}$

BE
loop?
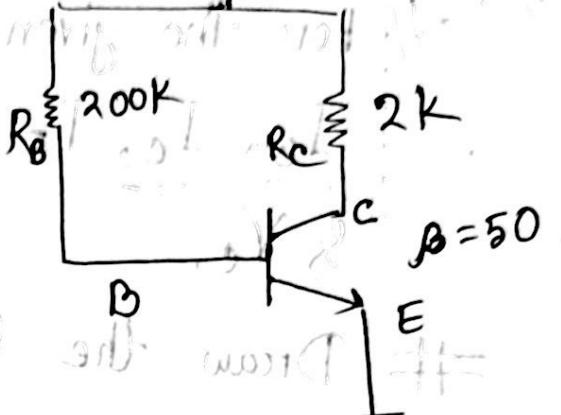
$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{20 - 0.7}{200k}$$



$$= 0.0965 \text{ mA (Ans)}$$


$$I_C = \beta I_B = 50 \times 0.0965 = 4.825 \text{ mA (Ans)}$$

$$V_{CE} = V_{CC} - I_C R_C = 20 - (4.825 \times 2)$$

$$= 10.35 \text{ V}$$

$$I_E = I_B + I_C = 4.925 \text{ mA (Ans)}$$

#

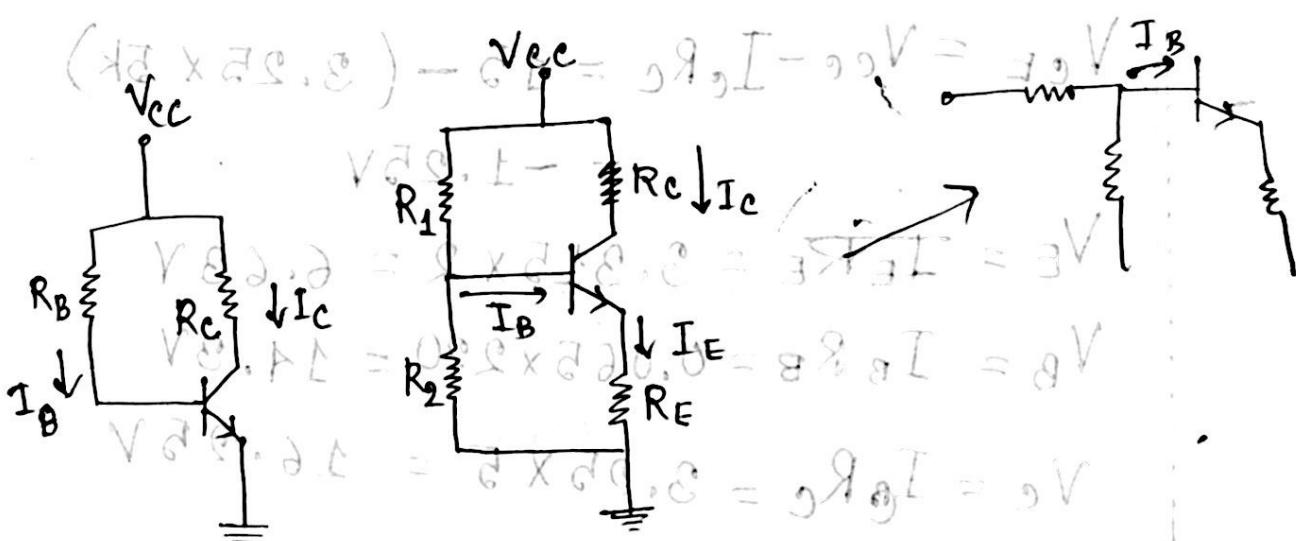

Fixed Bias

Voltage
divider bias

~~21/11/2021~~

~~Wrong~~

$V_{CC} = 15V$

For the given circuit determine

I_B , I_C , I_E , V_{BE} , V_B , V_E , V_{CE}

& V_c .

Draw the load line.

$$V_{BE} = 0.7V$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{15 - 0.7}{220} = 0.065mA$$

$$I_C = \beta I_B = 50 \times 0.065 = 3.25mA$$

$$I_E = I_B + I_C = 0.065 + 3.25$$

$$= 3.315mA$$

$$V_{CE} = V_{CC} - I_C R_C = 15 - (3.25 \times 5k)$$

$$= -1.25V$$


$$V_E = I_E R_E = 3.315 \times 2 = 6.63V$$

$$V_B = I_B R_B = 0.065 \times 220 = 14.3V$$

$$V_C = I_C R_C = 3.25 \times 5 = 16.25V$$

solid state
with biasing

solid load

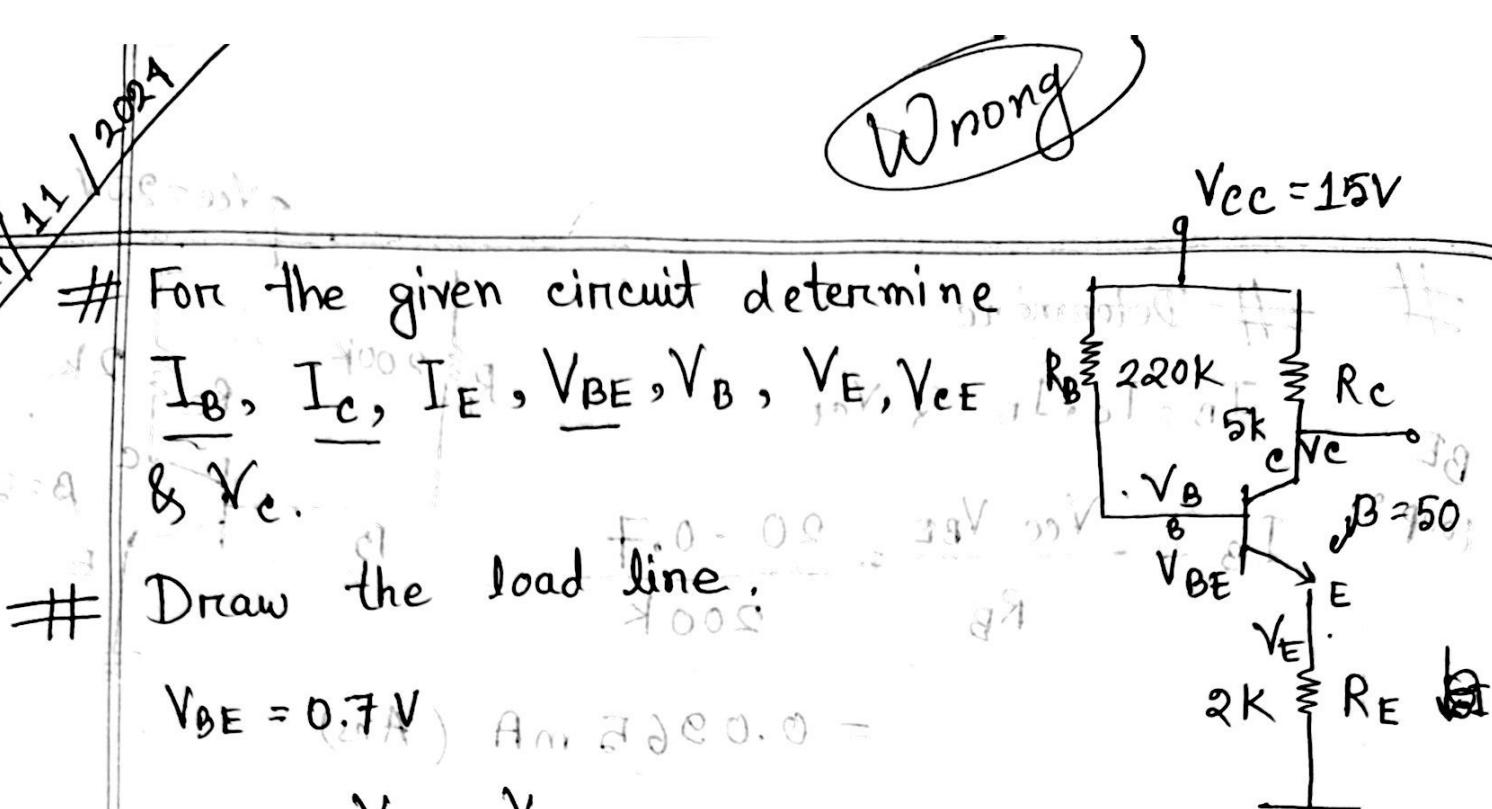

$$h_{ain} = \beta$$

$I_E = I_C + I_B$ (at 1mA input current)

$$\Rightarrow I_E = \beta I_B + I_B$$

$$\Rightarrow I_E = I_B (\beta + 1) = 0.044 (50 + 1) = 2.2 \text{ mA}$$

Soln:

∴ Applying KVL in B-E loop,

$$-V_{CC} + I_B R_B + V_{BE} + I_E R_E = 0$$

$$\Rightarrow -V_{CC} + I_B R_B + V_{BE} + (\beta + 1) I_B R_E = 0$$

$$\Rightarrow I_B (R_B + (\beta + 1) R_E) = V_{CC} - V_{BE}$$

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

$$= \frac{15 - 0.7}{220k + (50+1)2k} = 0.044 \text{ mA}$$

$$\therefore I_C = \beta I_B = 50 \times 0.044 = 2.2 \text{ mA}$$

$$\therefore V_E = I_E R_E = 2.2 \text{ mA} \times 2k = 4.4 \text{ V}$$

$$\therefore V_B = V_B - V_E \Rightarrow$$

$$V_B = V_{BE} + V_E = (0.7 + 4.4) = 5.1 \text{ V}$$

∴ Applying KVL in C-E Loop,

$$-V_{CE} + I_C R_C + V_{BE} + I_E R_E = 0 \quad \text{--- Eqn 1}$$

$$\text{Ans. } -V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$= 15 - (2.2 \text{ mA} \times 5) - (2.2 \text{ mA} \times 2k)$$

$$= -1.1 \text{ V}$$

$$\therefore V_{CE} = V_C - V_E$$

$$\Rightarrow V_C = V_{CE} + V_E = -1.1 \text{ V} + 4.4 \text{ V}$$

$$= 3.3 \text{ V} \quad (\text{Ans})$$

From equation ①

$$-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0$$


$$\because I_C \approx I_E$$

$$-V_{CC} + I_C R_C + V_{CE} + I_C R_E = 0$$

$$\text{Let, } V_{CE} = 0$$

$$I_C = \frac{V_{CC}}{R_C + R_E} = \frac{15}{(5+2)k} = 2.14 \text{ mA}$$



$$I_C = 2.14 \text{ mA}$$

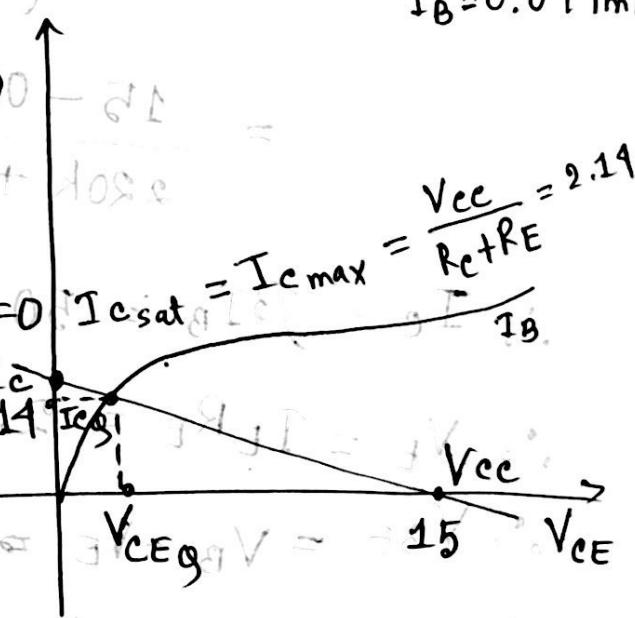

Let, $I_C = 0$

$$V_{CE} = V_{CC} = 15V$$


Voltage Divider Bias

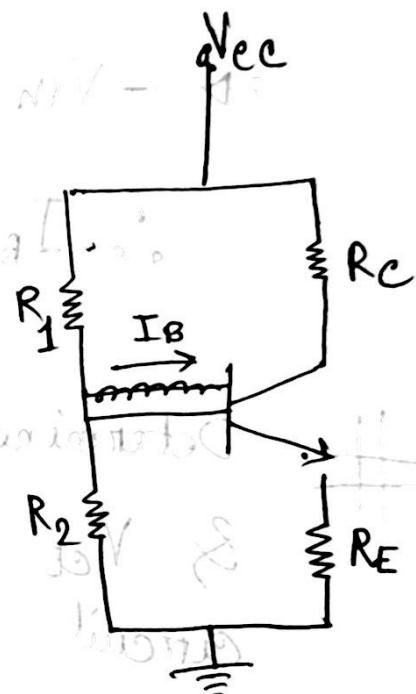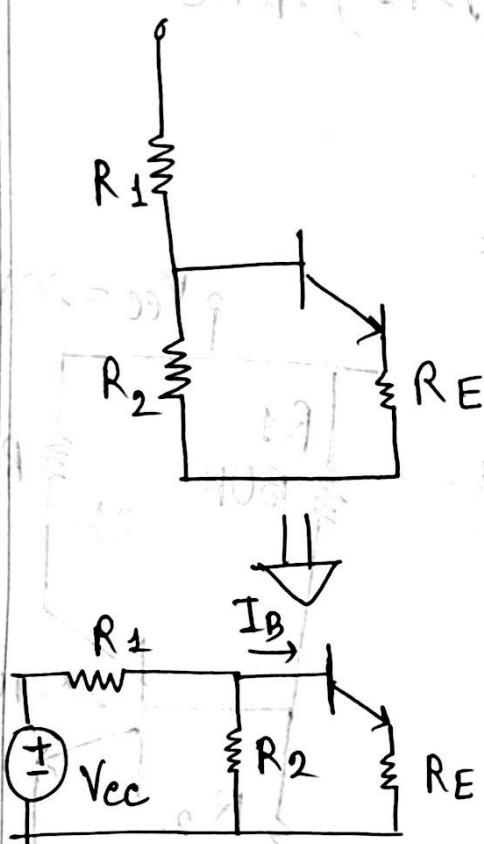


Using Thevenin's Theorem,

$$R_{th} : R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$
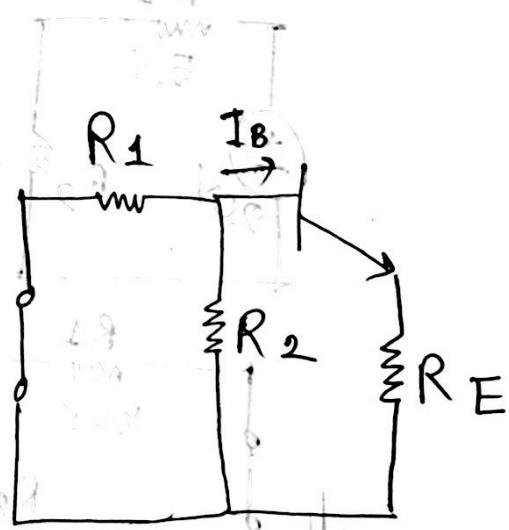
$$V_{th} : \frac{V_{CC} R_2}{R_1 + R_2} [VDR]$$



Theremin's eqv circuit;

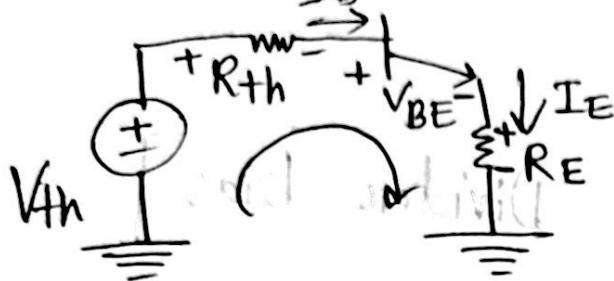

Applying KV L,




$$-V_{th} + I_B R_{th} + V_{BE} + I_E R_E = 0$$

$$\Rightarrow -V_{th} + I_B R_{th} + V_{BE} + (\beta + 1) I_B R_E = 0$$

$$\therefore I_B = \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1) R_E}$$


Determine I_B , I_c , I_E

& V_{CE} for the following circuit.

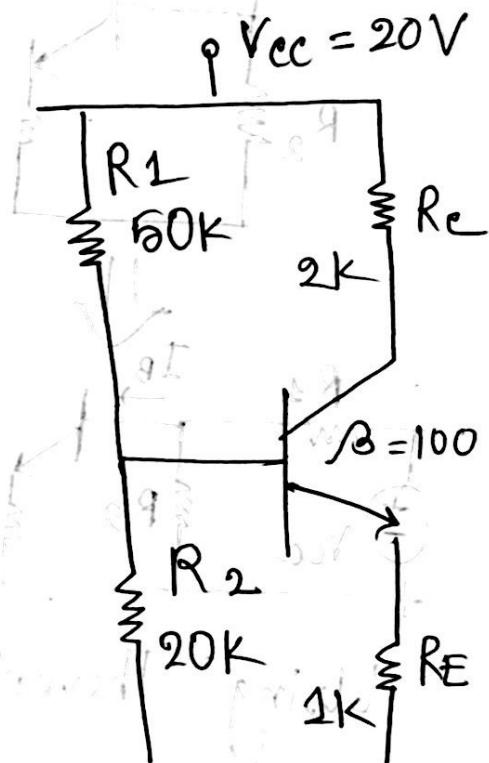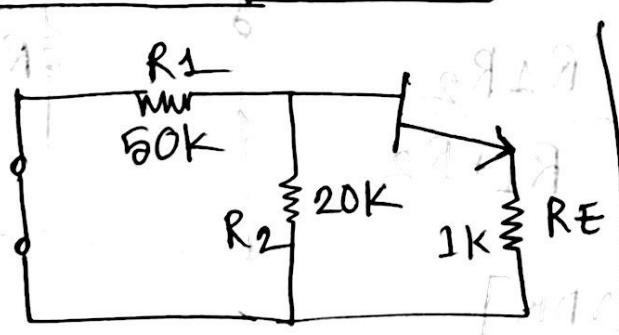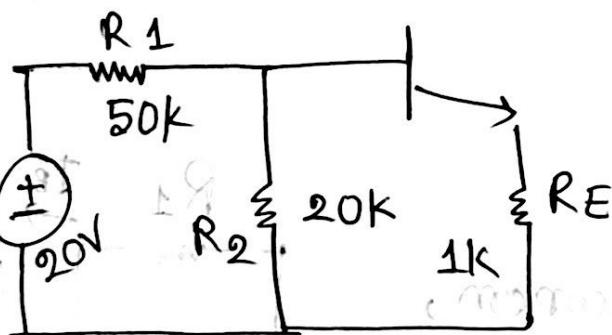

R_{th} :
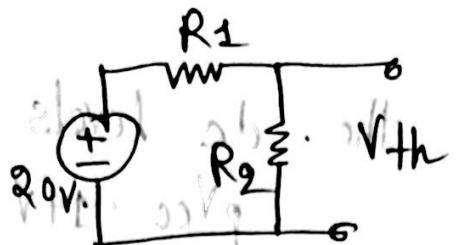
$$R_{th} = \frac{20 \times 50}{20 + 50} = 14.28 \text{ k}\Omega$$



$$V_{th} = \frac{20 \times 10}{20 + 50} = 5.714$$

14. $28k\Omega$
800mA

Applying KVL,

$$-5.714 + I_B R_{th} + V_{BE} + I_E R_E = 0$$

$$\Rightarrow -5.714 - I_B = \frac{5.714 - 0.7}{14.28 + (100+1) 1k}$$

$$= \frac{5.014}{115.28} = 0.043 \text{ mA}$$

$$I_C = \beta I_B = 14.13 \text{ mA}$$

$$I_E = I_B + I_C = 4.39 \text{ mA}$$

$$\text{KVL: } V_{CE} = V_{cc} + I_C R_C + V_{BE} + I_E R_E = 0$$

$$\Rightarrow V_{CE} = V_{cc} - I_C R_C - I_E R_E$$


$$= 6.8 \text{ V}$$

$$-0.112 \text{ V}$$



$$0.112 \text{ V}$$

26/11/2021

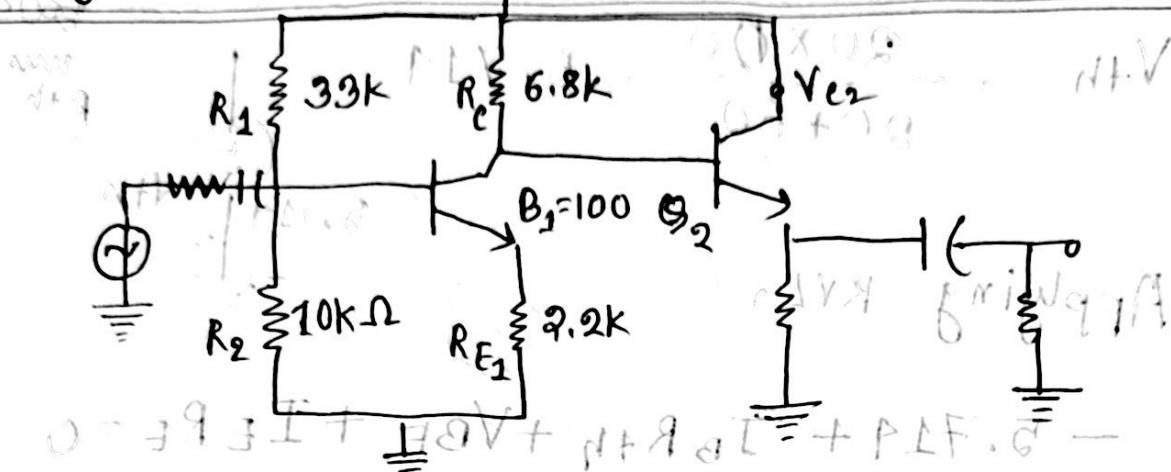Determine the dc levels for the currents and Voltages.




$$V_{ce} = F.0 - P.E.F. \delta$$

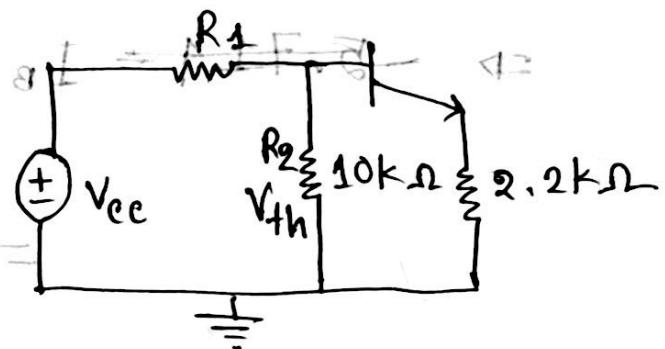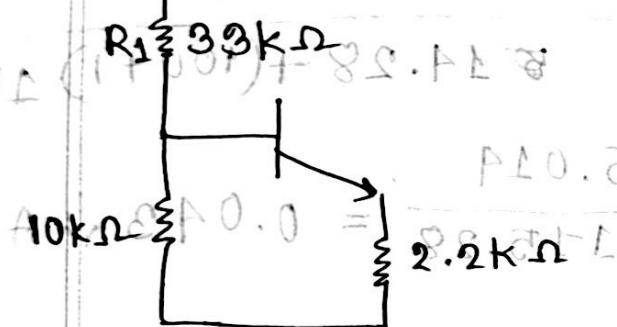

Applying Thévenin's equivalent,

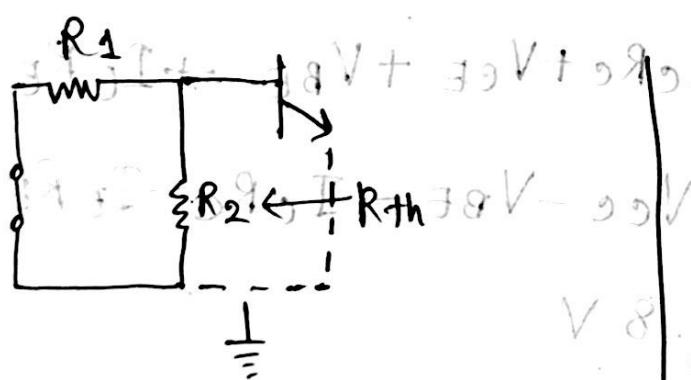
$$V_{th} = \frac{V_{cc}R_L}{R_1 + R_2} = \frac{14 \times 10k}{33k + 10k} = 3.25V$$



$$R_{th} = R_1 \parallel R_2$$

$$= 7.67k\Omega$$

Thévenin's equivalent circuit

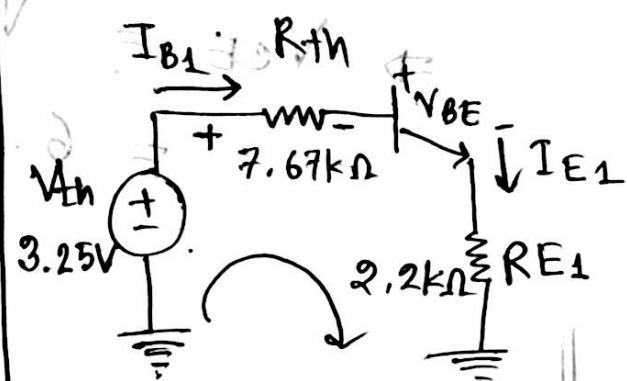


Applying KVL, $-V_{th} + I_{B1}R_{th} + V_{BE1} + I_{E1}R_{E1} = 0$

$$\Rightarrow -V_{th} + I_{B1}R_{th} + V_{BE1} + (\beta_1 + 1) I_{B1} R_{E1} = 0$$

$$\therefore I_{B1} = \frac{V_{th} - V_{BE1}}{R_{th} + (\beta_1 + 1)R_{E1}} = \frac{3.25 - 0.7}{7.67k + (100 + 1)2.2k}$$

$$= 0.011 \text{ mA} = 11 \mu\text{A}$$

Again,

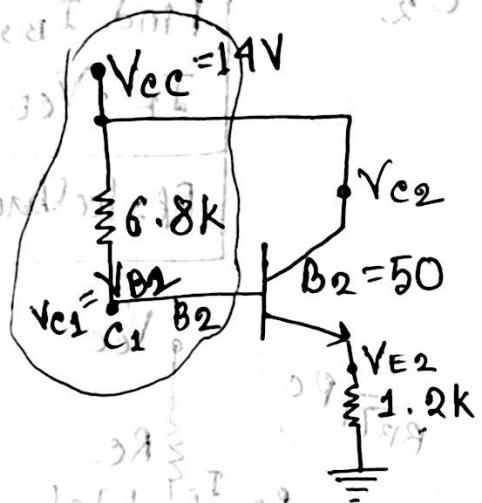

$$\therefore V_{c1} = V_{B2} = V_{cc} - I_{c1}R_c$$

$$= 19 - (1.1 \text{ mA} \times 6.8k)$$

$$= 6.52 \text{ V}$$

$$\therefore I_{E1} = I_{c1} + I_{B1} = 1.1 \text{ mA} + 0.011 \text{ mA} = 1.11 \text{ mA}$$

$$\therefore V_{E1} = I_{E1}R_{E1} = 1.11 \text{ mA} \times 2.2k = 2.44 \text{ V}$$

$$\therefore V_{BE2} = V_{B2} - V_{E2} = 0$$

$$\therefore V_{E2} = V_{B2} - V_{BE2} = (6.52 - 0.7) \text{ V} = 5.82 \text{ V}$$


$$\therefore I_{E2} = \frac{V_{E2}}{R_{E2}} = \frac{5.82}{1.2k} = 4.85 \text{ mA}$$

$$\therefore V_{c2} = V_{cc} = 19 \text{ V}$$

$$I_{C'} \gg I_B$$


$$I_C' = I_C$$

$$I_{C_2} \approx I_{E_2}$$

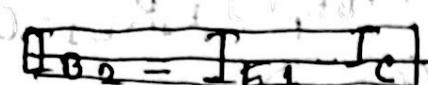

$$I_{E_2} = (\beta_2 + 1) I_{B_2}$$


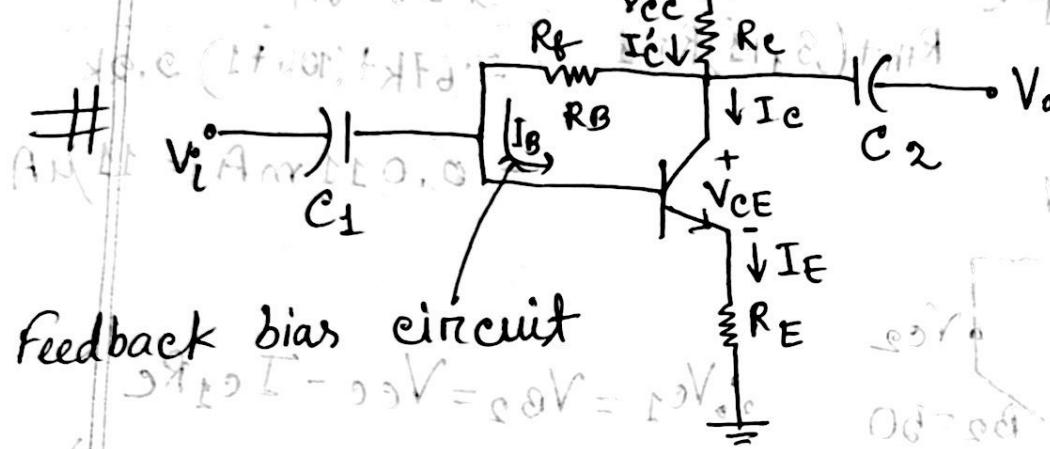
$$\therefore I_{B_2} = \frac{I_{E_2}}{\beta_2 + 1} = \frac{1.85}{50 + 1} = 0.035 \text{ mA}$$



Feedback bias circuit

Find I_B , I_C , I_E , V_{CE} ?

R_F = feedback R.

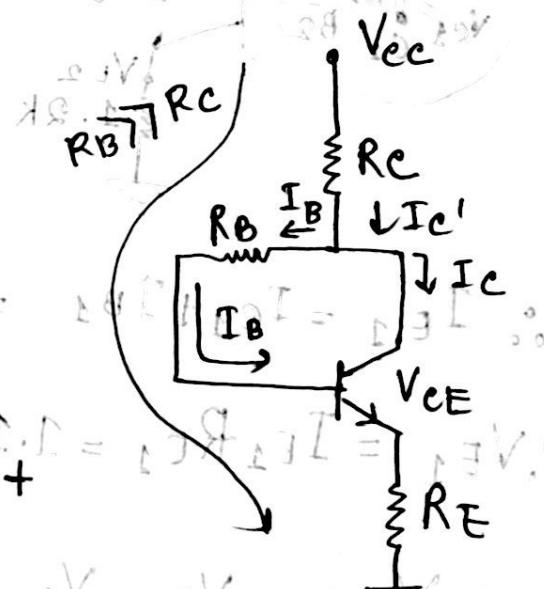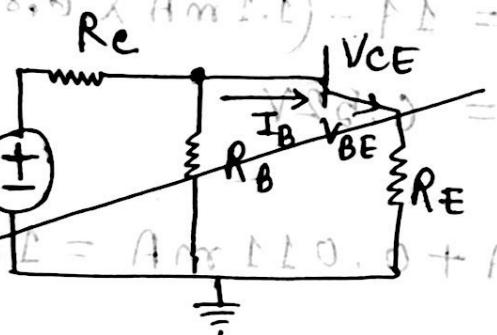

$$KVL \Rightarrow V_{CC} - I_C' R_C - I_B R_B - V_{BE} = 0$$

$$I_B = -V_{CC} + I_C' R_C + I_B R_B + V_{BE}$$

$$V_{BE} + I_E R_E = 0$$

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta R_C + (\beta + 1) R_E}$$


$$\boxed{\beta^2(\beta + 1) \approx \beta}$$

gain = output এর respect input
voltage ও এতে পার্শ্ব, current ও এতে পার্শ্ব

voltage ও এতে পার্শ্ব, current ও এতে পার্শ্ব

Operational Amplifiers & Application

অনেকগুলো Transistor এর cascade

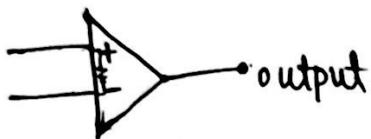


Amplifier


V^+ → Non inverting input

V^- → Inverting input

A → open circuit voltage gain

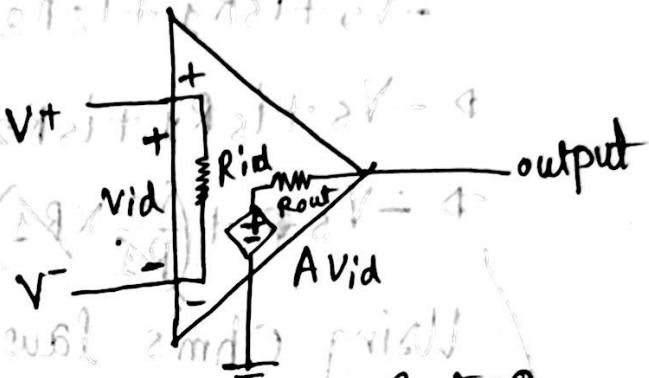


$R_{out} = 0$
 $R_{id} = \text{high}$

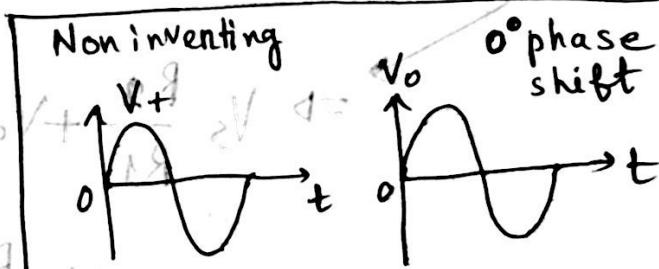


Inverting Amplifier?
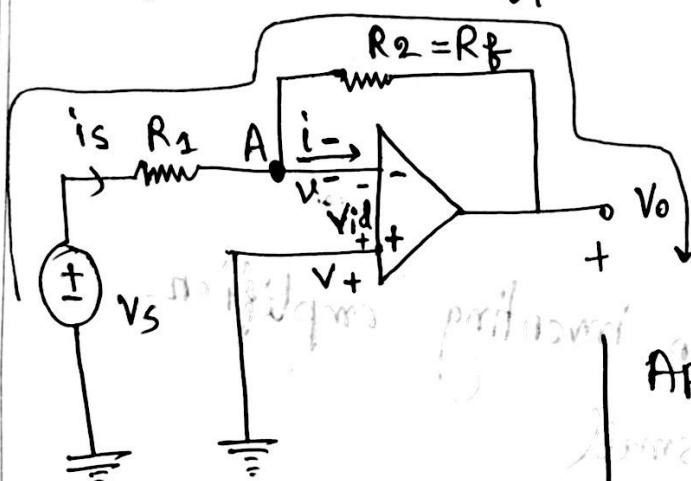
$$\text{Voltage gain} \approx A_V = \frac{V_o}{V_i}$$



$$\therefore V_{id} = V^+ - V^-$$
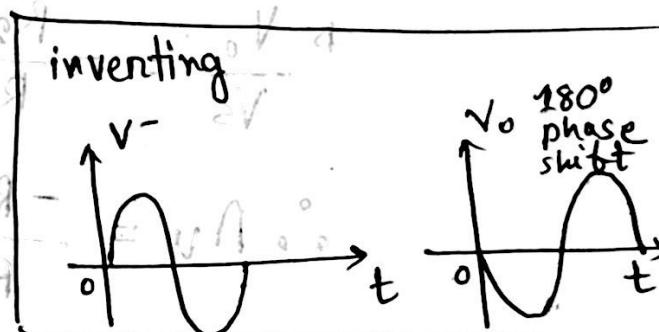
$$\therefore R_{id} = \text{infinity}, i_- = 0$$



Apply KCL at node A,

$$i_S = i_2 + i_-$$

$$\therefore i_S = i_2 + 0$$

$$\therefore i_S = i_2$$

Voltage Gain & Current Gain (Inverters)

Applying KVL,

$$-V_s + i_s R_1 + i_2 R_2 + V_o = 0$$

$$\Rightarrow -V_s + i_s R_1 + i_s R_2 + V_o = 0$$

$$\Rightarrow -V_s + \left(\frac{V_s}{R_1} \times R_1 \right) + \left(\frac{V_s}{R_1} \times R_2 \right) + V_o = 0$$

Using Ohm's law,

$$i_s = \frac{V_s}{R_1}$$

$$\Rightarrow V_s \frac{R_2}{R_1} + V_o = 0$$

$$\Rightarrow V_o = -V_s \frac{R_2}{R_1}$$

$$\Rightarrow \frac{V_o}{V_s} = -\frac{R_2}{R_1}$$

$$\therefore A_v = \frac{-R_2}{R_1}$$

Voltage gain for inverting amplifier

$R_1 > R_2$ = gain is small

$R_2 > R_1$ = gain বড় হবে

output resistance ক্ষুণ্ণ করা হয়। Voltage add করা হয়।

∞ = open circuit

To find output resistance, Thvenin's Theorem

Q) $A_v = 20 \text{ dB} = (-10^{\frac{20}{10}}) = -100$ [Inverting amplifier]

$$R_1 = 20 \text{ k}\Omega$$

$$\therefore A_v = -\frac{R_2}{R_1}$$

$$\Rightarrow -100 = -\frac{R_2}{20k}$$

$$\Rightarrow R_2 = 2M\Omega \quad (\text{Ans})$$

Non-Inverting :-

Using VDR,

$$V_1 = \frac{V_o R_1}{R_1 + R_2}$$

$$A.M.E.C.E \quad \frac{V_o}{R_1 + R_2} = \frac{V_o}{R_1 + R_2} = 1$$


$$V_{id} = V_+ - V_- = V_s - V_1$$

$$\text{As } i_- = 0, V_{id} = 0$$

$$\therefore V_{id} = V_s - V_1$$

$$\Rightarrow 0 = V_s - V_1$$

$$\Rightarrow V_s = V_1$$

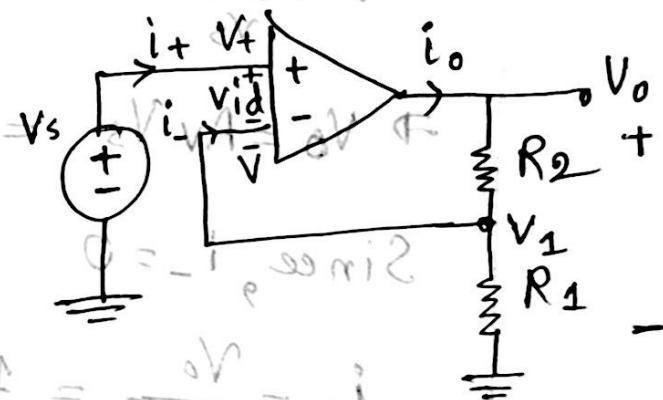

$$V_s = \frac{V_o R_1}{R_1 + R_2}$$

$$\Rightarrow \frac{V_s}{V_o} = \frac{R_1}{R_1 + R_2}$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{R_1 + R_2}{R_1}$$

$$\frac{V_o}{V_s} = 1 + \frac{R_2}{R_1}$$

$$\therefore A_v = 1 + \frac{R_2}{R_1}$$

Non inverting Example

$$R_1 = 3k\Omega$$

$$R_2 = 43k\Omega$$

$$V_s = 0.1V \quad (\text{mA})$$

$$\begin{aligned} \frac{V_o}{V_s} &= 1 + \frac{R_2}{R_1} \\ \frac{V_o}{0.1} &= 1 + \frac{43k\Omega}{3k\Omega} \\ V_o &\approx 15.3V \end{aligned}$$

$$A_v = \frac{V_o}{V_s}$$

$\Rightarrow V_o = A_v V_s$

Since, $i_- = 0$

$$i_o = \frac{V_o}{R_2 + R_1} = \frac{1.53}{43k\Omega + 3k\Omega} = 33.3\mu A$$

$$V_o = 2V$$

$$R_1 + R_2$$

$$\frac{1.53}{43+3} = \frac{2V}{20V}$$

$$\frac{1.53}{46} = \frac{2V}{20V}$$

$$V_o = 1.53V$$

$$\frac{V_o}{R_1} = 1V$$

$$1V - 2V = -1V = biV$$

$$0 = biV \Rightarrow 0 = i \cdot 2V$$

$$2V - 2V = 0V$$

$$2V - 2V = 0V$$

$$2V - 2V = 0V$$