

□ **Capacitor**: If we have an arrangement of two equal and opposite charges, we put such arrangement nearby conductors carrying equal and opposite charges, such arrangement is called capacitor. The conductors are called plates.


$$C = \frac{q}{V}$$

q = magnitude of charge of one plates
 V = potential difference between the two plates.

Simplest capacitor is the parallel plate capacitor.

□ A parallel-plate Capacitor

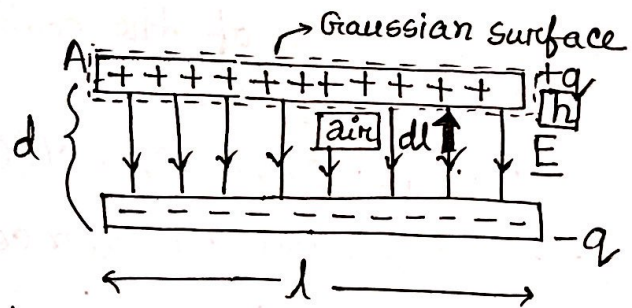Two Parallel-plate capacitor formed with two parallel conducting plates of area (A) separated by distance (d) in air. The electric field strength (E) between the plates is uniform. If we connect each plate to a battery, a charge +q and other charge -q will appear on the plates.



Gauss's law: $\epsilon_0 \oint E \cdot ds = q$

$$\Rightarrow \epsilon_0 \iint E ds \cos 0^\circ = q$$

$$\Rightarrow \epsilon_0 E \iint ds = q$$

$$\Rightarrow \epsilon_0 E A = q$$

We know, potential (V) = $-\int E \cdot dl$

$$= -\int E dl \cos 180^\circ = -E \int dl (-1)$$

$$\boxed{V = Ed}$$


$dl \rightarrow$ element of displacement from (-) plate toward the (+) plate

$$\therefore \text{The capacitance of parallel-plate } C = \frac{q}{V} = \frac{\epsilon_0 EA}{Ed} = \boxed{\frac{\epsilon_0 A}{d} = C}$$

□ A cylindrical Capacitor

$$\text{Capacitance, } C = \frac{2\pi\epsilon_0 l}{\ln(b/a)}$$

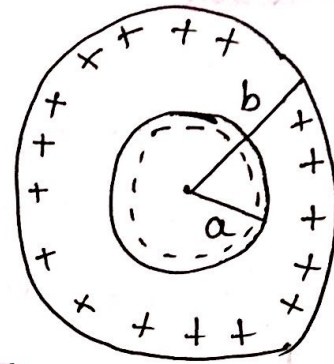l = length of the cylinder
(prove in slide 31-32)



□ Parallel Combination of Capacitors

We know, $C = \frac{q}{V}$

$$q_1 = C_1 V, \quad q_2 = C_2 V, \quad q_3 = C_3 V$$


The total charge of the combination

$$q = q_1 + q_2 + q_3$$

$$q = C_1 V + C_2 V + C_3 V = V(C_1 + C_2 + C_3)$$

If the equivalent Capacitance is C , then,

$$C = \frac{q}{V} = C_1 + C_2 + C_3$$

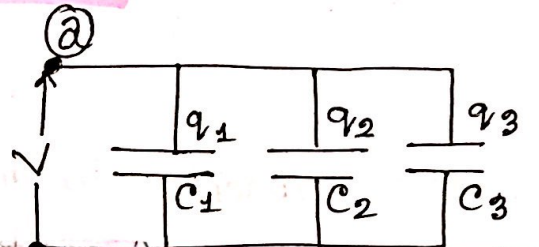

parallel plate capacitors

□ Series Combination of Capacitor

We know, $C = \frac{q}{V}$


$$V_1 = \frac{q}{C_1}, \quad V_2 = \frac{q}{C_2}, \quad V_3 = \frac{q}{C_3}$$

The potential difference between the series combination,

$$V = V_1 + V_2 + V_3 = q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$

If the equivalent Capacitance is C , then,

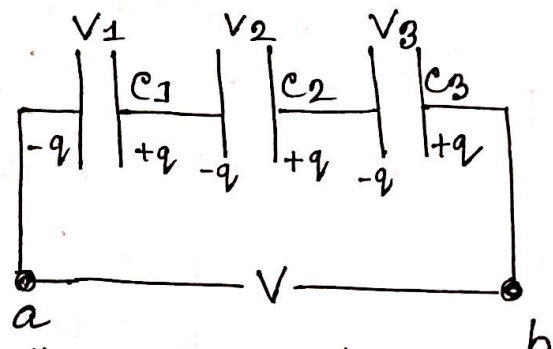
$$C = \frac{q}{V} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}} \quad \therefore \frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$



□ A Parallel-plate capacitor with a Dielectric

The capacitance

$$C = \frac{K \epsilon_0 A}{d}$$

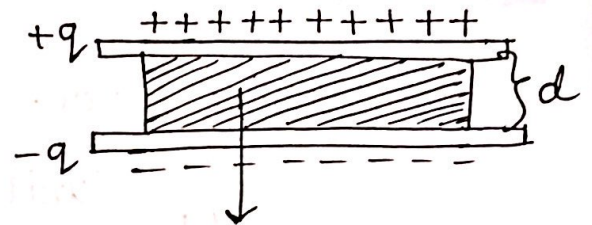

□ Energy Storage in an E

let us suppose, at a time (t)
a charge $q'(t)$ has been transferred from one plate to the other. The potential difference between the plates is, $V(t) = \frac{q'(t)}{C}$

if dq' is transferred, work will be, $dW = V dq' = \frac{q'}{C} dq'$

∴ total work will be,

$$W = \int dW = \int_0^q \frac{q'}{C} dq' = \frac{1}{2} \frac{q^2}{C} = \frac{q^2}{2C}$$

Since, $q = CV$

$$W = \frac{(CV)^2}{2C} = \frac{1}{2} CV^2 = U \rightarrow \text{potential energy stored in the capacitor resides in the electric field } E$$

□ The energy density (u)

↓
(stored energy per unit volume)

$$\text{energy density}(u) = \frac{\text{Energy}}{\text{Volume}} = \frac{U}{V} = \frac{U}{Ad} = \frac{CV^2/2}{Ad} \quad [\text{Volume} = Ad]$$

$$u = \frac{CV^2}{2Ad} = \frac{K \epsilon_0 A/d}{2Ad} (Ed)^2$$


$$\therefore \text{energy density, } (u) = \frac{1}{2} K \epsilon_0 E^2$$

Electromotive force and circuits

A simple Electric Circuit

electromotive force,
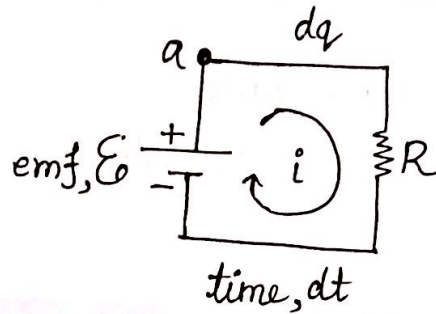
$$\mathcal{E} = \frac{dW}{dq} \quad (\text{unit: Volt})$$



(dW = small amount of work done to bring the charge dq from (-)ve to (+)ve terminal of the source)

Now, let us calculate the current in the simple circuit, We know, current $i = \frac{dq}{dt}$

Joule Heat $i^2 R dt$ (appear in the resistor)

$$\text{Work done, } dW = \mathcal{E} dq = \mathcal{E} i dt$$

\therefore From, energy principle,

$$\mathcal{E} i dt = i^2 R dt$$

$$\mathcal{E} = i R$$

$$\therefore \boxed{i = \frac{\mathcal{E}}{R}}$$

Law's of solving Circuit Equations:


Kirchhoff's Voltage Law: (Loop theorem)

"The algebraic sum of the changes in potential encountered in making a complete loop of the circuit must be zero."

$$V_a - iR + \mathcal{E} = V_a$$

$$\therefore -iR + \mathcal{E} = 0$$

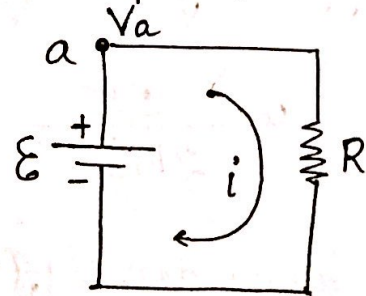
independent of the value V_a . (Rule: Slide-38)



□ Kirchhoff's current Law:
(slide 39 (2nd Para))

$$i_1 + i_3 - i_2 = 0$$

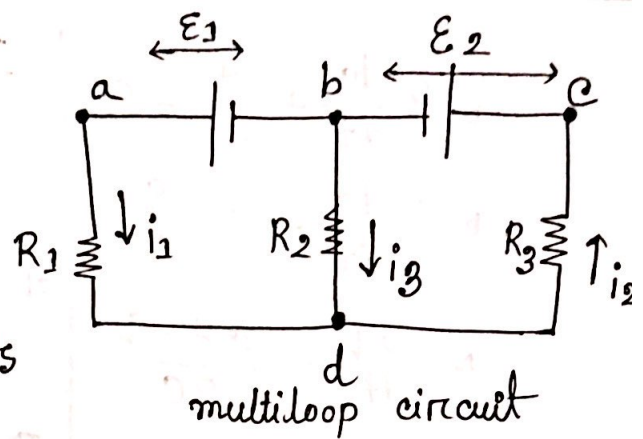"At any junction the algebraic sum of the currents must be zero."



It is also known as junction theorem.


□ A simple RC circuit:

$dt \rightarrow$ small time

$dq \rightarrow$ small amount of charge

$$dq = i dt$$

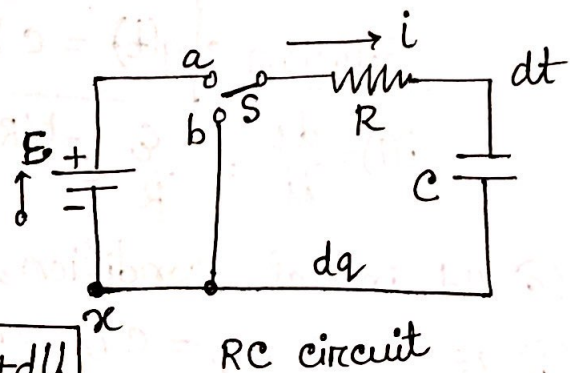Work done, $dW = \mathcal{E} dq = i^2 R dt + dU$



$$\therefore \mathcal{E} dq = i^2 R dt + d\left(\frac{q^2}{2C}\right) \quad \left[dU = d\frac{q^2}{2C}\right]$$

$$\Rightarrow \mathcal{E} dq = i^2 R dt + \frac{1}{2C} 2q dq$$

$$\Rightarrow \mathcal{E} dq = i^2 R dt + \frac{q}{C} dq \quad \text{changing capacitor}$$

dividing both sides by dt , we get,

$$\mathcal{E} \frac{dq}{dt} = i^2 R + \frac{q}{C} \frac{dq}{dt}$$

$$\Rightarrow \mathcal{E} i = i^2 R + \frac{q}{C} i \quad \left[i = \frac{dq}{dt}\right]$$

$$\Rightarrow \mathcal{E} = iR + \frac{q}{C}, \text{ can be derived by loop theorem:}$$

$$\Rightarrow \mathcal{E} = R \frac{dq}{dt} + \frac{q}{C} \quad \left[i = \frac{dq}{dt}\right]$$

$$\Rightarrow R \frac{dq}{dt} + \frac{q}{C} = \mathcal{E}$$

$$\Rightarrow R \frac{dq}{dt} = \mathcal{E} - \frac{q}{C}$$

$$\Rightarrow \frac{dq}{dt} = \frac{C\mathcal{E} - q}{RC}$$

$$\Rightarrow \frac{dq}{C\mathcal{E} - q} = \frac{1}{RC} dt$$

Integrating both sides we get,

$$\int_0^q \frac{1}{C\mathcal{E} - q} dq = \int_0^t \frac{1}{RC} dt$$

$$\Rightarrow \left[\frac{\ln(C\mathcal{E} - q)}{-1} \right]_0^q = \frac{1}{RC} [t]_0^t$$

$$\Rightarrow \ln(C\mathcal{E} - q) =$$

Solution : $q(t) = C\mathcal{E} (1 - e^{-t/RC})$


$$i(t) = \frac{dq}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC}$$

(a) At initial condition, $t=0$, $q=0$ and $i = \frac{\mathcal{E}}{R}$

(b) as $t \rightarrow \infty$, $q = C\mathcal{E}$ and $i \rightarrow 0$

charging the capacitor

w.r.to time

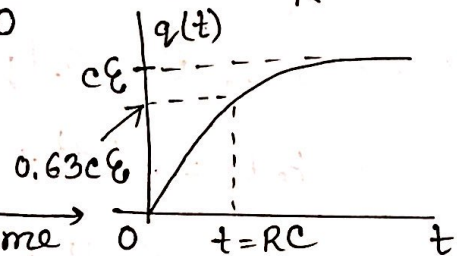



$RC \rightarrow RC$ time constant

□ Discharging the capacitor

$$R \frac{dq}{dt} + \frac{1}{C} q = 0 \text{ (No emf)}$$

Solution : $q(t) = q_0 e^{-t/RC}$

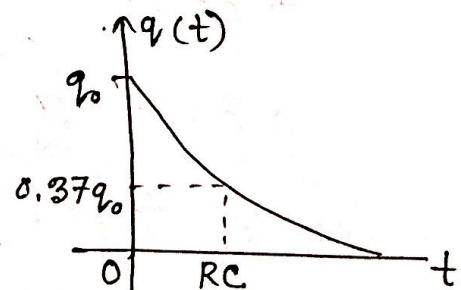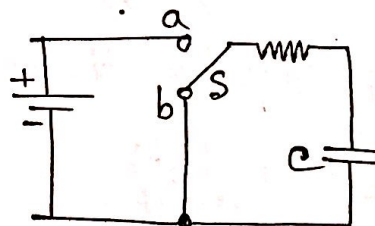$q_0 \rightarrow$ initial charge on the capacitor



Discharging capacitor w.r.to time