




C.W
21/12/2024

Metal oxide semiconductor field effect transistor

MOSFET

Active device
(Control flow of electron)

~~N P N~~

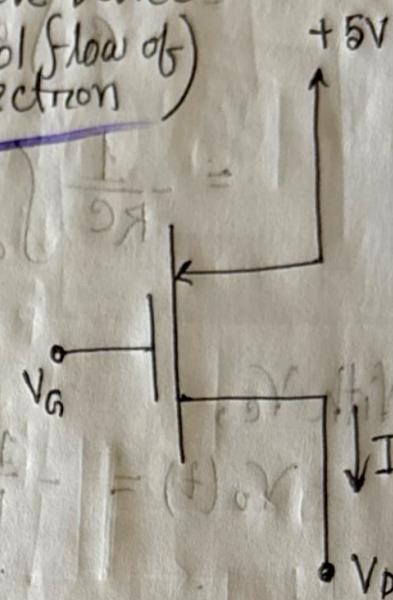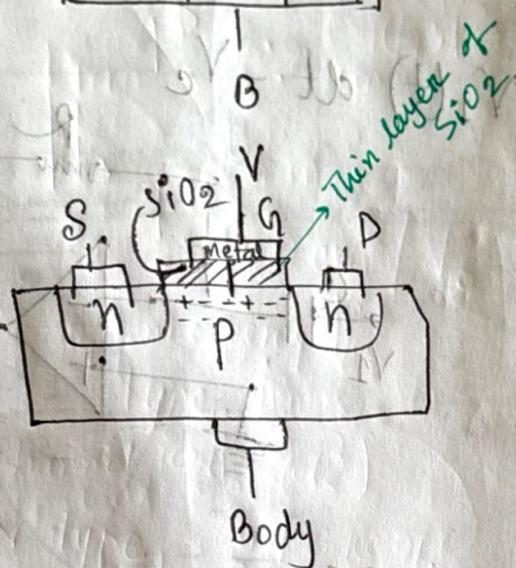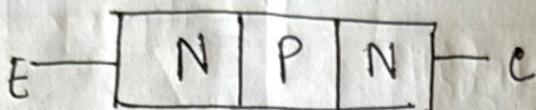

G \Rightarrow Gate

D \Rightarrow Drain

S \Rightarrow Source

- MOSFET \rightarrow Voltage Driven Device

Metal Oxide Semiconductor Field effect Transistor

- SiO_2 এর একটি capacitance রয়েছে,


- Channel টির মাঝে Channel off রয়েছে,

Depletion Type MOSFET বলে গোচি channel টি,

- যদি যদি channel টির মাঝে না, তাকে

Enhancement Type MOSFET. জ্বালন channel টির প্রতি হবে,


MOSFET



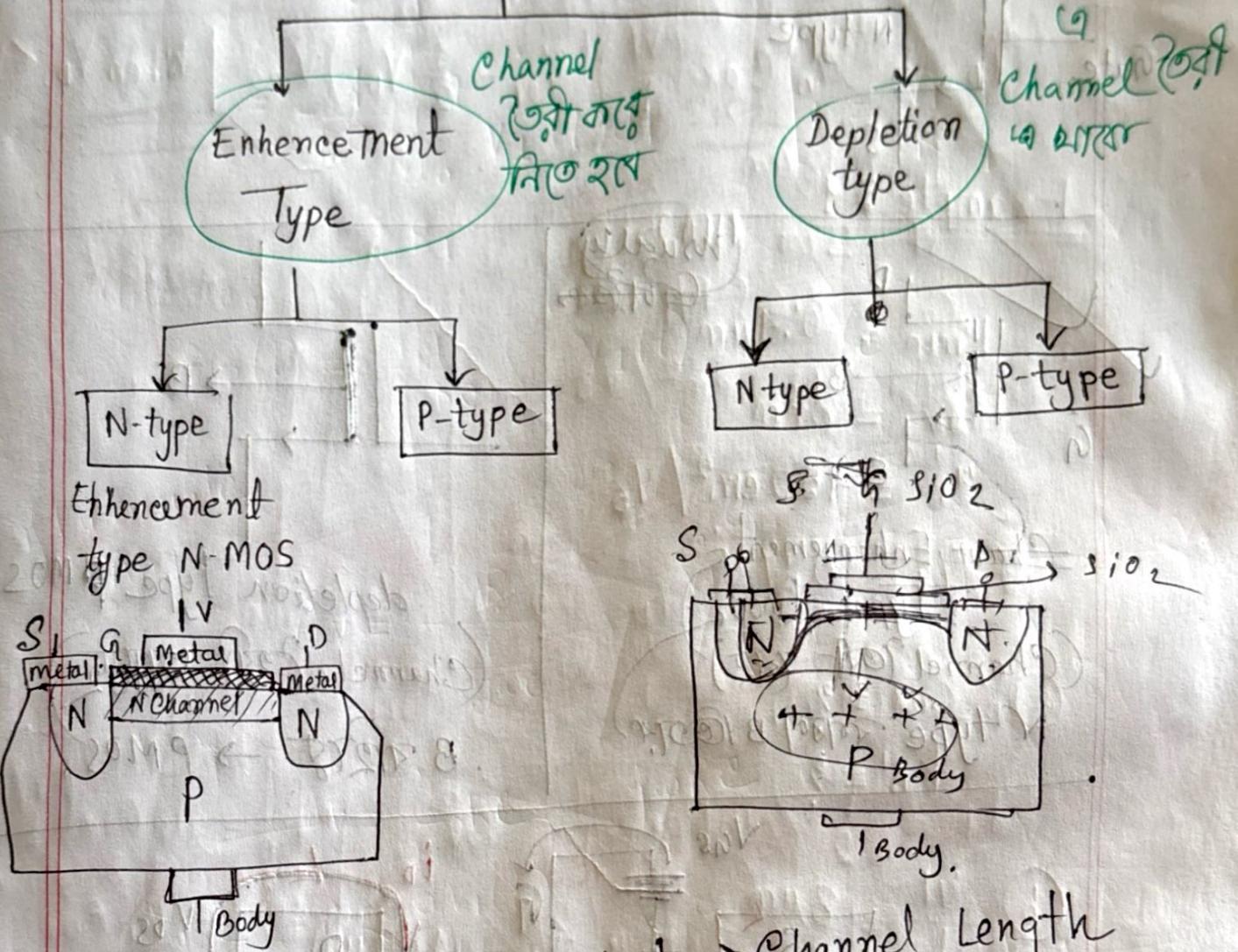


Gate SiO₂

- t_{ox} → Oxide thickness
- C_{ox} → II. Capacitance
- ϵ_0 → Permittivity
- μ → Permeability
- Metal → Polysilicone

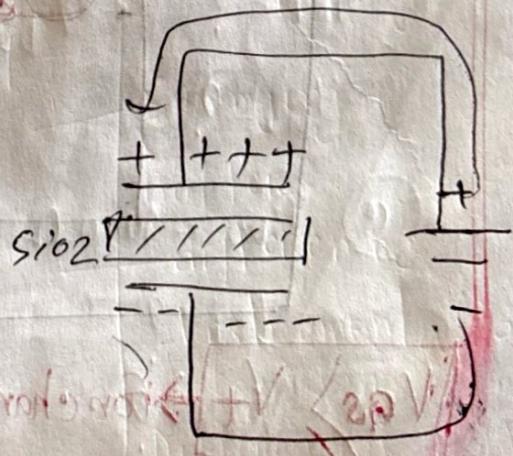$L \rightarrow$ Channel Length
 $W \rightarrow$ Channel width




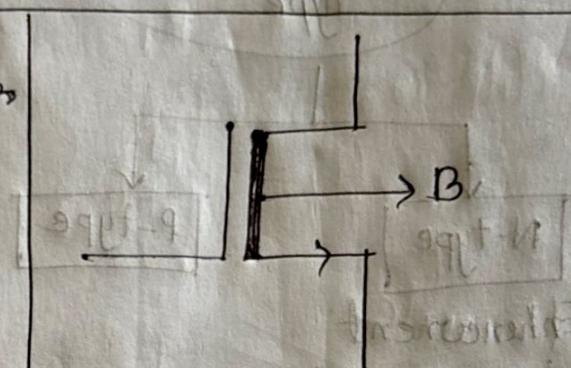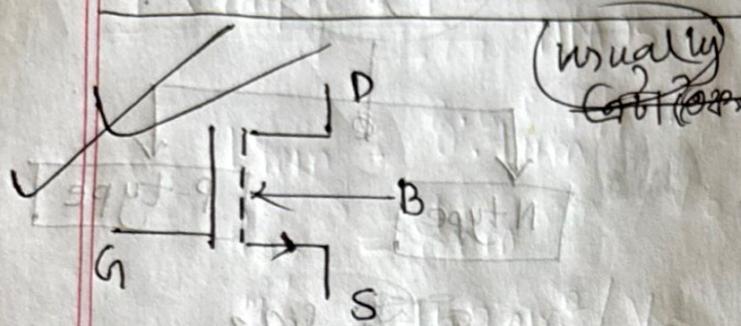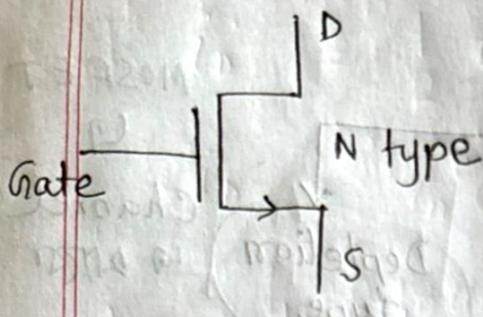

Channel Enhancement

Type NMOS
(Channel তৈরি নথি)
N type বলায় B কি হবে?

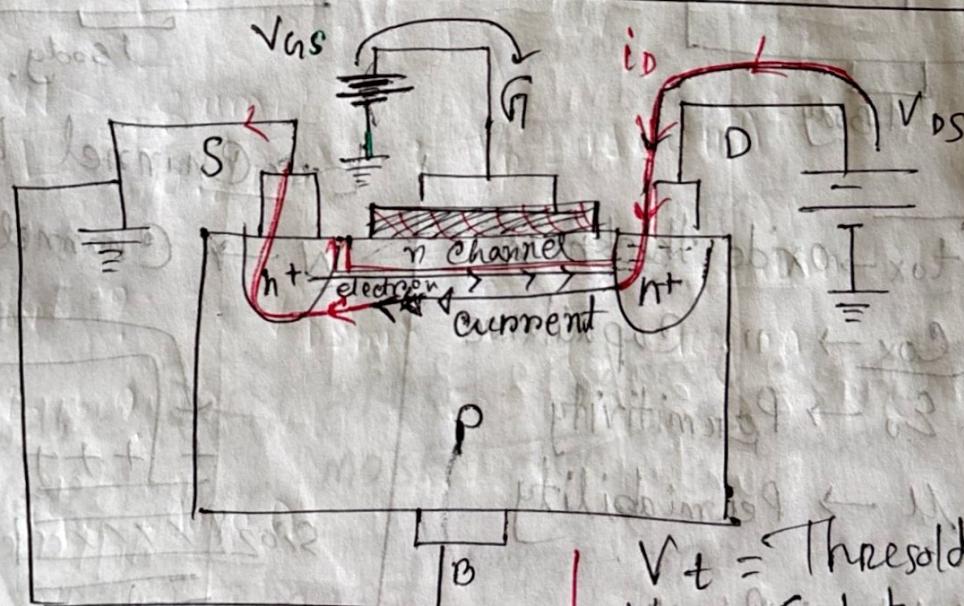depletion Type PMOS
(Channel তৈরি আস্তে)
B কি হবে? \rightarrow PMOS.



* $V_{GS} > V_t \rightarrow$ For channel creation

V_t = Threshold Voltage
 V_{GS} = Gate to source voltage
 V_{DS} = Drain voltage


V_{ov} → Overdrive Voltage

$$V_{ov} = V_{GS} - V_t$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

in $\frac{F/m^2}{\text{unit}}$

permittivity ϵ_{ox}
 3.45×10^{-11} F/m^2

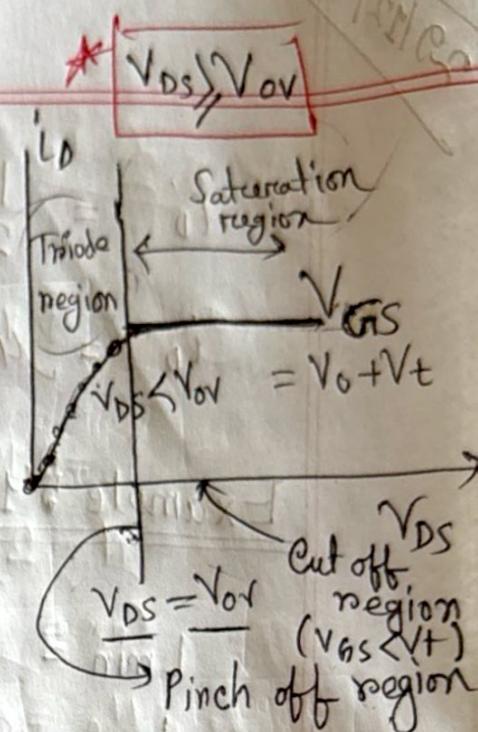

$$i_D = \begin{cases} \text{triode: } (\mu_n C_{ox}) \frac{W}{L} \left(V_{ov} - \frac{1}{2} V_{DS} \right) V_{DS} & [if V_{DS} < V_{ov}] \\ \text{saturation: } \frac{1}{2} (\mu_n C_{ox}) \frac{W}{L} V_{ov}^2 & \end{cases}$$

$$\mu_n C_{ox} = K_n' \quad (\text{MOSFET Transfer Characteristics})$$

Slide: 5:2.2 (কুবি)

Overdrive V_{ov} channel কে বড় করার পথ হল

current কে বড় করা হল

V_{tn} → n type threshold voltage

V_{pn} → p "

" "

minimum value of V_{GS} required to conduct channel between drain and source

C.W
29/12/2024

$$i_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) V_{ov}^2$$

[When, $V_{DS} > V_{ov}$]

$$i_D = \mu_n C_{ox} \left(\frac{W}{L}\right) \left(V_{ov} - \frac{1}{2} V_{DS}\right) V_{DS}$$

[When $V_{DS} < V_{ov}$]

Example 5.1

NMOS

$$L_{min} = 0.4 \mu m$$

$$t_{ox} = 8 nm$$

$$\mu_n = 450 \text{ cm}^2/Vs$$

$$V_t = 0.7 V$$

a) $C_{ox} = ?$

$$K_n' = ?$$

b) $\frac{W}{L} = \frac{8 \mu m}{0.8 \mu m} ; I_D = 100 \mu A$

$$V_{ov} = ?$$

$$V_{DSmin} = ?$$

Saturation
region

$$V_{GS} = ?$$

c) $R_{DS} = 1000 \Omega$

$$V_{ov} = ?$$


$$V_{GS} = ?$$

Answer:

$$\textcircled{a} \quad C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.45 \times 10^{-11}}{8 \times 10^{-9}} = 4.32 \times 10^{-3} \text{ F/m}^2$$

*→ ϵ_{ox} value
permittivity of SiO_2*
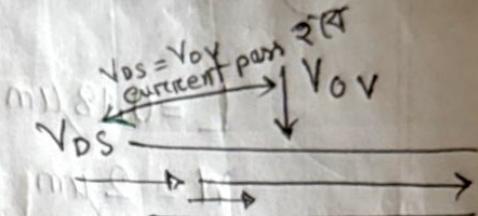
$$\therefore K_n' = \mu_n C_{ox} = 150 (\text{cm}^2/\text{V}) \times 4.32 \times 10^{-3} \\ = 194 \mu\text{A}/\text{V}^2$$



(b) For saturation region,

$$I_D = \frac{1}{2} (\mu_n C_{ox}) \left(\frac{W}{L} \right) V_{ov}^2$$

$$\Rightarrow 100 \mu\text{A} = \frac{1}{2} (194 \mu\text{A}/\text{V}^2) \times \left(\frac{0.8 \mu\text{m}}{0.8 \mu\text{m}} \right) \times V_{ov}^2$$

$$\therefore V_{ov} = 0.32 \text{ V} = V_{DS\min}$$

$$V_{GS} = V_{ov} + V_t = 0.32 + 0.7 = 1.02 \text{ V}$$

$V_{DS} = V_{ov}$, Saturation region \rightarrow current pass

হবে।

$$\textcircled{c} \quad r_{DS} = \frac{V_{ov}}{I_D} = \frac{0.32}{100 \mu\text{A}} = 3.2 \text{ k}\Omega$$

$$\Rightarrow 1000 = \frac{1}{K_n' \left(\frac{W}{L} \right) V_{ov}} = \frac{1}{194 \times \left(\frac{8}{0.8} \right) \times 0.32} = 1.57 \text{ k}\Omega$$

$$\therefore V_{ov} = 0.52 \text{ V}$$

$$\therefore V_{GS} = V_{ov} + V_t \\ = 0.52 + 0.7 = 1.22 \text{ V}$$

$\mu_n C_{ox}$

Example 5.2

NMOS Homework

(a)

Given,

$$L = 0.18 \mu m$$

$$W = 2 \mu m$$

$$C_{ox} = 8.6 fF/\mu m^2$$

$$\mu_n = 150 \text{ cm}^2/Vs$$

$$V_{tn} = 0.5 V$$

(a)

$$V_{GS} = ?$$

$$V_{DS} = ?$$

$$I_D = 100 \mu A$$

Saturation
region

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) V_{ov}^2$$

$$K_n = \mu_n C_{ox} \left(\frac{W}{L} \right)$$

$$= 4.3 \text{ mA/V}^2$$

$$K_n' = \mu_n C_{ox}$$

$$= 450$$

$$= 450 \times 10^{-9} \times 8.6 \times 10^{-9}$$

$$10^{12} \text{ mA/V}^2$$

$$= 387 \text{ mA/V}^2$$

$$V_{GS} = V_{ov} + V_t = 0.22 + 0.5$$

$$= 0.72 V$$

$$V_{ov} \times \left(\frac{8}{8.0} \right) \times 10^{-12}$$

$$V_{ov} \left(\frac{W}{L} \right) \times 10^{-12}$$

$$+ V_t + V_{ov} = 2.2 V$$

$$V_{DS,0} = V_{ov} - V_{GS}$$

unit
কুলোর
বিবরণ
নির্দেশ

$$(b) I_D = \mu_n C_{Ox} \left(\frac{W}{L} \right) \left(V_{ov} - \frac{1}{2} V_{DS} \right) V_{DS}$$

$$\Rightarrow I_D = k_n \left[V_{ov} - \frac{1}{2} V_{DS} \right] V_{DS}$$

$$\Rightarrow 50 = 4.3 \text{ mA/V}^2 [0.22 V_{DS} -$$

$$V_{DS} - \frac{1}{2} V_{DS}^2]$$

$$\Rightarrow V_{DS}^2 - 0.44 V_{DS} + 0.023 = 0$$

$$\therefore V_{DS} = 0.06 \text{ V}$$

~~जबकि वाले का नियम~~

$$\text{तभी } V_{DS} = 0.22 \text{ V}$$

$$(c) V_{DS} = 0.3 \text{ V}$$

$$V_{GS} = 0.7 \pm 0.1 \text{ V}$$


$$i_D = ??$$

$$i_D = \frac{1}{2} \mu_n C_{Ox} \left(\frac{W}{L} \right) V_{ov}^2 = 7.0 \times 0.1 = 0.7 \text{ mA}$$

$$= \frac{1}{2} k_n V_{ov}^2 \rightarrow V_{GS} = 0.7 \text{ V}$$

$$i_{D1} = \frac{1}{2} k_n V_{ov}^2 \rightarrow V_{GS} = 0.7 + 0.1 = 0.8 \text{ V}$$
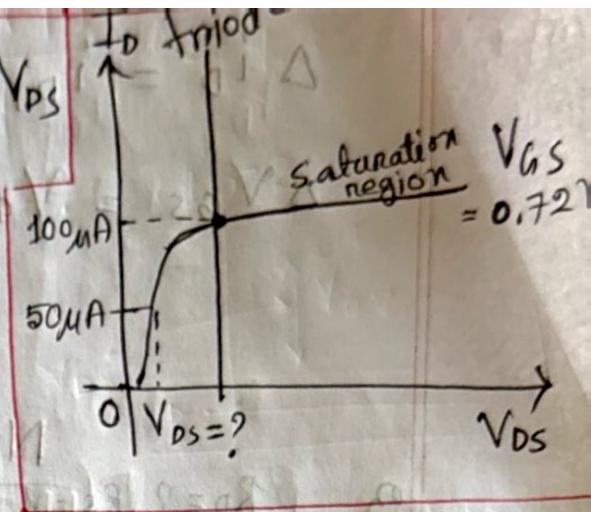
$$i_{D2} = \frac{1}{2} k_n V_{ov}^2 \rightarrow V_{GS} = 0.7 - 0.1 = 0.6 \text{ V}$$



$$V_{GS} = V_G - V_{GS}$$

$$V_{GS} = V_{GS} - V_t$$

$$V_{GS} = V_G - V_t$$

$$V_{GS} = V_{GS} - V_t$$

$$V_{GS} = V_{GS}$$

$$\Delta i_D = i_{D1} - i_{D2}$$

$$\Delta V_{GS} = V_{GS1} - V_{GS2}$$

N MOS Transistor

$$R_D = ?, R_S = ?$$

$$\text{Ex-5.3}$$


$$\therefore R_D = \frac{V_{DD} - V_D}{I_D}$$

$$= \frac{2.5 - 0.5}{0.4} = 5 \text{ k}\Omega$$

$$\therefore I_D = \frac{1}{2} (\mu_n C_{ox}) \left(\frac{W}{L} \right) V_{ov}^2$$

$$\Rightarrow 0.4 \text{ mA} = \frac{1}{2} (100) \left(\frac{32}{1} \right) V_{ov}^2$$

$$\Rightarrow V_{ov} = 0.15 \text{ V}$$

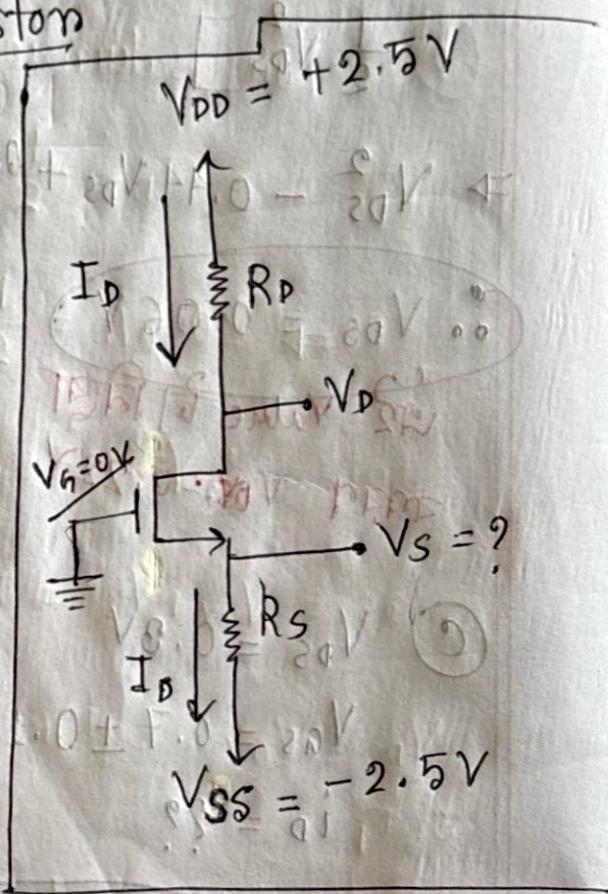

$$\therefore V_{GS} = 0.5 + 0.7 = 1.2 \text{ V}$$

$$-V_{GS} = V_S$$

$$\therefore V_S = -1.2 \text{ V}$$

$$\therefore R_S = \frac{-1.2 \text{ V} - (-2.5)}{0.4 \text{ mA}} = 3.25 \text{ k}\Omega$$

$$V_{ov} = V_{GS} - V_t$$

$$\Rightarrow V_{GS} = V_{ov} + V_t$$

$$V_{GS} = V_G - V_S$$

$$= 0 - V_S$$

$$\therefore V_S = -V_{GS}$$

$$V_T = V_D - V_{DS} = n_s V - eV = v_0 V$$


Example-5.4

Find I-V relationship of the resulting two terminal device in terms of MOSFET parameters

$$k_n = k_n' \left(\frac{W}{L} \right) \text{ and } V_{DS}$$

$$V_{DS} = V_{GS} - V_t \\ = V - V_t$$
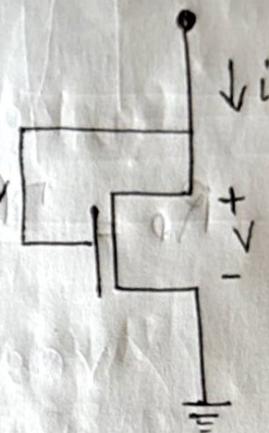
$$i = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V - V_t)^2$$



Example-5.5

effective resistance $R_{DS} = ?$


$$k_n = 1 \text{ mA/V}^2$$

$$V_{DS} = 1 \text{ V} \quad I_D = \frac{1}{2} \times 1 \times V_{DS}^2$$

$$V_{GS} = 5 \text{ V} \quad I_D = (\mu_n C_{ox}) \left(\frac{W}{L} \right) (V_{GS} - \frac{1}{2} V_{DS}) V_{DS}$$

Wrong
Ans
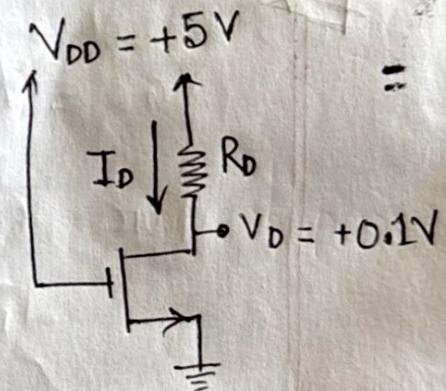
$$R_{DS} = \frac{V_{DS}}{I_{DS}} = \frac{1}{\frac{1}{2} k_n V_{DS}^2} \\ = 2 \text{ k}\Omega$$



$$R_D = \frac{V_{DD} - V_D}{I_D} \\ = 9.8 \text{ k}\Omega$$

$$V_{ov} = V_{as} - V_{fn} = 5 - 1 = 4V$$

$$I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) \left(V_{DS} - \frac{1}{2} V_{DS} \right)^{V_{DS}}$$

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{5 - 0.1}{0.1} = 49 \Omega$$

Y₂O₃-SiO₂

四百一

$$20V \left(20V \frac{1}{2} - 10^2 \right) \left(\frac{1}{2} \right) (10) \ln \left(\frac{c}{c+6} \right) = 41 \quad \text{and} \quad \sqrt{c} = 12.6 \text{ V}$$

$$\cancel{d^2} - 99V = 69$$

47


~~2 x 8.0 =~~

31/12/21
Example - 5.6

31/12/2024

MOSFET

Problem:

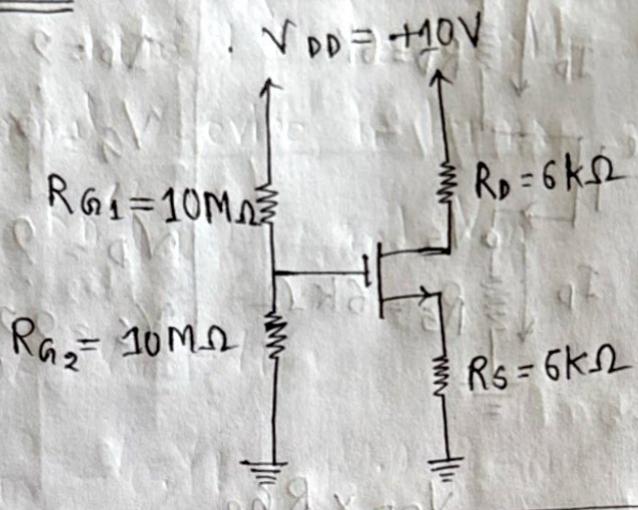



$$I_D = ?$$

$$V_G = ?$$


$$V_D = ?$$

$$V_S = ?$$


Theory

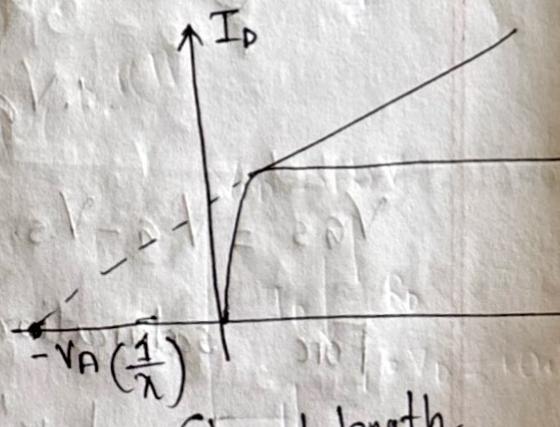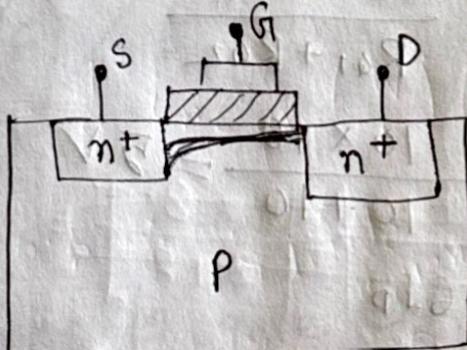

Channel length modulation effect

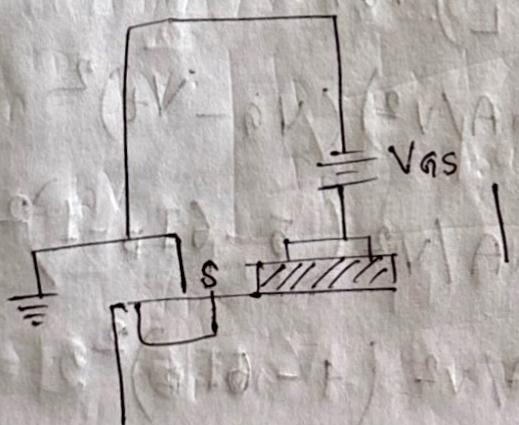

5.6 Slide

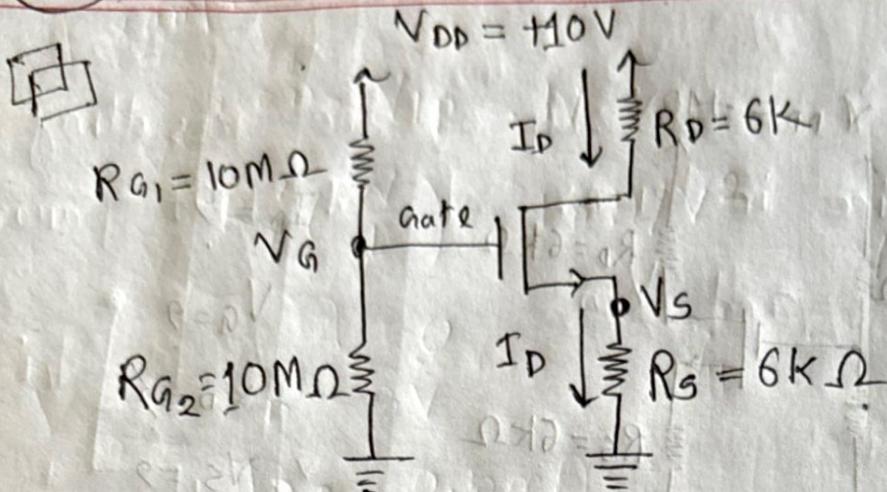

$I_D = ?$
 $V_g = ?$
 $V_D = ?$
 $V_S = ??$

Using V_{DR} , $V_g = \frac{V_{DD} \times R_{G2}}{R_{G1} + R_{G2}}$

$$\therefore V_g = -\frac{10 \times 10}{10 + 10} = 5V$$

$$V_{GS} = V_g - V_s = 5 - 6I_D$$

For saturation region,

$$I_D = \frac{1}{2} K_n' \left(\frac{W}{L} \right) V_{GS}^2$$

$$\Rightarrow I_D = \frac{1}{2} \times (1mA/V^2) (5 - 6I_D)^2$$

$$\Rightarrow I_D = \frac{1}{2} \times 1mA/V^2 (5 - 6I_D - 1)^2$$

$$\Rightarrow I_D = \frac{1}{2} \times 1mA/V^2 (4 - 6I_D)^2$$

$$\Rightarrow I_D = \frac{1}{2} \times (1mA/V^2) (16 - 48I_D + 36I_D^2)$$

$$\Rightarrow I_D = 2 \times (1mA/V^2) (9I_D^2 - 12I_D + 4)$$

$$\Rightarrow I_D = \frac{2 \times (4 \text{ mA})}{V^2} \quad 18I_D^2 - 25I_D + 8 = 0$$

$$\therefore I_D = 0.89 \text{ mA}$$

$$I_D = 0.5 \text{ mA}$$

$$\begin{aligned} V_{GS} &= V_S = 6 I_D \\ &= 6 \times 0.89 \\ &= 5.34 \text{ V} \end{aligned}$$

$$\begin{aligned} V_{GS} &= 5 - 5.34 \\ &= -0.34 \text{ V} \end{aligned}$$

$$\begin{aligned} V_S &= 6 I_D \\ &= 6 \times 0.5 \\ &= 3 \text{ V} \quad (\text{Ans}) \end{aligned}$$

$$V_{GS} = 5 - 3 = 2 \text{ V}$$

NMOS এ gate এর voltage negative হওয়া
চলে, $I_D = 0.89 \text{ mA}$ is not appropriate.

$$\text{So, } I_D = 0.5 \text{ mA}.$$

$$\begin{aligned} V_D &= 10 - 6 I_D \\ &= 10 - (6 \times 0.5) \\ &= 10 - 3 \\ &= 7 \text{ V} \quad (\text{Ans}) \end{aligned}$$

$$\begin{aligned} V_{DS} &= V_D - V_S \\ &= 7 - 3 \\ &= 4 \text{ V} \quad (\text{Ans}) \end{aligned}$$

Example - 5.7given, $V_{TP} = 1V$

$$K_p \left(\frac{W}{L} \right) = 1 \text{ mA/V}^2$$

$$\lambda = 0$$

$$V_D = 3V$$

$$I_D = 0.5 \text{ mA}$$

$$\text{Let, } R_{G1} = 2 \text{ k}\Omega$$

$$R_{G2} = 3 \text{ k}\Omega$$

~~$$\text{Let } V_G = \frac{V_{DD} \times R_{G2}}{R_{G1} + R_{G2}} = \frac{5 \times 3}{3 + 2} = 3V$$~~

$$\text{For saturation region, } I_D = \frac{1}{2} K_n V_{ov}^2$$

$$\Rightarrow 0.5 \text{ mA} = \frac{1}{2} (1 \text{ mA/V}^2) V_{ov}^2$$


$$\therefore |V_{ov}| = 1V$$

$$V_{GS} = V_{SG} = |V_{ov}| + |V_{TP}| = 1 + 1 = 2V$$

$$\text{if } V_{SG} = V_S - V_G$$

$$\therefore |V_G| = 5 - 2 = 3V$$
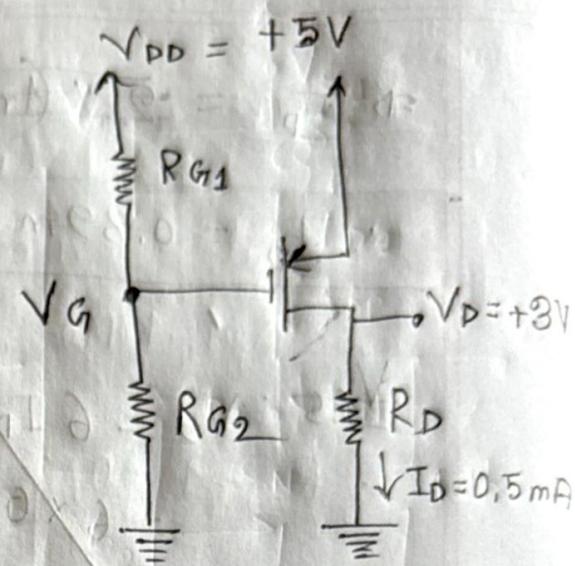
$$\therefore R_D = \frac{V_D - 0}{I_D} = \frac{+3V}{0.5 \text{ mA}} = 6 \text{ k}\Omega$$



$$|N_{D\max}| = |3+1| = 4V$$

$$R_{D\max} = \frac{1}{0.5} = 8k\Omega$$

$$V_0 = 5V$$

$$V_0 = 5V$$


Note: * PMOS এর Gate এবং nিচের R এর Gate এর
উপরের R এর চেমে কষি হ'ব। $P \rightarrow R_{G2}, R_{G1}$

* NMOS এর $R_{G1} > R_{G2}$

Exercise 5.8

C-MOS (Complementary MOS)

• PMOS ও NMOS এর Cascade

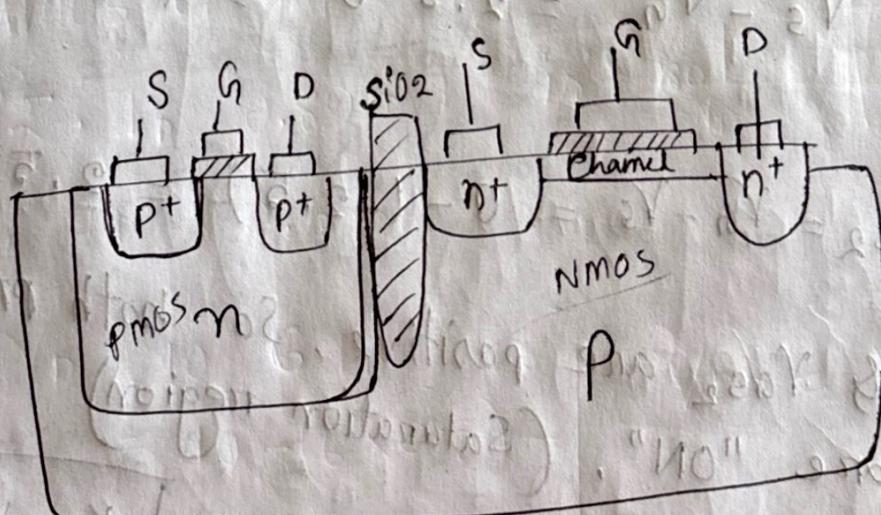

$$V_1 = 0, +2.5 \text{ V}, -2.5 \text{ V}$$

When $V_1 = 0$,

$$V_{G1} = 0 \text{ V}$$

$$V_{G2} = 0 \text{ V}$$

$$V_{S1} = 2.5 \text{ V}$$

$$V_{S2} =$$

$$I_D = \frac{1}{2} K_n' \left(\frac{W_p}{L_p} \right) V_{DS}^2$$

$$\frac{1}{2} \times (1 \text{ mA/V}^2)$$

For PMOS

$$V_{SG1} = V_S - V_{G1} = 2.5 - 0 = 2.5 \text{ V}$$

For NMOS,

$$V_{GS2} = V_G - V_S = 0 - (-2.5) = 2.5 \text{ V}$$

$\therefore V_{SG1}$ & V_{GS2} are positive. So both PMOS & NMOS are "ON". (Saturation region)

$$I_D = I_{DP} = I_{DN} = \frac{1}{2} K_n V_{DS}^2$$

$$= \frac{1}{2} K_n (V_{GS} - V_t)^2$$


$$= \frac{1}{2} \times 1 \times (2.5 - 1)^2$$

$$K_n = K_n' \left(\frac{W_n}{L_n} \right)$$

$$= K_p' \left(\frac{W_p}{L_p} \right)$$

$$= 1 \text{ mA/V}^2$$

$$V_{tN} = V_s - V_{tp} = 1 \text{ V}$$

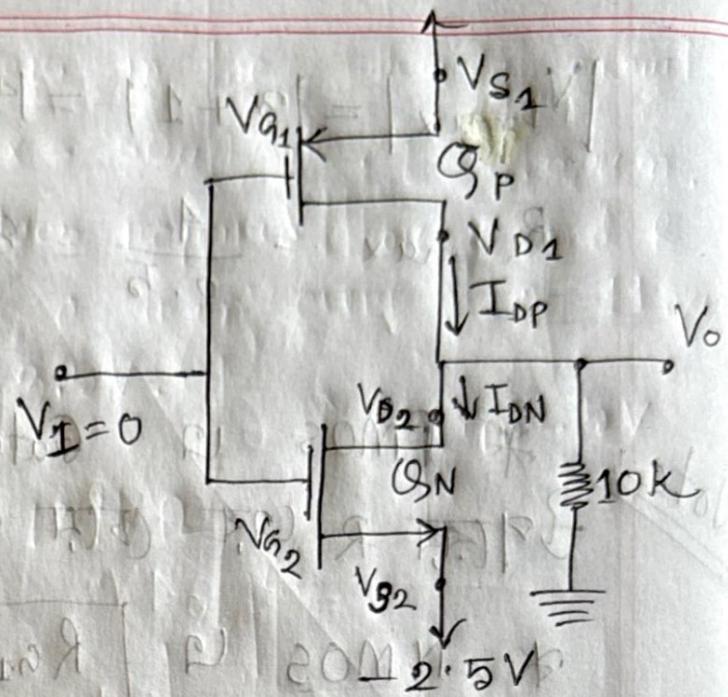

Saturation region
current same

$$\therefore I_D = 1.125 \text{ mA}$$

Again, for $V_I = 2.5V$

for PMOS

$$V_{SG} = V_S - V_S \\ = 2.5 - 2.5 \\ = 0V$$


for NMOS is bias

$$V_{GS} = 0V \\ V_{GS} = V_g - V_S \\ = 2.5 - (-2.5) \\ = 5V$$

\therefore NMOS is in "ON" state.
But in triode region.

$$I_{D_N} = k_n (V_{DS} - \frac{1}{2} V_{DS}) V_{DS}$$
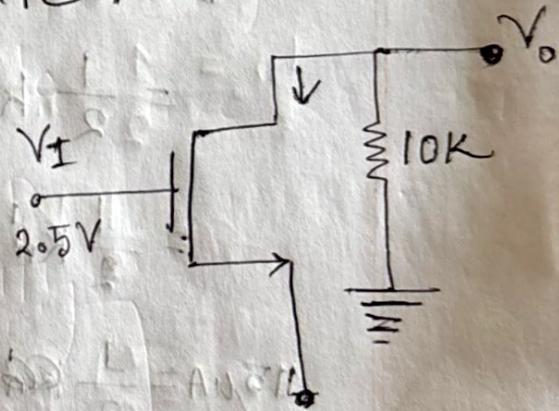
$$\approx k_n V_{DS} V_{DS} \text{ (Approx.)}$$



Again, for $V_I = -2.5$

PMOS will be "ON"

$$I_{D_P}$$

We apply V_{GS} to create channel
 $V_{DS} \rightarrow$ Max current 20mA

The PMOS transistor in the following circuit has $V_t = -0.7\text{V}$, $M_p C_{ox} = 60\mu\text{A}/\text{V}^2$, $L = 0.8\mu\text{m}$, and $\lambda = 0$. Find the values required for w and R in order to establish a drain current of $115\mu\text{A}$ and a voltage V_D of 3.5V .

$$R = \frac{V_D}{I_D} = \frac{3.5\text{V}}{115\mu\text{A}} = 30.439\text{k}\Omega$$

For saturation region,


$$I_D = \frac{1}{2} k_n \left(\frac{w}{L} \right) V_{GS}^2$$

$$= \frac{1}{2} k_n \left(\frac{w}{L} \right) (V_{GS} - V_t)^2$$

$$= \frac{1}{2} k_n \left(\frac{w}{L} \right) ((V_{DD} - V_D) - V_t)^2 \quad \left| \begin{array}{l} V_{GS} = V_{DD} - V_D \\ V_t = -0.7\text{V} \end{array} \right.$$


$$115\mu\text{A} = \frac{1}{2} \times 60\mu\text{A}/\text{V}^2 \left(\frac{w}{0.8\mu\text{m}} \right) (1.5 - 0.7)^2$$

$$\therefore w = 4.79\mu\text{m}$$

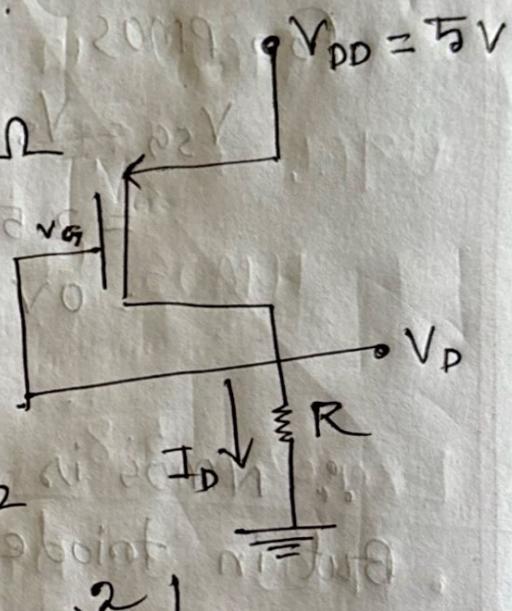

C.W
07/01/2022

5.4.2 Voltage transfer circuit

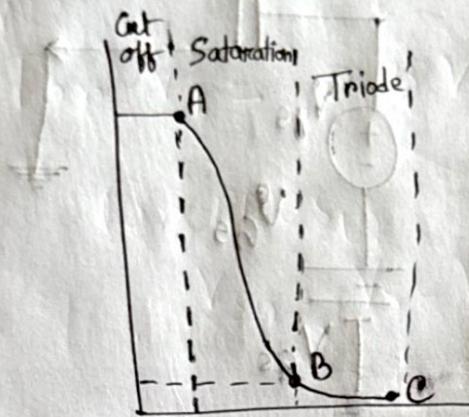


$$e\beta U + e\delta V = 20V$$

V_{DD}

i_D

\leq

R_D

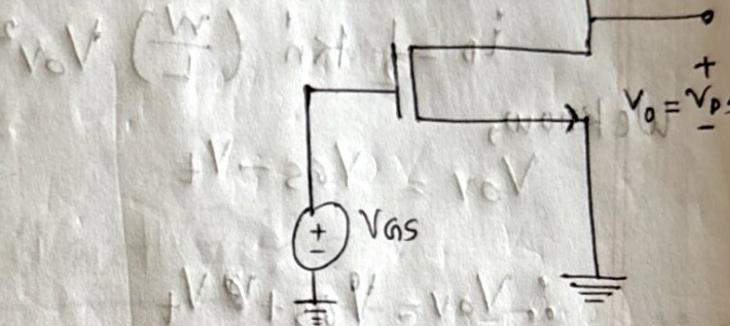

A = Pinch off region

B = " " "

Slide

$$(+V - e\beta U + 20V) \text{ and } \frac{1}{R_D} = \alpha$$

V_{DS}

5V

V_{DS}

5

-5

পুরো মাপ

10

5

0

-5

-10

-15

-20

-25

-30

-35

-40

-45

-50

-55

-60

-65

-70

-75

-80

-85

-90

-95

-100

-110

-120

-1000

Threshold 3 DC $\text{V}_G = 2V$

$$V_{DS} = V_{GS} + V_{GS}$$

We know,

$$i_D = \frac{1}{2} K_n \left(\frac{W}{L} \right) V_{DS}^2$$

We know,

$$V_{DS} = V_{GS} - V_t$$

$$\therefore V_{DS} = V_{GS} - V_t$$

$$= (V_{GS} + V_{GS} - V_t) \rightarrow \text{threshold.}$$

$$i_D = \frac{1}{2} K_n (V_{GS} + V_{GS} - V_t)^2$$

$$= \frac{1}{2} K_n \left(\underbrace{V_{GS} - V_t}_A + \underbrace{V_{GS}}_B \right)^2$$


$$= \frac{1}{2} K_n \left[\underbrace{(V_{GS} - V_t)^2}_{A^2 + 2AB + B^2} + 2(V_{GS} - V_t)V_{GS} + V_{GS}^2 \right]$$

$$= \frac{1}{2} K_n (V_{GS} - V_t)^2 + \cancel{\frac{1}{2} K_n 2(V_{GS} - V_t)V_{GS}} + \frac{1}{2} K_n V_{GS}^2$$

$$= \frac{1}{2} K_n (V_{GS} - V_t)^2 + K_n (V_{GS} - V_t)V_{GS} + \frac{1}{2} K_n V_{GS}^2$$

Since, $K_n (V_{GS} - V_t) \gg \frac{1}{2} K_n V_{GS}^2$

ignore

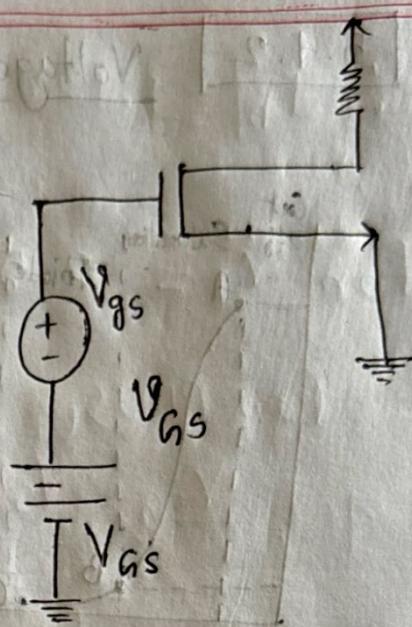

$$= \frac{1}{2} K_n (V_{GS} - V_t)^2 + K_n (V_{GS} - V_t) V_{GS}$$

DC I_D $i_D(t)$ for AC

MOSFET transconductance $= g_m = \text{conductance}$

$$g_m = \frac{i_D}{V_{DS}}$$

$$= \frac{K_n (V_{GS} - V_t) V_{GS}}{V_{GS}}$$

$[V_{DS} > V_{GS}]$

$$\therefore g_m = K_n (V_{GS} - V_t)$$

$$V_{DS} = V_{DD} - i_D R_D$$

$$= V_{DD} - \left(\frac{I_D}{DC} + \frac{i_d}{AC} \right) R_D$$

$$= \underbrace{V_{DD} - I_D R_D}_{V_{DS}} - \underbrace{\frac{i_d R_D}{AC}}$$

$$= V_{DS} - i_d R_D \rightarrow V_{DS}$$

$$V_{DS} = -i_d R_D$$

$$g_m = \frac{i_d}{V_{DS}}$$

$$\therefore i_d = g_m V_{DS}$$

$$V_{DS} = -i_d R_D$$

$$\Rightarrow V_{DS} = -(g_m V_{DS}) R_D$$


$$\Rightarrow V_{DS} = -g_m V_{GS} R_D$$

$$\Rightarrow \frac{V_{ds}}{V_i} = -g_m R_D$$

$$\Rightarrow A_V = -g_m R_D$$

$$\frac{\alpha}{2dV} = m\beta$$

Small Signal Eqn Model

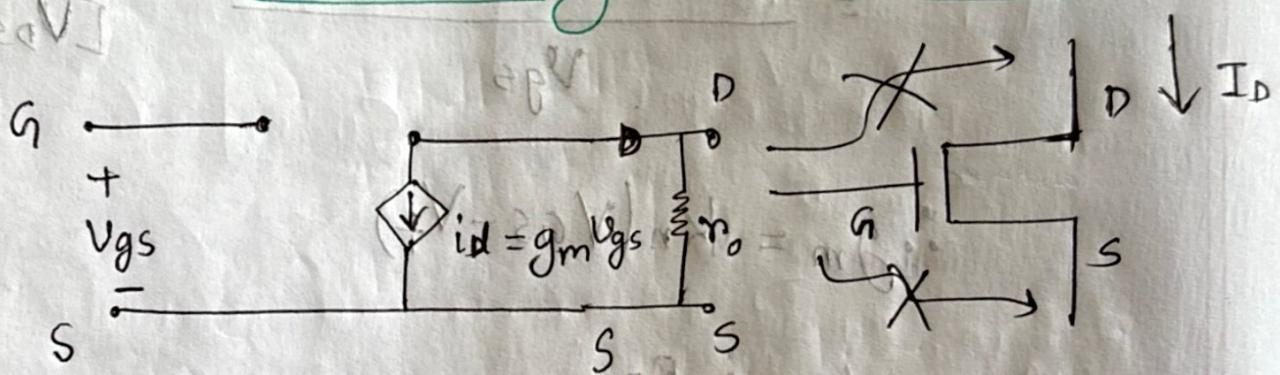


No question অনুশাস্তি থাকলেও পাঠে, নিও যোগাযোগ

পারে,


5.5.6

g_m এর বোঝা কোথা থাএ

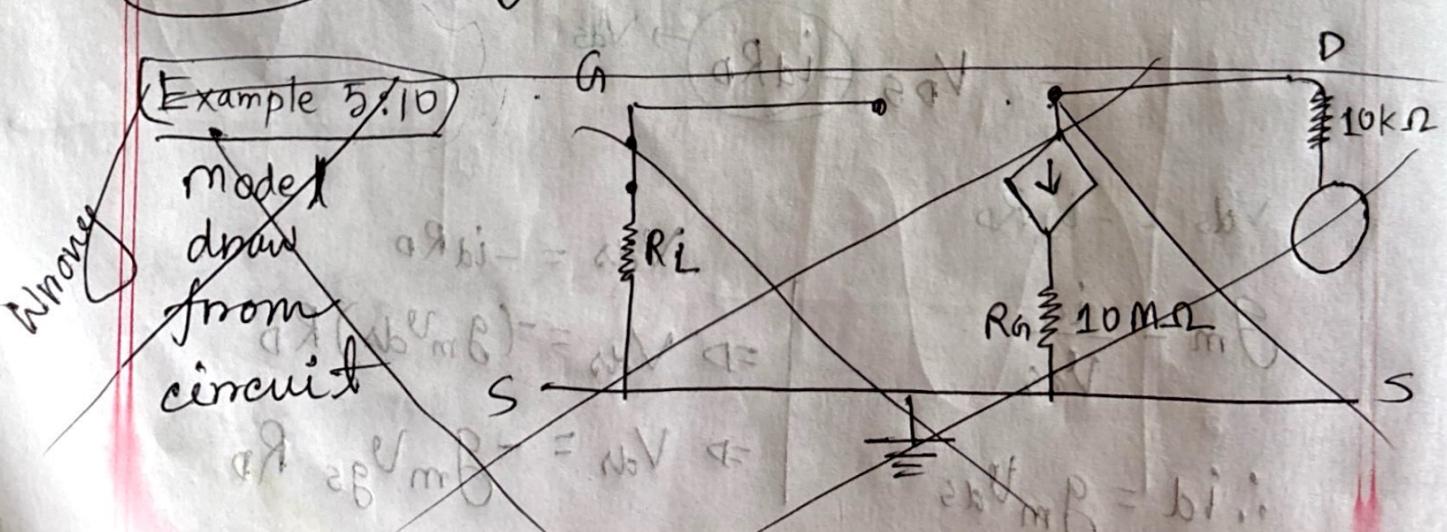

Example 5.10

Small Signal

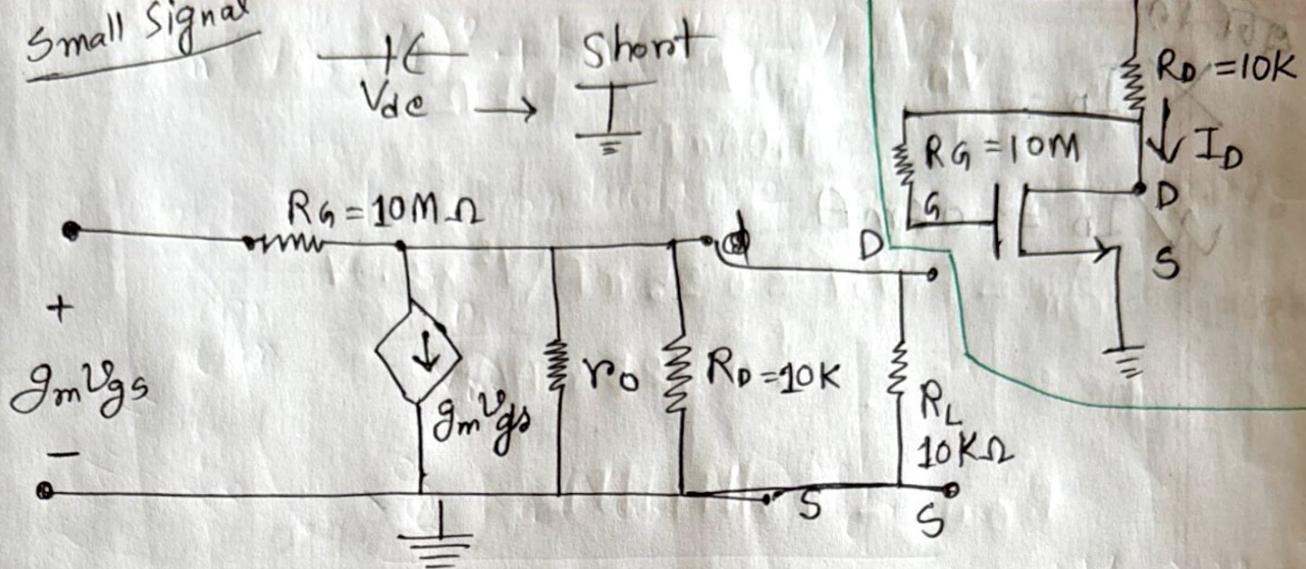

$$I_D = \frac{V_{DD} - V_D}{R_D} = \frac{15 - }{10K} =$$

$$\frac{DC}{I_D} = \frac{1}{2} K_n V_{ov}^2 = \frac{1}{2} K_n' \left(\frac{W}{L}\right) (V_{GS} - V_t)^2$$

[For saturation region]

$$V_{GS} = V_{DS} = V_{DD} - I_D R_D \\ = (15 - 10 I_D)$$

$$I_D = \frac{1}{2} \times 0.25 \text{ mA/V}^2 \times (15 - 10 I_D - 1.5)^2$$


$$= \frac{1}{2} \times 0.25 \text{ mA/V}^2 \times (13.5 - 10 I_D)^2$$

$$I_D = 0.125 \times (182.25 - 270 I_D + 100 I_D^2)$$

~~Find I_D~~

$$\times I_D =$$

$$\checkmark I_D = 1.06 \text{ mA}$$

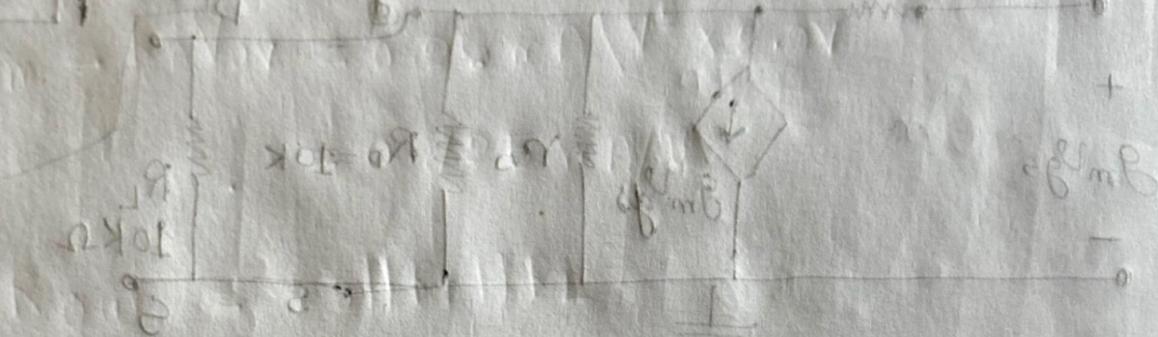

$$I_D = \frac{V_D - V}{R_D} = \frac{12 - 10}{10k\Omega} = 2 \text{ mA}$$

$$2(12 - 10) = 2 \text{ V} = 2 \text{ V}$$

$$(10 + 10) \times 2 = 40 \text{ V} = 40 \text{ V}$$


$$2(10 + 10) \times 2 = 40 \text{ V} = 40 \text{ V}$$

$$2(10 + 10) \times 2 = 40 \text{ V} = 40 \text{ V}$$

$$(10 + 10 + 10 + 10) \times 2 = 40 \text{ V} = 40 \text{ V}$$

12/10/2024

Ex: 5.10 amplifier circuit (slide)

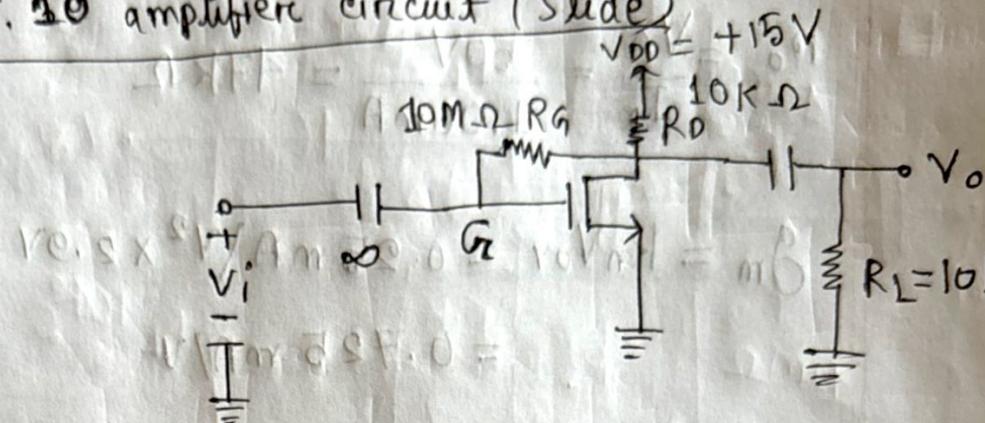

$$V_t = 1.5 \text{ V}$$

$$k_n' \left(\frac{W}{L} \right) = 0.25 \text{ mA/V}^2$$

$$V_A = 50 \text{ V}$$

(a) Small signal voltage gain = ?

(b) Input resistance = ? The Largest allowable input signal = ?

Ans: For saturation region,

$$\begin{aligned} I_D &= \frac{1}{2} k_n' \left(\frac{W}{L} \right) V_{DS}^2 \\ &= \frac{1}{2} \times 0.25 \text{ mA/V}^2 \times (V_{GS} - V_t)^2 \\ &= \frac{1}{2} \times 0.25 \text{ mA/V}^2 \times (V_{DD} - I_D R_D - V_t)^2 \end{aligned}$$

$$\therefore I_D = \frac{1}{2} \times 0.25 \text{ mA/V}^2 \times (15 - 10 I_D - 1.5)^2$$

$$I_D = 1.06 \text{ mA}$$

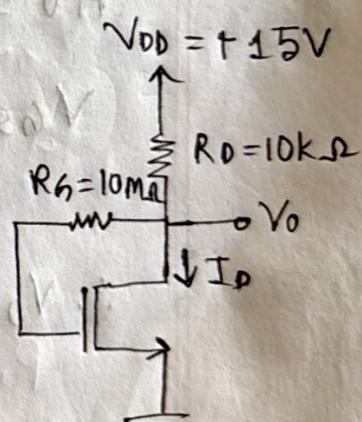


Fig 1

$$r_o = \frac{V_A}{I_D} = \frac{50V}{1.06mA} = 47k\Omega$$

$$g_m = k_n V_{ov} \pm 0.25 \text{ mA/V}^2 \times 2.9V \\ = 0.725 \text{ mA/V}$$

$$V_G, I = +V$$

$$R_{out} = r_{o1} || R_{o2} || R_L$$

$$= 47k \parallel 10k \parallel 10k$$

$$= 47k \parallel 5k$$

$$= 4.52k$$

$$Av = -g_m R_{out} = -0.725 \times 4.52 = +3.3$$

$$V_{GS} = V_{DS} = V_{DD} - I_D R_D$$


$$= 15 - 10 I_D = 4.4V$$

$$\therefore V_{ov} = V_{GS} - V_t = 4.4 - 1.5 = 2.9V$$

$$= 4.4 - 1.5 = 2.9V$$

Small Signal Model:
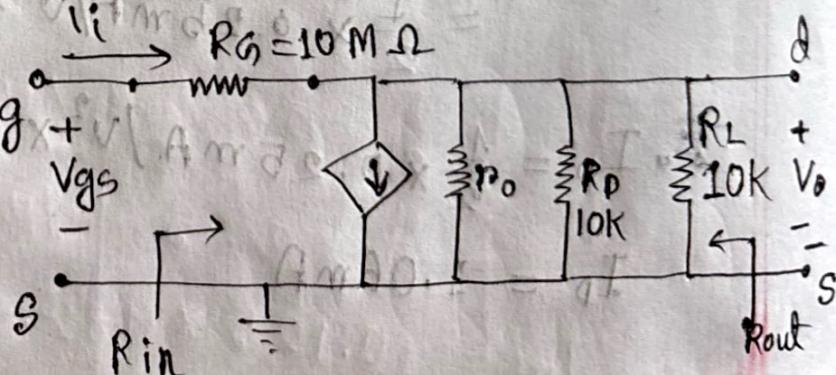
$$\left\{ \begin{array}{l} r_o = \frac{V_A}{I_D} \\ r_o' = \frac{V_A' L}{I_D} \end{array} \right.$$




Applying KCL at node A

$$i_i = i + g_m V_{gs}$$

$$\Rightarrow i = i_i - g_m V_{gs}$$
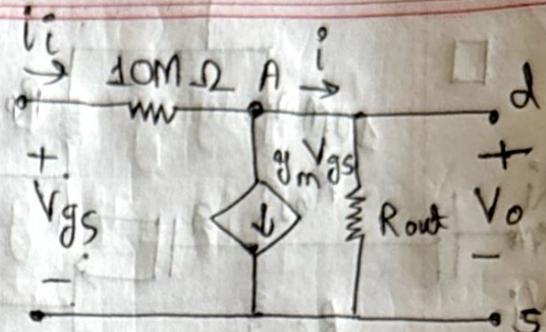
$$\Rightarrow i_i = \frac{V_{gs} - V_o}{R_G}$$



$$R_{in} = \frac{V_i}{i_i} = \frac{V_{gs}}{i_i} = \frac{V_{gs}}{\frac{V_{gs} - V_o}{R_G}} = \frac{R_G V_{gs}}{V_{gs} - V_o}$$

$$= \frac{R_G V_{gs}}{V_{gs} - (-A_v V_{gs})}$$

$$= \frac{R_G V_{gs}}{V_{gs}(1 + A_v)} = \frac{R_G}{1 + A_v}$$

$$\left| \begin{array}{l} \frac{V_o}{V_{gs}} = -A_v \\ \Rightarrow V_o = -A_v V_{gs} \end{array} \right.$$

$$\therefore R_{in} = \frac{R_G}{1 + A_v} = \frac{10M\Omega}{1 + (+3.3)} = 2.32k\Omega$$

$$\underline{\text{Sat}} \quad V_{DS} \geq V_{OR}$$


$$V_{DS} \geq (V_{GS} - V_t)$$

$$V_{DS} - A_v V_{GS} \leq V_{GS}$$


$$= V_{GS} - A_v V_{GS} - V_i$$

Allowable largest
input signal
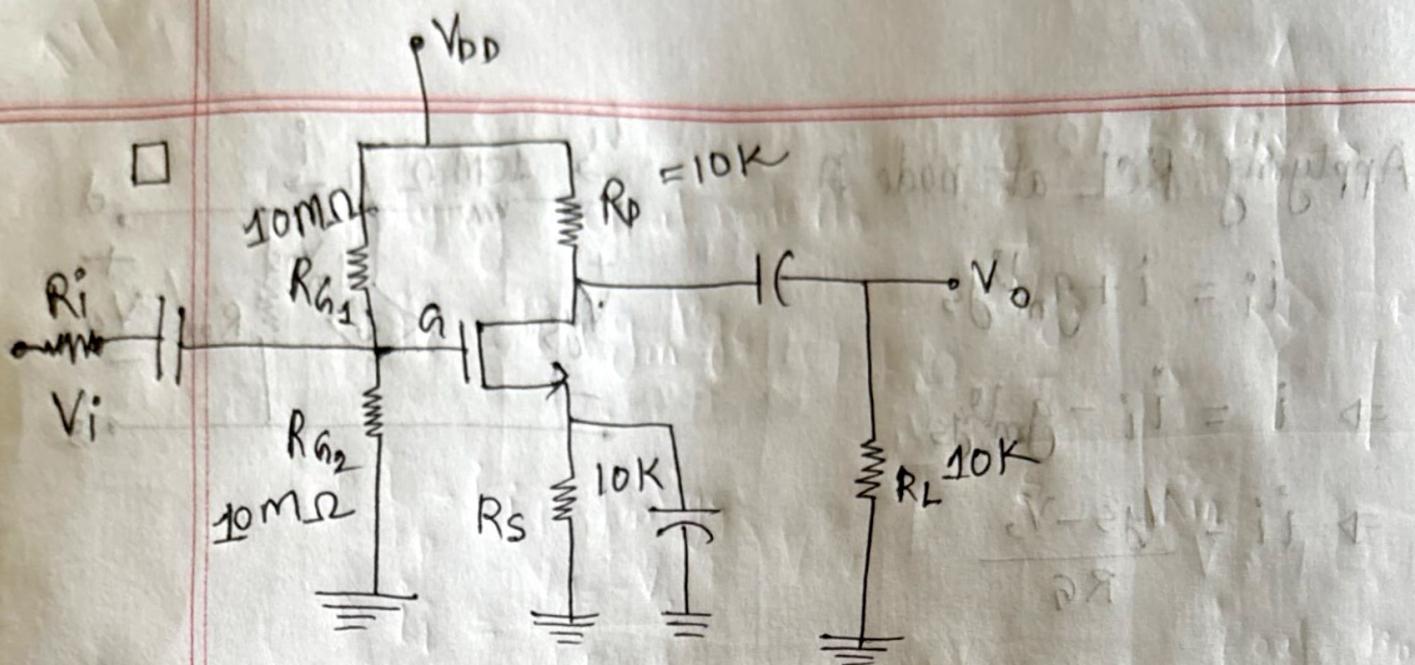
$$V_i = \frac{V_t}{A_v + 1} = \frac{1.5}{3.3 + 1} = 0.35V$$



Small Signal Model


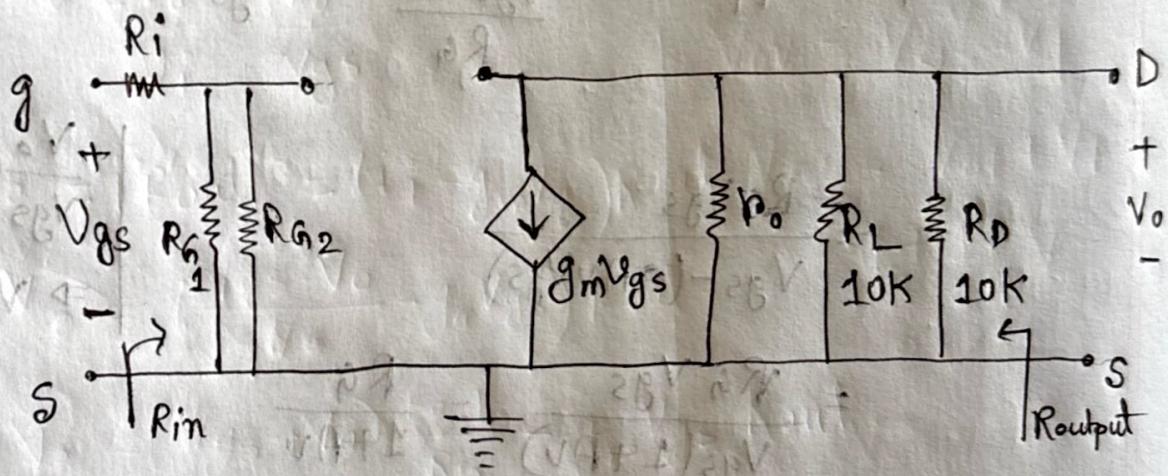


$$R_{in} = R_i + (R_{G1} \parallel R_{G2})$$

$$R_{out} = R_o \parallel R_D \parallel R_L$$

$$A_v = -g_m R_{out}$$

$R_{out} = ?$, Small Signal Model

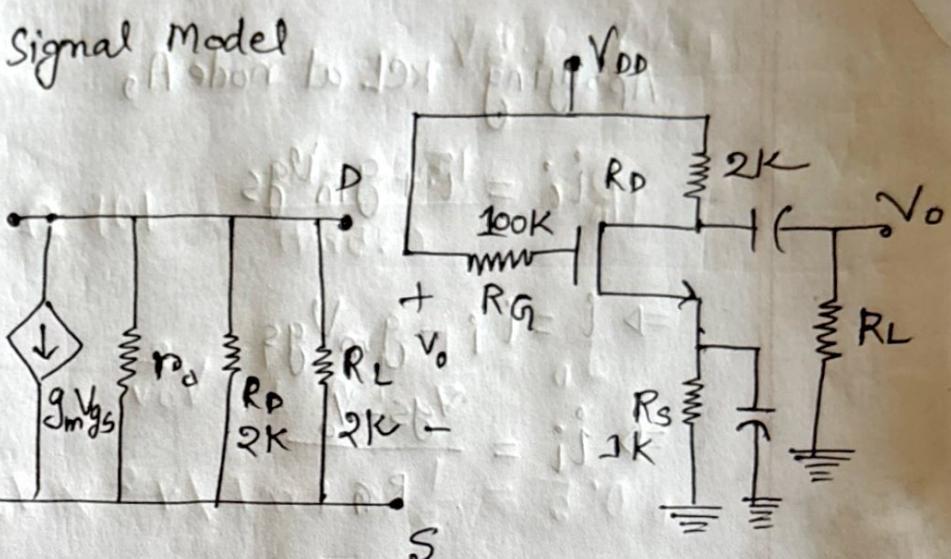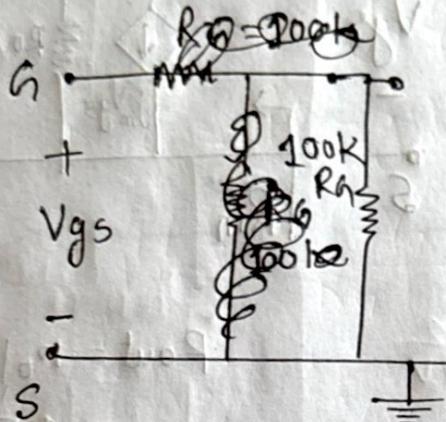

$$R_{out} = r_o \parallel R_D \parallel R_L$$

$$= 0.5k \parallel 2k \parallel 2k = 0.33k\Omega$$

$$\text{from } (eB V_m \beta - \frac{0V - eB V}{R_D}) = 0V$$

$$eB V_m \beta - \frac{0V - eB V}{R_D} (0V + eB V) = 0V$$

$$(eB V_m \beta - \frac{0V - eB V}{R_D}) eB V = 0V$$

$$(eB V_m \beta - \frac{0V - eB V}{R_D}) eB V = \frac{0V - eB V}{R_D} eB V + 0V$$

$$(eB V_m \beta - \frac{0V - eB V}{R_D}) eB V = \left(\frac{0V - eB V}{R_D} + 1 \right) eB V$$

$$\left(1 - \frac{1}{R_D} \right) eB V_m \beta eB V = \left(\frac{0V - eB V}{R_D} + 1 \right) eB V$$

C.W
14/07/29

Applying KCL at node A,

$$i_i = i + g_m V_{gs}$$

$$\Rightarrow i = i_i - g_m V_{gs}$$

$$\Rightarrow i_i = \frac{V_{gs} - V_o}{R_g}$$

$$A_v = \frac{V_o}{V_i} = \frac{V_o}{V_{gs}}$$

$$V_o = i R_{out} = (i_i - g_m V_{gs}) R_{out}$$

$$\Rightarrow V_o = \left(\frac{V_{gs} - V_o}{R_g} - g_m V_{gs} \right) R_{out}$$


$$\Rightarrow V_o = (V_{gs} - V_o) \frac{R_{out}}{R_g} - g_m V_{gs} R_{out}$$

$$\Rightarrow V_o = V_{gs} \frac{R_{out}}{R_g} - V_o \frac{R_{out}}{R_g} - g_m V_{gs} R_{out}$$

$$\Rightarrow V_o + V_o \frac{R_{out}}{R_g} = V_{gs} \frac{R_{out}}{R_g} - g_m V_{gs} R_{out}$$

$$\Rightarrow V_o \left(1 + \frac{R_{out}}{R_g} \right) = V_{gs} \left(\frac{R_{out}}{R_g} - g_m R_{out} \right)$$
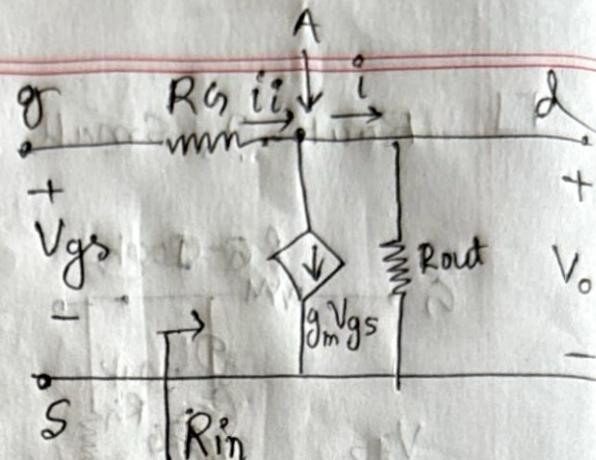
$$\Rightarrow V_o \left(1 + \frac{R_{out}}{R_g} \right) = V_{gs} g_m R_{out} \left(\frac{1}{R_g g_m} - 1 \right)$$



$$R_{out} = r_o || R_d || R_L \\ = 4.5 \text{ k}\Omega$$

$$\therefore \frac{V_o}{V_{gs}} = -g_m R_{out} \left(\frac{1 - \frac{1}{R_g g_m}}{1 + \frac{R_{out}}{R_g}} \right)$$

V_{GS} = 1V ①

$$\therefore A_v = -g_m R_{out} \left(\frac{1 - \frac{1}{R_g g_m}}{1 + \frac{R_{out}}{R_g}} \right)$$


$$\boxed{\therefore A_v \approx -g_m R_{out}}$$

□ # Determine the percentage change in I_D when $K_n \left(\frac{W}{L} \right)$ remain same but


$$V_t = 1.5V$$

Find R_{in} and R_{out} of the small signal model.

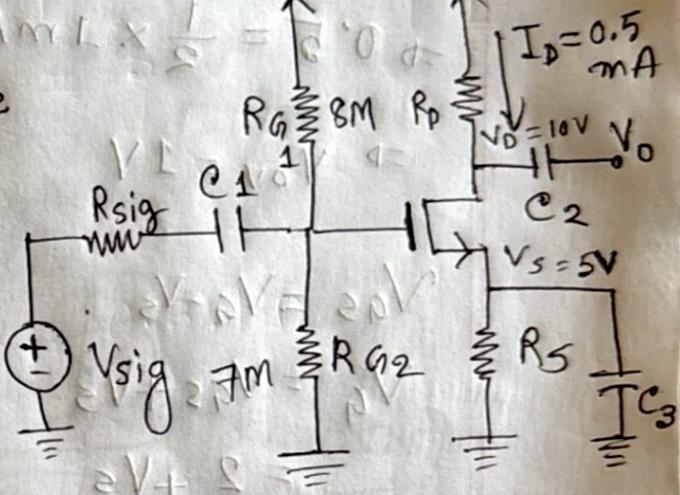
$$A_v = -g_m \left(r_o \parallel R_D \right)$$



②

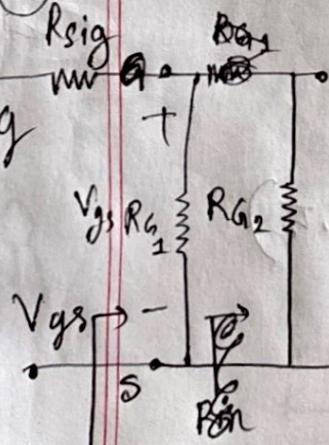

$$R_{in} = R_{G1} \parallel R_{G2}$$

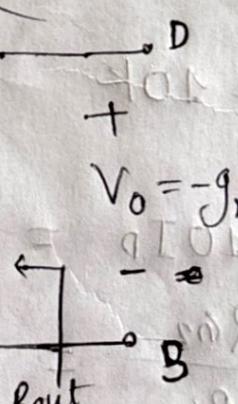

$$V_o = -g_m V_{gs} \left(r_o \parallel R_D \right)$$

$$V_t = 1V$$

$$K_n \left(\frac{W}{L} \right) = 1 \text{ mA/V}^2$$

$\pi = 0$ (Channel length modification)
modulation

$$\textcircled{1} V_t = 1.5V$$

$$R_D = \frac{15 - 10}{0.5mA} = 10K\Omega$$

$$I_D = \frac{1}{2} K_n \left(\frac{W}{L} \right) V_{ov}^2$$

$$\Rightarrow 0.5 = \frac{1}{2} \times 1mA/V^2 \times V_{ov}^2$$

$$\Rightarrow V_{ov} = 1V$$

$$V_{GS} = V_G - V_S$$

$$V_G = V_{GS} + V_S$$

$$= 2 + V_S$$

$$V_1 = V_{GS} + I_D R_S$$

$$V_{ov} = V_{GS} + V_t$$

$$\Rightarrow V_{GS} = V_{ot} + V_t \\ = (1+1)V$$

$$R_S = \frac{5}{0.5mA} = 10K$$

$$V_{GS} = V_{GS} + 10 I_D = 2 + (10 \times 0.5)$$

$$V_G = \frac{V_{DD} \times R_{G2}}{R_{G1} + R_{G2}} = 7V$$